


# Phasors 004

Problem has been graded.

You are given  $v_S = A_1 \cdot \sqrt{2} \cdot \cos(100t + B_1)$

$$v_C = A_2 \cdot \cos(100t + B_2)$$

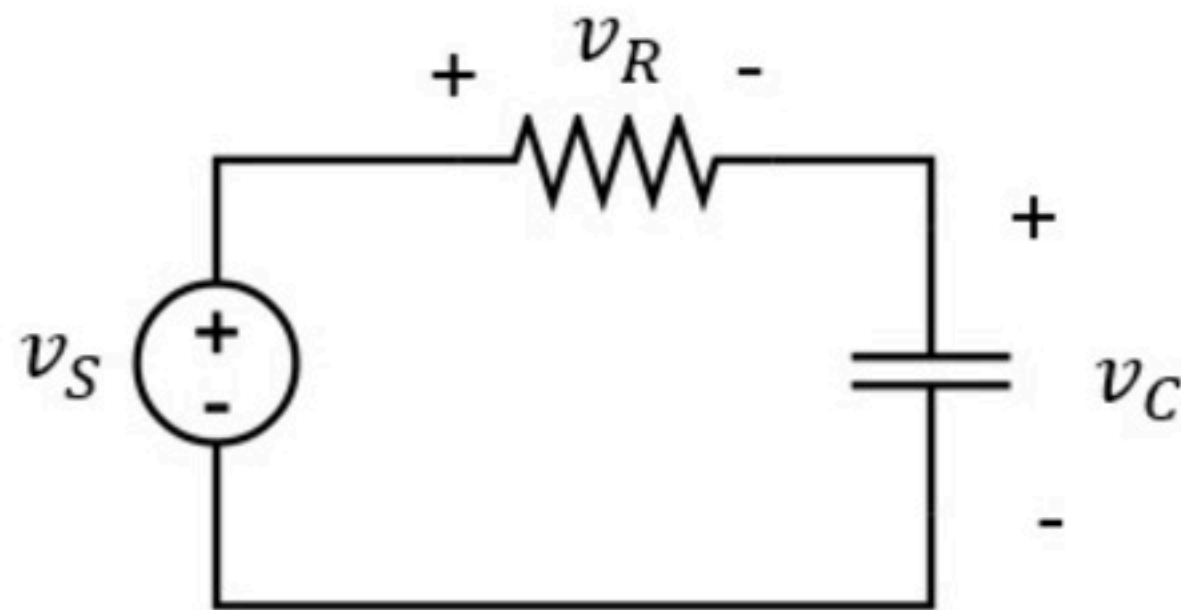Find  $v_R = A_3 \cdot \cos(100t + B_3)$  with  $-180^\circ \leq B_3 \leq 180^\circ$



Solve without using a calculator.

Given Variables:

A1 : 4 V

B1 : 20 degrees

A2 : 4 V

B2 : -25 degrees

Calculate the following:

A3 (V) :

4

✓

B3 (degrees) :

65

✓

Hint: Convert to phasors. Multiply out the common  $\exp(jB)$  factor.