

**UNIVERSITY OF CALIFORNIA, SAN DIEGO**

Electrical and Computer Engineering Department

ECE 65 – Spring 2023

*Components and Circuits lab*

Final Exam *Solutions*

- Closed books, three one-sided cheat sheets, and calculators are allowed.
- Electronic devices are not allowed.
- Please put all answers in the provided sheets.
- You can use the back of every page as a scratch paper.
- Please scan your answers and cheat sheets and submit them to Gradescope by 2:30 pm.

**Please do not begin until you are told to do so.**


Show your work and good luck!

**Problem 1.**

Consider the following op-amp circuit. Assume an ideal op-amp.

Choose the op-amp saturation voltage, maximum output current, and a sinusoidal input voltage such that the output voltage would be distorted because of op-amp's maximum output current.

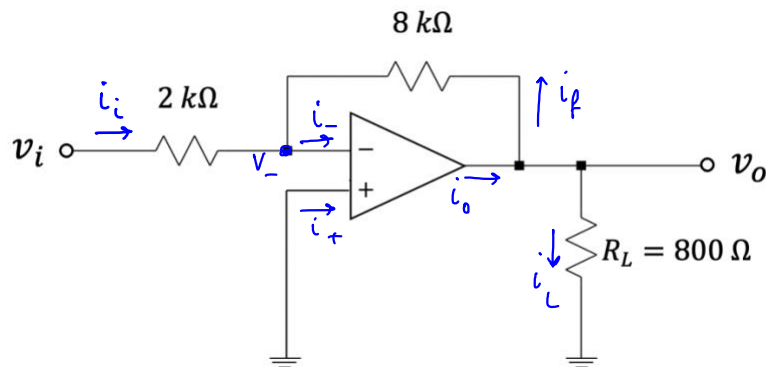- What are your selected saturation voltage, maximum output current, and input voltage?
- Analyze the circuit and show why the output voltage is distorted.
- Draw the input and output waveforms.



There is more than one correct answer to this problem.

**Show your work.**

op-amp is ideal:  $i_+ = i_- = 0$

there is negative feedback:  $V_+ = V_- = 0$

KCL at the inverting input terminal:  $i_i + i_f = i_- = 0$

$$\frac{V_i - V_-}{2 \text{ k}\Omega} + \frac{V_o - V_-}{8 \text{ k}\Omega} = 0 \quad \rightarrow \quad \frac{V_i}{2 \text{ k}\Omega} + \frac{V_o}{8 \text{ k}\Omega} = 0 \quad \Rightarrow \quad \frac{V_o}{V_i} = -\frac{8}{2} = -4 \text{ V/V}$$

Name

PID

$v_o = -4 v_i$  when we have linear amplification

KCL at the output node:  $i_o = i_f + i_L$

$$i_f = \frac{v_o - v_-}{8k} = \frac{v_o}{8k}, \quad i_L = \frac{v_o}{0.8k}$$

$$i_o = \frac{v_o}{8k} + \frac{v_o}{0.8k} = \frac{11}{8} v_o \text{ (mA)}$$

choose some values for  $V_{sat}$ ,  $I_{o_{max}}$  and choose  $v_i$ :




$$V_{sat} = \pm 25, \quad \hat{v}_i = 4 \text{ V} \rightarrow |\hat{v}_o| = 16 \text{ V} < V_{sat}$$

linear amplification will not be limited by the saturation voltage.

Assume  $I_{o_{max}} = 11 \text{ mA}$ . To have  $\hat{v}_o = 16 \text{ V}$ , we need  $\hat{i}_o = 22 \text{ mA}$ , which can not be supplied


The output voltage will be distorted because of the op-amp max output current.

$$i_{o_{max}} = \frac{11}{8} v_{o_{max}} = 11 \text{ mA} \rightarrow v_{o_{max}} = \frac{8 \times 11}{11} = 8 \text{ (V)}$$

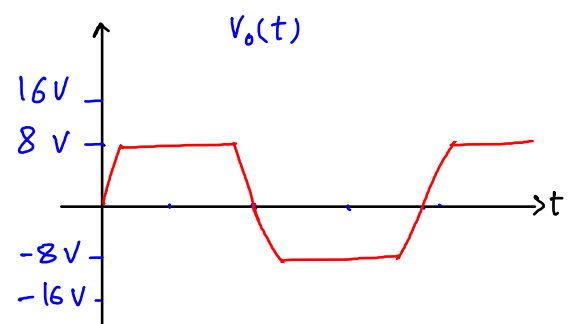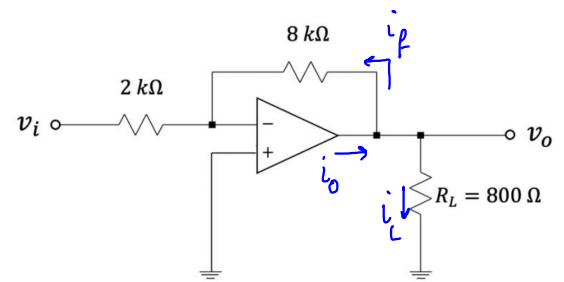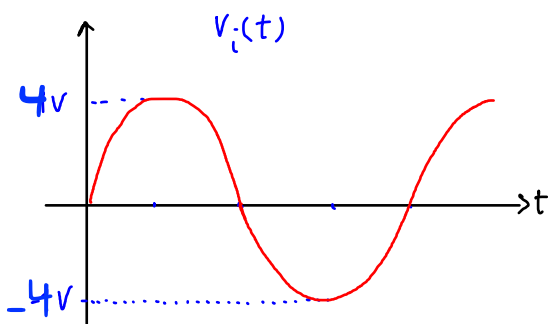

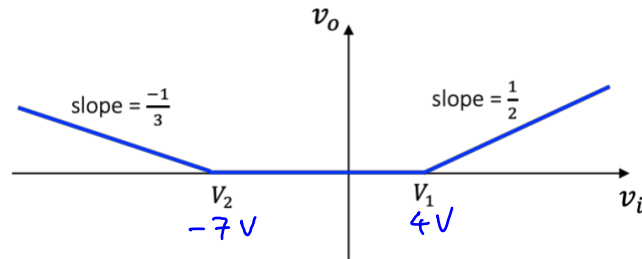**Problem 2.**

In the below transfer characteristics (transfer function) graph,  $V_1 = 4\text{ V}$ ,  $V_2 = -7\text{ V}$



a) Design a diode waveform shaping circuit that would have the above transfer function.


- You can use PN junction diodes with  $V_{D0} = 0.7\text{ V}$ , Zener diodes with  $V_z = 2.3\text{ V}$ , DC voltage sources and resistors in your design.
- You should indicate the resistor values and the DC voltage sources' values in your design.
- Make sure to include the input voltage source in your circuit schematic and label the output terminals.
- Make sure that at least one Zener diode and one DC voltage source are used in your design.

b) Parametrically solve your circuit. That means find the relationship between  $v_i$  and  $v_o$  and the range of  $v_i$ .

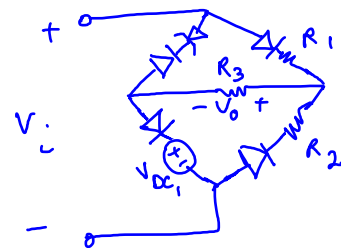**Write complete equations and show your work.**


From the transfer characteristic graph:

$$V_o = \begin{cases} \frac{1}{2} V_i - 2, & V_i \geq 4\text{ V} \\ 0, & -7 < V_i < 4\text{ V} \\ -\frac{1}{3} V_i - \frac{7}{3}, & V_i \leq -7\text{ V} \end{cases}$$



Name

PID

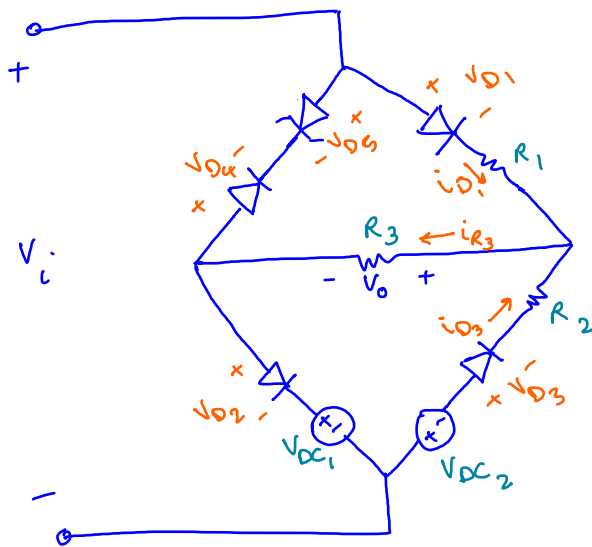


$$V_o = \begin{cases} \frac{1}{2} V_i - 2, & V_i \geq 4V \\ 0, & -7 < V_i < 4V \\ -\frac{1}{3} V_i - \frac{7}{3}, & V_i \leq -7V \end{cases}$$

Case 1:  $D_1$  &  $D_2$  ON,  $D_3$  &  $D_4$  &  $D_5$  off

Case 2:  $D_1$  &  $D_2$  off,  $D_3$  &  $D_4$  ON and  $D_5$  in Zener

Case 3: All diodes are off

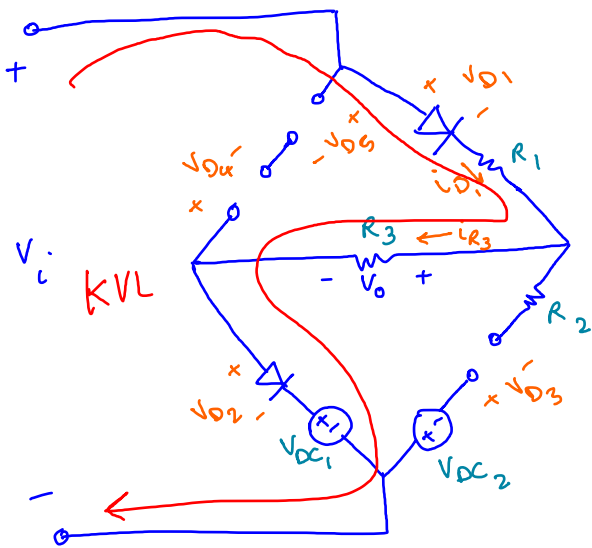

Case 1:  $D_1$  &  $D_2$  ON  
 $D_3$  &  $D_4$  &  $D_5$  off

$$V_{D1} = V_{D2} = 0.7 \text{ V} \quad i_{D1} \geq 0, i_{D2} \geq 0$$

$$V_{D3} < V_{D0}, V_{D4} < V_{D0}, -V_2 < V_{D3} < V_{D0}$$

$$i_{D3} = i_{D4} = i_{D5} = 0$$

$$\text{KVL: } V_i = V_{D1} + R_1 i_{D1} + i_{D1} \times R_3 + V_{D2} + V_{DC1}$$

$$V_i = 0.7 + R_1 i_{D1} + i_{D1} \times R_3 + 0.7 + V_{DC1}$$

$$i_{D1} = \frac{V_i - 1.4 - V_{DC1}}{R_1 + R_3}$$

$$i_{D1} \geq 0 \rightarrow V_i \geq 1.4 \text{ V} + V_{DC1}$$

$$V_0 = R_3 \times i_{D1} = \frac{R_3}{R_1 + R_3} V_i - \frac{R_3}{R_1 + R_3} (1.4 + V_{DC1})$$


$$\begin{cases} V_i \geq 1.4 V + V_{DC1} \\ V_o = \frac{R_3}{R_1 + R_3} V_i - \frac{R_3}{R_1 + R_3} (1.4 + V_{DC1}) \end{cases}$$

comparing the above conditions with the ones obtained from the graph we can find  $V_{DC1}$  and choose values for  $R_1$  and  $R_3$ .

From the graph:  $V_o = \frac{1}{2} V_i - 2$  when  $V_i \geq 4V$

$$1.4 V + V_{DC1} = 4V \longrightarrow V_{DC1} = 2.6 V$$
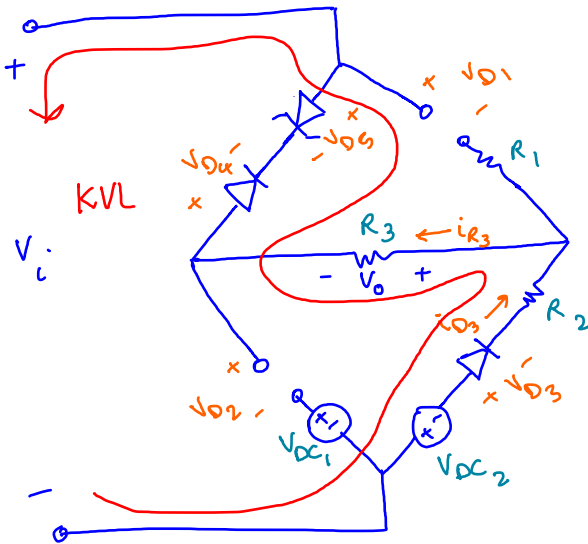
$$\frac{R_3}{R_1 + R_3} = \frac{1}{2}, \text{ choose } R_3 = 1 k\Omega, R_1 = 1 k\Omega$$



$D_3$  &  $D_4$  ON and  $D_5$  in Zener

$$V_{D_3} = V_{D_4} = 0.7 \text{ V} \quad i_{D_3} > 0, \quad i_{D_4} > 0$$

$$V_{D5} = -V_Z, \quad i_{D5} \leq 0$$

$$V_{D_1} < V_{D_0}, V_{D_2} < V_{D_0}$$

$$i_{D_1} = i_{D_2} = 0$$

KVL:  $V_i = V_{D5} - V_{D4} - i_{R3} \times R_3 - i_{D3} \times R_2 - V_{D3} - V_{DC2}$

$$V_{D_5} = -V_Z = -2.3 \text{ V} \quad , \quad V_{D_4} = 0.7 \quad , \quad V_{D_3} = 0.7 \text{ V}$$

$$i_{R_3} = i_{D_3}$$

$$V_i = -2.3V - 0.7V - i_{D_3} \times R_3 - i_{D_3} \times R_2 - 0.7V - V_{DC_2}$$

$$i_{D_3} = \frac{-V_i - 3.7V - V_{OC2}}{R_3 + R_2}$$

$$i_{D3} \geq 0 \rightarrow V_i \leq -3.7V - V_{Dc2}$$

$$V_o = R_3 i_3 = \frac{-R_3}{R_3 + R_2} V_i - \frac{R_3}{R_3 + R_2} (3.7 + V_{DC_2})$$




$$\begin{cases} V_i \leq -3.7V - V_{DC_2} \\ V_o = \frac{-R_3}{R_3 + R_2} V_i - \frac{R_3}{R_3 + R_2} (3.7 + V_{DC_2}) \end{cases}$$

comparing the above conditions with the ones obtained from the graph we can find  $V_{DC_2}$  and choose a value for  $R_2$ .

From the graph:  $V_o = -\frac{1}{3} V_i - \frac{7}{3}$  when  $V_i \leq -7V$

$$-3.7 - V_{DC_2} = -7 \longrightarrow V_{DC_2} = 3.3V$$

$$\frac{-R_3}{R_2 + R_3} = -\frac{1}{3} \quad \text{and } R_3 = 1k\Omega \longrightarrow R_2 = 2k\Omega$$

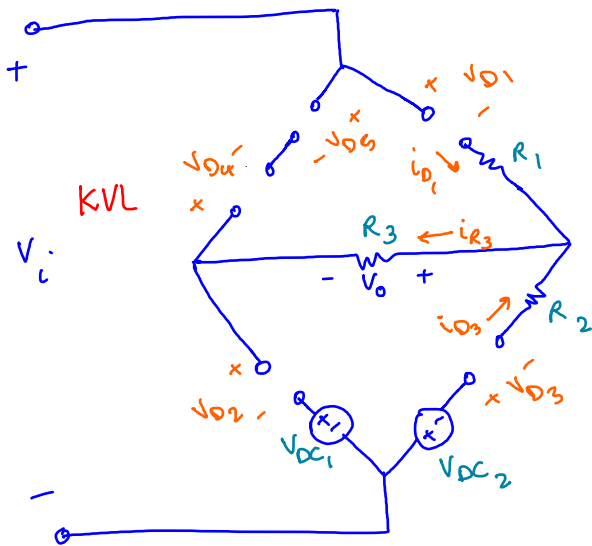

Case 3 :

All diodes are off.

$$V_{D1} < V_{D0}, V_{D2} < V_{D0}, V_{D3} < V_{D0}$$

$$-V_2 < V_{D5} < V_{D0}$$

$$i_{D1} = i_{D2} = i_{D3} = i_{D4} = i_{D5} = 0$$

This is the only other case, so for this case  $-7 < V_i < 4$ .


$$i_{R3} = i_{D1} + i_{D3} = 0$$

$$V_0 = R_3 i_{R3} = 0$$

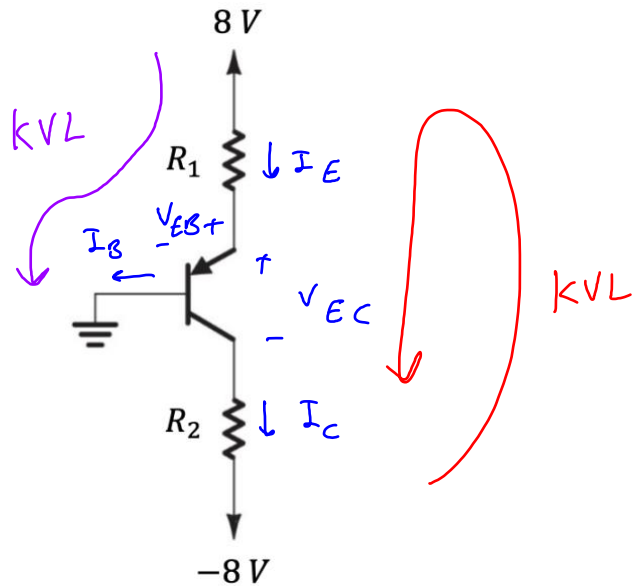**Problem 4.**

Design the following circuit to have the BJT operate in the saturation mode.

Assume  $\beta = 200$ ,  $V_{sat} = 0.2\text{ V}$ , and  $V_{D0} = 0.7\text{ V}$



**Show your work.**

BJT is in saturation :  $V_{EC} = V_{sat} = 0.2\text{ V}$

$$\text{KVL: } 8\text{ V} = R_1 I_E + V_{EB} \rightarrow 8\text{ V} = R_1 I_E + 0.7 \rightarrow R_1 I_E = 7.3\text{ V}$$

$$\text{KVL: } 8\text{ V} = R_1 I_E + V_{EC} + R_2 I_C - 8\text{ V}$$

$$16\text{ V} - 0.2\text{ V} = R_1 I_E + R_2 I_C \rightarrow \underbrace{R_1 I_E}_{7.3\text{ V}} + R_2 I_C = 15.8\text{ V}$$

$$\Rightarrow R_2 I_C = 8.5\text{ V}$$

$$R_1 I_E = 7.3 \text{ V}$$

$$R_2 I_C = 8.5 \text{ V}$$

$$I_C < \beta I_B \rightarrow I_B > \frac{1}{\beta} I_C$$

$$I_B + I_C > \frac{1}{\beta} I_C + I_C$$

$$I_E > \frac{\beta+1}{\beta} I_C$$

$$I_E > \frac{201}{200} I_C \rightarrow I_E > 1.005 I_C$$

We can choose  $I_C = 1 \text{ mA}$  and  $I_E = 1.2 \text{ mA}$

$$R_1 I_E = 7.3 \text{ V} \rightarrow R_1 = \frac{7.3 \text{ V}}{1.2 \text{ mA}} = 6.08 \text{ k}\Omega$$


$$R_2 I_C = 8.5 \text{ V} \rightarrow R_2 = \frac{8.5 \text{ V}}{1 \text{ mA}} = 8.5 \text{ k}\Omega$$

**Problem 4.**

Design the following amplifier circuit for  $I_D = 8 \text{ mA}$ .

- Design the circuit and find the Bias point.
- Find the small signal parameters and draw the signal circuit.
- Assume  $R_L = 1 \text{ k}\Omega$  and  $V_{sig}$  is a triangular wave with a peak-to-peak amplitude of  $400 \text{ mV}$  and DC voltage of zero. Find and draw the instantaneous (total) drain to source voltage.
- What is the maximum amplitude of the signal at the drain if a symmetrical signal swing is desired? What is the amplitude of the corresponding input signal?

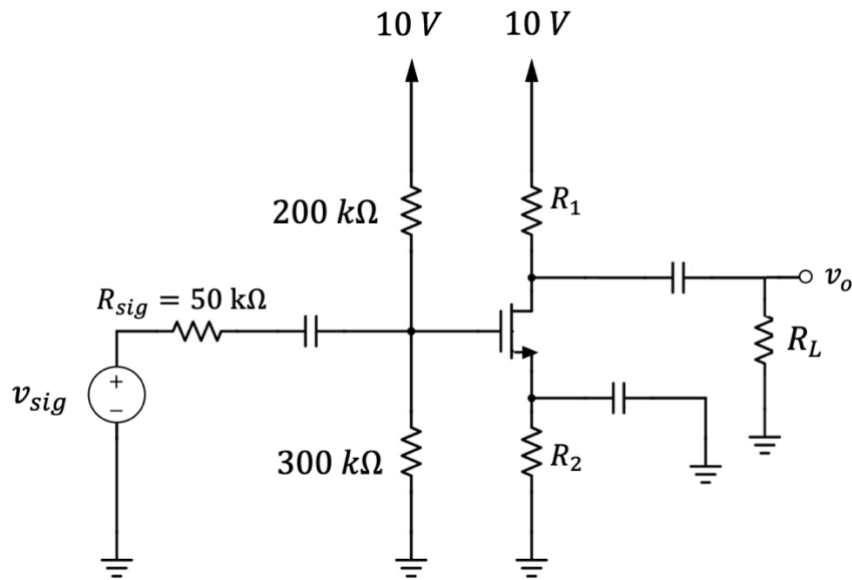Assume  $V_t = 0.5 \text{ V}$ ,  $\mu C_{ox} \frac{W}{L} = 4 \text{ mA/V}^2$ , and  $\lambda = 0$ .



There is more than one correct answer to this problem.

**Show your work.**

a)

$$V_G = \frac{300 \text{ k}\Omega}{500 \text{ k}\Omega} \times 10 = 6 \text{ V}$$

$$I_D = 8 \text{ mA}$$

NMOS is in saturation

$$I_D = \frac{1}{2} k_n V_{ov}^2$$

$$8 \text{ mA} = \frac{1}{2} \times 4 \text{ mA/V} \times V_{ov}^2 \Rightarrow V_{ov} = \sqrt{4} = 2 \text{ V}$$

$$V_{GS} - V_t = 2 \rightarrow V_{GS} = 2 + 0.5 = 2.5 \text{ V}$$

$$V_{GS} = V_G - V_S = 6 - V_S = 2.5 \Rightarrow V_S = 3.5 \text{ V}$$

$$V_S = R_2 \times I_D \Rightarrow R_2 = \frac{3.5}{8 \text{ mA}} = 437.5 \Omega$$

$$R_2 = 437.5 \Omega$$


NMOS must operate in saturation region.  $\rightarrow V_{DS} > V_{ov}$ 

$$V_D - V_S > 2 \rightarrow V_D > 3.5 + 2 \rightarrow V_D > 5.5 \text{ V}$$

$$\text{select } V_D = 8 \text{ V} \rightarrow V_{DS} = 4.5 \text{ V}$$

$$V_D = 10 \text{ V} - R_1 I_D \rightarrow 8 = 10 - R_1 \times 8 \text{ mA} \rightarrow R_1 = \frac{2 \text{ V}}{8 \text{ mA}} = 250 \Omega$$

$$R_1 = 250 \Omega$$

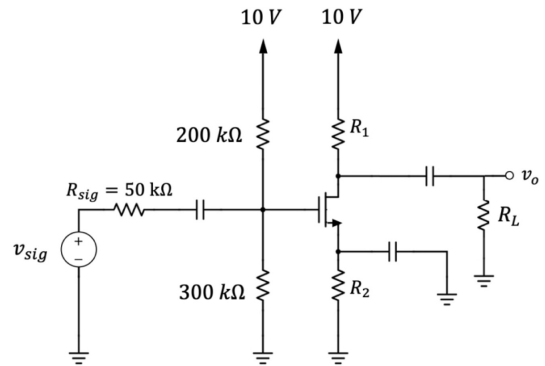



Name

PID

b)

$$g_m = \frac{2 I_D}{V_{ov}} = \frac{2 \times 8 \text{ mA}}{2 \text{ V}} = 8 \text{ mA/V}$$
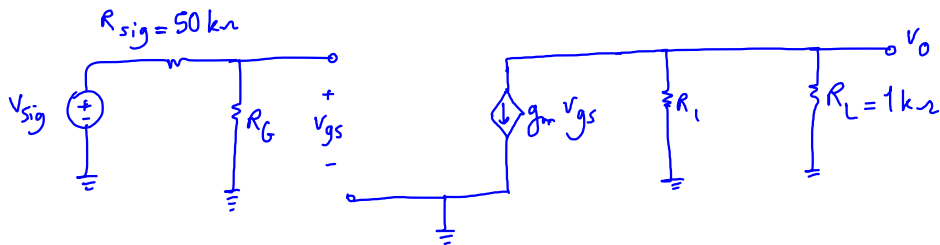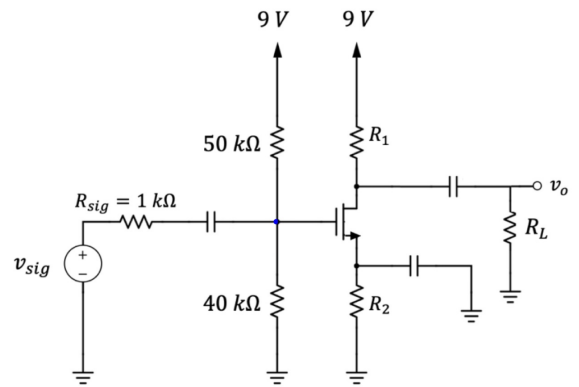
$$r_o \approx \frac{1}{\lambda I_D} = \infty$$



$$c) \quad V_o = -g_m v_{gs} (R_1 \parallel R_L) \quad , \quad v_{gs} = \frac{R_G}{R_G + R_{sig}} V_{sig}$$

$$V_o = V_d = V_{ds} = -g_m (R_1 \parallel R_L) \frac{R_G}{R_G + R_{sig}} V_{sig}$$

$$R_G = 300 \text{ k}\Omega \parallel 200 \text{ k}\Omega = 120 \text{ k}\Omega \quad , \quad \frac{R_G}{R_G + R_{sig}} = \frac{120 \text{ k}\Omega}{170 \text{ k}\Omega} = 0.71$$

$$R_1 \parallel R_L = 0.25 \text{ k}\Omega \parallel 1 \text{ k}\Omega = 200 \text{ }\Omega \quad , \quad V_{sig} \approx 1.42 V_{gs}$$



$$V_o = V_{ds} = \left( -8 \text{ mA/V} \times 0.2 \text{ k}\Omega \times 0.71 \right) V_{sig} \approx -1.136 V_{sig}$$

Name

PID

$$\begin{aligned} \text{Total } v_{DS} &= V_{DS} + v_{ds} \\ &= 4.5 \text{ V} - 1.136 v_{sig} \end{aligned}$$
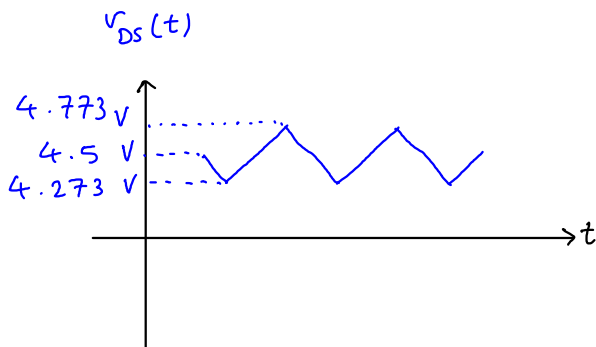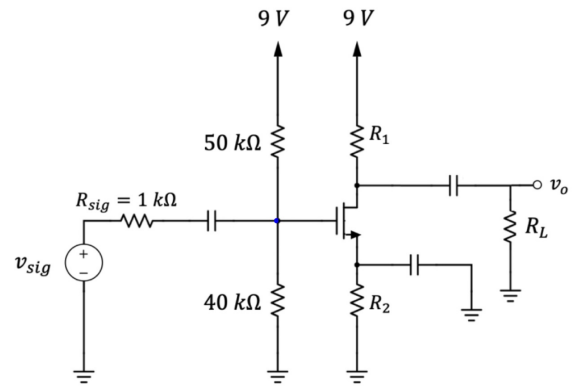
$$\hat{v}_{sig} = 200 \text{ mV} \rightarrow \hat{v}_{ds} = 227.2 \text{ mV} = 0.227 \text{ V}$$



$$d) \quad v_{DS} > v_{ov} \quad \rightarrow \quad V_{DS} - \hat{v}_{ds} > V_{GS} + \hat{v}_{gs} - V_t$$

$$V_{ds} = 1.136 v_{sig} = 1.136 \frac{v_{sig}}{v_{gs}} \times v_{gs} = 1.136 \times 1.42 v_{gs} \approx 1.61 v_{gs}$$

$$4.5 - \hat{v}_{ds} > 2.5 + \frac{\hat{v}_{ds}}{1.61}$$

$$2 > \hat{v}_{ds} + \frac{\hat{v}_{ds}}{1.61} \quad \rightarrow \quad \hat{v}_{ds} < 1.23 \text{ V}$$

$$\hat{v}_{ds} = 1.136 \hat{v}_{sig} \Rightarrow \hat{v}_{sig} < 1.08 \text{ V}$$