

ECE 35, Fall 2019
Quiz 2

Grade

/ 10

Sequence
number

Last name

First + middle
name(s)


PID

Instructions:

- Read each problem completely and thoroughly before beginning.
- All calculations need to be done on these sheets.
- Write your answers in the answer boxes for each question. Make sure you list units!
- Answers without supporting calculations will receive zero credit.



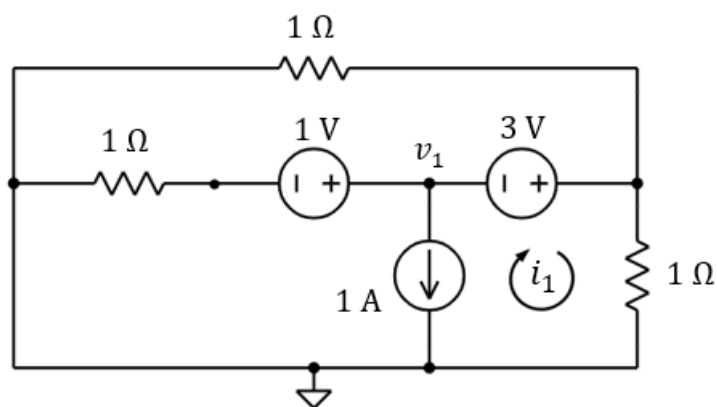- (1) Find the value of **node voltage** v_1 and of **mesh current** i_1 .
You can use any analysis technique you want. (5 points)



v_1

i_1


(2) (5 points)

(a) In circuit (a) below, find the Thevenin equivalent resistance as seen between A and B.


R_{Th}

(b) I attach the load shown in (b) between A and B in the circuit of part (a). What value of R will result in the maximum power being received by this load (i.e., all the resistors of the load combined)?

R

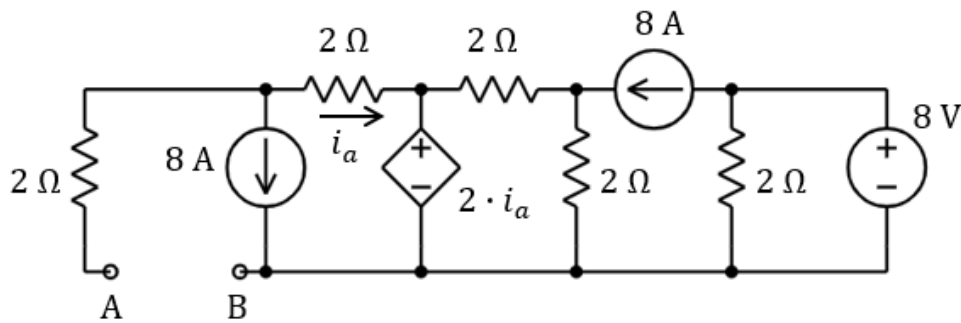

(a)

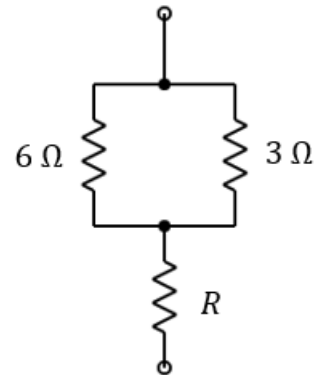

(b)