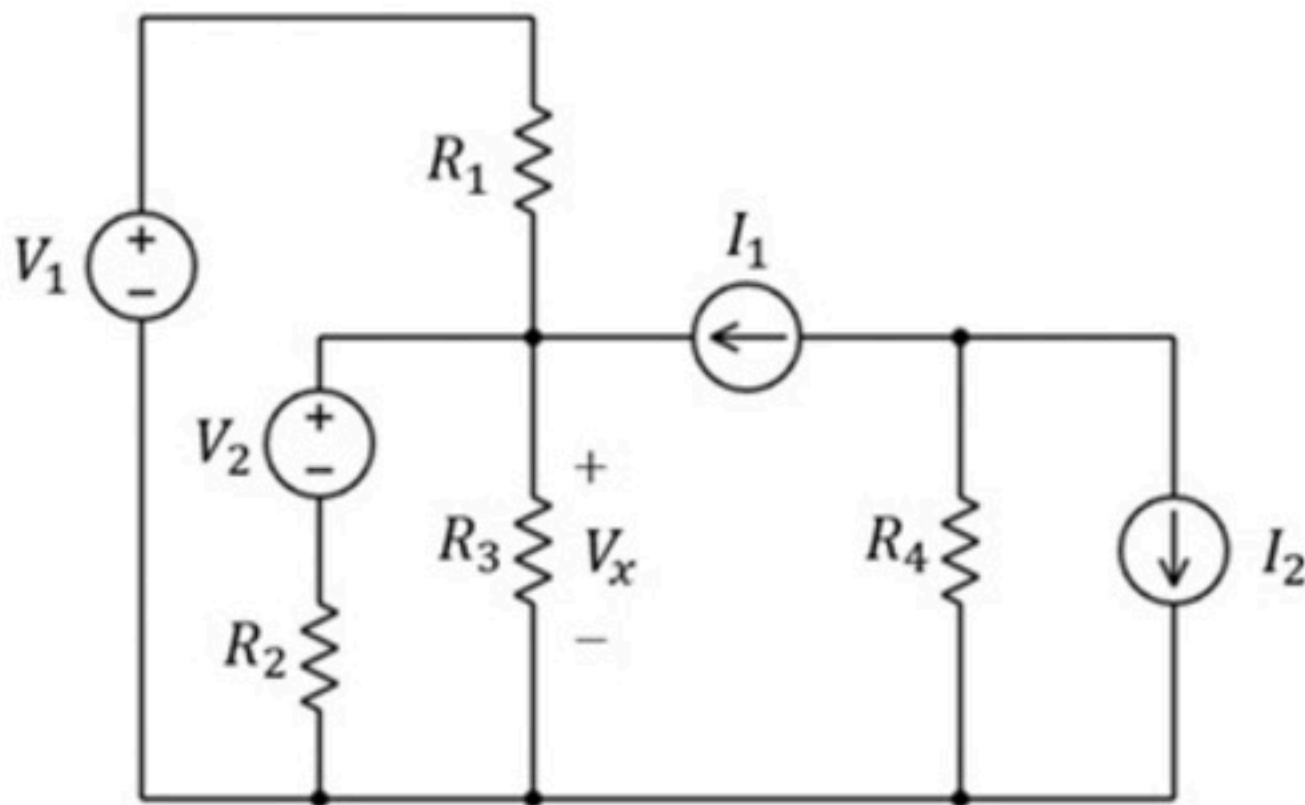


Circuit theorems 015

Problem has been graded.

Consider the circuit below. You are not given the values of V_1 , V_2 and I_2 . However, you are told the values of the other components and that of V_x .

- (a) What is the new value of V_x when all the source values (i.e., V_1 , V_2 , I_1 and I_2) are doubled? We will call this new value V_{x1} .
- (b) What is the new value of V_x when only I_1 is doubled and the other sources are what they were originally? We will call this new value V_{x2} .



Given Variables:

R_1 : 10 ohm

R_2 : 10 ohm

R_3 : 5 ohm

R_4 : 7 ohm

I_1 : 2 A

V_x : 16 V

Calculate the following:


V_{x1} (V) :

V_{x2} (V) :

Hint: Use linearity and superposition to express V_x as a linear combination of all sources

Consider the circuit below. You are not given the values of V_1 , V_2 and I_2 . However, you are told the values of the other components and that of V_x .

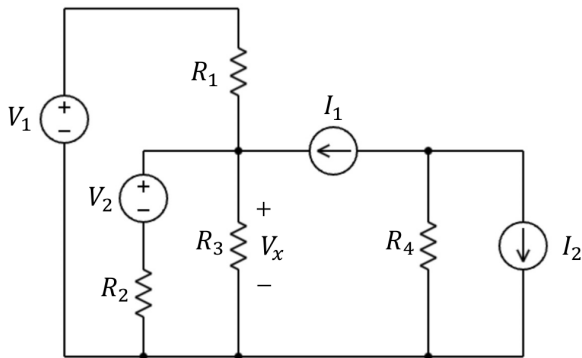- (a) What is the new value of V_x when all the source values (i.e., V_1 , V_2 , I_1 and I_2) are doubled? We will call this new value V_{x1} .
- (b) What is the new value of V_x when only I_1 is doubled and the other sources are what they were originally? We will call this new value V_{x2} .



$$R_1 = 15\Omega$$

$$R_2 = 5\Omega$$

$$R_3 = 15\Omega$$

$$R_4 = 7\Omega$$

$$I_1 = 2A$$

$$V_x = 15$$

a. Generally,

$$V_x = aV_1 + bV_2 + cI_1 + dI_2 \quad \text{from linearity and superposition}$$

If all sources are doubled,

$$\begin{aligned} V_{x1} &= a(2V_1) + b(2V_2) + c(2I_1) + d(2I_2) = 2(aV_1 + bV_2 + cI_1 + dI_2) \\ &= 2V_x \\ &= 2 \cdot 15 \end{aligned}$$


$$\boxed{V_{x1} = 30V}$$

b. If only I_1 is doubled

$$\begin{aligned} V_{x2} &= aV_1 + bV_2 + c(2I_1) + dI_2 = (aV_1 + bV_2 + cI_1 + dI_2) + cI_1 \\ &= V_x + cI_1 \end{aligned}$$

find the contribution of I_1 using superposition

When only I_1 is on,

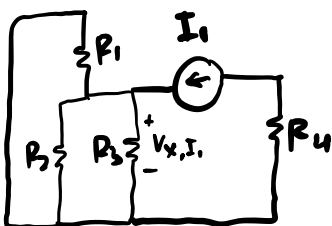

$$V_{x,I_1} = I_1 \left(\frac{R_1 // R_2}{R_1 // R_2 + R_3} \right) R_3$$

$$\begin{aligned} V_{x,I_1} &= 2 \left(\frac{\frac{15}{4}}{\frac{15}{4} + 15} \right) 15 \\ &= 2 \left(\frac{15}{15 + 60} \right) 15 \\ &= 2 \cdot \frac{1}{5} \cdot 15 \\ &= 6V \Rightarrow cI_1 \end{aligned}$$

$$\begin{aligned} V_{x2} &= V_x + cI_1 \\ &= 15 + 6 \end{aligned}$$

$$\boxed{V_{x2} = 21V}$$