

ECE 65: Components & Circuits Lab

Lecture 7

Diode waveform shaping circuits

Clipper circuits


Reference notes: sections 2.9

Sedra & Smith (7th Ed): sections 4.4-4.6

Saharnaz Baghdadchi



Course map

2. Diodes


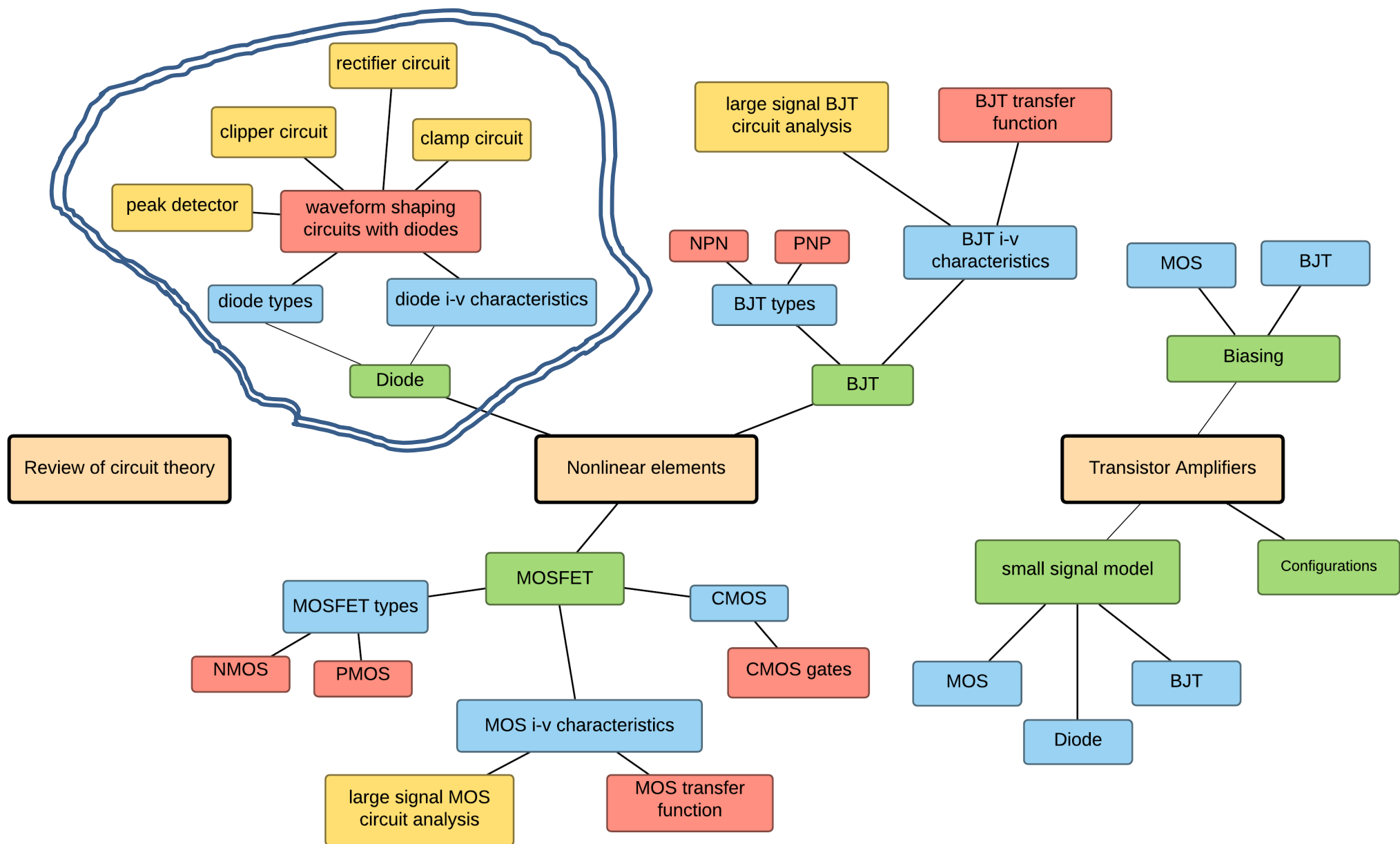


Rectifier & clipper circuits

Half-wave Rectifier

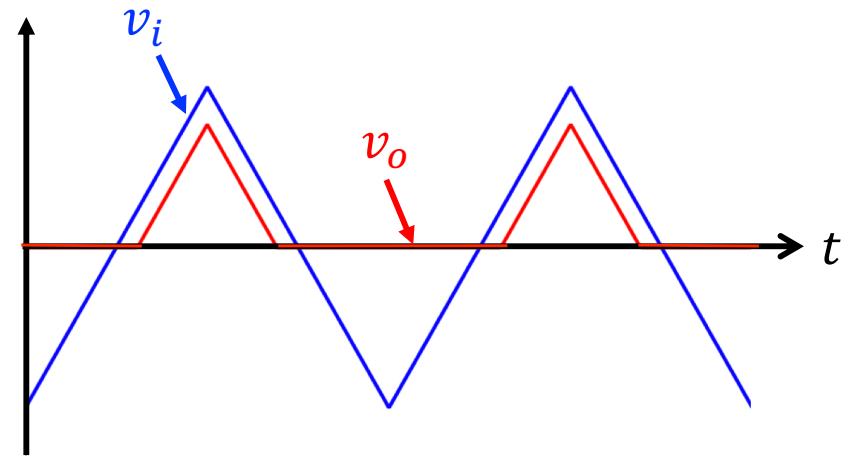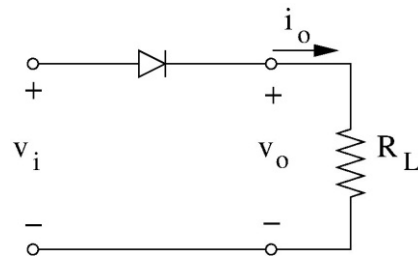

Clipper

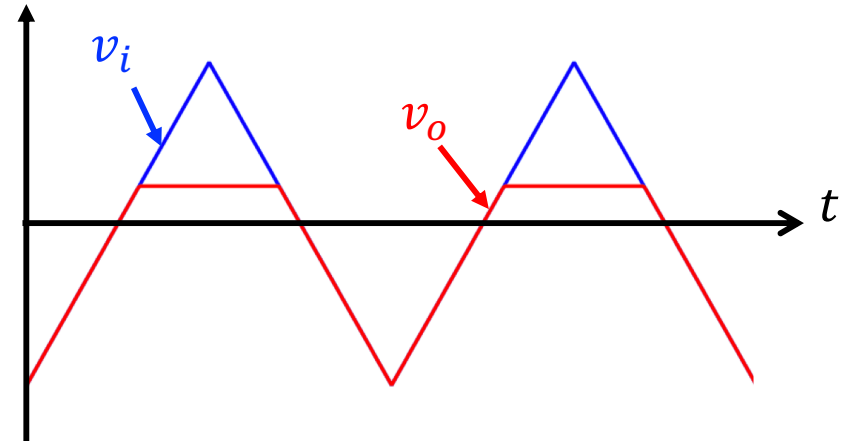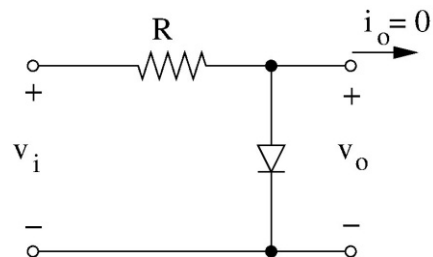


Clipper or Limiter Circuit

$$\text{KVL: } v_i = v_R + v_D \quad \checkmark$$

$$\text{KVL: } v_o = v_D \quad \checkmark$$

$$\text{Ohm's law: } i_D = v_R / R$$

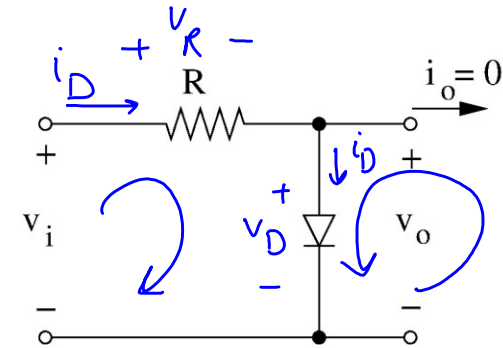

$$-v_o + v_D = 0$$

$$v_o = v_D$$

Diode OFF: $i_D = 0$ & $v_D < V_{D0}$

$$v_i = v_R + v_D = v_R + v_o = R \times i_D + v_o \rightarrow v_i = v_o$$

$$v_i = v_R + v_D \rightarrow v_i = v_D < V_{D0} \rightarrow v_i < V_{D0}$$

Diode ON: $v_D = V_{D0}$ & $i_D \geq 0$

$$v_o = v_D = V_{D0}, \quad v_o = V_{D0}$$



$$i_D = \frac{v_i - V_{D0}}{R} \geq 0 \rightarrow v_i \geq V_{D0}$$

Clipper Circuit




open loop transfer function

Transfer Function is non-linear:





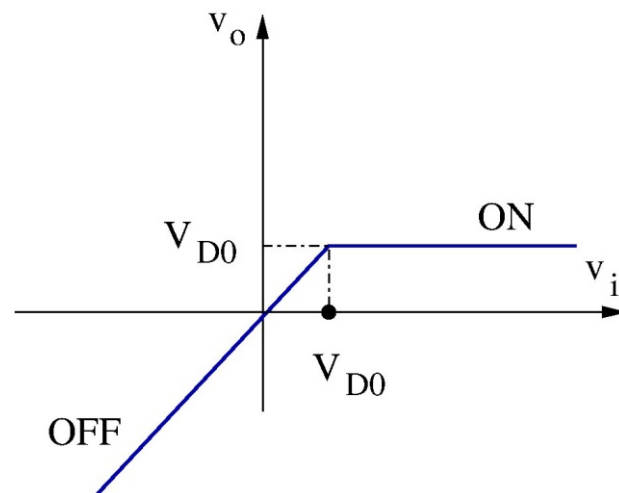
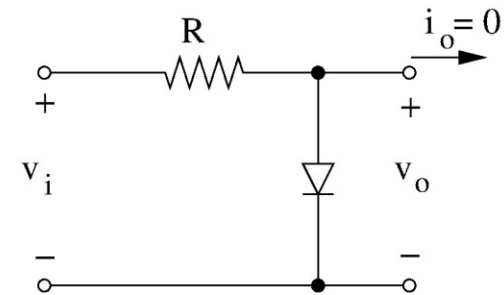
$$\left\{ \begin{array}{ll} \text{For } v_i \geq V_{D0}, & v_o = V_{D0} \quad (\text{Diode is ON}) \\ \text{For } v_i < V_{D0}, & v_o = v_i \quad (\text{Diode is OFF}) \end{array} \right.$$



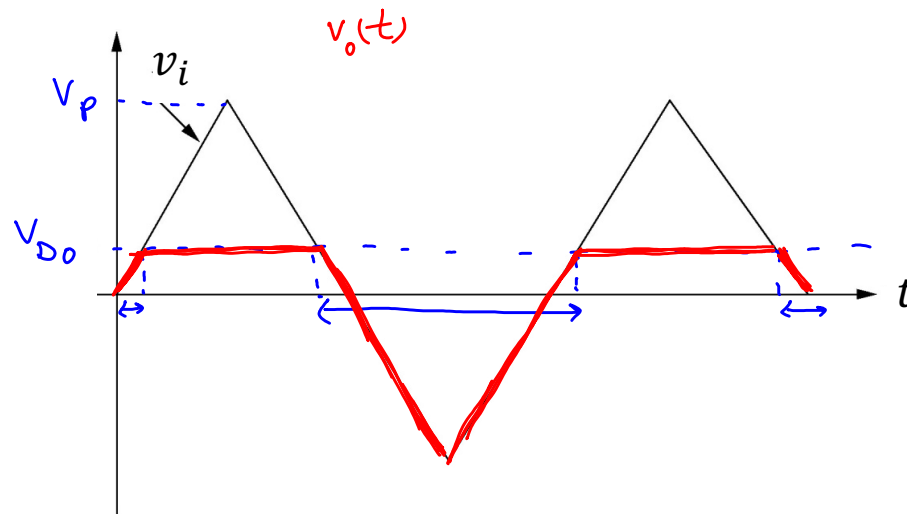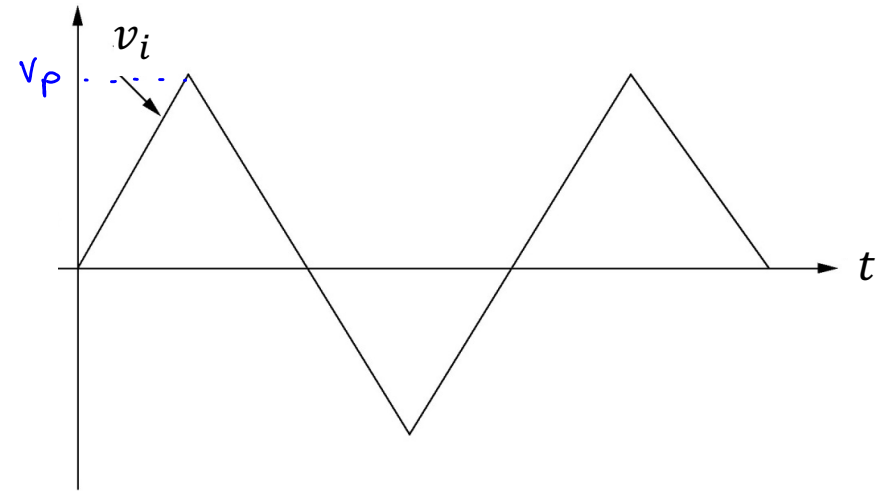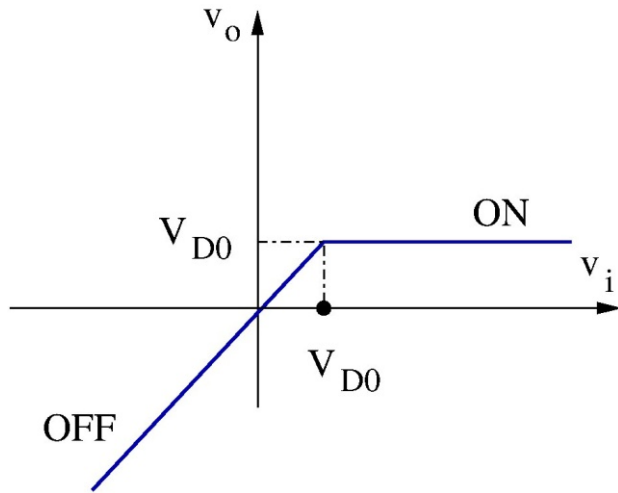Clipper Circuit: example input-output waveforms



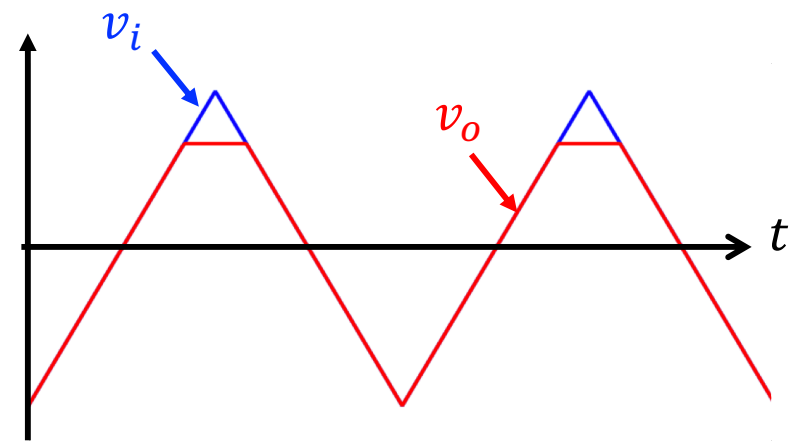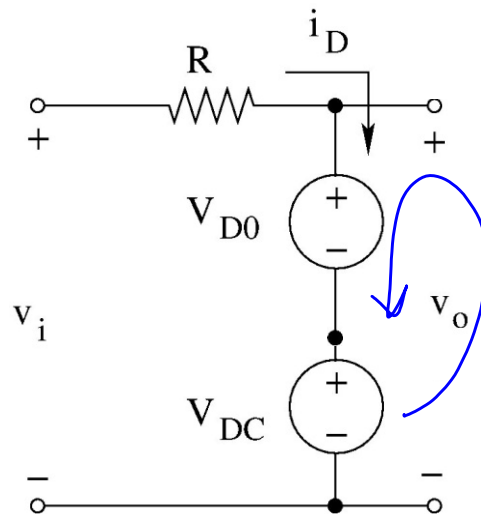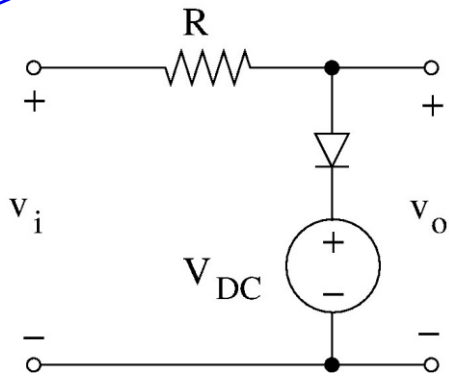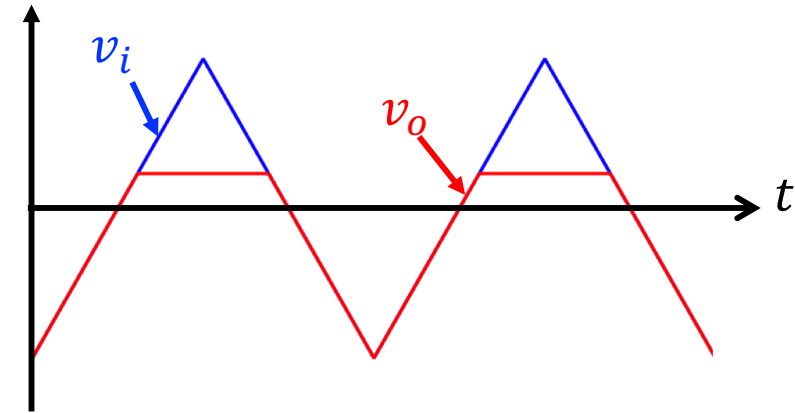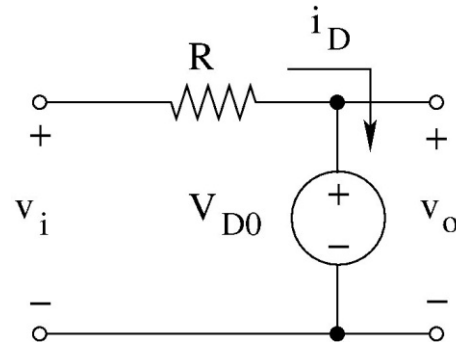
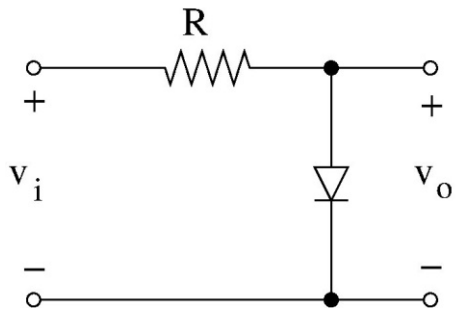
Adjusting the limiting voltage in the clipper circuit



$$v_o = v_{D0} + v_{DC}$$

Using Zener diodes to adjust the limiting voltage in the clipper circuit

v_o limited to $\leq V_{D0} + V_Z$

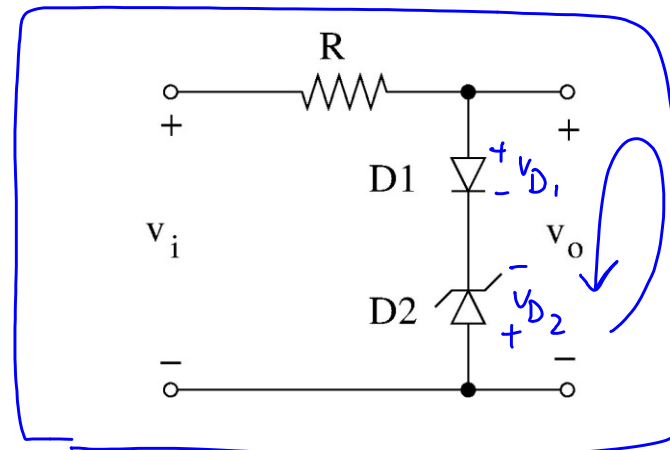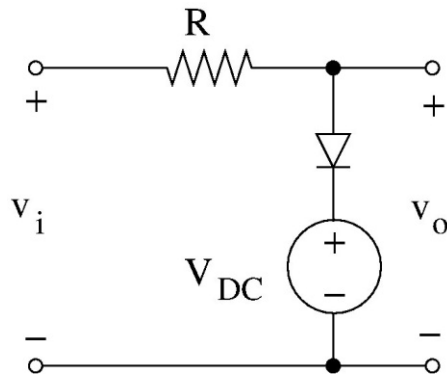

D_1 is ON
 D_2 is Zener


$$v_{D1} = v_{D0}$$

$$v_{D2} = -V_Z$$

$$v_o = v_{D1} - v_{D2}$$


$$v_o = v_{D0} + V_Z$$

v_o limited $\geq -V_{D0} - V_Z$

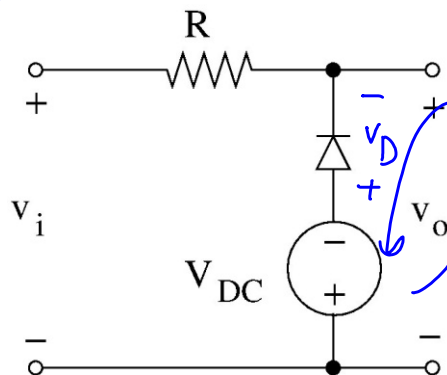

$$v_o = -v_D - V_{DC}$$

$$v_o = -v_{D0} - V_{DC}$$

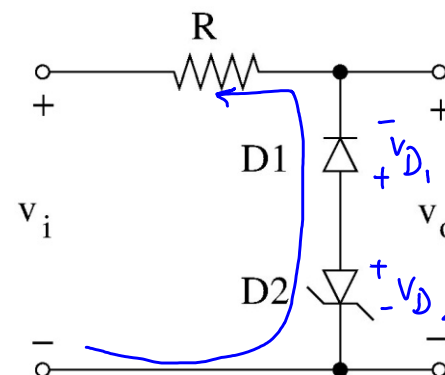

$$v_{D1} = v_{D0}$$



$$v_{D2} = -V_Z$$

$$v_o = -v_{D0} - V_Z$$


$$v_o = -v_{D1} + v_{D2}$$

Clipping both the top & bottom portions of the signal simultaneously

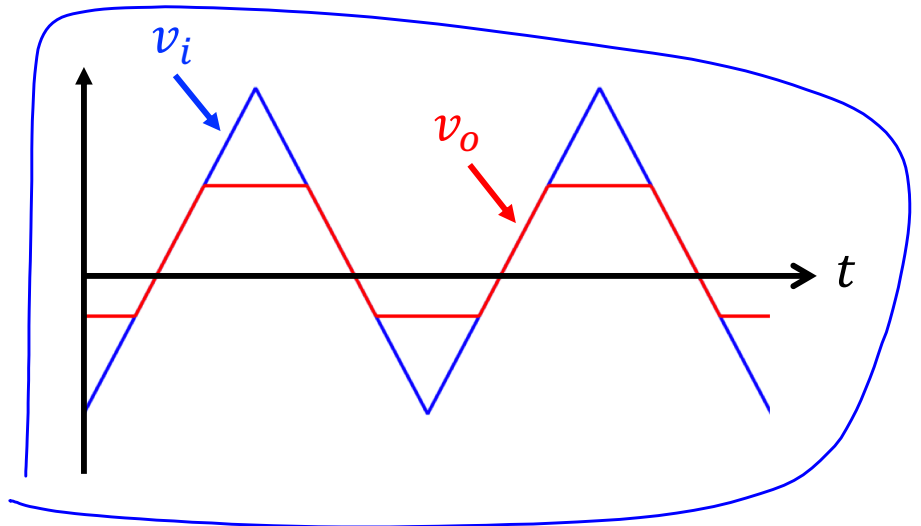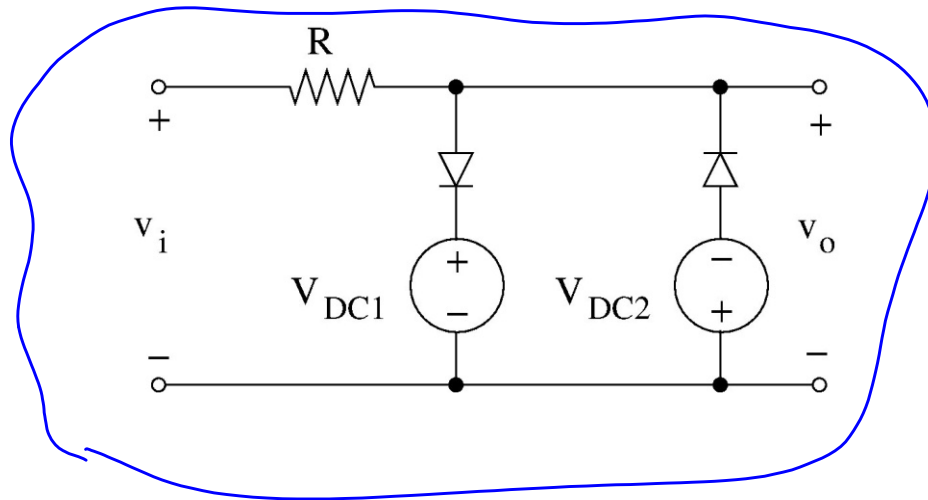v_o limited to $\leq V_{D0} + V_{DC1}$ and $\geq -V_{D0} - V_{DC2}$





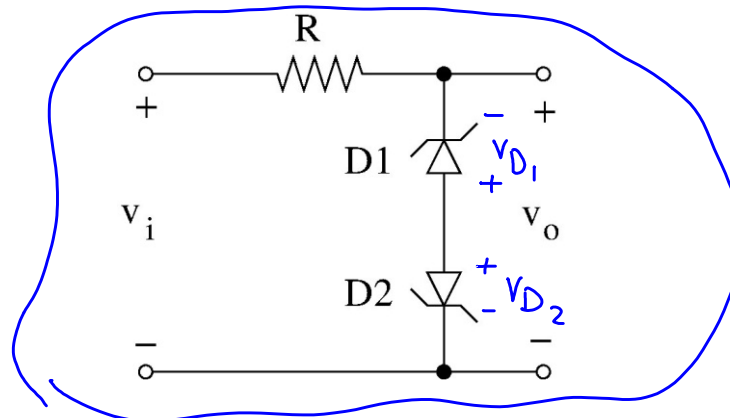v_o limited to $\leq V_{D0} + V_{Z1}$ and $\geq -V_{D0} - V_{Z2}$




Lecture 7 reading quiz

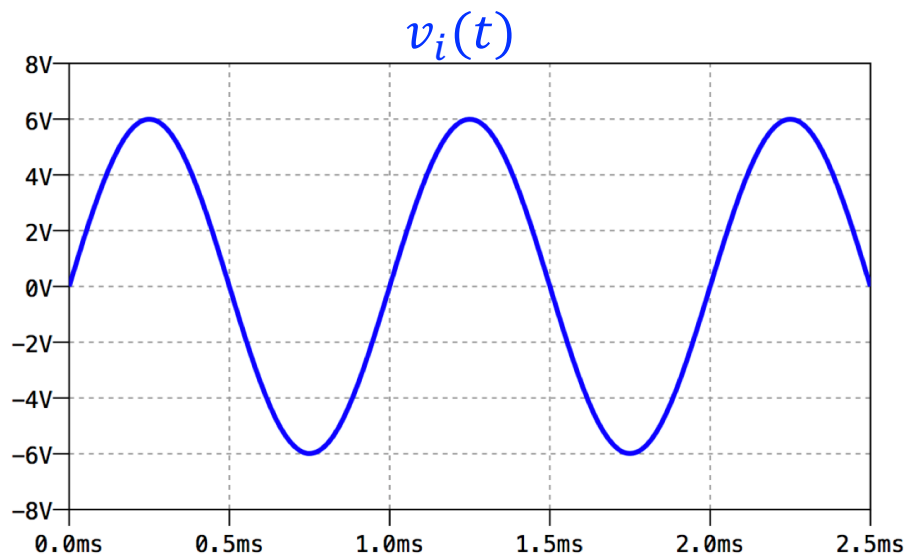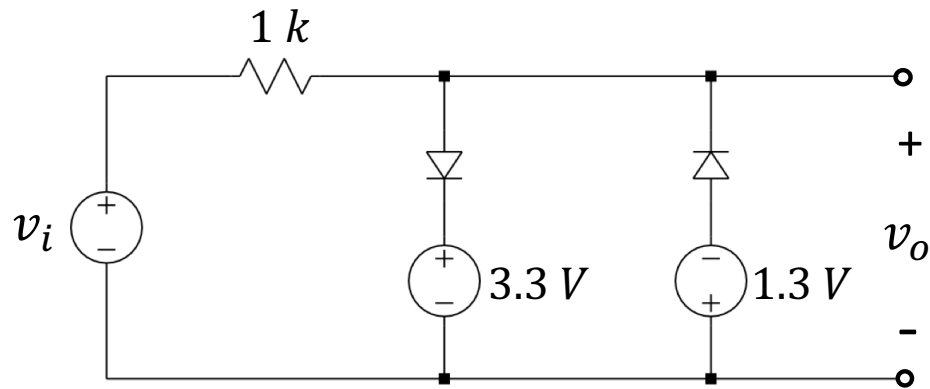Calculate and draw the output of the following two-port network for the given input signal.




Clicker question 1

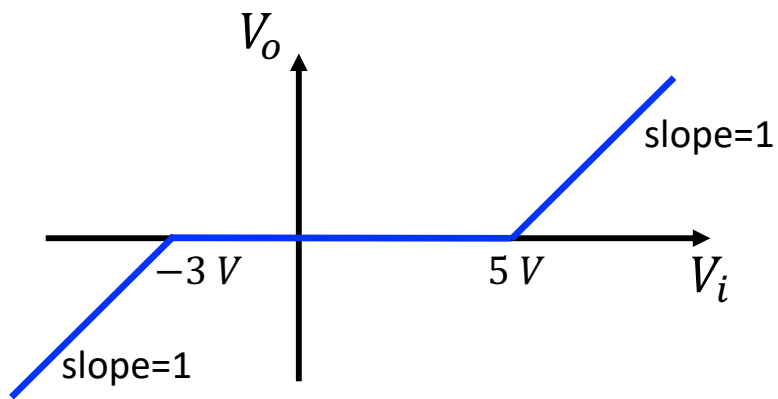
Which one of the waveforms could be the output of a two-port network with the below transfer function for the input $v_i(t) = 2\sin(\omega t)$?




A.

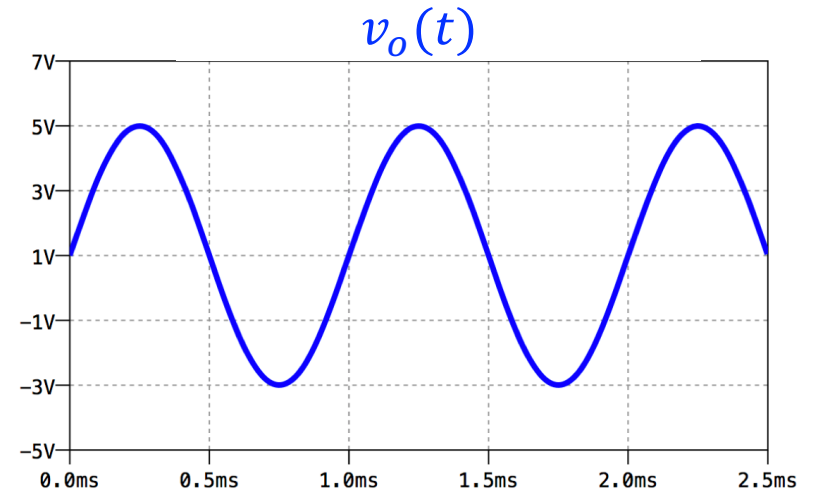

B.

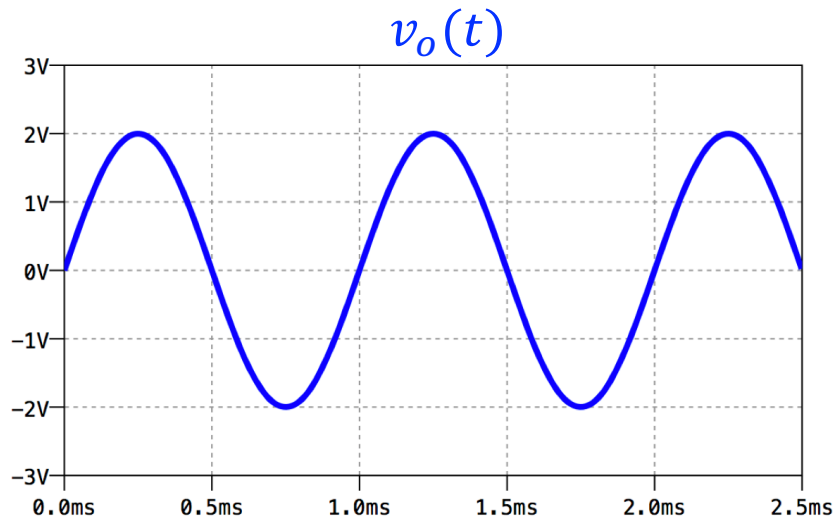


C.

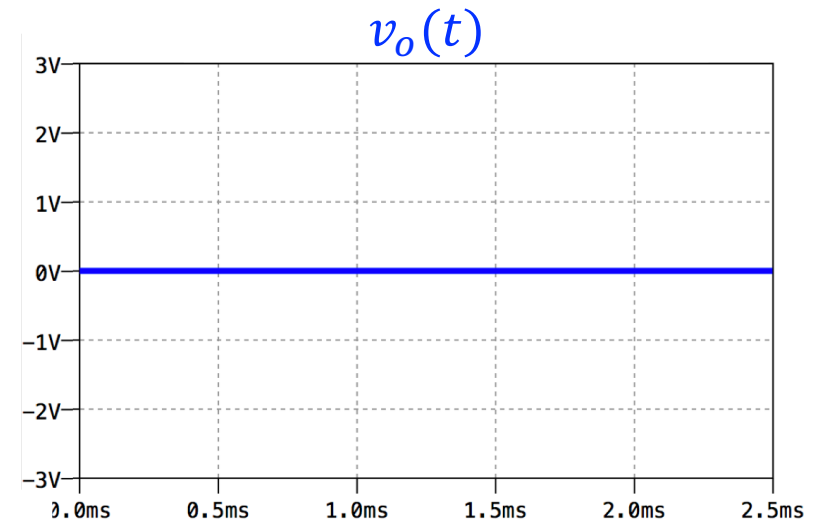

Clicker question 1


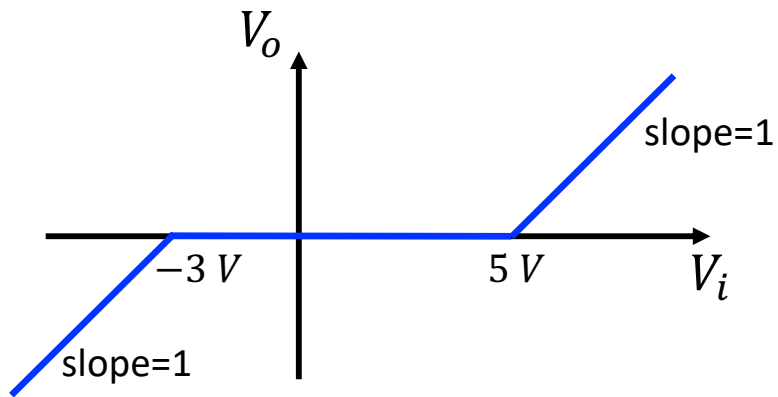
Which one of the waveforms could be the output of a two-port network with the below transfer function for the input $v_i(t) = 2\sin(\omega t)$?



- Looking at the transfer characteristic graph, for what range of V_i values, will the output be equal to zero?
- What is the range of V_i values for the given input signal?

Discussion question 1.

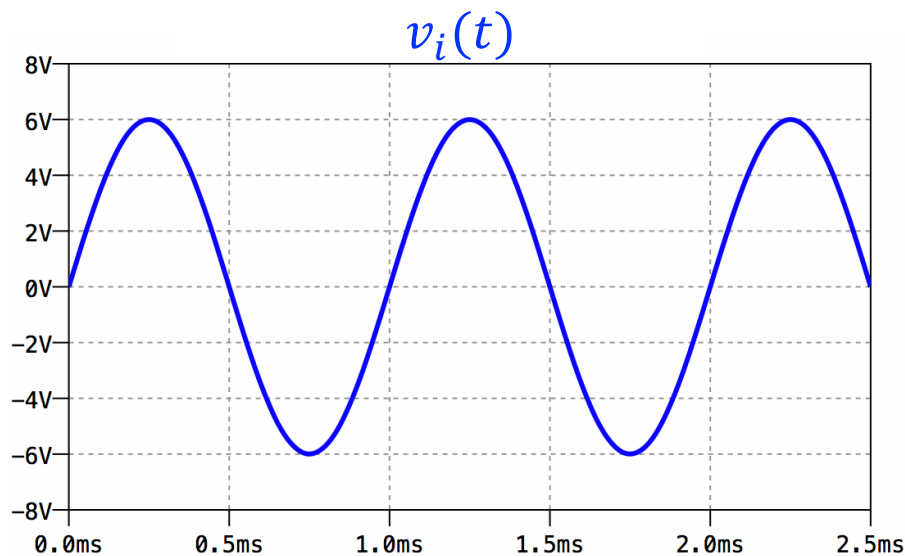
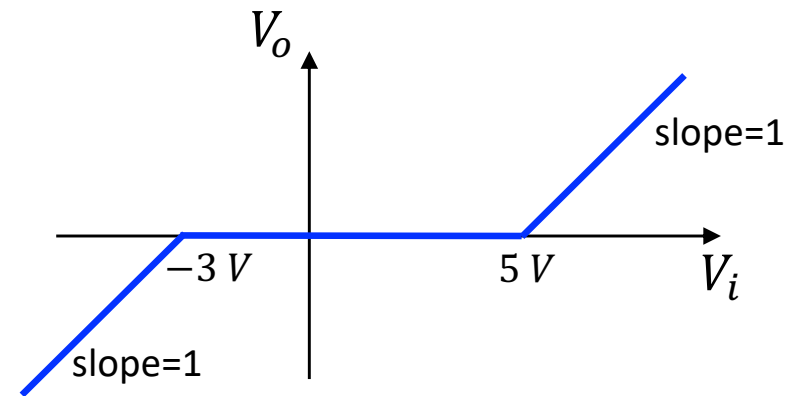
Draw the output of a two-port network with the shown transfer function to the below input signal.



Discussion question 1.

Draw the output of a two-port network with the shown transfer function to the below input signal.

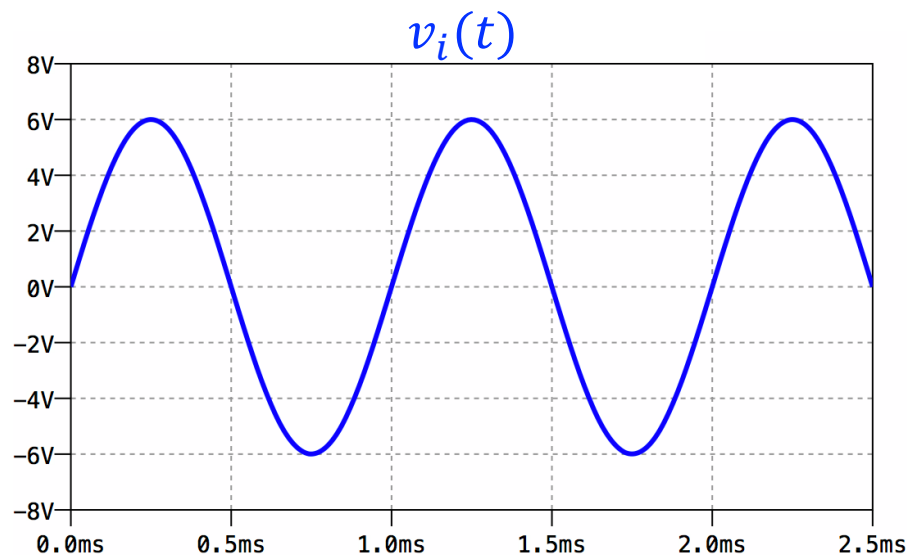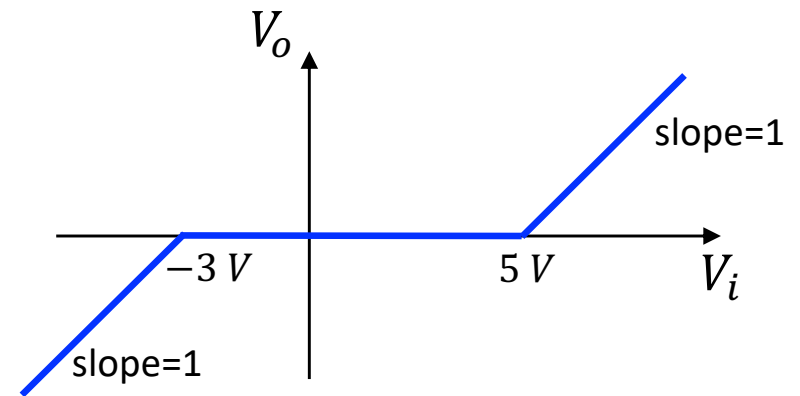
- Write the equation of a line that relates V_o to V_i when V_i is greater than 5V?
- Write the equation of a line that relates V_o to V_i when V_i is less than -3V?
- On the graph of $v_i(t)$, find and label when v_i is less than -3, greater than 5, and in between. Follow the V_i vs. V_o equations that you found and draw $v_o(t)$.



Discussion question 2

Calculate and draw the transfer function for the following two-port network.


$$(V_{D0} = 0.7V)$$

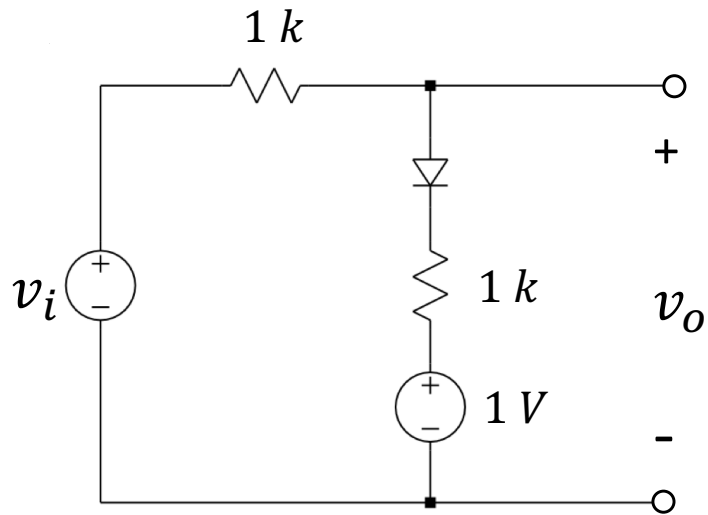

Discussion question 2

Calculate and draw the transfer function for the following two-port network.

$$(V_{D0} = 0.7V)$$

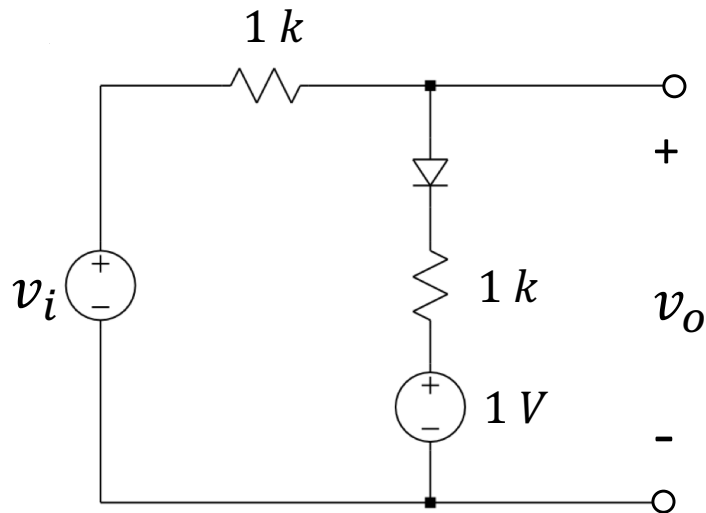

- Label the diode voltage and current.
- List the cases of operation of the diode. You have two cases in this circuit.
- You need to find the range of v_i values for each case and the relationship between v_i and v_o for each case.
- Use KVL to complete the above task.
- Using the ranges of v_i and the relationship between V_i and V_o for each range, draw the transfer function or transfer characteristic graph, which is a graph showing the relationship between V_o and V_i .