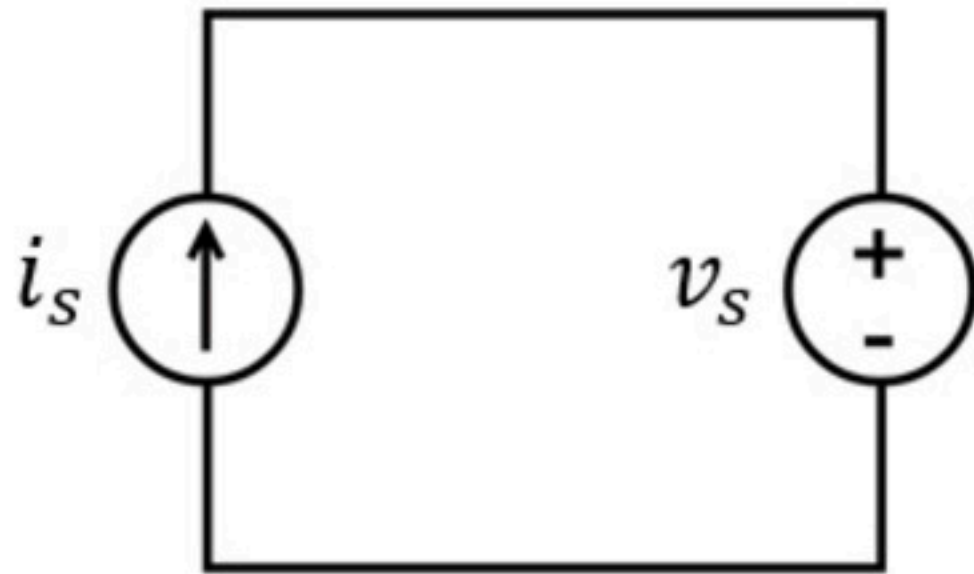


# Basic concepts 007

Problem has been graded.

Find the power  $P_1$  supplied by the current source and the power  $P_2$  supplied by the voltage source.



Given Variables:

$v_s$  : 10 V

$i_s$  : 6 A

Calculate the following:

$P_1$  (W) :

$P_2$  (W) :

Hint: The voltage across a current source can be non-zero