

PP AC power 006

Unlimited Attempts.

$$v_S(t) = 10\sqrt{2} \cdot \cos\left(10^6 t + \frac{\pi}{6}\right) \text{ V}$$


Find the average power P_1 supplied by the source v_S .

Find the average power P_2 received by the $5\ \Omega$ resistor.

Find the average power P_3 received by the $4\ \Omega$ resistor.

Find the average power P_4 received by the capacitor.

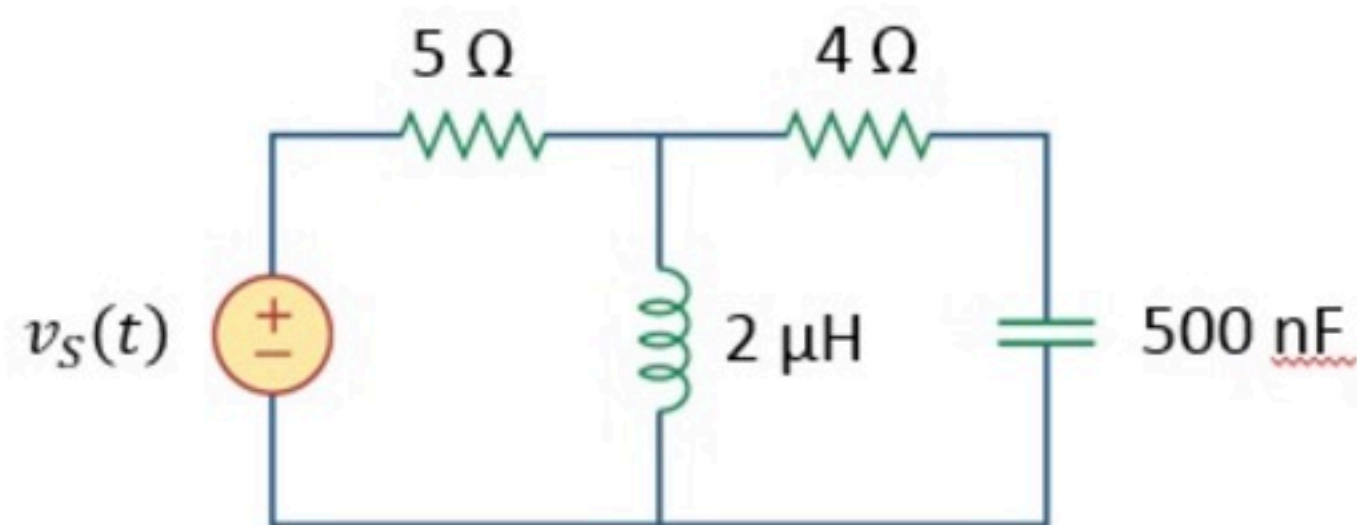Find the average power P_5 received by the inductor.



Given Variables:

. . .

Calculate the following:

P1 (W) :

15



P2 (W) :

12.5



P3 (W) :

2.5



P4 (W) :

0



P5 (W) :

0



Hint: Find S first for each element. Keep V_s algebraic. Can you predict P for the cap and inductor? Check.