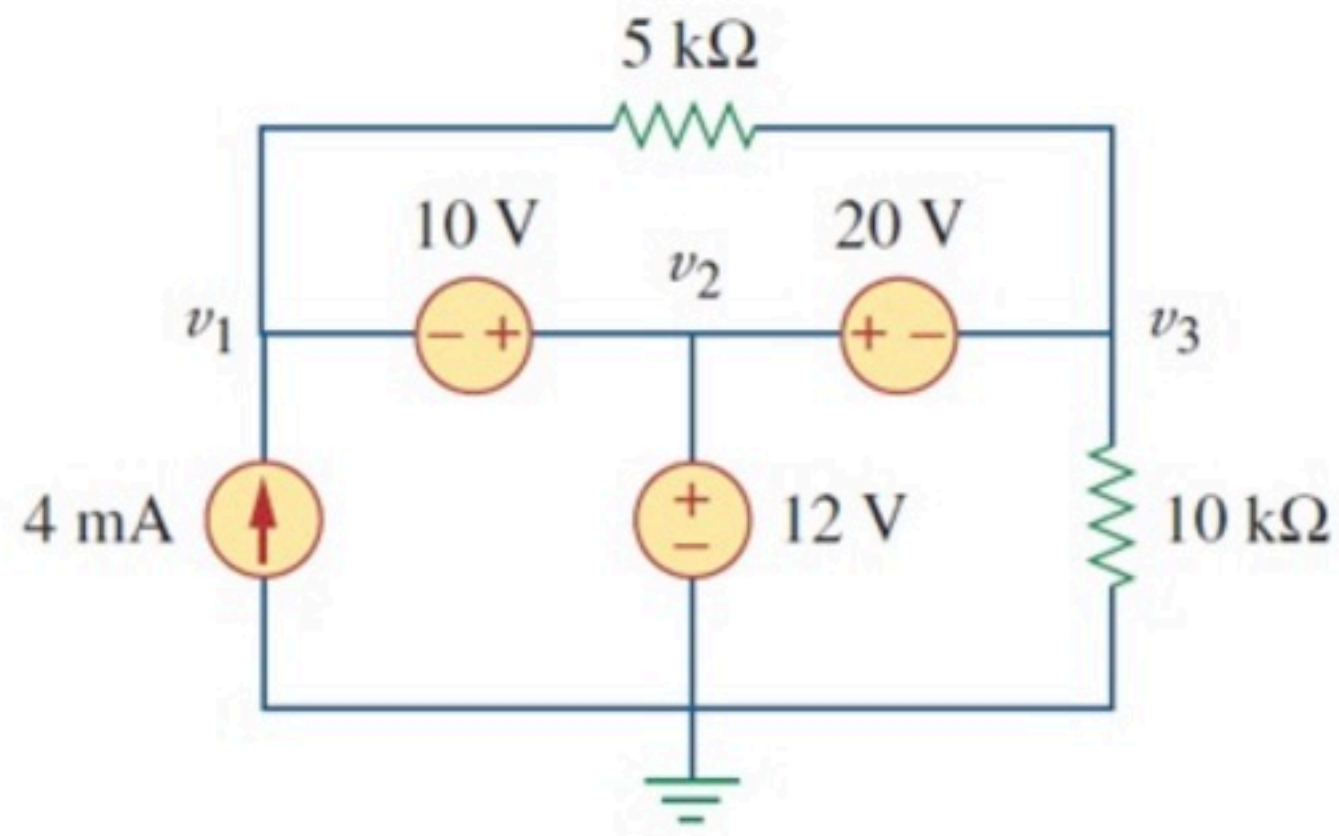


PP - Nodal Mesh 009

Problem has been graded.

Find v_1 , v_2 and v_3 . Solve using nodal analysis.

For extra practice: Afterwards solve again using mesh analysis.



Given Variables:

...

Calculate the following:

v_1 (V) :

2



v_2 (V) :

12



v_3 (V) :

-8



Hint: Check the V-sources