

ECE 65: Components & Circuits Lab

Lecture 20

Transistor Amplifier Biasing


Reference notes: sections 5.3

Sedra & Smith (7th Ed): sections 7.4



Saharnaz Baghdadchi

Course map

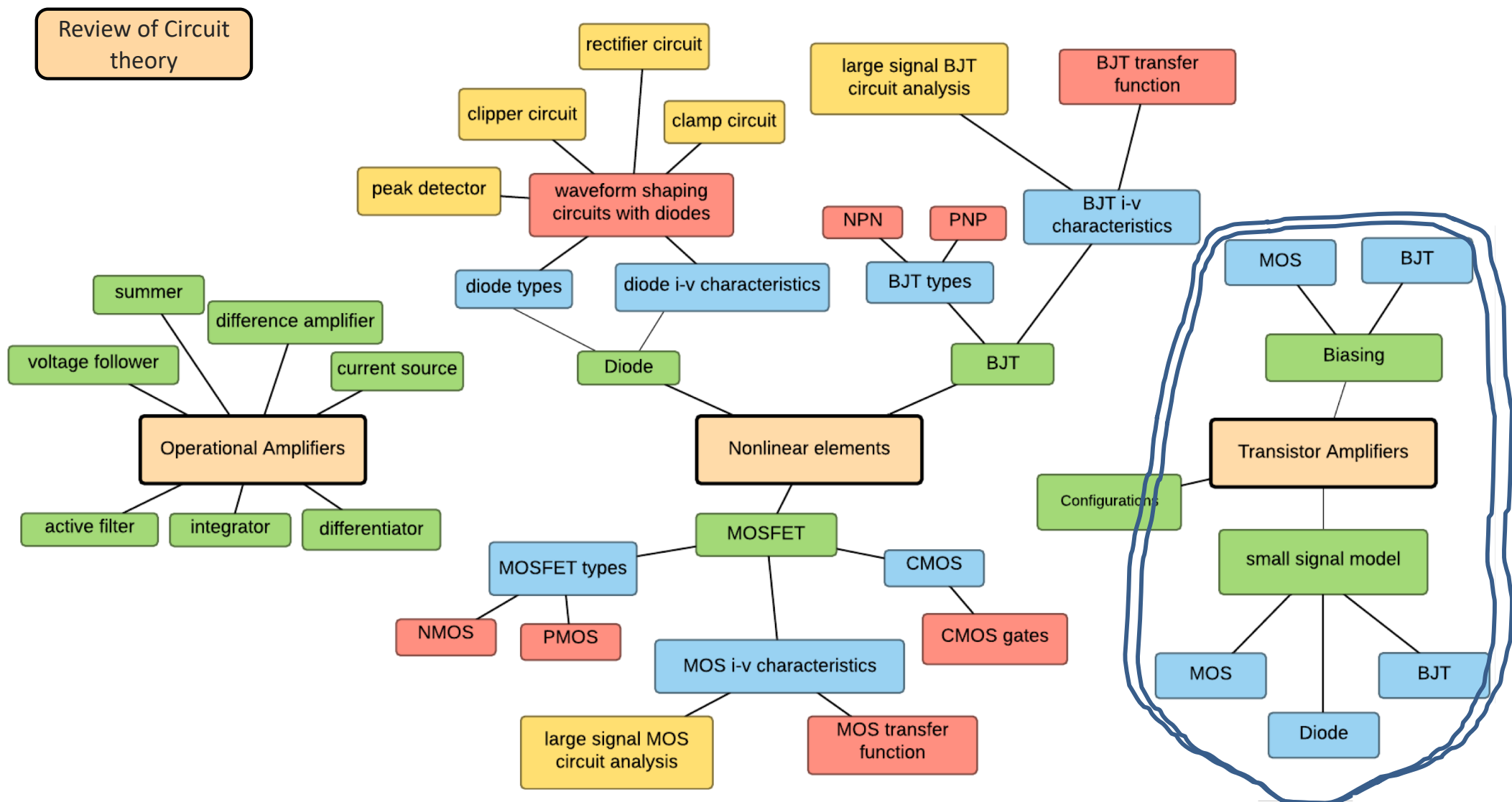6. Transistor Amplifiers – Bias and small signal




How to establish a Bias point

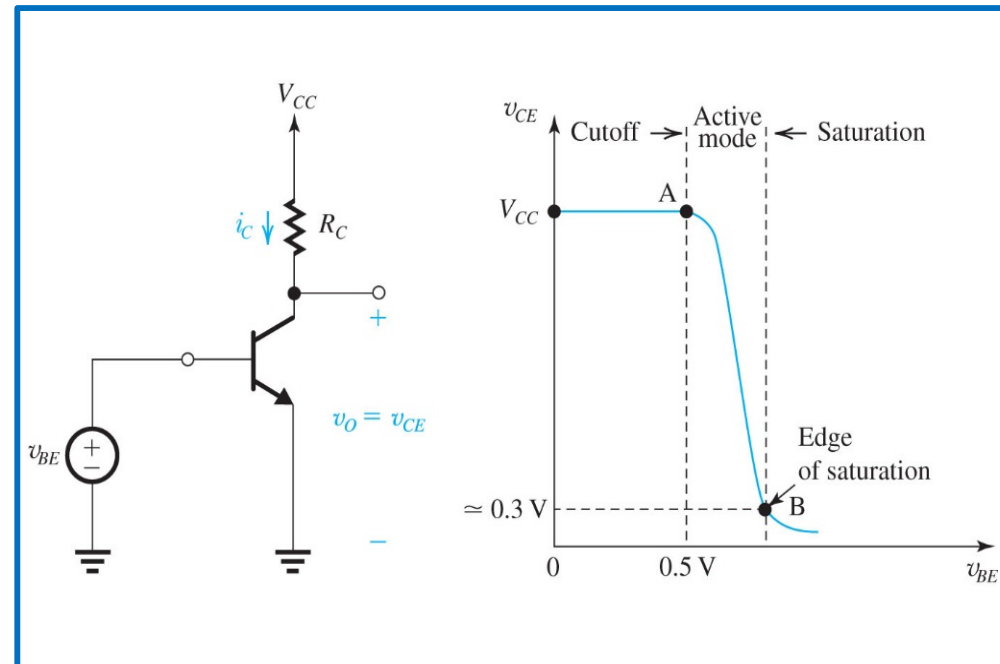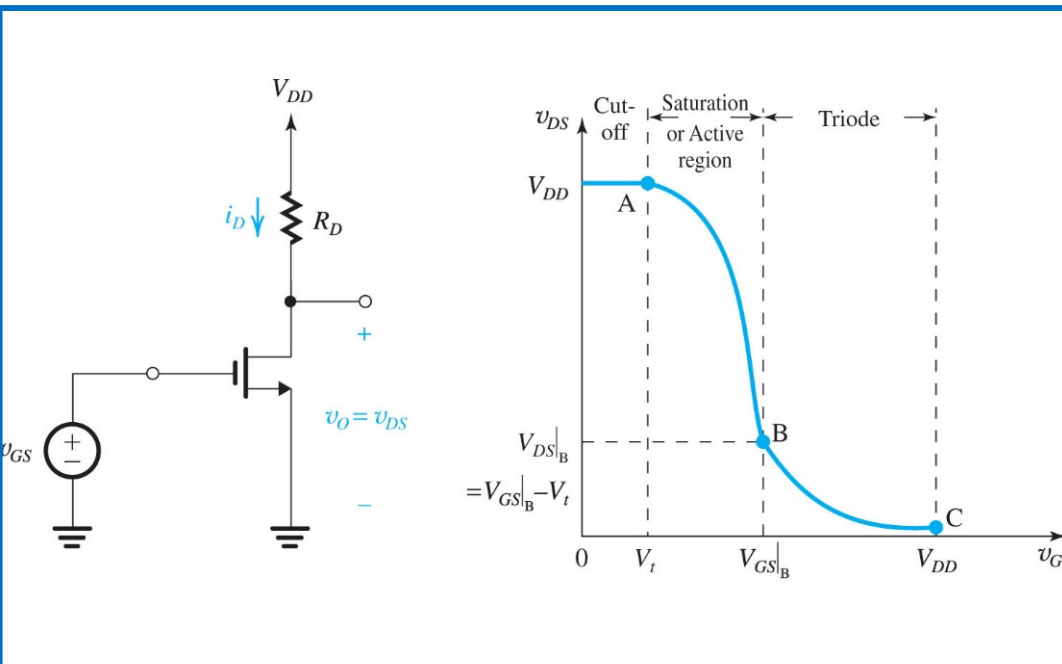

- Stable and robust bias point should be predictable and insensitive to variations in temperature and to the manufacturing variability in the transistor parameter values such as V_t , μ_n , C_{ox} , (W/L) and β .
- Bias point details impact the small signal response (e.g., gain of the amplifier).

BJT Fixed Bias

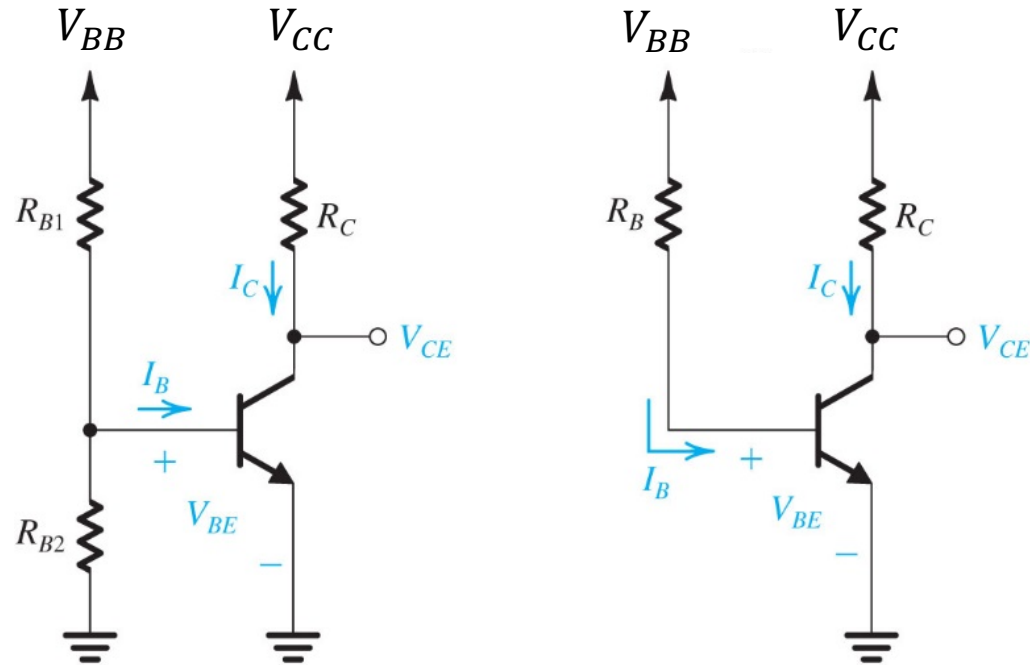


BE KVL: $V_{BB} = I_B R_B + V_{BE}$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} \quad , \quad I_C = \beta I_B = \beta \frac{V_{BB} - V_{BE}}{R_B}$$

CE KVL: $V_{CC} = I_C R_C + V_{CE}$

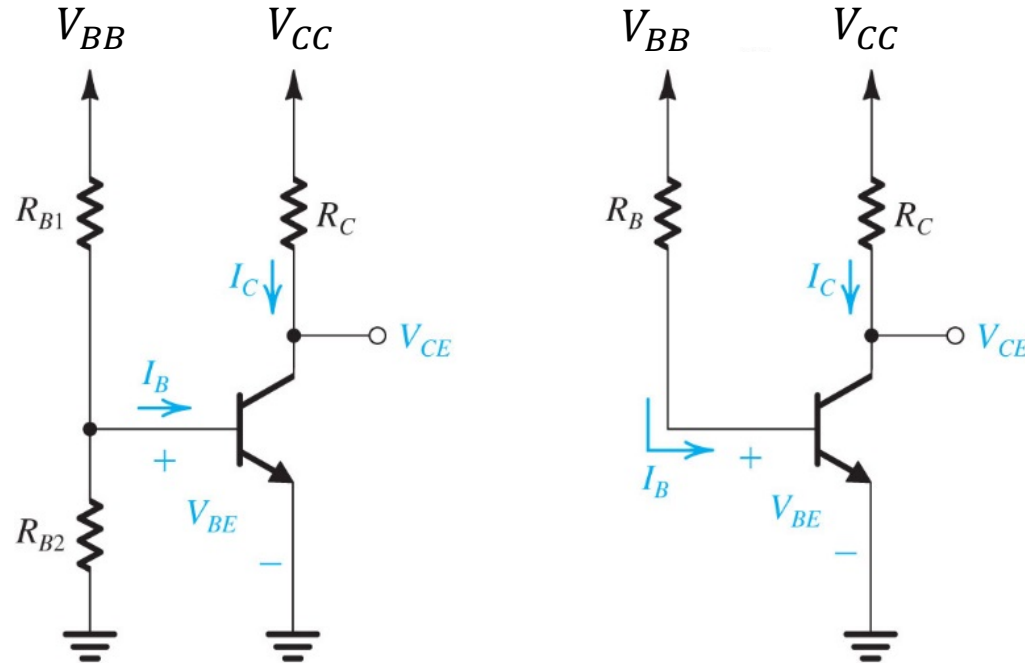Why biasing with base voltage (fixed bias) does not work?



Changes in BJT β or V_{BE} values, changes the bias point drastically.

- BJT can end up in saturation or in cut-off easily.

To operate a BJT in the active region, $I_C > 0$, $V_{CE} > V_{D0}$

Biasing with Emitter Degeneration

Requires a resistor in the emitter circuit!

BE KVL: $V_{BB} = I_B R_B + V_{BE} + I_E R_E$

$$V_{BB} - V_{BE} = I_E \left(\frac{R_B}{\beta + 1} + R_E \right)$$


If $R_B \ll (\beta + 1)R_E$

$$V_{BB} - V_{BE} \approx I_E R_E$$

$$I_E \approx I_C \approx \frac{V_{BB} - V_{BE}}{R_E}$$




I_C is independent of β

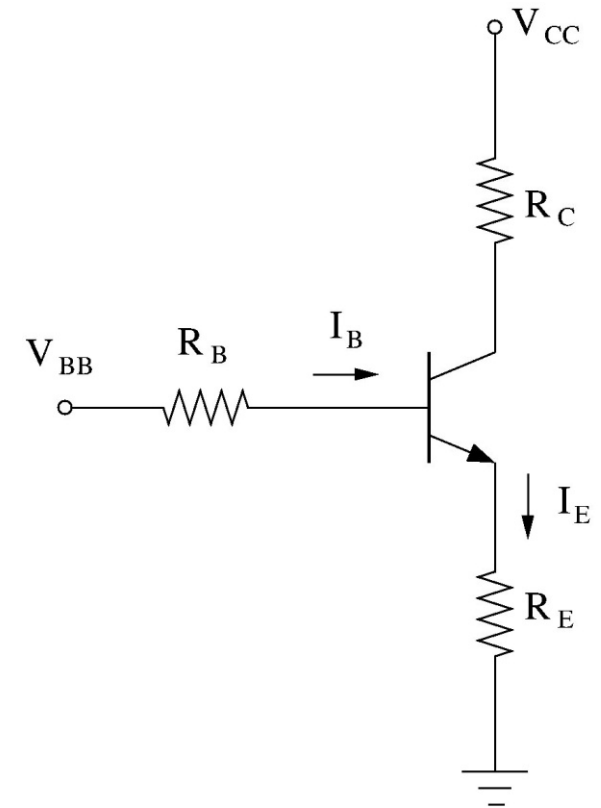

Emitter resistor provides negative feedback!

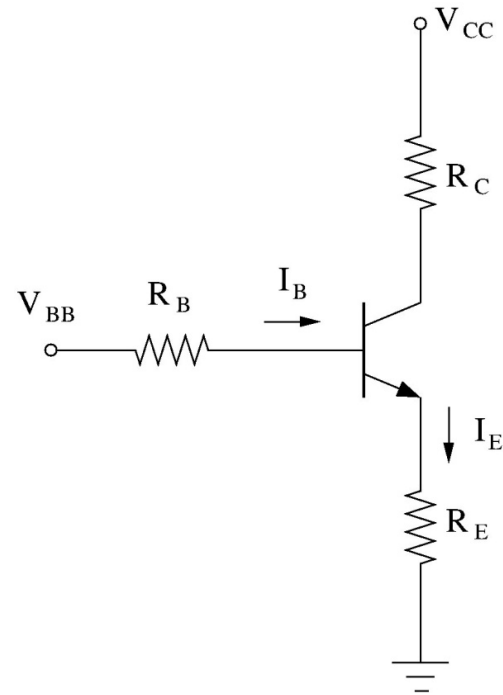
$$\left\{ \begin{array}{l} V_{BB} - V_{BE} \approx I_E R_E \\ I_C \propto e^{V_{BE}/V_T} \end{array} \right.$$



Negative Feedback:


- If $I_C \approx I_E \uparrow$ (because $\beta \uparrow$), $\xrightarrow{\text{BE-KVL}} V_{BE} \downarrow \xrightarrow{\text{BE junction}} I_C \approx I_E \downarrow$
- If $I_C \approx I_E \downarrow$ (because $\beta \downarrow$), $\xrightarrow{\text{BE-KVL}} V_{BE} \uparrow \xrightarrow{\text{BE junction}} I_C \approx I_E \uparrow$

Emitter-degeneration bias circuits

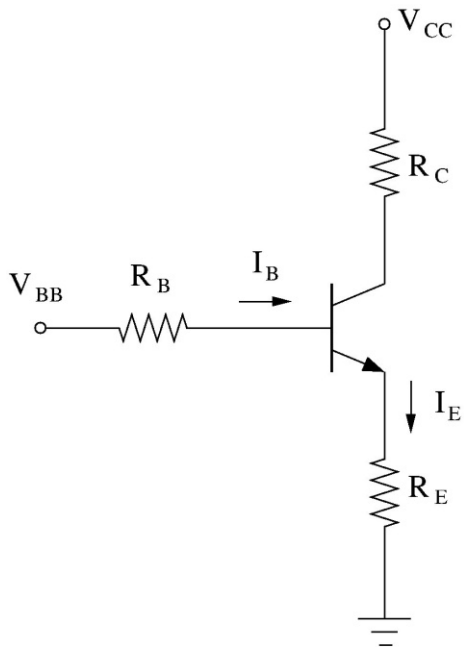


Basic Arrangement

$$V_{BB} = I_B R_B + V_{BE} + I_E R_E$$

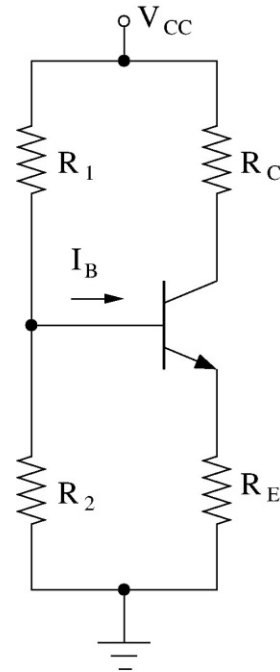

**Bias with one power supply
(voltage divider)**

$$V_{BB} = I_B R_B + V_{BE} + I_E R_E$$

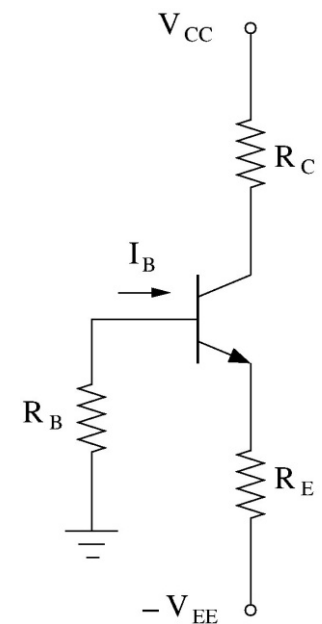


Bias with two power supplies

$$V_{EE} = I_B R_B + V_{BE} + I_E R_E$$

MOS Fixed Bias

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$V_{DS} = V_{DD} - I_D R_D$$

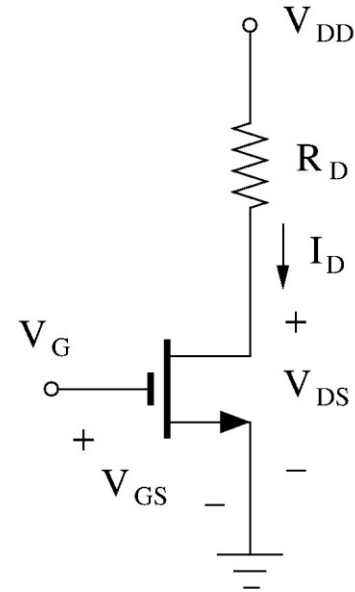


This method is NOT desirable as $\mu_n C_{ox} (W/L)$ and V_t vary widely among devices of the same manufacturer's part number.

Bias point (i.e., I_D and V_{DS}) can change drastically due to temperature and/or manufacturing variability.

MOS bias with Source Degeneration

(Resistor R_S provides negative feedback!)

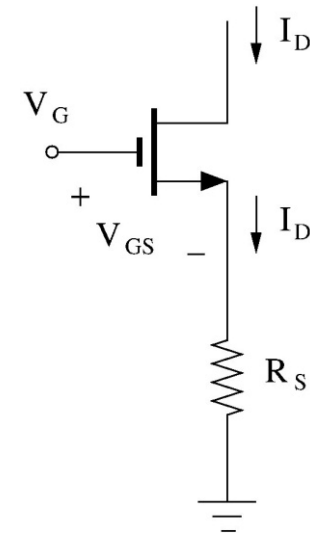
$$\left\{ \begin{array}{l} V_{GS} = V_G - I_D R_S \\ I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2 \end{array} \right.$$



Negative Feedback:


- If $I_D \uparrow$ (because $\mu_n C_{ox} (W/L) \uparrow$ or $V_t \downarrow$) $\xrightarrow{\text{GS KVL}}$ $V_{GS} \downarrow \xrightarrow{I_D \text{ Eq.}}$ $I_D \downarrow$
- If $I_D \downarrow$ (because $\mu_n C_{ox} (W/L) \downarrow$ or $V_t \uparrow$) $\xrightarrow{\text{GS KVL}}$ $V_{GS} \uparrow \xrightarrow{I_D \text{ Eq.}}$ $I_D \uparrow$

Source-degeneration bias circuits

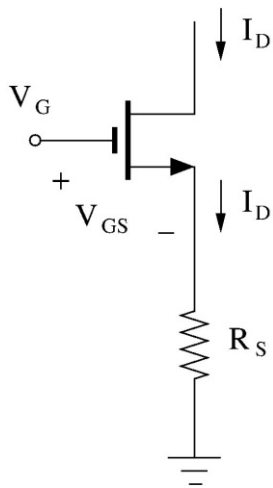


Basic Arrangement

$$V_G = V_{GS} + I_D R_S$$

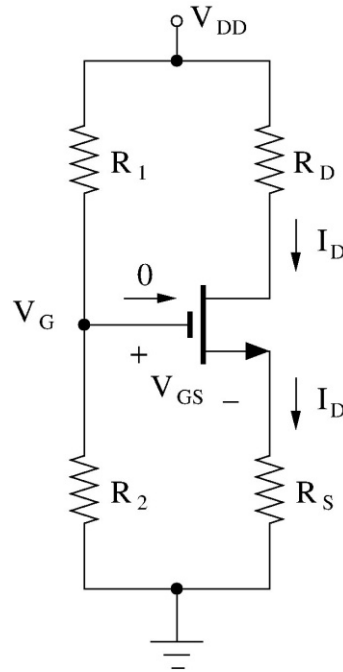

**Bias with one power supply
(voltage divider)**

$$V_G = V_{GS} + I_D R_S$$

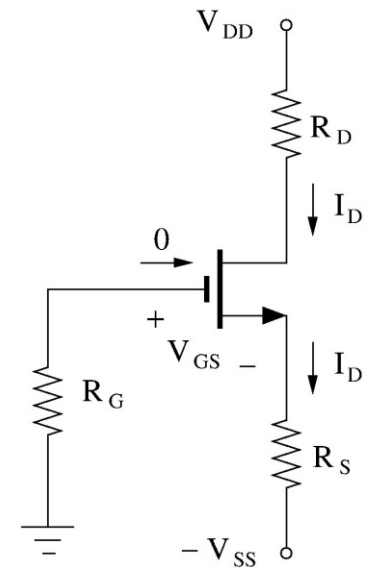


Bias with two power supplies

$$V_{SS} = V_{GS} + I_D R_S$$

Biasing circuit examples


Lecture 20 reading quiz.

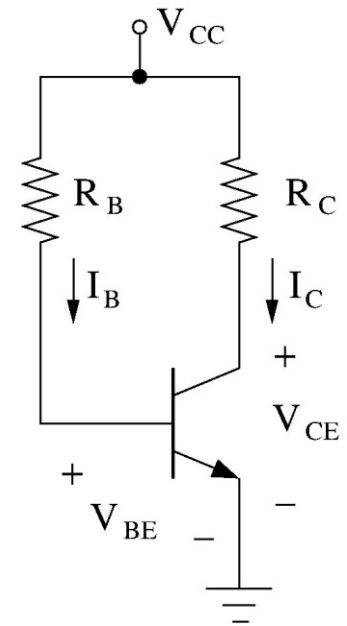Find R_C and R_B such that BJT would be in active with $V_{CE} = 5\text{V}$ and $I_C = 25\text{ mA}$. ($V_{CC} = 15\text{ V}$, Si BJT with $\beta = 100$ and $V_A = \infty$).




Discussion question 1.

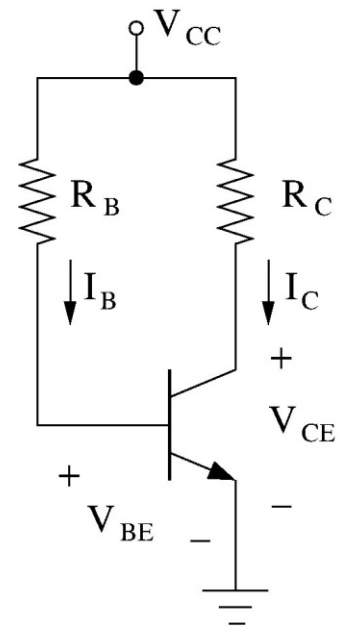Consider the circuit designed in the reading quiz ($R_C = ?$, $R_B = ?$, $V_{CC} = 15 \text{ V}$). Find the operating point of BJT if $\beta = 200$. ($V_A = \infty$).




Discussion question 2.

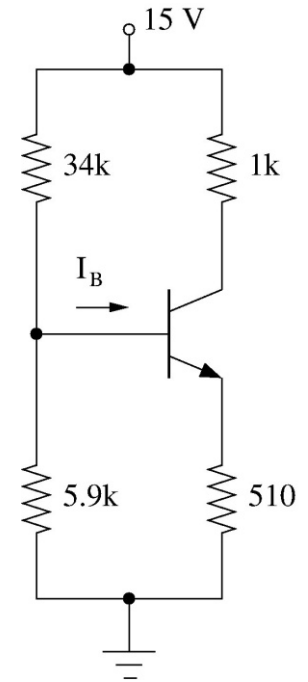Find the bias point of the BJT (Si BJT with $\beta = 200$ and $V_A = \infty$).
Compare your results for both beta values.




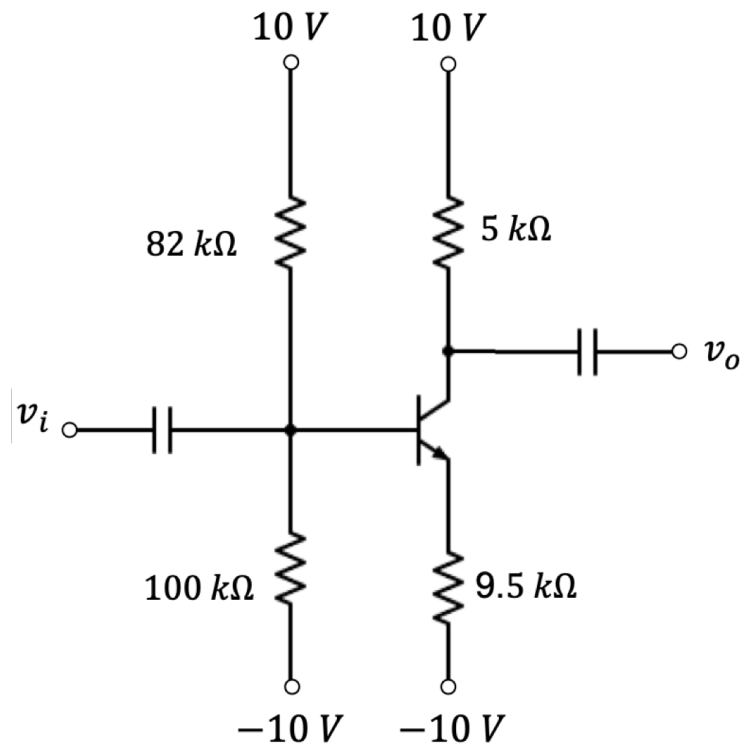Example of finding the Bias point/Thevenin equivalent circuit


$$\beta = 100 \quad V_T = 25 \text{ mV} \quad V_A = \infty$$





Bias circuit:

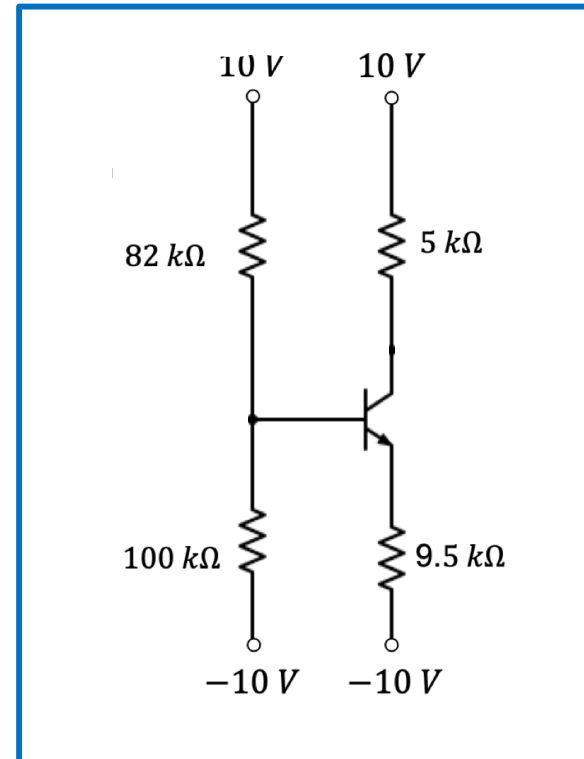


Example cont.

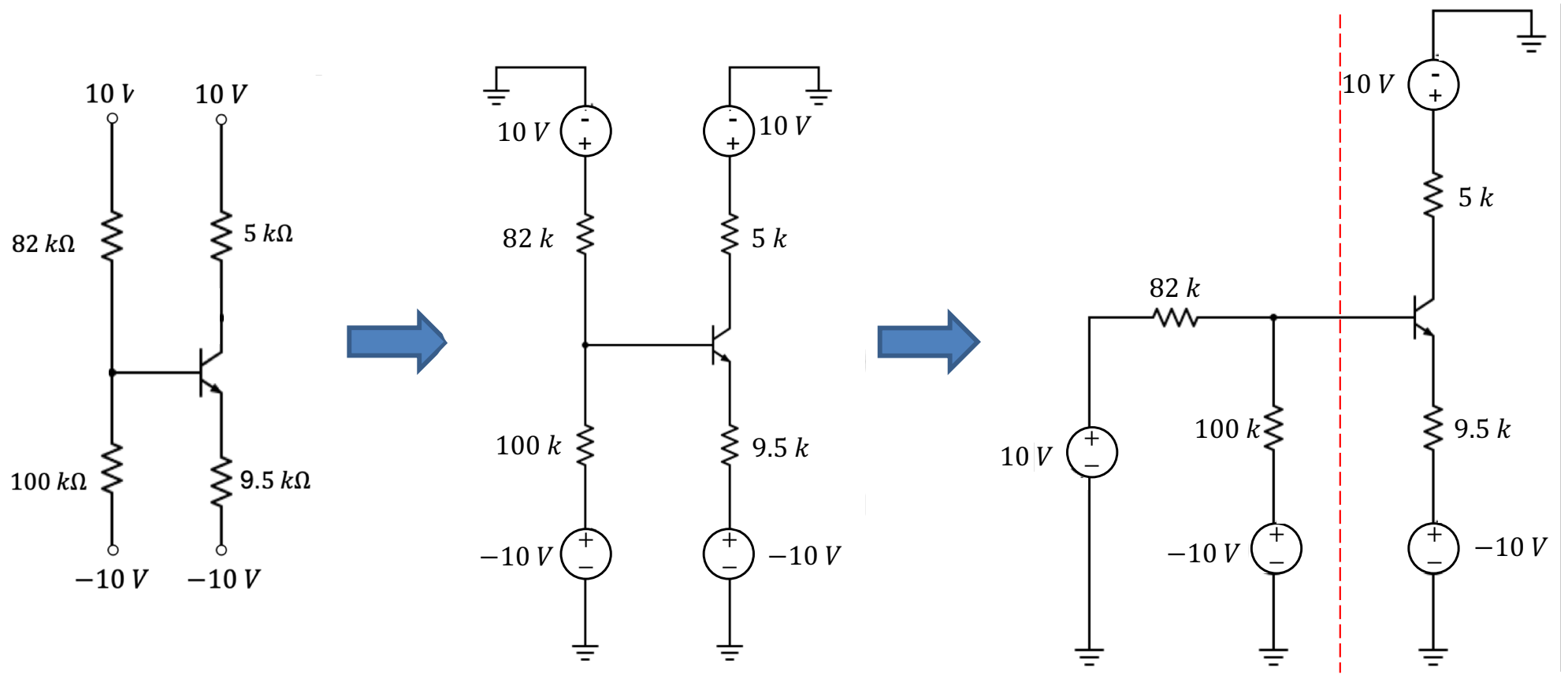

Example cont.

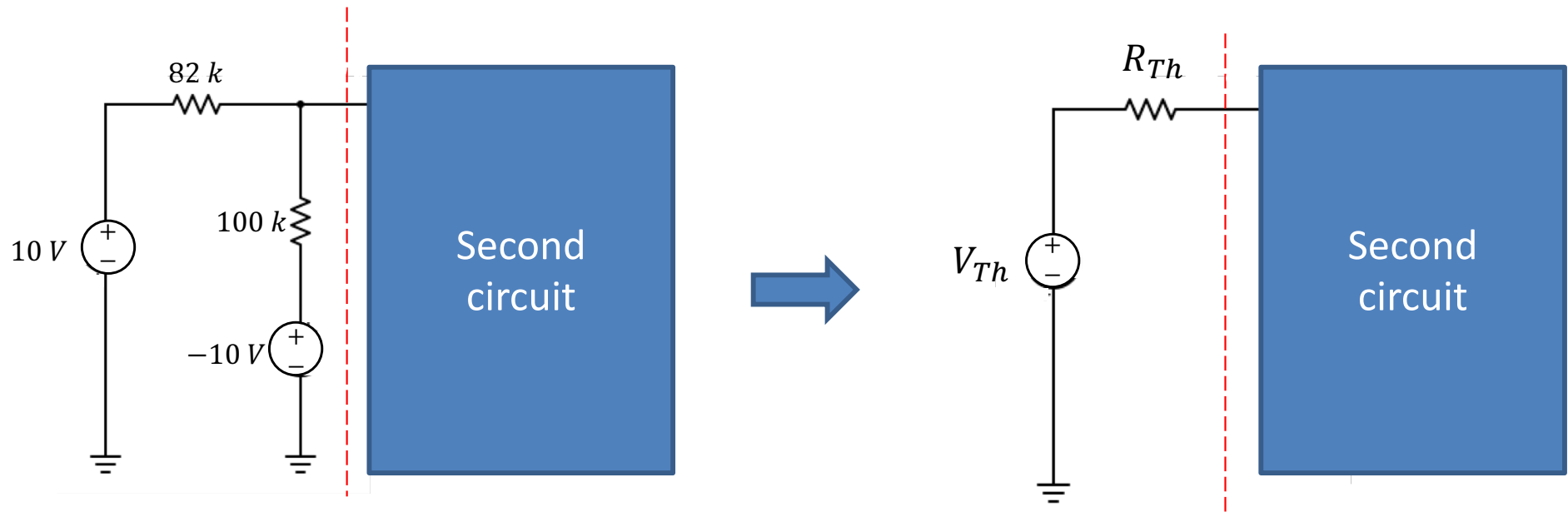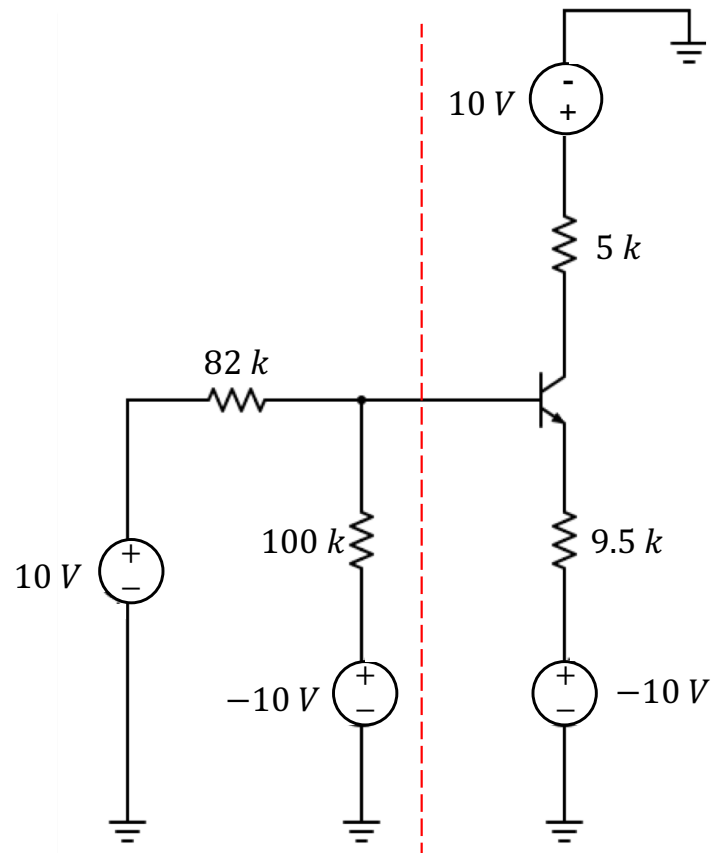


Example cont.

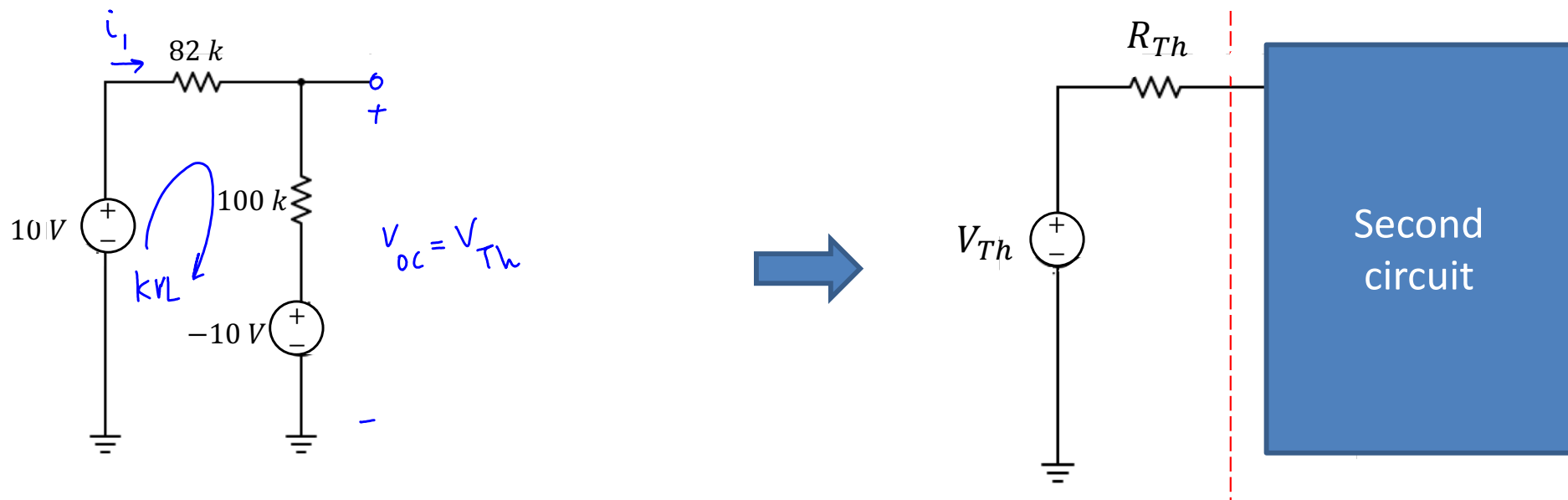

$$\text{KVL: } -10\text{ V} + 82\text{ k} \times i_1 + 100\text{ k} \times i_1 - 10 = 0$$

$$\rightarrow i_1 = \frac{20\text{ V}}{182\text{ k}} \rightarrow V_{Th} = 100\text{ k} \times i_1 - 10\text{ V} \rightarrow V_{Th} = 0.989\text{ V}$$

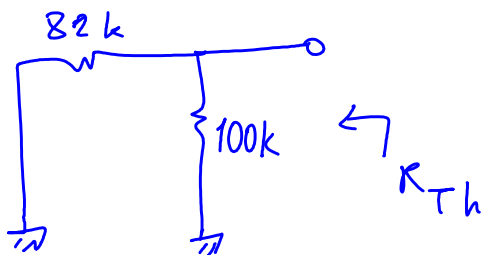R_{Th} : Zero the independent voltage sources.



$$R_{Th} = 100\text{ k} \parallel 82\text{ k} \approx 45.05\text{ k}\Omega$$

Clicker question 1.

Which one of the options is correct for the following bias circuit?

$V_t = 1\text{ V}$ and $k_n = 1.0\text{ mA/V}^2$, $\lambda = 0$.

A. $V_G = V_{GS} + I_D R_S = 7\text{ V}$

B. $5V_{OV}^2 + V_{OV}^2 - 6 = 0$

C. $V_S = 5\text{ V}$


D. $I_D = 0.5\text{ mA}$

E. All of the above.

Required equations:

$$I_D = 0.5 k_n V_{OV}^2$$

$$V_{OV} = V_{GS} - V_t$$

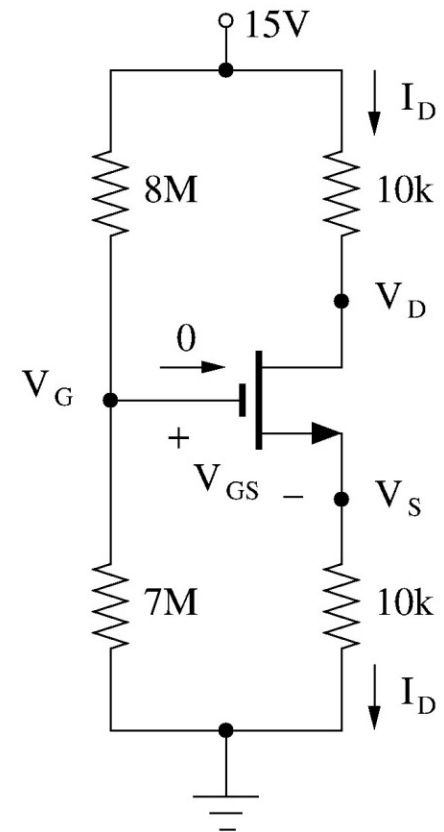

Discussion question 3.

Design the below circuit so that the transistor operates in saturation with V_{SD} biased 1-V from the edge of the saturation, with $I_D = 1\text{ mA}$ and $V_D = 3\text{ V}$. Use a $10\text{ }\mu\text{A}$ current in the voltage divider. $|V_t| = 1\text{ V}$, $k_p = 0.5\text{ mA/V}^2$

