

## Quiz 4

/ 12

Last name

First + middle  
name(s)

PID


**Instructions:**

- Read each problem completely and thoroughly before beginning
- All calculations need to be done on these sheets
- Put a box around your answer for each question. Make sure you list units!
- Answers without supporting calculations will receive zero credit

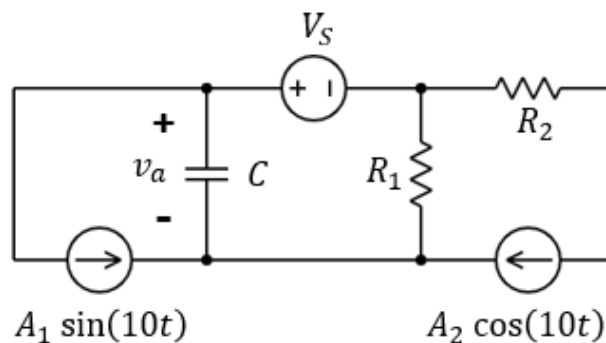**(1) (6 points)**

Consider the circuit below. You may assume it is in steady state.


- Find the voltage  $v_a$  at time  $t = \frac{\pi}{40}$ .
- Find a time  $t_0$  where the voltage  $v_a$  reaches its maximum value. If there are multiple possible answers, giving only one is sufficient.



$A_1$ : 2 A  
 $A_2$ : 2 A  
 $V_s$ : 1 V  
 $R_1$ : 2  $\Omega$   
 $R_2$ : 2  $\Omega$   
 $C$ : 50 mF

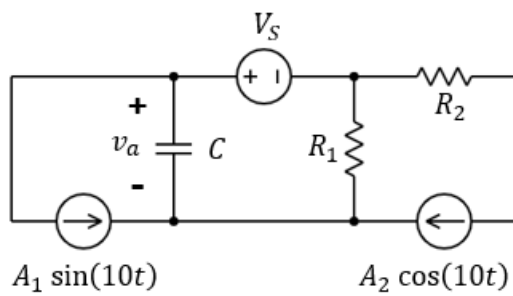*The circuit is also copied on the next page for your convenience.*





$A_1$ : 2 A  
 $A_2$ : 2 A  
 $V_s$ : 1 V  
 $R_1$ : 2  $\Omega$   
 $R_2$ : 2  $\Omega$   
 $C$ : 50 mF

(2) (6 points)

Consider the circuit below. You may assume it has reached steady state. The phasor diagram shows the phasors of  $i_1$  and  $i_2$  (the angles are as shown; the magnitudes are not drawn to scale).

Each rectangular box represents a connection of mystery elements in series/parallel. The impedances of the two boxes are  $Z_a = aj$  and  $Z_b = b(1 + j)$  but you are not told which one is which.



Note: you are given the values for  $a$ ,  $b$  and  $|V|$ .

(a) We want to build the impedance  $Z_b$  using two elements in series.

What elements would you use and what are their values?

(b) Consider the source  $v_S(t)$ . Find the value of  $X$ .

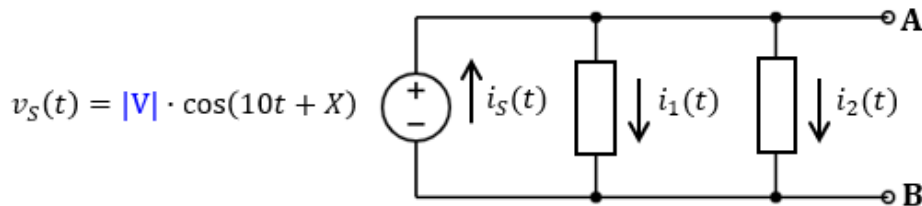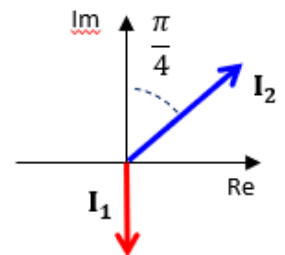(c) Between A and B, we add a third impedance  $Z_3$ , such that the current  $i_S(t)$  through the voltage source becomes equal to  $i_1(t)$ . What is the value of this impedance  $Z_3$ ?



a: -2  
b: 3  
 $|V|$ : 2 V

