

# **ECE 65: Components & Circuits Lab**

## **Lecture 9**

### **Diode waveform shaping circuits**

### **Clamp circuits**


Reference notes: sections 2.9

Sedra & Smith (7<sup>th</sup> Ed): sections 4.4-4.6

Saharnaz Baghdadchi

# Course map



## 2. Diodes

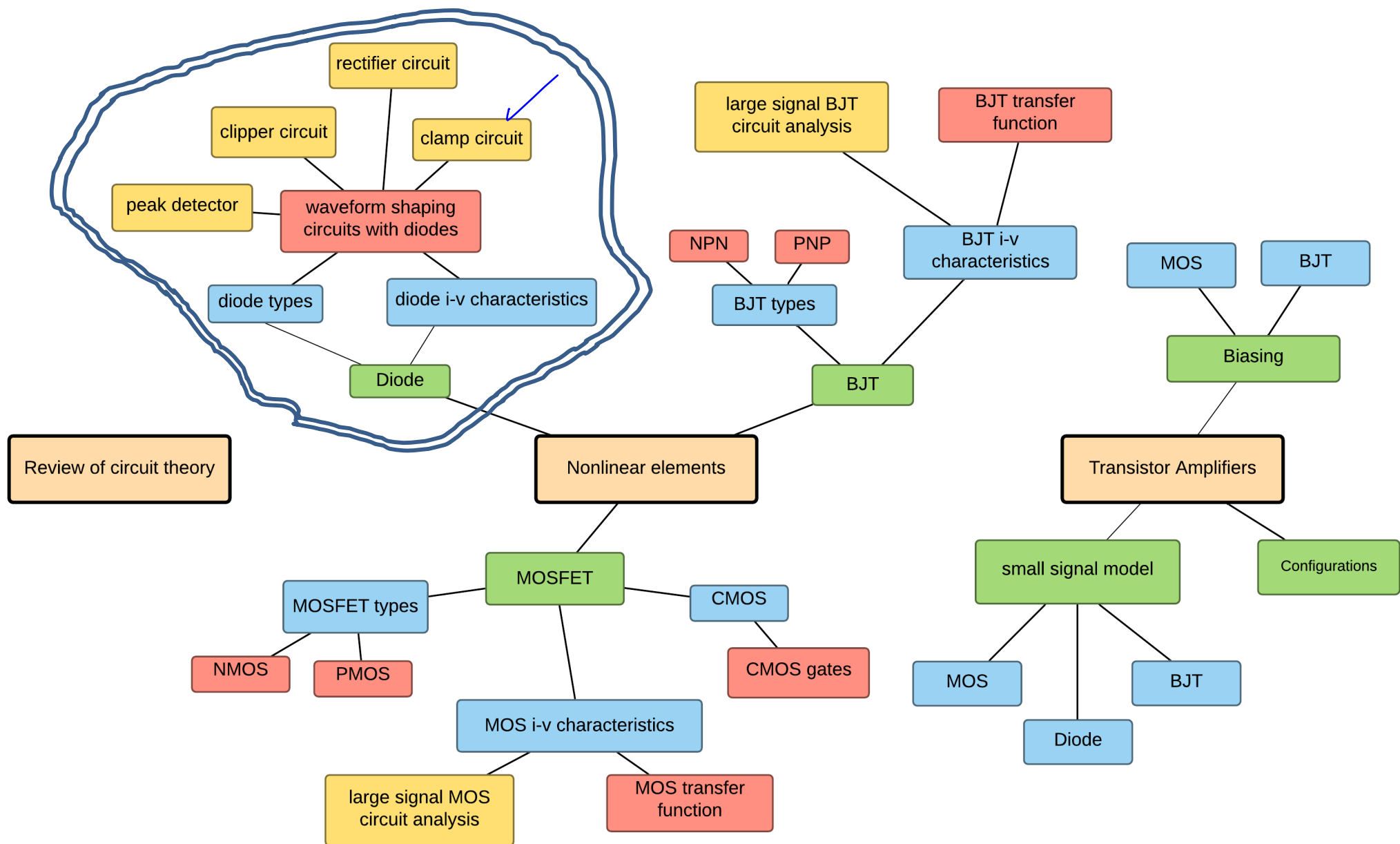

# Clamp circuit and peak detector circuit



Ideal peak detector:

$$v_o = V_p - V_{D0}$$

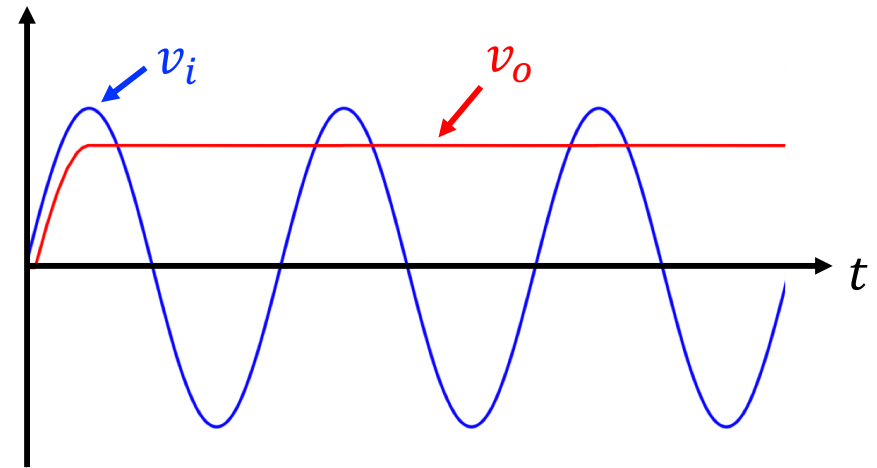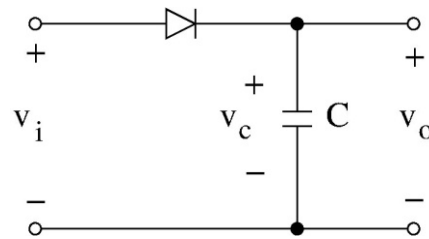


Clamp circuit:

$$v_o = v_i - (V_p - V_{D0})$$

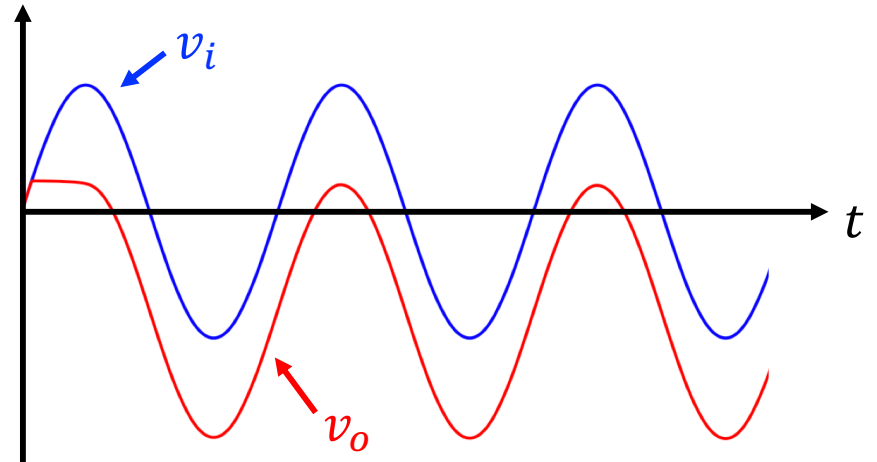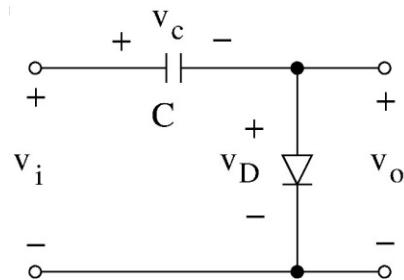


# Clamp Circuit

$$v_D = -v_c + v_i$$

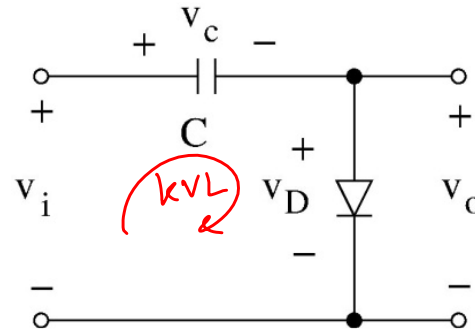

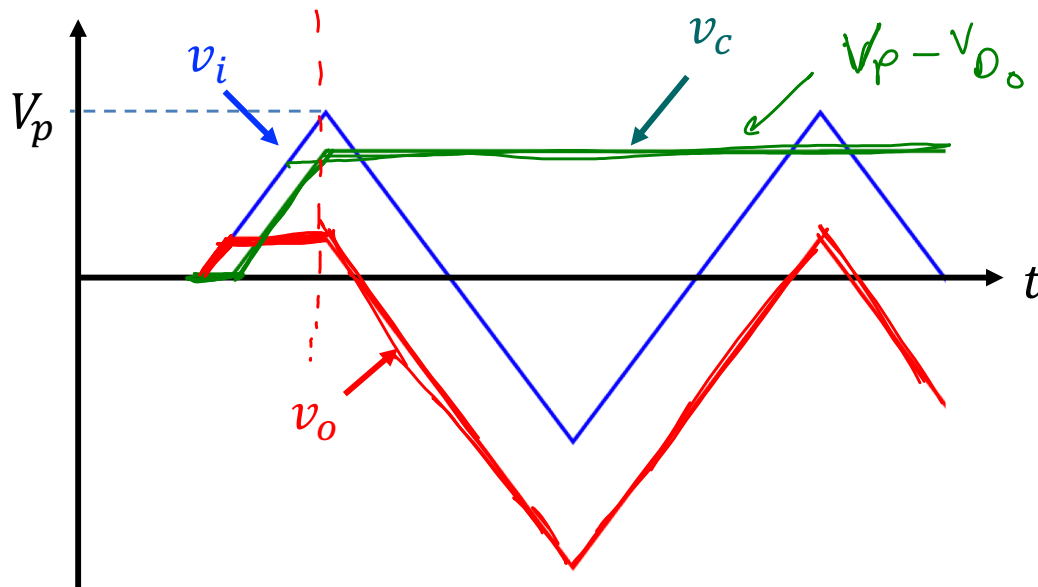The diode turns OFF when the capacitor is charged to  $v_c = \underline{V_p - V_{D0}}$





$$\underline{v_o = v_D = v_i - v_c}$$


Diode off:

$$v_o = \underline{v_i} - (V_p - V_{D0})$$

# Clamp Circuit with a Load

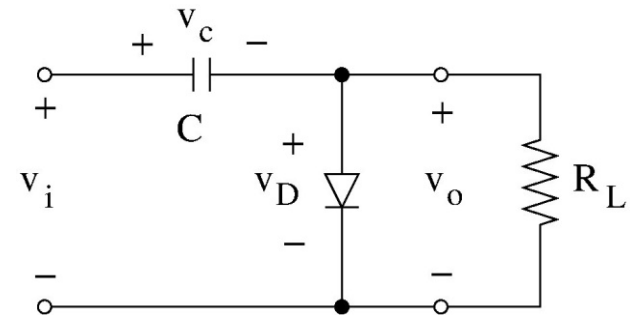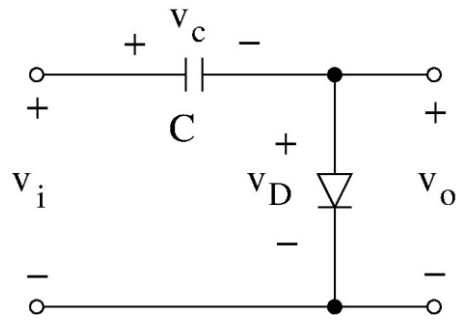


$$\tau = CR_L$$

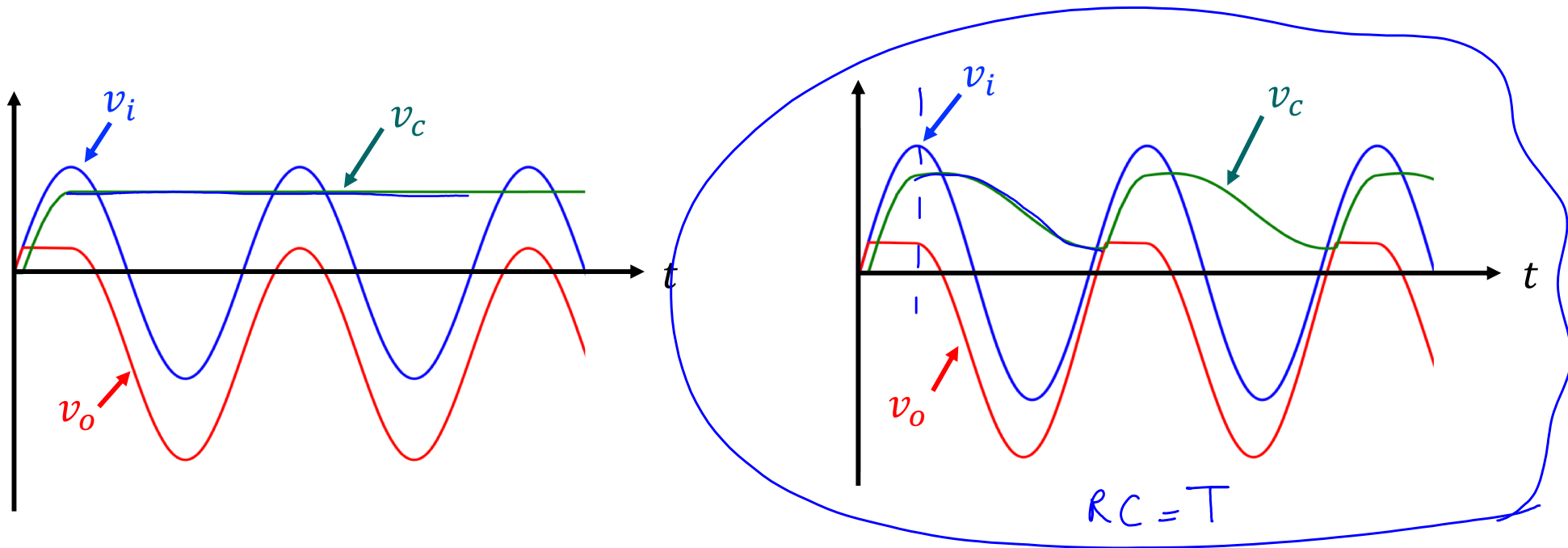

If  $\tau = R_L C \gg T$  capacitor does not discharge substantially and clamp circuits work fine

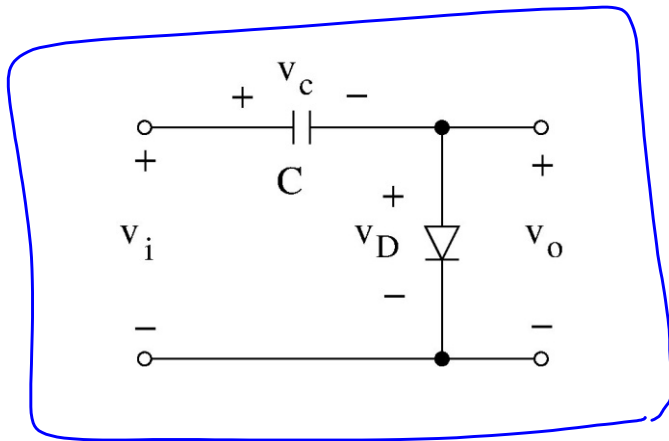
# Voltage shift in a clamp circuit can be adjusted



$$V_c = V_p - V_{D_0}$$

$$V_o = -V_c + V_i$$


$$V_o = V_i - (V_p - V_{D_0})$$

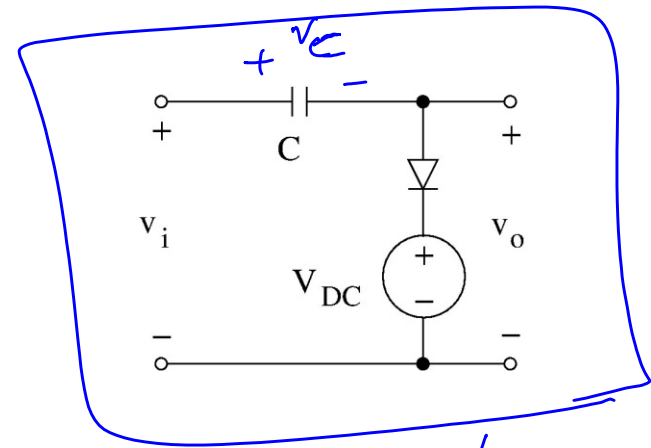

$$V_c = V_p - (V_{D_0} + V_{DC})$$

$$V_o = -V_c + V_i$$

$$= V_i - (V_p - V_{D_0} - V_{DC})$$


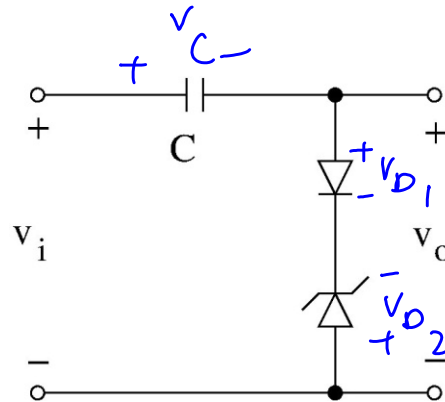


$$V_o = -V_c + V_i$$

$$= V_i - (V_p - V_{D_0} - V_Z)$$

# Clamp circuit can introduce a “positive” shift by reversing the diode terminals

Peak detector (diode is reversed):

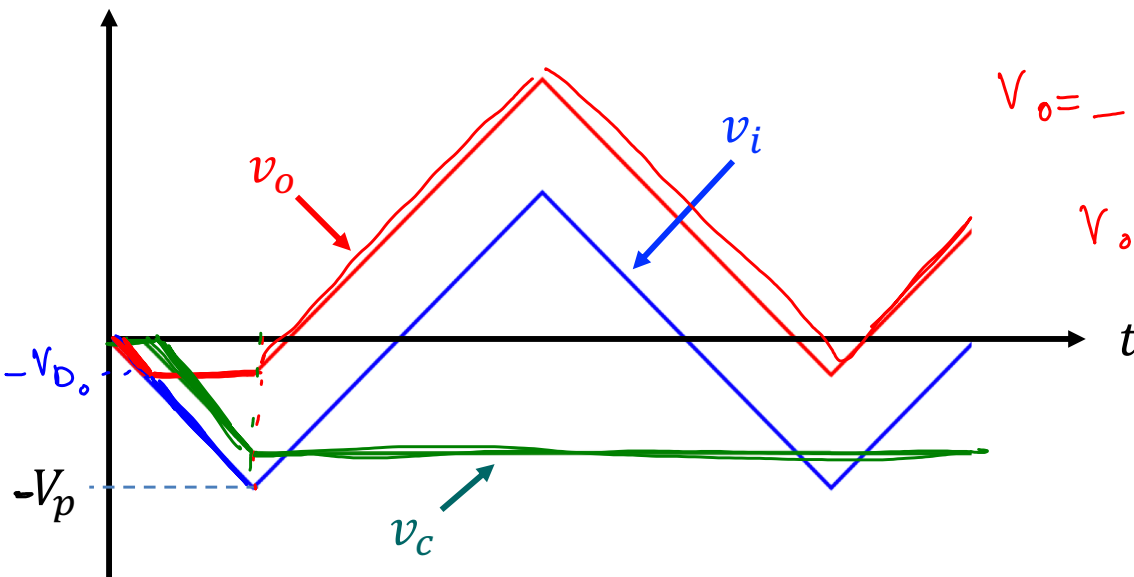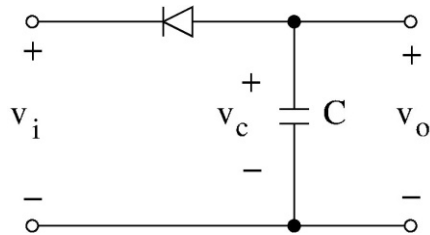


$$V_o = -V_c + V_i$$

$$V_o = -(-V_p + V_{D_o}) + V_i$$

$$V_o = V_i + (V_p - V_{D_o})$$

After the diode turned off

Clamp circuit (diode reversed):

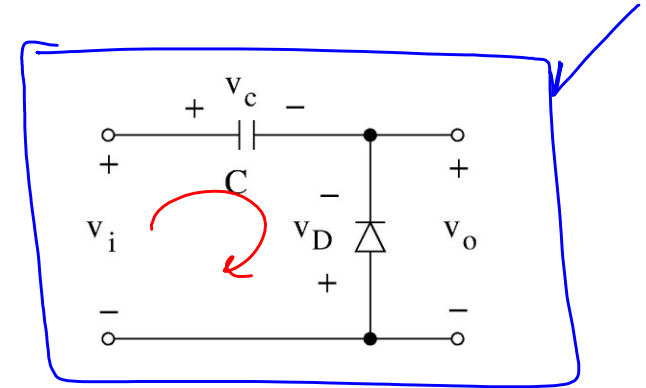

$$V_D = -V_i + V_c = -V_i$$

$$V_o = -V_D$$


$$\Rightarrow V_o = +V_i$$

$$V_o = -V_{D_o}$$

$$V_c = V_i + V_{D_o}$$


$$V_c = -V_p + V_{D_o}$$
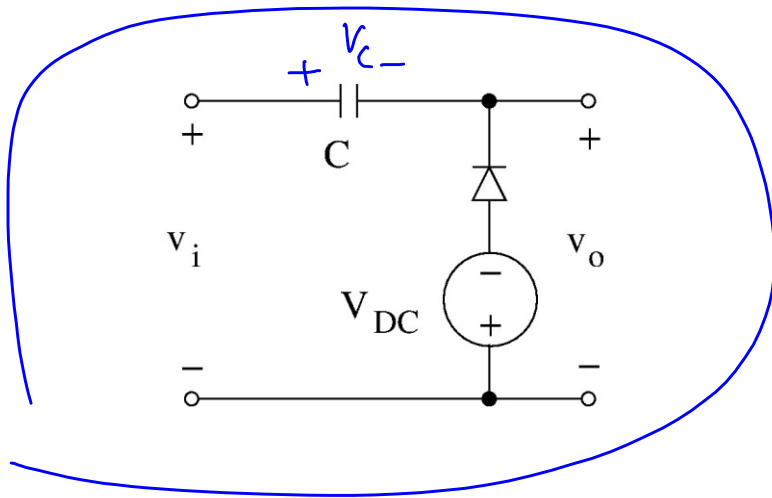
# The positive shift can also be adjusted.



$$V_c = -V_p + V_{DC} + V_{D_o}$$

$$V_o = V_i + (V_p - V_{DC} - V_{D_o})$$

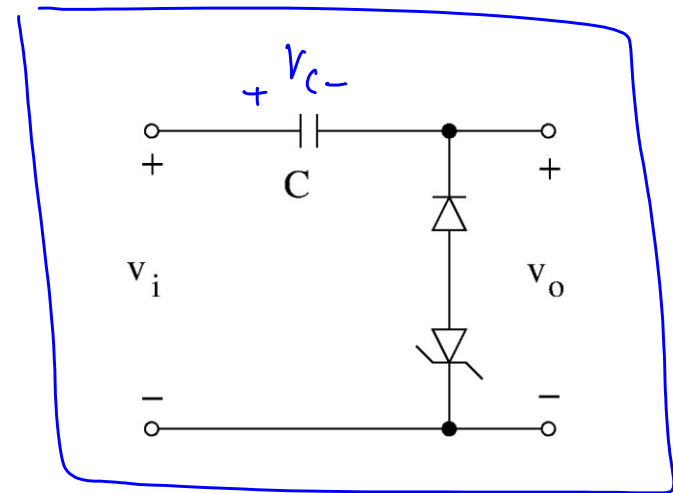

$$V_o = V_i + (V_p - V_z - V_{D_o})$$






## Lecture 9 reading quiz

For  $0 < V_i < 2$ , the diode is off &  $V_c = 0$

$$V_o = -V_c + V_i = 0 + V_i = V_i$$

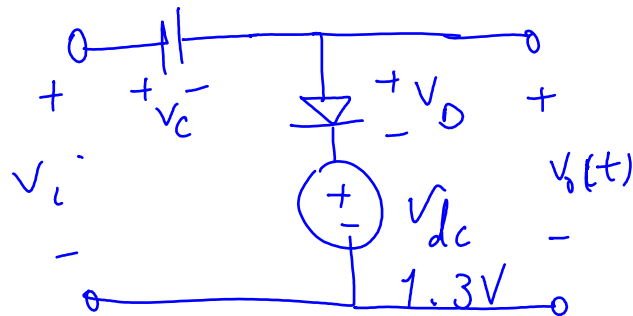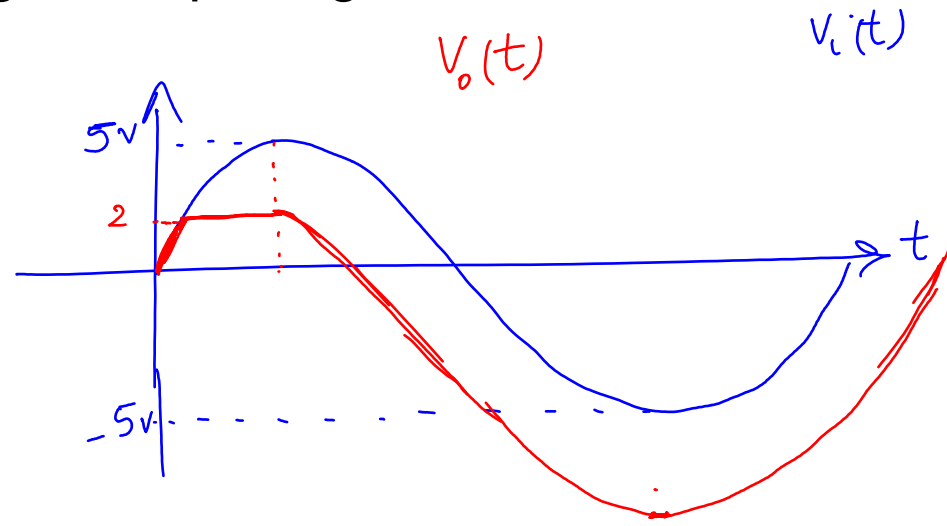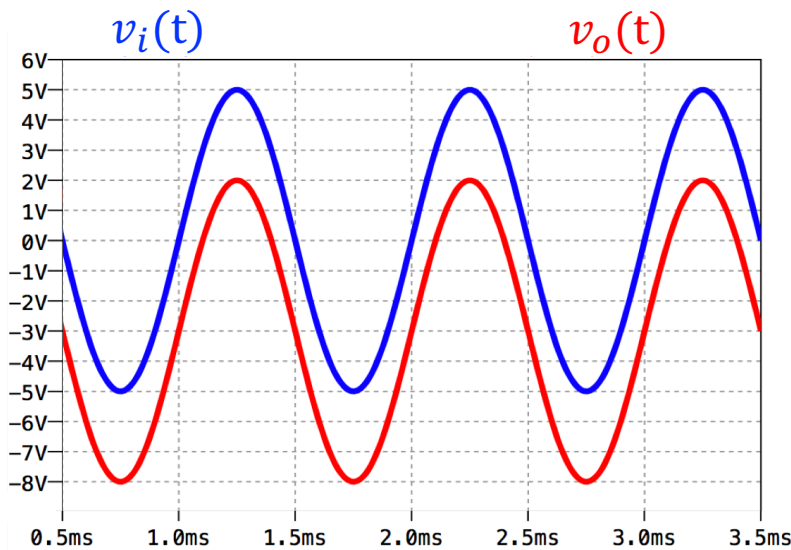Which one of the circuits in the provided options could produce the shown output waveform for the given input signal?



When the cap is charging:



$$V_c(t) = V_i(t) - V_{dc} - V_{D0}$$

When the diode turns off:

$$V_c = V_p - V_{dc} - V_{D0}$$
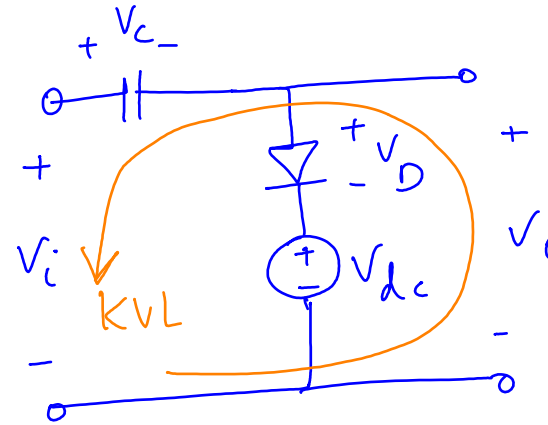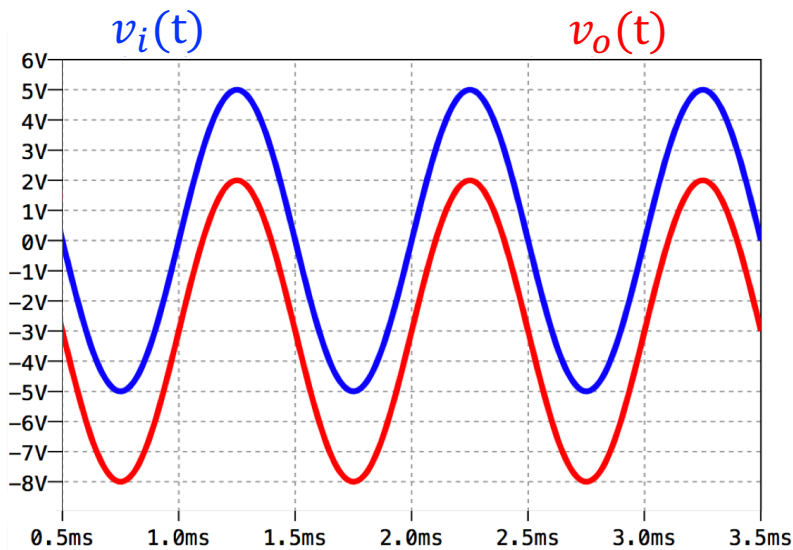
## Lecture 9 reading quiz

Which one of the circuits in the provided options could produce the shown output waveform for the given input signal?



after the diode turns off:




$$V_c = V_p - V_{dc} - V_{D_0}$$

$$\text{KVL: } V_o = v_i - V_c$$

$$V_o = v_i - (V_p - V_{dc} - V_{D_0}) = v_i - 3V \Rightarrow V_p - V_{dc} - V_{D_0} = 3V \rightarrow 5 - V_{dc} - 0.7 = 3 \rightarrow V_{dc} = 1.3V$$
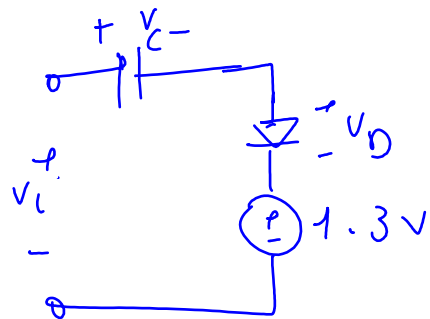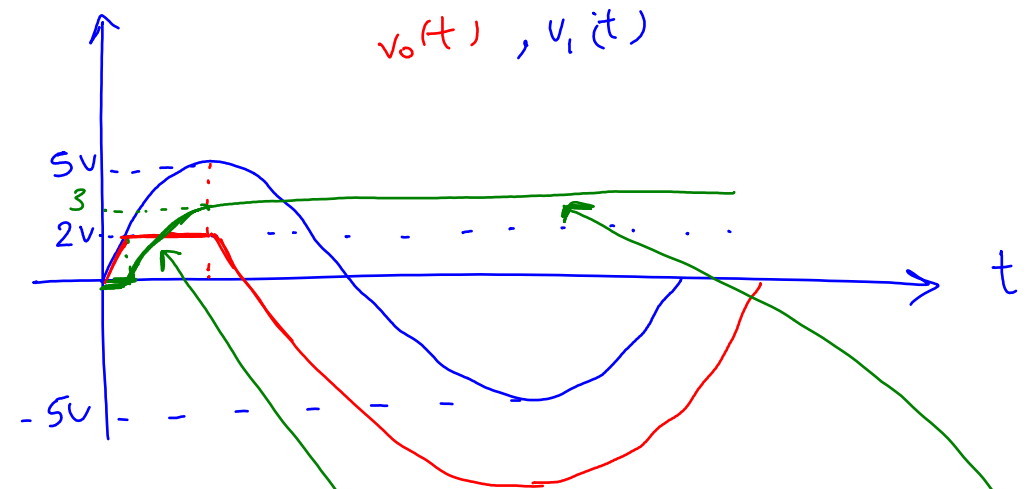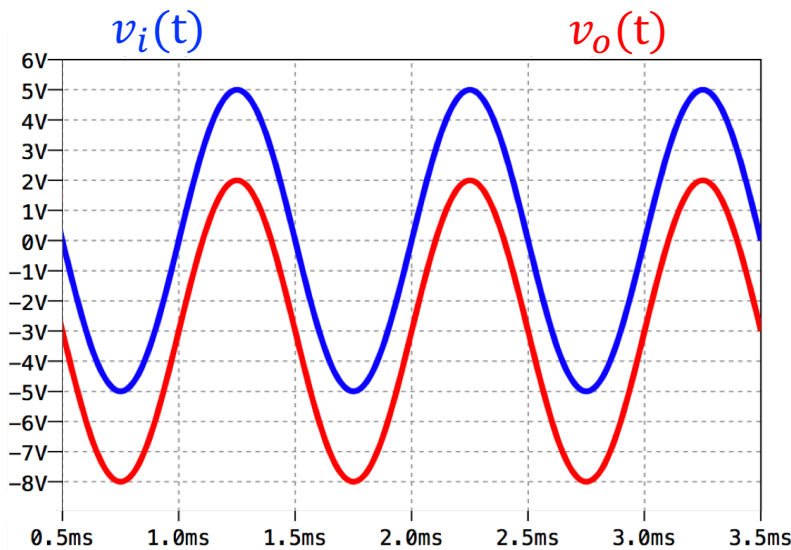
# Lecture 9 reading quiz

Which one of the circuits in the provided options could produce the shown output waveform for the given input signal?



When the cap is charging :


$$V_c(t) = V_i - V_{dc} - V_{D_0}$$

When the diode turns off :

$$V_c(t) = V_p - V_{dc} - V_{D_0}$$
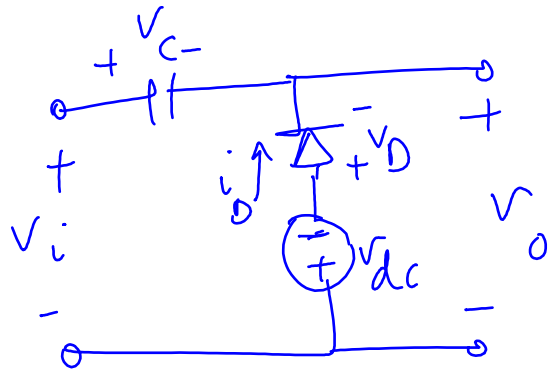
# Discussion question 1

Consider a sinusoidal source  $v_i(t) = 10 \sin(\omega t) \text{ V}$ . Using a DC power supply, design a clamp circuit that adds a DC offset of 5V to  $v_i(t)$ . Draw two cycles of the input and output voltage waveforms.



$$\text{KVL: } V_c = V_i + V_{dc} + V_D$$

when the diode is ON

$$V_c(t) = V_i(t) + V_{dc} + V_{D_0}$$

when  $V_i(t)$  reaches its negative peak


$$V_c = -V_p + V_{dc} + V_{D_0}$$

$$V_{dc} = 4.3 \text{ V}$$

$$V_o = -V_c + V_i = V_i - (-V_p + V_{D_0} + V_{dc})$$

$$= V_i - (-10 + 0.7 + V_{dc})$$

$$V_o = V_i + 5 \text{ V}$$

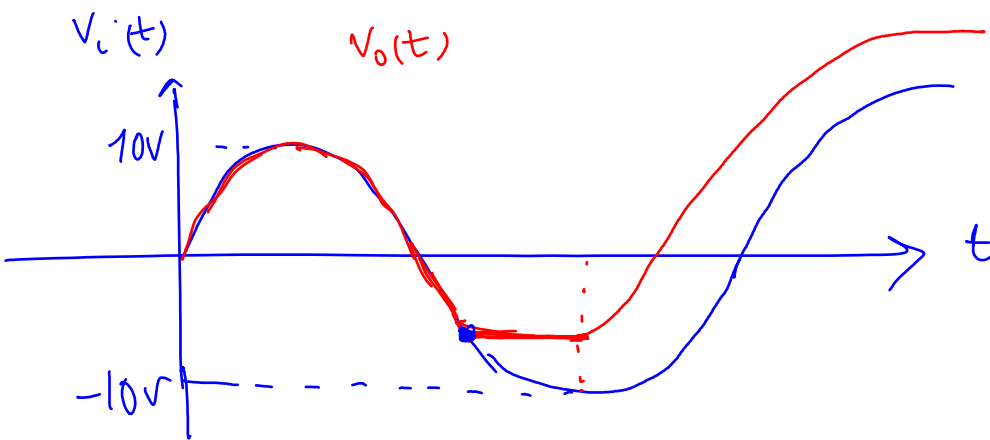

before the diode turns ON :  $V_c = 0$  ,  $V_o = -V_c + V_i = V_i$