
PP Phasors 012

$$i_x(t) = 3\sqrt{2} \cdot \sin(5000t + 30^\circ)$$
 A

Find
$$v_S(t) = A \cdot \cos(W \cdot t + B)$$
.

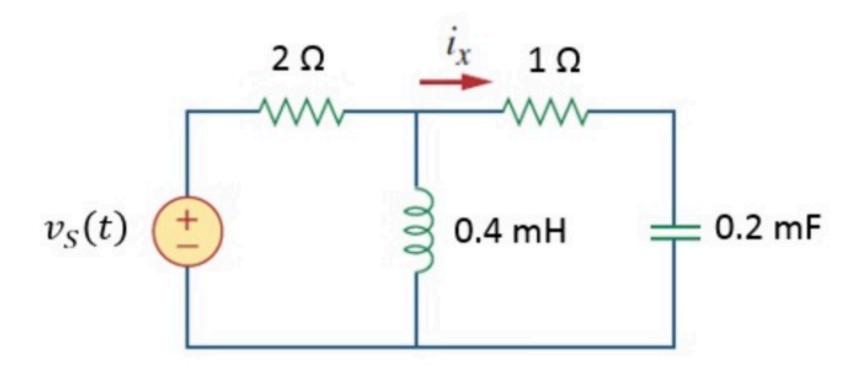(with $0 \le A$ and $-180^{\circ} \le B \le 180^{\circ}$)



Given Variables:

: . .

Calculate the following:

A (V):

12

W (rad/s):

5000

B (degrees):

-105

Hint: Stay algebraic with Vs as long as you can