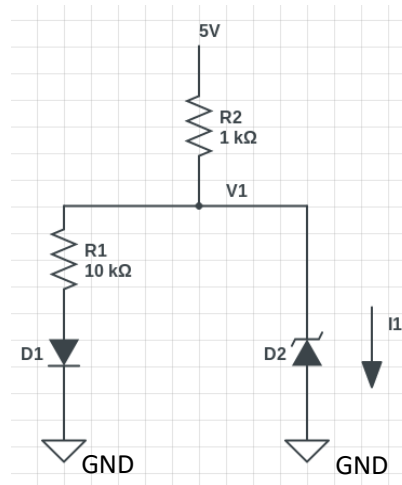



Problem 1.

In the following circuit find V_1 and I_1 . ($V_Z = 3\text{ V}$ and $V_{D0} = 0.7\text{ V}$)



Problem 2.

Design a diode waveform shaping circuit that would have the below transfer function. Assume $X = 0.5$, $V_1 = 1$, and $V_2 = -2$.

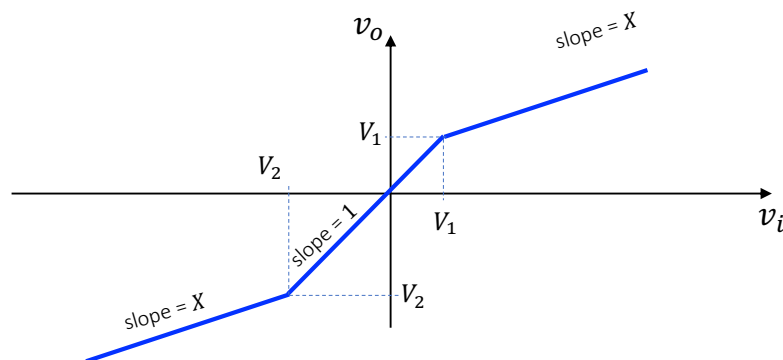



Problem 3.

The circuits (a) and (b) shown below are connected as follows:

The two input terminals are tied together, and the two output terminals are tied together.


- Find, sketch and label the transfer function. (Assume $V_{D0} = 0.7 \text{ V}$).
- Draw the output voltage waveform if $v_i(t) = 5 \sin(\omega t)$. There is no need for labeling the time axis.

Show your work.

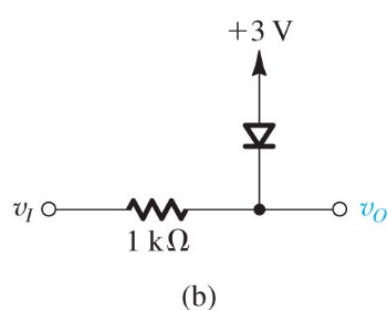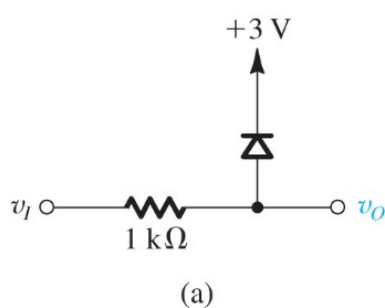

Problem 4.

Plot the transfer function of the following full-wave rectifier. Find v_o for different ranges of v_i and plot a graph that shows the relationship between v_i and v_o .

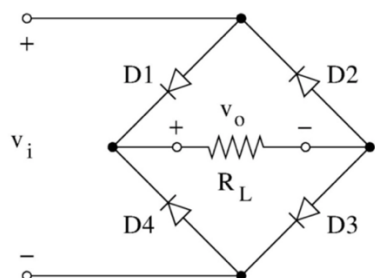

Problem 5.

In the circuit below, $v_i(t) = 10 \sin(\omega t)$ where $\omega = 1000 \text{ rad/s}$, Assume $V_{D0} = 0.7 \text{ V}$ and $v_o(0) = 0 \text{ V}$. Calculate and plot $v_o(t)$ for $0 \leq t \leq 5 \text{ ms}$.

