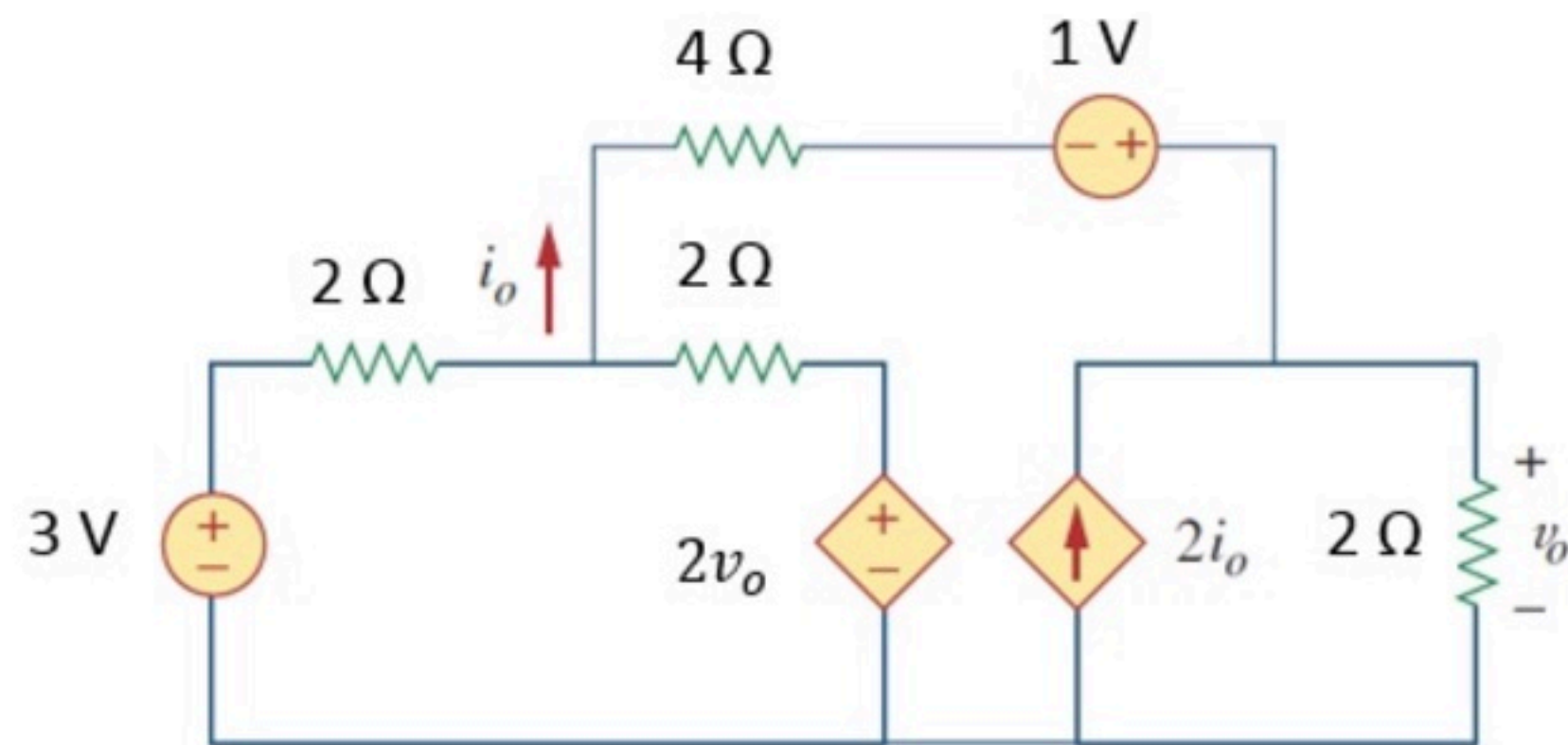


PP - Nodal Mesh 010

Problem has been graded.

Find v_o and i_o . Solve using nodal analysis.

For extra practice: Afterwards solve again using mesh analysis.



Given Variables:

...

Calculate the following:

v_o (V) :

3



i_o (A) :

0.5



Hint: Select GND strategically and use supernode