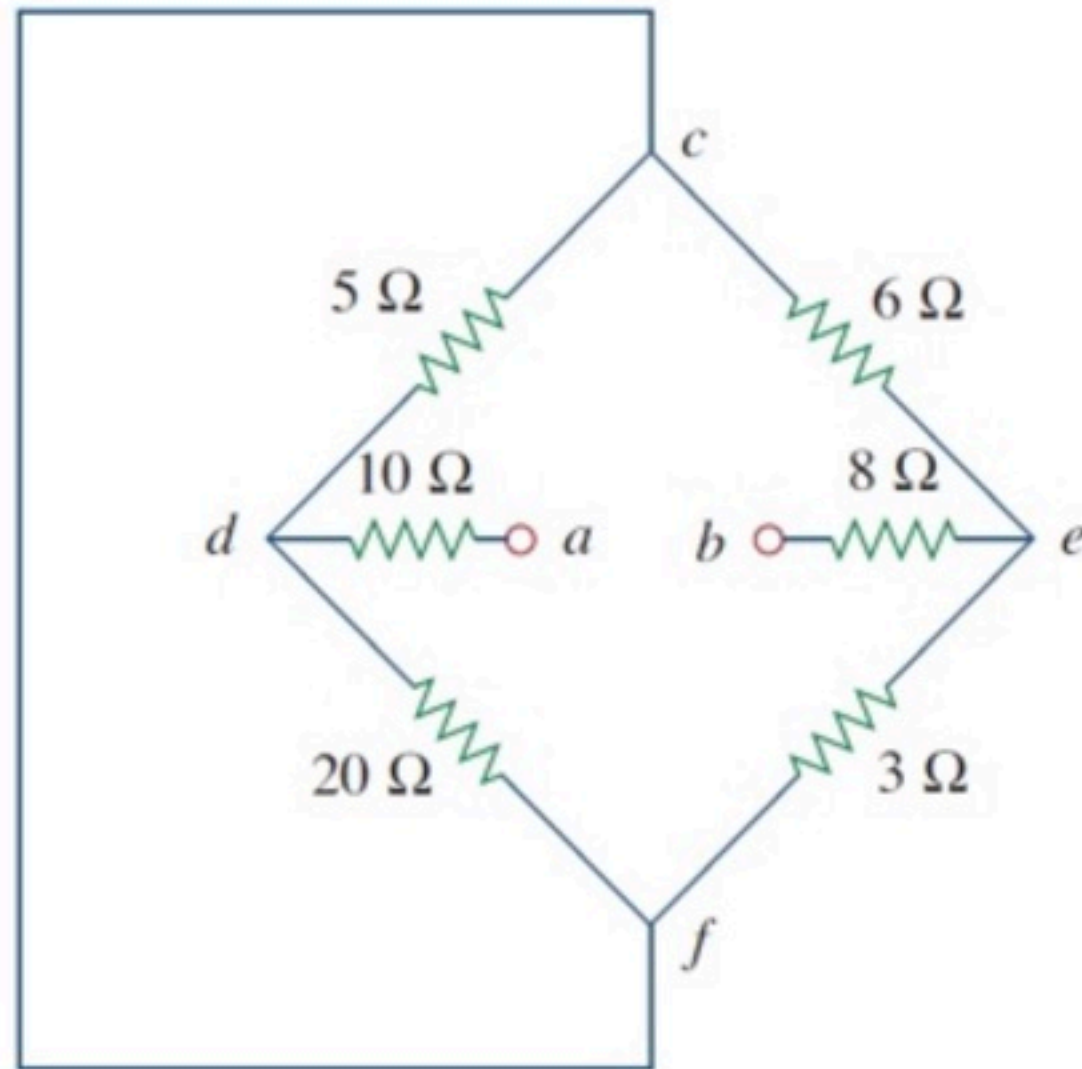


PP - Basic analysis 011

Unlimited Attempts.

Find R_{eq} looking into the terminals.



Given Variables:

...

Calculate the following:

Req (ohm) :

24



Hint: Use series and parallel connections of resistors