
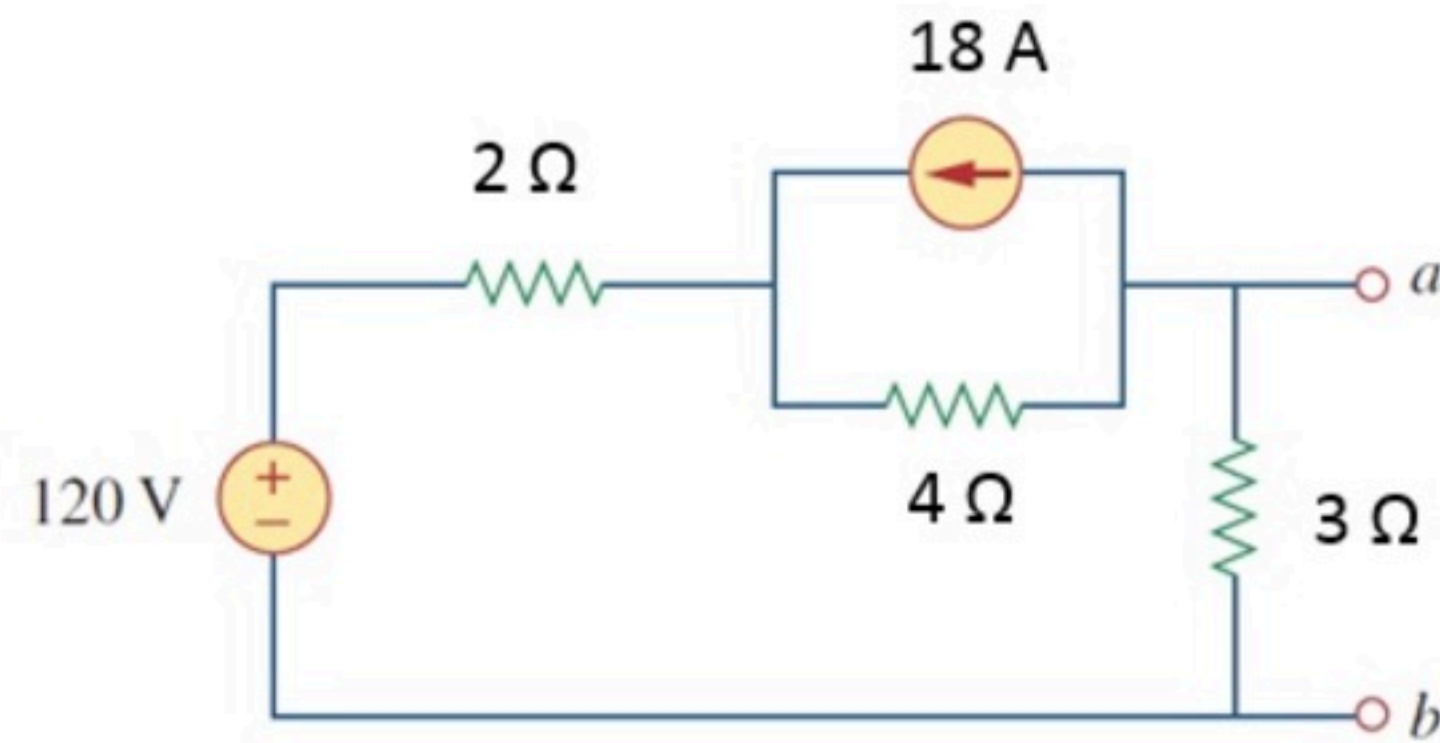


PP Circuit theorems 010

Unlimited Attempts.

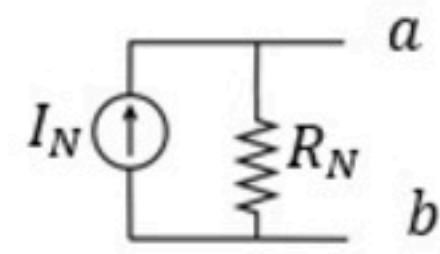Find the Norton equivalent model of this circuit, as seen between a and b.



Given Variables:

...

Calculate the following:

I_N (A) :

8



R_N (ohm) :

2



Hint: You can find I_{sc} using superposition.