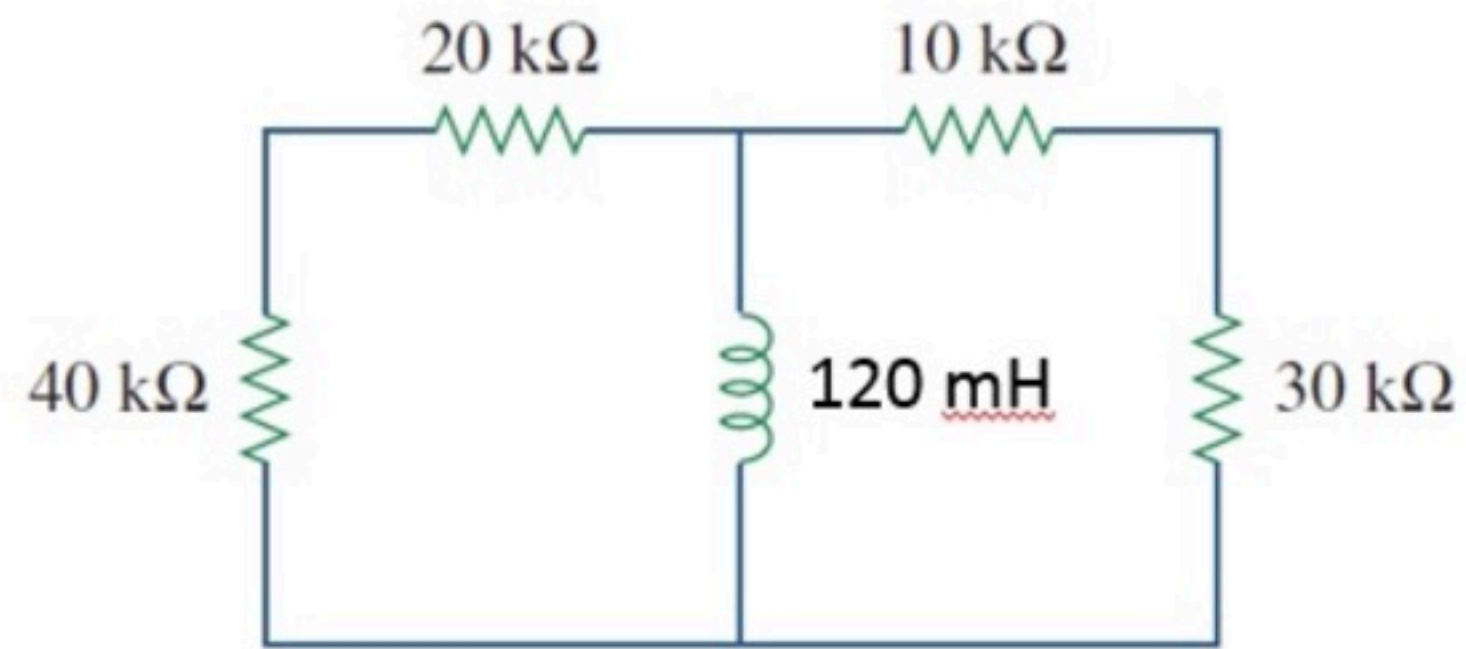


# PP First order circuits 003

Unlimited Attempts.

What is the time constant  $\tau$  in this circuit?



Given Variables:

...

Calculate the following:

$\tau$  (us) :

5



Hint: Find  $R_{eq}$