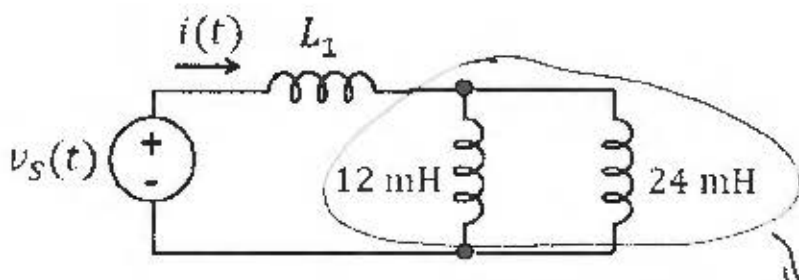


Find the current i (i.e., the constant B).

$$A = 4.8 \text{ V}$$

$$L_1 = 4 \text{ mH}$$


(For this problem, ignore the initial conditions. As we will see later in this course, this means we assume the system is in what is called "steady state".)



$$v_s(t) = A \cdot \cos(2000t)$$

$$i(t) = B \cdot \sin(2000t)$$
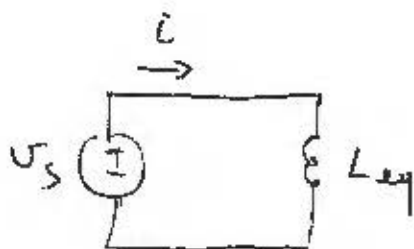
$$\text{PARALLEL} \quad \frac{1}{\frac{1}{12} + \frac{1}{24}} = \frac{1}{\frac{3}{24}} = 8 \text{ mH}$$



$$L_{eq} = L_1 + 8 = 12 \text{ mH}$$

$$v = L \frac{di}{dt} \Rightarrow 4.8 \cos(2000t) = L_{eq} \cdot B \cdot 2000 \cos(2000t)$$

$$\Rightarrow B = \frac{4.8}{2000 \cdot 12 \cdot 10^{-3}} = \frac{4.8}{24} = 0.2 \text{ A}$$

$$B = 200 \text{ mA}$$