

# ECE 35, Fall 2022 – Section A

## Final

Your sequence number

--

Grade

/ 31
------

Last name

First + middle  
name(s)**PID**

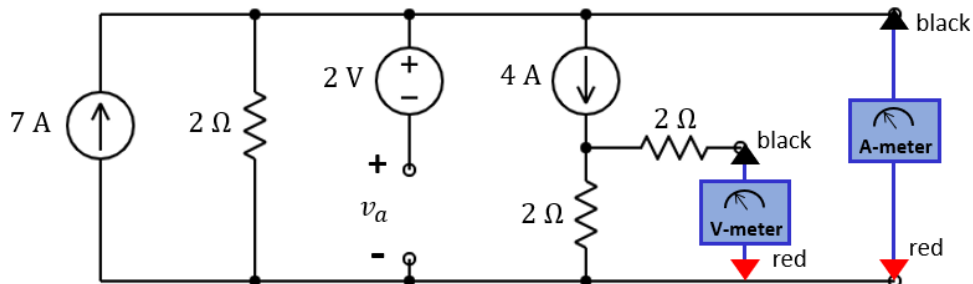
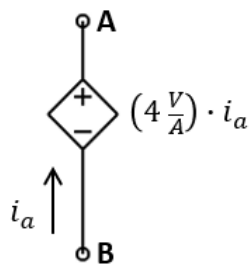

### Instructions:

- Do not look at the questions or start writing until it is announced that you can do so.
- You must follow the Final Exam Procedures that were posted on Canvas. If you are unsure of anything, ask. As a reminder:
  - Your phone should be turned off and put inside your bag
  - Calculators are not allowed.
  - This is a closed book exam.
  - Follow the Academic Integrity standards
- These pages contain the exam questions.
  - Do not write any of your work here except for scratch work. It will not be graded.
  - You need to write your final answer in the answer boxes here. Make sure you list units.
  - Keep these question pages stapled together. The last page is the equation sheet; you may detach this if you want.
  - Make sure you write your PID on EACH page.
  - Read each problem completely and thoroughly before beginning.



(1) (7 points)

(a) In the circuit below, the ammeter and voltmeter are ideal.

What is the reading  $X$  of the voltmeter? $X$ What is the reading  $Y$  of the ammeter? $Y$ What is the voltage  $v_a$ ? $v_a$ What is the power  $P$  received by the 4 A current source ? $P$ (b) What is the Thevenin resistance  $R_{th}$  between A and B ? $R_{th}$ 


(2) (7 points) For this question, you should make reasonable numerical approximations if needed.

- (a) Consider the circuit below. For  $t < 0$  s, the switch is closed, and the system has reached steady state. At time  $t = 0$  s, the switch opens.

Find the current  $i_a$  at time  $t = 0^-$  s (i.e., immediately before the switch opens).

 $i_a(0^-)$ 

Find the current  $i_a$  at time  $t = 0^+$  s (i.e., immediately after the switch opens).

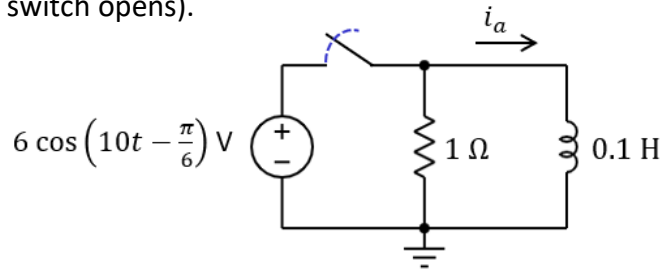 $i_a(0^+)$ 


- (b) Consider the circuit below. For  $t < 0$  s, the switch is in position 1, and the system has reached steady state. At time  $t = 0$  s, the switch moves to position 2 (and stays there). Just before the switch moves,  $i_x$  is 4 A.


Find the current  $i_b$  at time  $t = 0^+$  s (i.e., immediately after the switch moves to position 2).

 $i_b(0^+)$ 

Find the current  $i_b$  at time  $t = 2$  s.

 $i_b(2 \text{ s})$ 

Find the current  $i_b$  at time  $t = \infty$ .

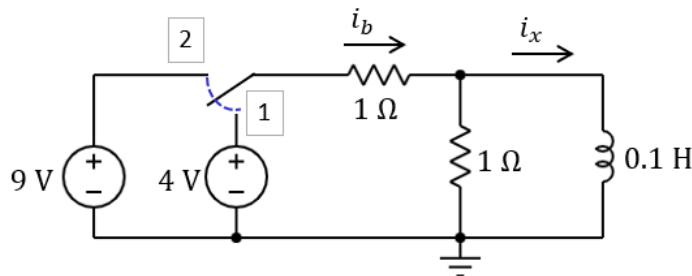 $i_b(\infty)$ 


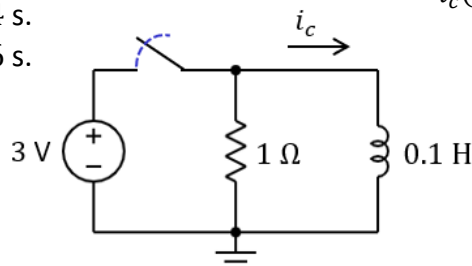
- (c) Consider the circuit below. For  $t < 2$  s, the switch is open, and the system may not have reached steady state. At time  $t = 2$  s, the switch closes. Just after the switch closes,  $i_c$  is 5 A.

 $i_c(4 \text{ s})$ 

Find the current  $i_c$  at time  $t = 4$  s.

 $i_c(6 \text{ s})$ 

Find the current  $i_c$  at time  $t = 6$  s.



(3) (6 points) Consider the circuit below. You may assume it is in steady-state.

(a) Find the current of current source  $i_{S1}$  at time  $t = \frac{\pi}{20}$  s.


$$i_{S1}\left(\frac{\pi}{20} \text{ s}\right)$$

(b) Find the voltage  $v_a$  at time  $t = \frac{\pi}{20}$  s.

$$v_a\left(\frac{\pi}{20} \text{ s}\right)$$

(c) Find the maximum value of the waveform  $i_a(t)$ .

$$i_{a \max}$$

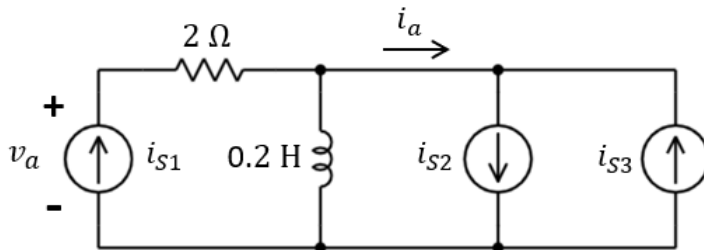

$$i_{S1} = 3 + 5 \cos(10t) \text{ A}$$

$$i_{S2} = 6 \sin\left(20t + \frac{\pi}{4}\right) \text{ A}$$

$$i_{S3} = 3\sqrt{2} \cos(20t) \text{ A}$$

- (4) (6 points) The circuit below represents an AC circuit in steady-state in the phasor domain (for the complex numbers, you may assume units are V, A,  $\Omega$ , etc. as appropriate). The voltage source  $v_s$  is an AC source with  $\omega = 5$  rad/s. Each box represents the impedance of a single circuit element (a resistor, capacitor or inductor).



(a) Find the average power  $P_s$  supplied by the voltage source.

 $P_s$ 

(b) Find the average power  $P_1$  received by the element with impedance  $\mathbf{Z}_1$ .

 $P_1$ 

(c) Find the RMS value of  $i_x$ .

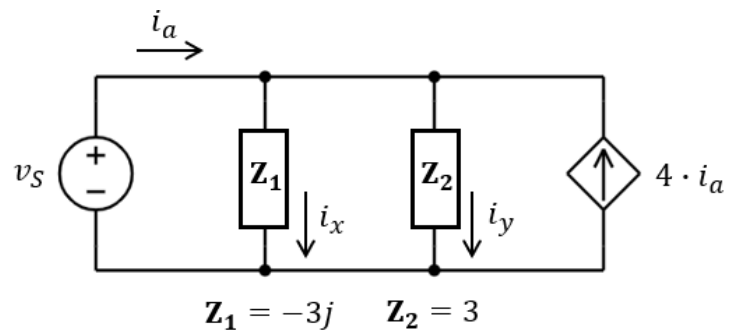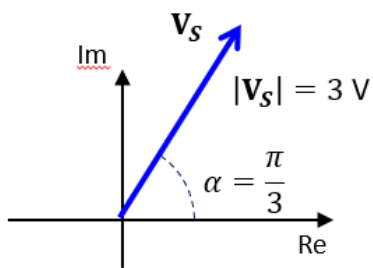 $i_{xRMS}$ 


## (5) (5 points)

(a) Consider the circuit below. You are not given the values of  $k$  and  $V_s$  (but you are told that all sources are DC sources). We are considering the circuit after the switch closes.

- The time constant  $\tau$  associated with  $i_L(t)$  during this transition is  $\tau = 2$  s.
- You also measure that when current  $i_L$  reaches 4 A, the voltage  $v_L$  drops to 0 V.


What is the current  $i_L$  when the system reaches steady state?

 $i_L$ 

Find the Norton equivalent resistance  $R_N$  between A and B if we were to remove the inductor from the circuit.

 $R_N$ 

During the transition (in our original circuit with the inductor in there), when the current  $i_L$  has a value of 1 A, what is the value of the voltage  $v_L$ ?

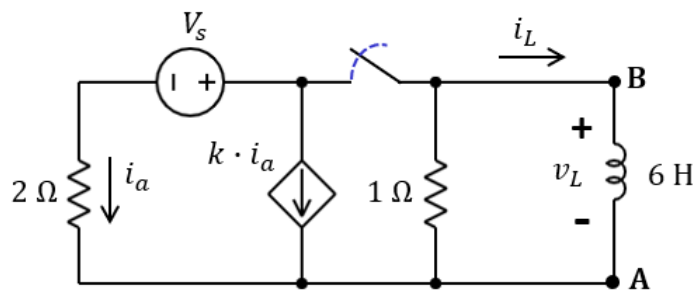
 $v_L$ 

(b) Consider the circuit below. The unknown values of  $k$  and  $V_s$  are the same as in the circuit above. The switch closes at time  $t = 400$  s (you do not know if the system has reached steady state before the switch closes).

Find the time constant  $\tau_1$  associated with  $v_c(t)$  for  $t > 400$  s.

 $\tau_1$ 

Find the time constant  $\tau_2$  associated with  $i_a(t)$  for  $t > 400$  s.

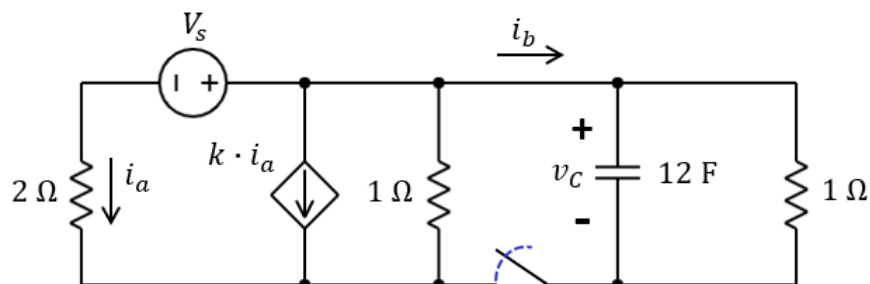 $\tau_2$ 

## ECE35 Equation Sheet

**Basics:**  $i \triangleq \frac{dq}{dt}$   $v_{ab} \triangleq \frac{dw}{dq}$   $R = \rho \frac{l}{A}$

**Capacitors:**  $C = \epsilon \cdot \frac{A}{d}$   $Q = C \cdot v$   $w_C = \frac{1}{2} C v^2$

**Inductors:**  $L = \mu \cdot \frac{N^2 A}{l}$   $B \sim i$   $w_L = \frac{1}{2} L i^2$

**AC power:**  $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \quad X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$

**Trigonometry:**

$\sin(-\alpha) = -\sin(\alpha)$	$\cos(-\alpha) = \cos(\alpha)$
$\sin(\pi - \alpha) = \sin(\alpha)$	$\cos(\pi - \alpha) = -\cos(\alpha)$
$\sin\left(\frac{\pi}{2} - \alpha\right) = \cos(\alpha)$	$\cos\left(\frac{\pi}{2} - \alpha\right) = \sin(\alpha)$
$\sin\left(\alpha - \frac{\pi}{2}\right) = -\cos(\alpha)$	$\cos\left(\alpha - \frac{\pi}{2}\right) = \sin(\alpha)$
$\sin(2\alpha) = 2 \sin(\alpha) \cos(\alpha)$	$\cos(2\alpha) = \cos^2(\alpha) - \sin^2(\alpha)$

$$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$$

$$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$$

$$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$$

$$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$$

$$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$$

$\alpha:$	0	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$
$\sin(\alpha):$	0	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	1
$\tan(\alpha):$	0	$\frac{\sqrt{3}}{3}$	1	$\sqrt{3}$	$\infty$