

Lecture 9: More Procedural Statements

UCSD ECE 111

Prof. Farinaz Koushanfar

Fall 2024

Important announcements (Details in Canvas)

- **Next class on Tues 10/29 will be virtual – posted online (Not in person)**
- **Class on Thurs 10/31 will be in person as usual so please be here in the class**
- **Prof office hours next week:** Thurs 10/31 from 12-2pm or by email appointment
- **TA office hours:** are now MWF 9-11am for Fall'24
 - Zoom Meeting ID: 948 6397 0932; Passcode 004453
 - <https://ucsd.zoom.us/j/94863970932?pwd=iXcQXbLYjOaAQtdOjlrmgICyMSyeir.1>
- **TA Discussion session:** Wed 4-4:50PM (in person) Location: CNTRE 214
- **Oct 22:** Homework 4 was posted on Canvas
 - Due on Wed Oct 30, **10/30/24**
 - **Late homework policy:** Max of 2 late days, with 20% grade reduction per day

Homework 4 overview

- Design of Linear Feedback Shift Register (LFSR), Barrel Shifter, Gray to Binary Code Convertor
- You will learn how to:
 - Create synthesizable SystemVerilog code
 - Better learn how to use testbenches
 - Design functional SystemVerilog code that can compile post synthesis.
- There will be three parts for this homework:
 - **Homework-4a:** Developing a Synthesizable SystemVerilog Model for a Linear Feedback Shift Register (LFSR)
 - **Homework-4b:** Developing a synthesizable SystemVerilog model of a Barrel Shifter
 - **Homework-4c:** Developing a synthesizable SystemVerilog model of a Gray to Binary Code Convertor

Recap

always Procedural Blocks

Category	Usage Example	Purpose	Introduced in Verilog or SV?
<code>always@(<level sensitivity list>)</code>	<code>always@(a, b) begin // assignment statements end</code>	Model Combinational Logic	Verilog
<code>always@(<edge sensitivity list>)</code>	<code>always@(posedge clk, negedge reset) begin // assignment statements end</code>	Model Sequential Logic	Verilog
<code>always@(*)</code>	<code>always@(*) begin // assignment statements end</code>	Model Combinational Logic	Verilog
<code>always_comb</code>	<code>always_comb begin // assignment statements end</code>	Model Combinational Logic	SystemVerilog
<code>always_ff@(<edge sensitivity list>)</code>	<code>always_ff@(posedge clk, negedge reset) begin // assignment statements end</code>	Model Edge-Sensitive Sequential Logic	SystemVerilog
<code>always_latch</code>	<code>always_latch begin // assignment statements end</code>	Model Level-Sensitive Sequential Logic	SystemVerilog

Which Statements are True?

- ❑ `always_comb` does infer a complete sensitivity list when the `always_comb` block contains functions
- ❑ `always_comb` automatically executes once at time zero, whereas `always@(*)` waits until a change occurs on a signal in the inferred sensitivity list
- ❑ `always@(*)` may not infer a complete sensitivity list when the `always @(*)` block contains functions
- ❑ `always_comb` does infer a complete sensitivity list when the `always_comb` block contains functions

always_ff Block

- **always_ff** procedure is used to model **sequential flip-flop logic**
- In **always_ff**, **sensitivity list** must be specified by designer
 - This is because since synthesis and compiler tools cannot infer the clock name and edge automatically from the body of **always_ff**
 - Synthesis and compiler tools does not know whether a reset is asynchronous or synchronous. If asynchronous then reset information is required to be specified in sensitivity list

```
always_ff@(posedge clk)  
  q<=d
```

```
always_ff@(posedge clock or posedge reset)  
begin  
  if (reset) out <= 0;  
  else out <= out + 1;  
end
```

Mixing Single and Double Edge in Sensitivity List

D-FlipFlop with Asynchronous Reset

```
module dff1(  
  input logic clk, d, reset,  
  output logic q  
);  
always_ff@(posedge clk, reset)  
begin  
  if(reset)  
    q <= 0;  
  else  
    q <= d;  
end  
endmodule: dff1
```

Mixing single and double edge
in sensitivity list is not allowed
and code will not synthesize




- ✖ 10122 Verilog HDL Event Control error at dff1.v(5): mixed single- and double-edge expressions are not supported
- ⚠ 10235 Verilog HDL Always Construct warning at dff1.v(9): variable "d" is read inside the Always Construct but isn't in the Always Construct's Event Control
- ✖ 12153 Can't elaborate top-level user hierarchy
- > ✖ Quartus Prime Analysis & Synthesis was unsuccessful. 2 errors, 2 warnings

D-FF model with Reset


D-FlipFlop with Synchronous Active High Reset
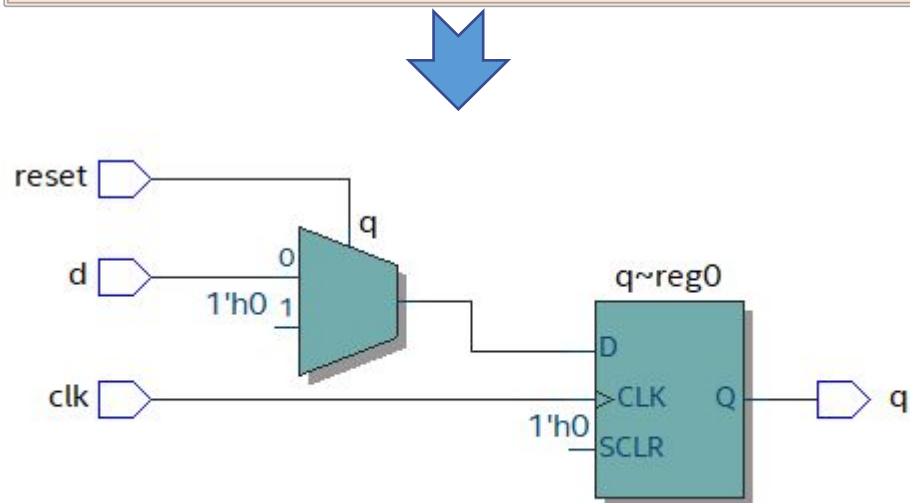
```
module dff(  
  input logic clk, d, reset,  
  output logic q  
);  
always_ff@(posedge clk) begin  
  if(reset)  
    q <= 0;  
  else  
    q <= d;  
  end  
endmodule: dff
```



D-FlipFlop with Asynchronous positive edge reset


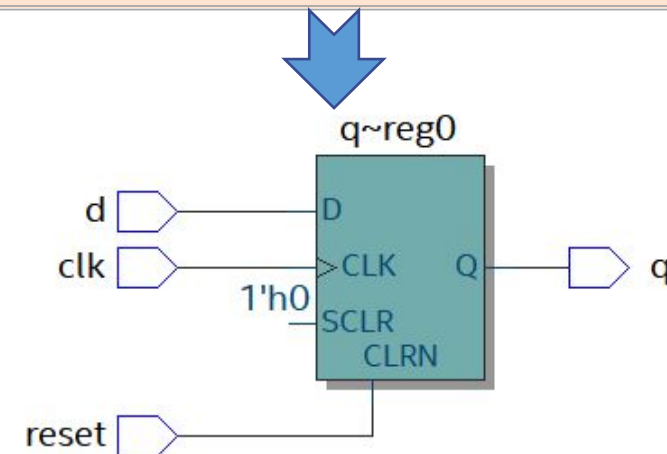
```
module dff(  
  input logic clk, d, reset,  
  output logic q  
);  
always_ff@(posedge clk, posedge reset) begin  
  if(reset)  
    q <= 0;  
  else  
    q <= d;  
  end  
endmodule: dff
```



Resettable D-FF Model

D-FlipFlop with Asynchronous Negedge Reset

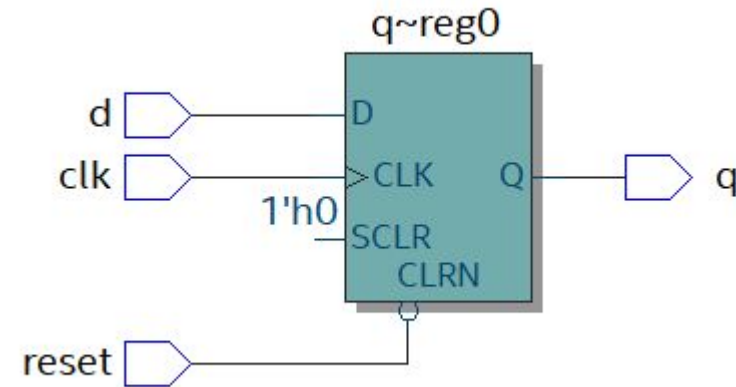 
```
module dff(  
  input logic clk, d, reset,  
  output logic q  
);  
always_ff@(posedge clk, negedge reset) begin  
  if(!reset)  
    q <= 0;  
  else  
    q <= d;  
  end  
endmodule: dff
```



D-FF Model with Clock Enable and Asynch Reset

D-FlipFlop with **Clock Enable** and Asynchronous Reset
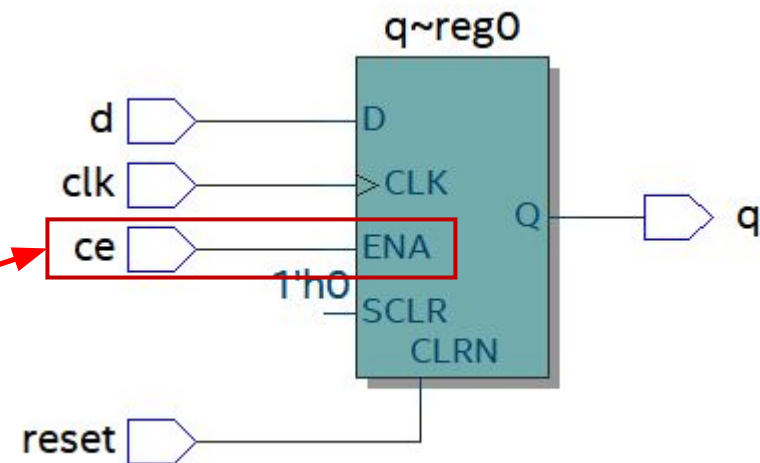
```
module dff(  
  input logic clk, d, reset, ce,  
  output logic q  
);  
always_ff@(posedge clk, posedge reset)  
begin  
  if(reset)  
    q <= 0;  
  else  
    if(ce) // synchronous clock enable  
      q <= d;  
  end  
end  
endmodule: dff
```




always_latch

always Block: always_latch

- **always_latch** indicates to EDA tools, that designer of RTL code intents to model a latch
- Similar to **always_comb**, i.e., all signals read within **always_latch** block are **automatically inferred in sensitivity list**. Including in case of **function calls with partial list of signals** in argument list.
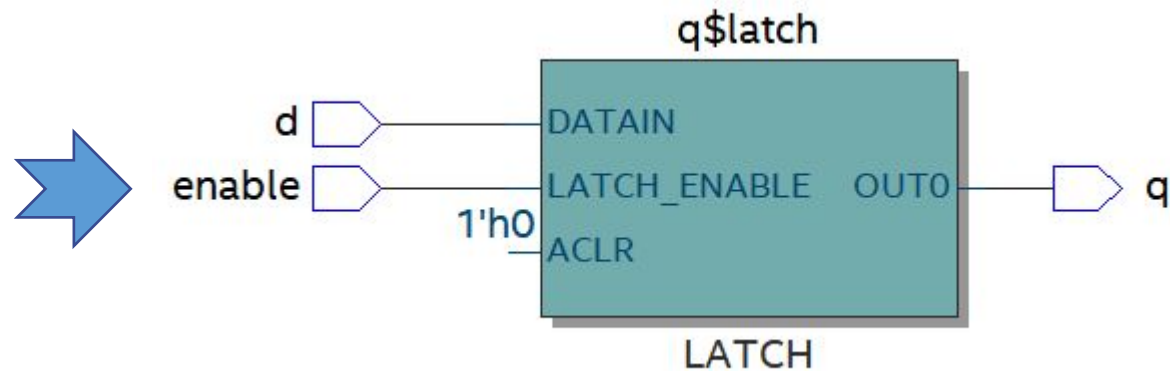
```
module latch(  
  input logic d, enable,  
  output logic q  
);  
  
always_latch begin  
  if(enable)  
    q <= d;  
end  
  
endmodule: latch
```



always_latch Coding Rules

- **always_latch** enforces some of the coding guidelines for synthesis
 1. Any constructs such as **#, @ and wait**, which delays execution of statements are **not permitted** within `always_latch`
 2. Variables assigned in `always_latch` **cannot be assigned by any other** procedure or continuous assignment statement.

always Block: always_latch

Approach-A : Latch Model using
always@(<explicit sensitivity list>)

```
module latch(  
  input logic d, enable,  
  output logic q  
);  
always@(d, enable) begin  
  if(enable)  
    q <= d;  
end  
endmodule: latch
```

Missing else branch will
result in latch inference


Synthesis compiler throws a warning for a
potentially unintentional latch

Warning (10240): Verilog HDL Always
Construct warning at latch.v(6) : inferring
latch(es) for variable "q", which holds its
previous value in one or more paths
through the always construct

Approach-B: Latch Model using
always@(*) auto sensitivity list

```
module latch(  
  input logic d, enable,  
  output logic q  
);  
always@(*) begin  
  if(enable)  
    q <= d;  
end  
endmodule: latch
```

 Missing else branch will
result in latch inference



Approach-C Latch Model using
always_latch auto sensitivity list

```
module latch(  
  input logic d, enable,  
  output logic q  
);  
always_latch begin  
  if(enable)  
    q <= d;  
end  
endmodule: latch
```


Best
Practice

Synthesis compiler does not generate any
warning message since always_ff instructs
synthesis compiler to infer an intentional latch.
Instead generates a info message

Info (10041): Inferred latch for "q" at latch.v(6)


Latch Model Simulation Results

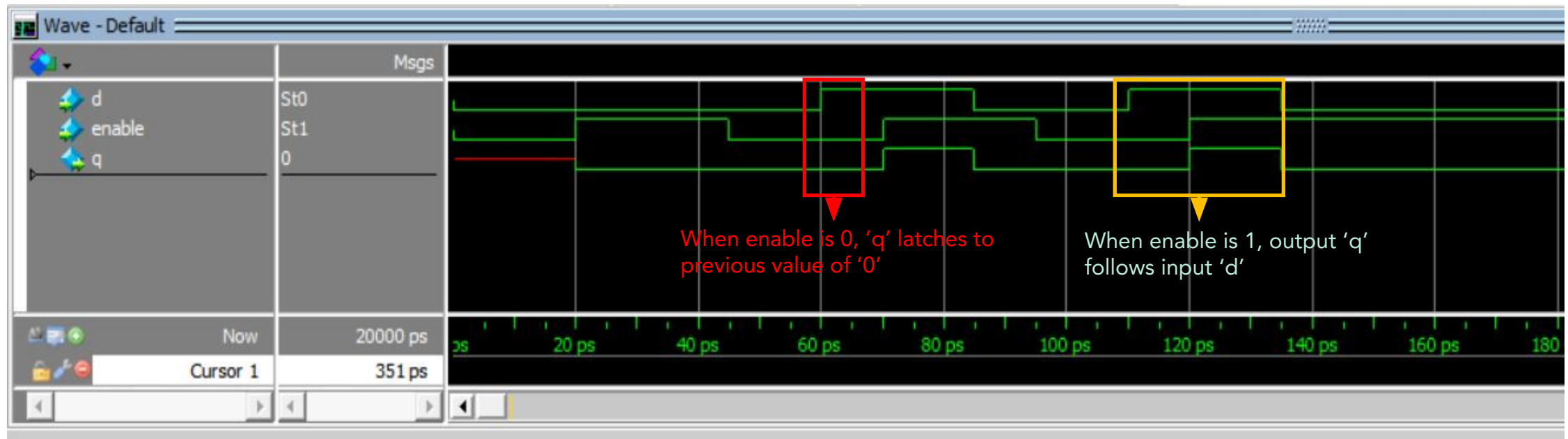- All three approaches give an identical simulation result




Latch with Asynchronous Negedge clear
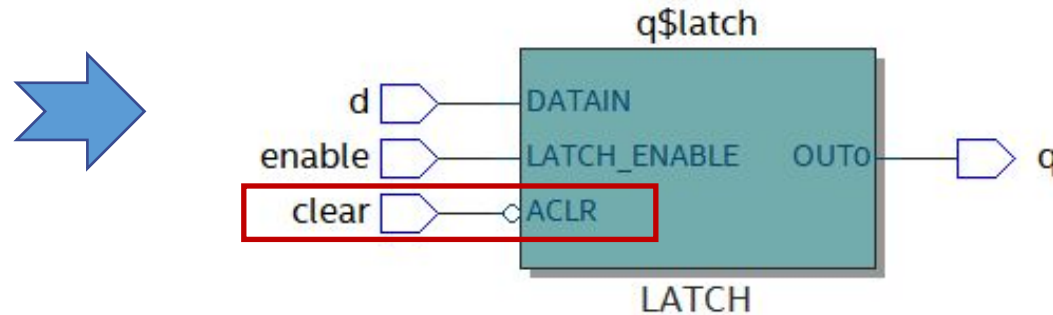
```
module latch(  
  input logic d, enable, clear,  
  output logic q  
);  
always_latch begin  
  if(!clear) // asynchronous !clear  
    q <= 0;  
  else if(enable)  
    q <= d;  
end  
endmodule: latch
```



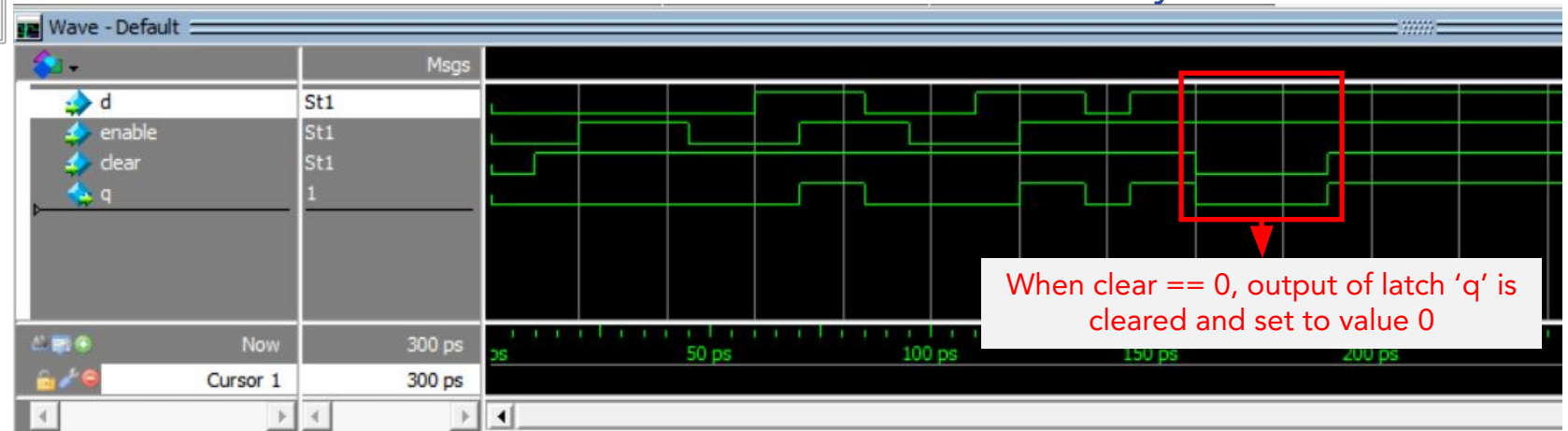Simulation result of latch with asynchronous clear



Latch Model with Function Calls

- Both implementations will infer a latch when synthesizing the logic, however simulation behavior will be different with **always_latch** vs **always@(*)** implementations.

Latch RTL model using always@(*)

```
module latch(  
  input logic d, enable,  
  output logic q  
);  
  
function logic func_latch();  
  func_latch = d;  
endfunction  
  
always@(*) begin  
  if(enable)  
    q <= func_latch();  
end  
endmodule: latch
```

func_latch will not trigger when there is change in value of "d" and when enable is '1' but enable value did not change

Same synthesis results.
(latch will be inferred)



Different simulation results




Latch RTL model using always_latch

```
module latch(  
  input logic d, enable,  
  output logic q  
);  
  
function logic func_latch();  
  func_latch = d;  
endfunction  
  
always_latch begin  
  if(enable)  
    q <= func_latch();  
end  
endmodule: latch
```


func_latch will be triggered whenever there is change in value of "d" and when enable is '1' but enable value did not change

Latch Model Simulation Results
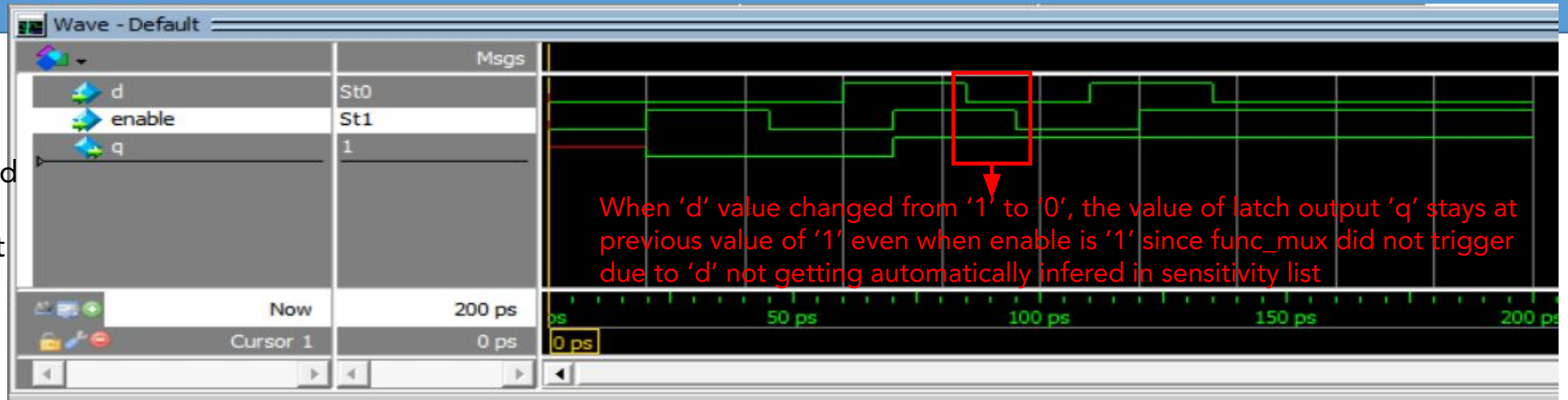
`always@(*)` based
implementation
simulation result


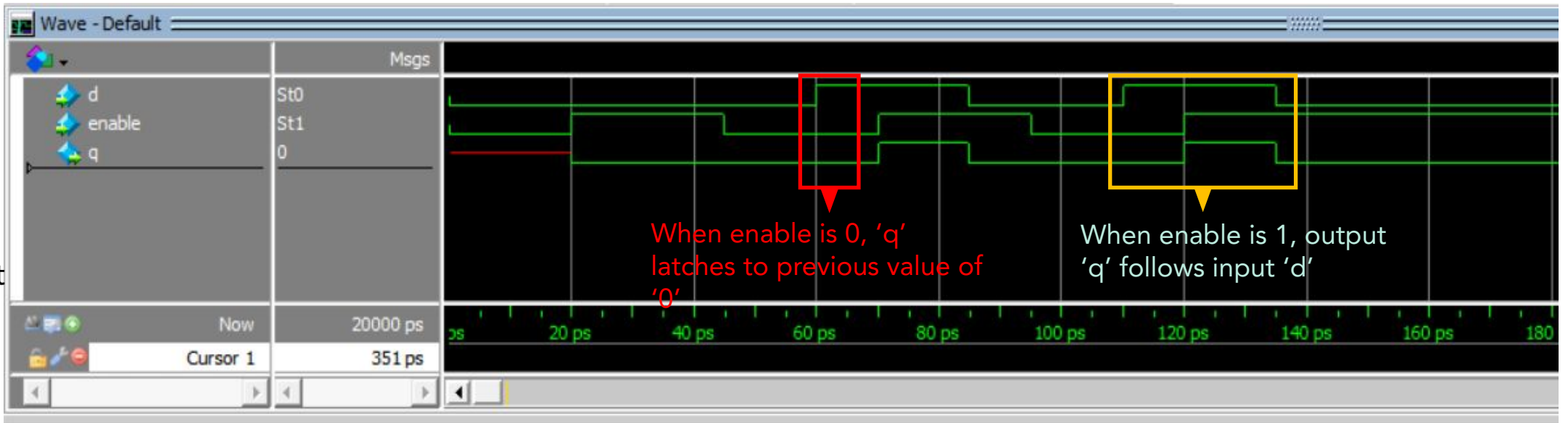
`always_latch`
based
implementation
simulation result



Summary on always Procedures

- **Verilog-2001** supported below mentioned always procedures :
 - `always@(<explicit sensitivity list>)` to model combinational and sequential logic
 - `always@(*)` to model combinational and sequential logic

Note : Avoid Verilog `always@(*)` usage!
- **SystemVerilog** introduced three more always procedures which brings some enhanced capabilities and addressed ambiguity in Verilog Language :
 - **`always_comb`** to model combinational logic
 - **`always_latch`** to model latch
 - **`always_ff@(<explicit sensitivity list>)`** to model sequential logic
- SystemVerilog always procedures addressed some of the limitations of Verilog-2001 always procedures and **clearly conveys design** intent to EDA tools
 - Hence suggestion is to **use SystemVerilog always procedures wherever possible** in RTL model!

Summary on always Procedures

- **always_comb** and **always_latch** will execute at time zero of the simulation, ensuring the variables on the left-hand side of assignments within the block correctly reflect the values on the right and side at time 0.
- **always_comb** and **always_latch** are sensitive to signal changes within a function called by the procedural block, and not just the function arguments, which was a bug with **always @(*)**
- **always_latch** and **always_ff** procedural blocks can prevent serious modeling errors, and they enable software tools to verify that design intent has been met.
- **Recommendation** — Use **always_comb**, **always_latch** and **always_ff** in all RTL code.
 - Only use the general purpose **always** procedure in models that are not intended to be synthesized, such as bus-functional models, abstract RAM models, and verification testbenches.

always Procedural Blocks
Example...

Example 1

```
module ex1(  
  input logic clk,  
  input logic t, c,  
  output logic f  
);  
  
  always_ff@(posedge clk)  
  begin  
    f <= t & c;  
  end  
endmodule: ex1
```

Example 1: Creating Combinational Logic and D-flipflop

```
module ex1(  
  input logic clk,  
  input logic t, c,  
  output logic f  
);
```

```
  always_ff@(posedge clk)
```


```
  begin
```

```
    f <= t & c;
```

```
  end
```

```
endmodule: ex1
```

- Positive edge triggered D Flip-flop produced for "f"
- "And" gate produced for t & C

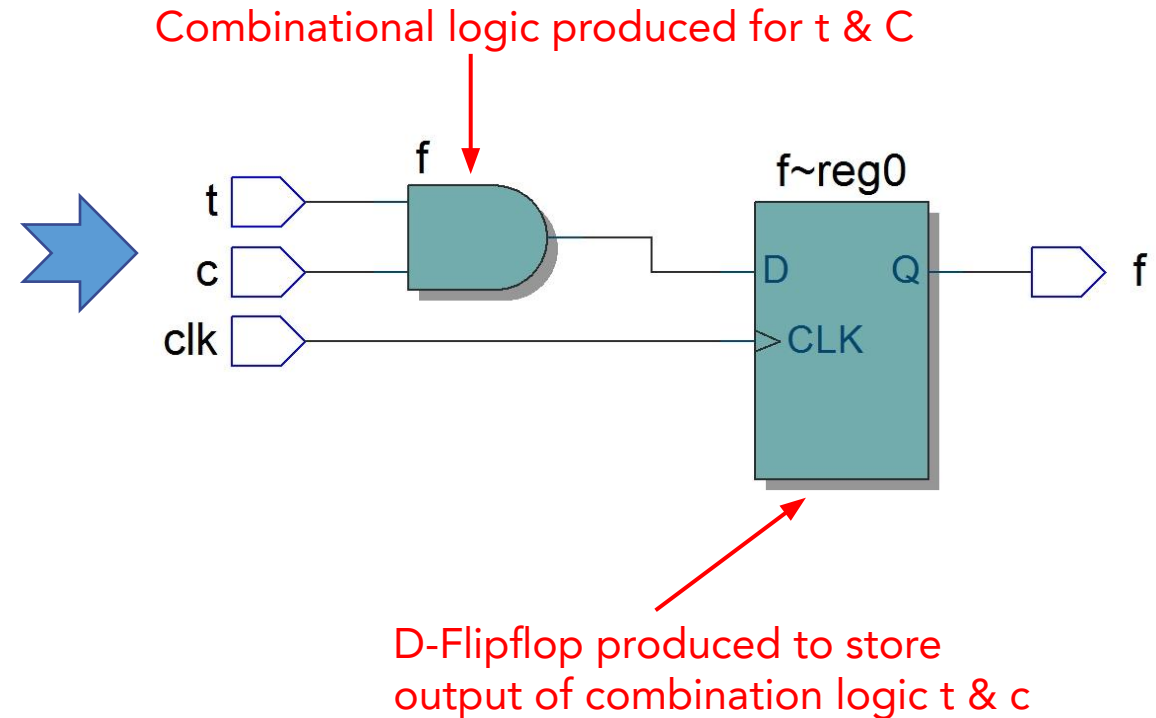

Example 2

```
module counter #(parameter N=4)
(
  input  logic clk, clr,
  output logic[N-1:0] q
);

  logic[N-1:0] cnt;

  always_ff@(posedge clk or posedge clr)
  begin
    if(clr)
      cnt <= 'b0;
    else
      cnt <= cnt + 1'b1;
    end

    assign q = cnt;
  endmodule: counter
```

Example 2: N-bit Up-Counter/Asynch clear

```
module counter #(parameter N=4)
```

```
(  
  input  logic clk, clr,  
  output logic[N-1:0] q  
);
```

```
  logic[N-1:0] cnt;
```

```
  always_ff@(posedge clk or posedge clr)
```

```
  begin
```

```
    if(clr)
```

```
      cnt <= 'b0;
```


```
    else
```

```
      cnt <= cnt + 1'b1;  '+' operator will infer an  
    end                adder
```

```
    assign q = cnt;
```

```
endmodule: counter
```

Feedback from q to input of adder is created due to counter incrementing from the previous output value

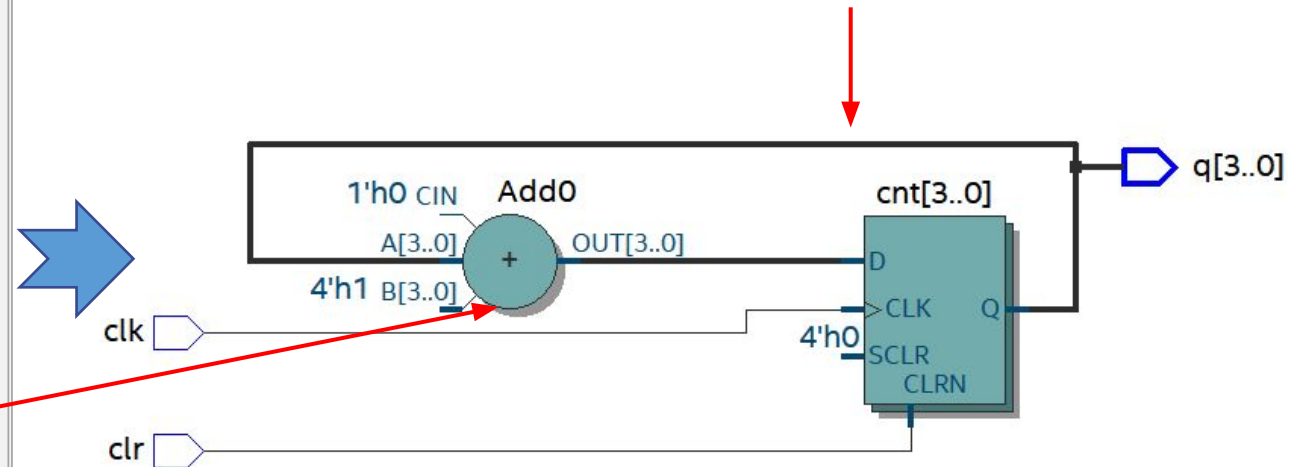


Example 3

```
module ex3(  
    input logic clk,  
    input logic a, b, c,  
    output logic f);  
  
    logic t;  
  
    always_ff@(posedge clk) begin  
        t <= a & b;  
        f <= t & c;  
    end  
endmodule: ex3
```

Example 3: Serially connected D Flip-flops with Combination Logic

```
module ex3(  
  input logic clk,  
  input logic a, b, c,  
  output logic f);  
  
  logic t;  
  
  always_ff@(posedge clk) begin  
    t <= a & b; ← LHS stores output of AND-gate to "t" register  
    f <= t & c; ← RHS reads from "t" register  
  end  
endmodule: ex3
```

D-FF produced
for "t" and "f"

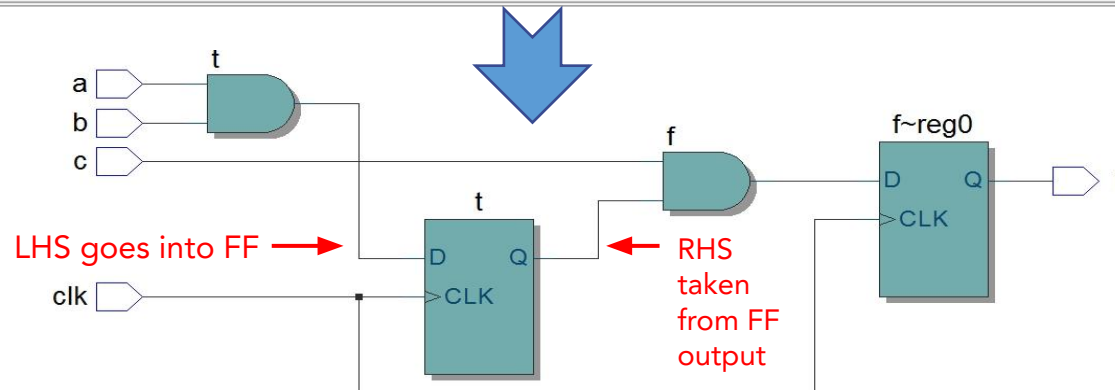


Example 4

```
module ex4 (  
    input logic clk, reset_n, op,  
    input logic[3:0] x,  
    output logic[3:0] dataout);  
  
    always_ff@(posedge clk, negedge reset_n)  
    begin  
        if(!reset_n)  
            dataout <= 4'b0000;  
        else  
            if (op)  
                dataout <= dataout + x;  
            else  
                dataout <= dataout - x;  
        end  
    end  
  
endmodule: ex4
```

Example 4: Clocked always_ff Statement with (Negedge) Reset

```
module ex4 (  
    input logic clk, reset_n, op,  
    input logic[3:0] x,  
    output logic[3:0] dataout);  
  
    always_ff@(posedge clk, negedge reset_n)  
    begin  
        if(!reset_n)  
            dataout <= 4'b0000;  
        else  
            if (op)  
                dataout <= dataout + x;  
            else  
                dataout <= dataout - x;  
        end  
    end  
  
endmodule: ex4
```

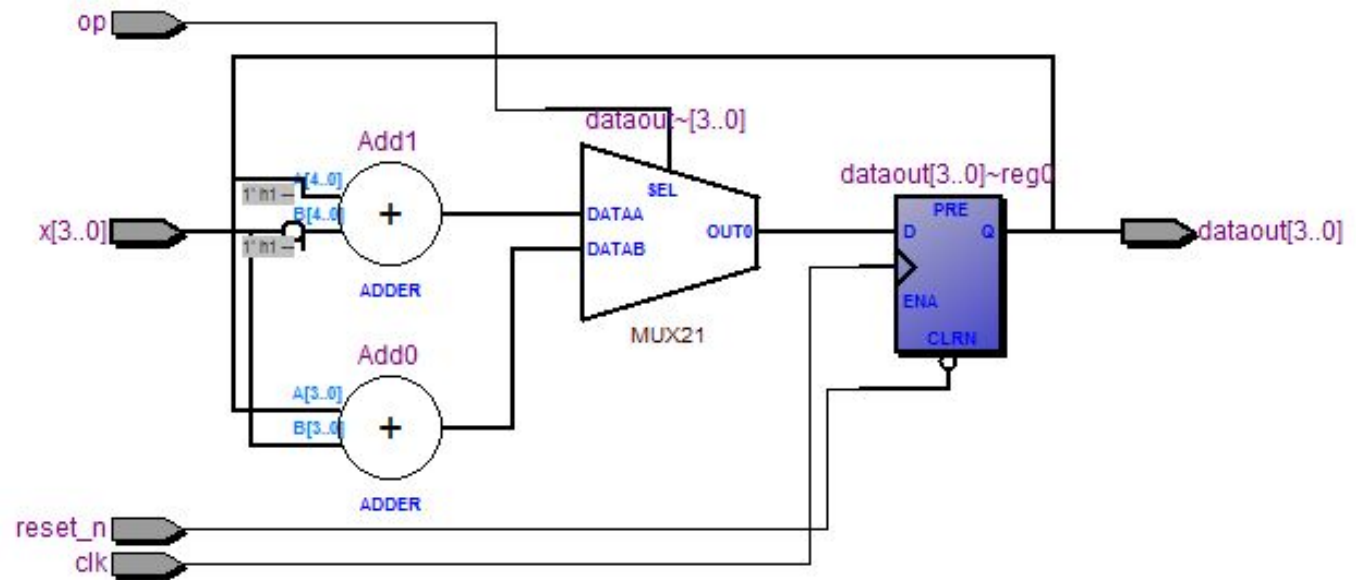


Example 5: Mixing Procedural Blocks and Continuous Assignment Statements

```
module ex5 (input logic clk, reset_n, op,  
            input logic [3:0] x,  
            output logic [3:0] dataout);  
            logic [3:0] y, z;
```

```
always_ff@(posedge clk, negedge reset_n)  
begin  
    if (!reset_n)  
        y <= 4'b0000;  
    else  
        if (op)  
            y <= y + x;  
        else  
            y <= y - x;  
    end  
end
```


```
assign z = y + 1;  
assign dataout = z + 1;  
endmodule: ex5
```

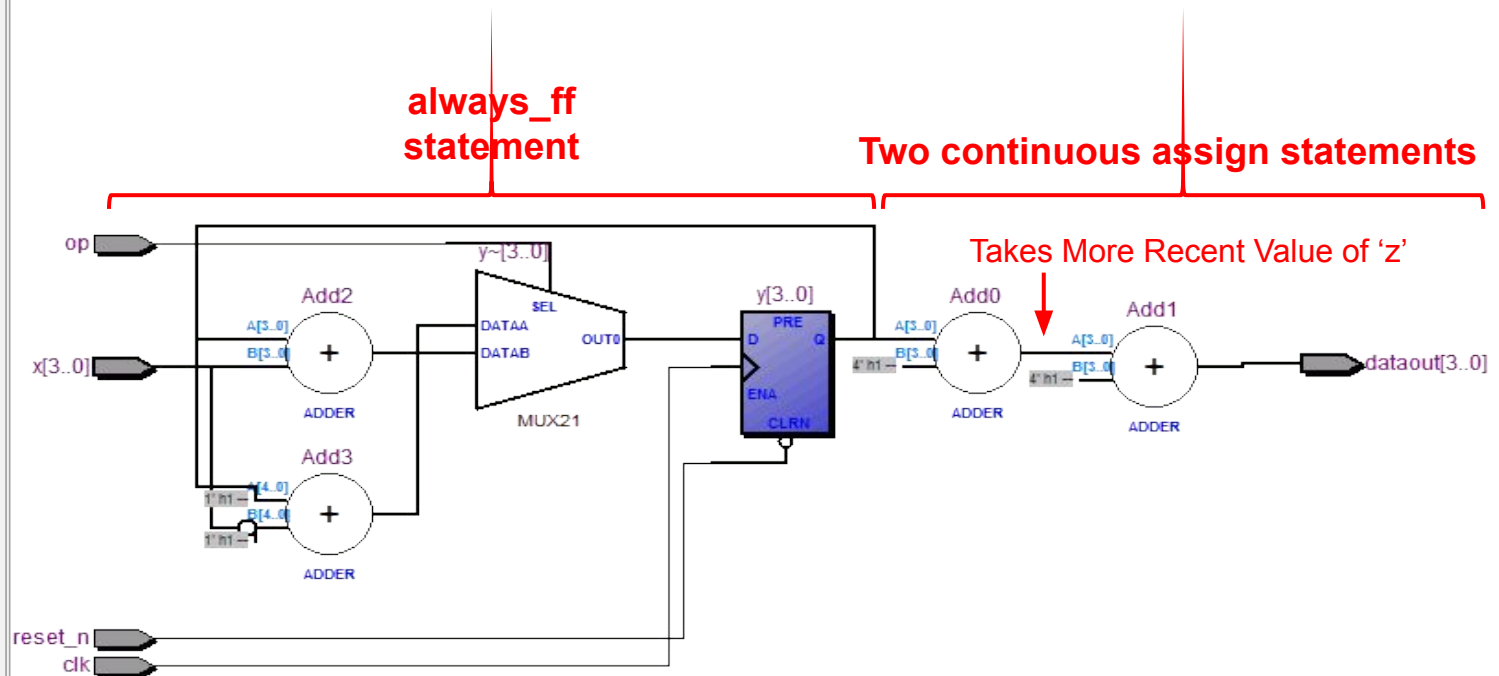

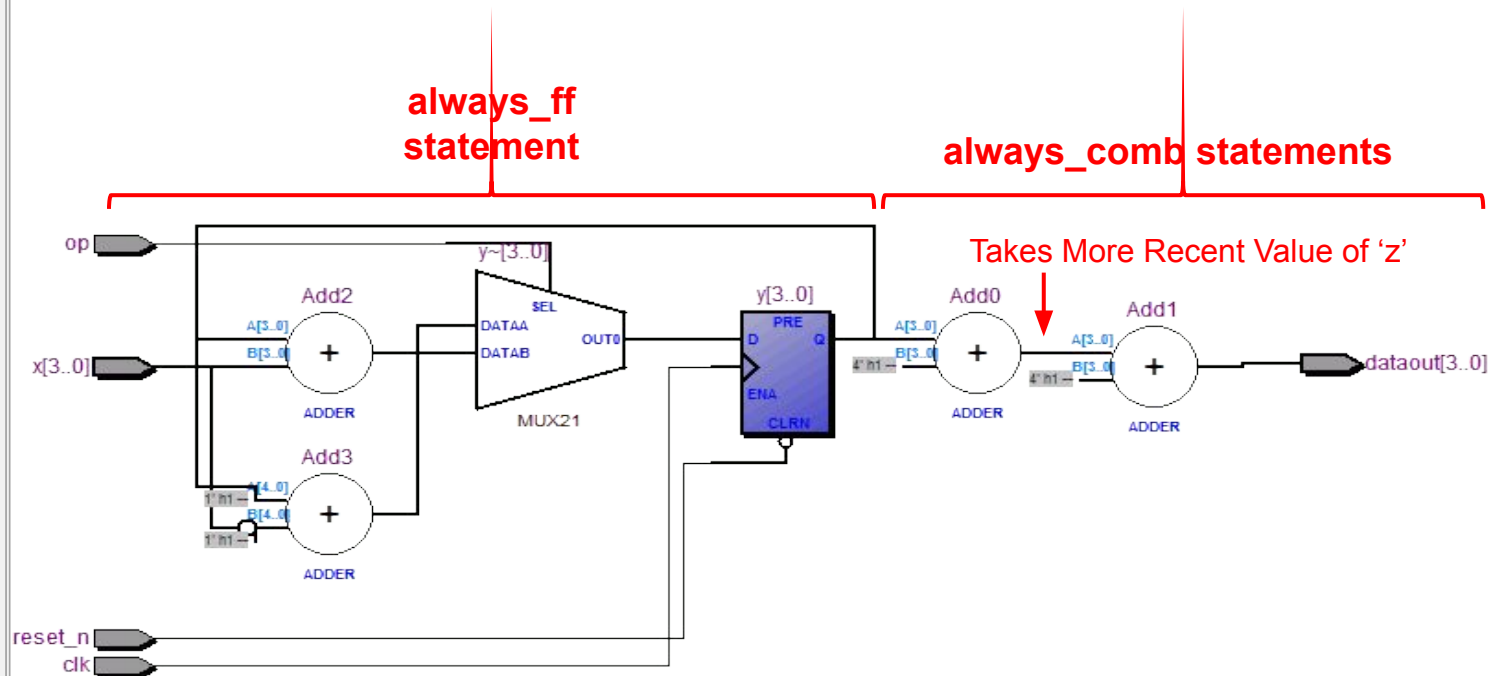Example 6: Mixing Procedural Blocks and Continuous Assignment Statements

```
module ex6 (input logic clk, reset_n, op,  
            input logic [3:0] x,  
            output logic [3:0] dataout);  
            logic [3:0] y, z;
```

```
always_ff@(posedge clk, negedge reset_n)  
begin  
    if (!reset_n)  
        y <= 4'b0000;  
    else  
        if (op)  
            y <= y + x;  
        else  
            y <= y - x;  
    end  
end  
always_comb begin  
    z = y + 1;  
    dataout = z + 1;  
end  
endmodule: ex6
```



`always_ff` Good and Bad Coding
Styles

D-Similar D-FF (Bad Coding...)

```
module bad_FF_coding(  
    input logic clk, d, reset_n,  
    output logic q2);  
  
    logic q1;  
  
    always_ff@(posedge clk) begin  
        if(!reset_n)  
            q1 <= 1'b0;  
        else begin  
            q1 <= d;  
            q2 <= q1;  
        end  
    end  
  
endmodule: bad_FF_coding
```


D-Similar D-FF (Bad Coding...)

Synchronous Reset D-FlipFlop with
Non-Reset Follower FlipFlop

```
module bad_FF_coding(  
    input logic clk, d, reset_n,  
    output logic q2);  
  
    logic q1;  
  
    always_ff@(posedge clk) begin  
        if(!reset_n)  
            q1 <= 1'b0;  
        else begin  
            q1 <= d;  
            q2 <= q1;  
        end  
    end  
  
endmodule: bad_FF_coding
```



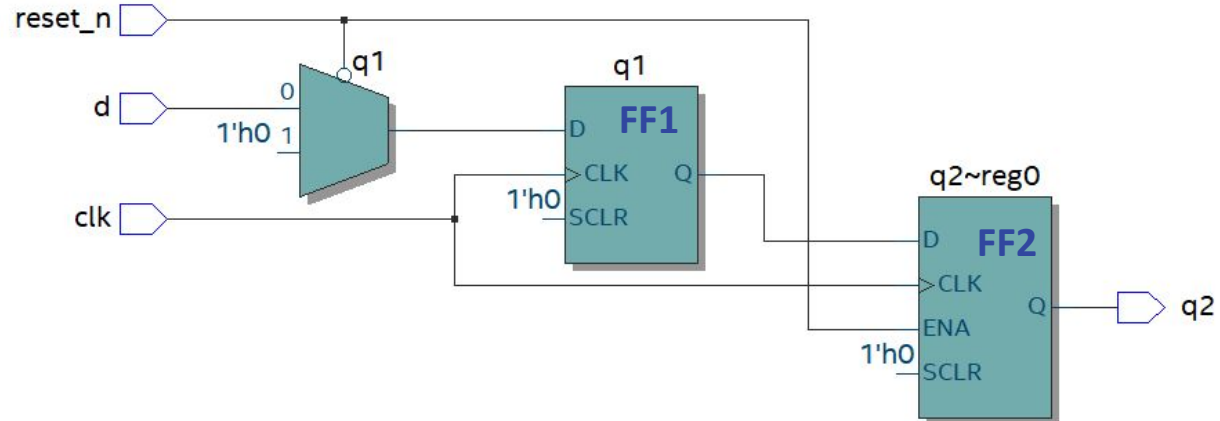Since the two flip-flops (FF1 and FF2) were inferred in the **same** procedural always_ff block and second flip-flop FF2 is not resettable, the reset signal reset_n will be used as a data enable for the second flop FF2




D-Similar D-FF (Good Coding...)

Synchronous Reset D-FlipFlop with Non-Reset Follower FlipFlop

```
module good_FF_coding(  
    input logic clk, d, reset_n,  
    output logic q2);  
  
    logic q1;  
  
    always_ff@(posedge clk) begin  
        if(!reset_n)  
            q1 <= 1'b0;  
        else  
            q1 <= d;  
        end  
    end  
  
    always_ff@(posedge clk) begin  
        q2 <= q1;  
    end  
  
endmodule: good_FF_coding
```

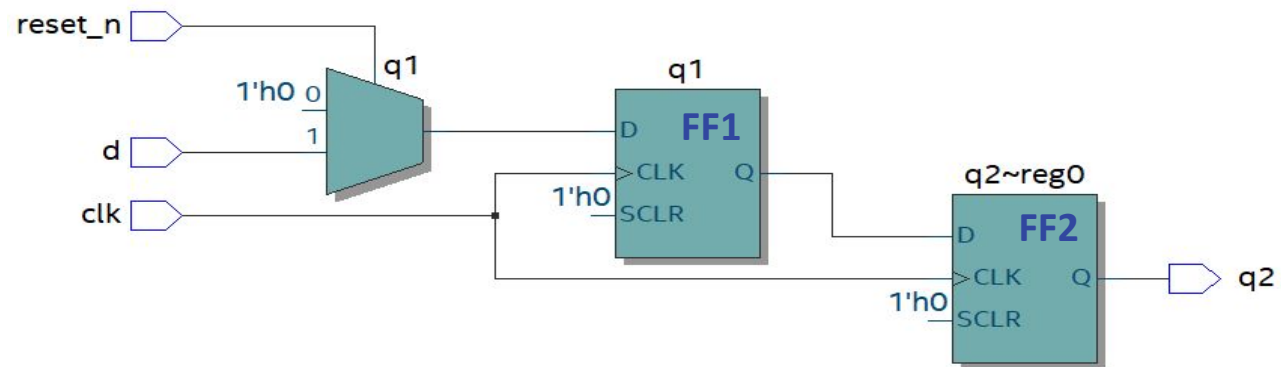Since the two flip-flops (FF1 and FF2) were inferred in different procedural always_ff, the reset signal reset_n will not be used as a data enable for the second flop FF2



Multiple Assignment Statements on Same Variable

```
module adder(  
  input logic clk, add1, add2,  
  output logic result  
);  
  
always_ff@(posedge clk) begin  
  if(add1) result <= result + 1;  
  if(add2) result <= result + 2;  
end  
  
endmodule: adder
```



Code will synthesize however circuit will not function correctly.

Why? (watch the lecture discussion!)

Initial Procedural Blocks

Initial Procedural Blocks

- **Initial block** is used to develop testbench code to **simulate** design/RTL code
 - Create and specify how stimulus will be applied to input signals in design
 - Specifies initialization of local variables in testbench code and forcing of internal design signals
 - Specifies how the design signals are monitored and displayed
 - Specifies simulation pass and fail criteria and checking mechanism
 - Specifies the file where the signal waveform information is to be dumped

- **Syntax**

```
initial
    <optional delay> <programming statement>
end
```

```
Initial begin
    <optional delay> <programming statement>
    ....
    ....
    <optional delay> <programming statement>
end
```

Initial Procedural Blocks

- Initial block is executed at the beginning of the simulation at time 0
- Initial block is executed **only once** in simulation
 - Initial block finishes once all the statements within the block are executed and does not execute again for a given run of a simulation
 - Initial block will advance simulation

```
module tesbench;  
  logic reset, enable;  
  initial begin  
    reset = 1;  
    enable = 0;  
    #10ns reset = 0;  
    enable = 1;  
    #5ns;  
    enable = 0;  
  end  
endmodule
```

initial block starts execution at time 0

- reset will get value 1 and enable will get value 0 at time 0ns
- simulation will advance to 10ns and then reset will get new value 0 and enable is assigned new value 1;
- simulation will advance 5ns to reach at 15ns (10ns + 5ns) timestamp and then enable will be assigned new value 0

initial block terminates forever once enable is assigned value 0 at time 15ns

Multiple Initial Blocks can result in Race Conditions

```
module multiple_initial_block_with_race;  
  logic reset, enable;  
  // initial block-1  
  initial begin  
    reset = 1;  
    #20ns reset = 0;  
  end  
  // initial block-2  
  initial begin  
    enable = 0;  
    #20ns enable = reset;  
  end  
endmodule
```



Not recommended!

Brief Summary on initial and always Procedural Blocks

Initial Procedural Blocks

- **Not synthesizable** and does not generate hardware logic
- Used for **simulation purpose**
- Starts **execution from beginning** of a simulation at time 0
- **Executes only once** during simulation and it terminates when all statements within it are executed
- **Any number** of initial blocks can be defined within a module
- **Multiple** initial blocks executes **concurrently**

Always Procedural Blocks

- **Synthesizable** and it can generate hardware logic
- Used for **specifying design behavior** (RTL code)
- Starts **execution from beginning** of a simulation at time 0
- **Executes repeatedly**. Its activity shall cease only when the simulation is terminated
- **Any number** of always blocks can be defined within a module
- **Multiple** always blocks executes **concurrently**

Quiz