


First order circuits 007

Problem has been graded.

The switch closes at time $t = 0$ and we measure

$$v(t) = 24 - 12e^{-t/2\mu s} \text{ V} \quad \text{for } t > 0$$

Find the values of R_1 , R_2 , and L_1 .

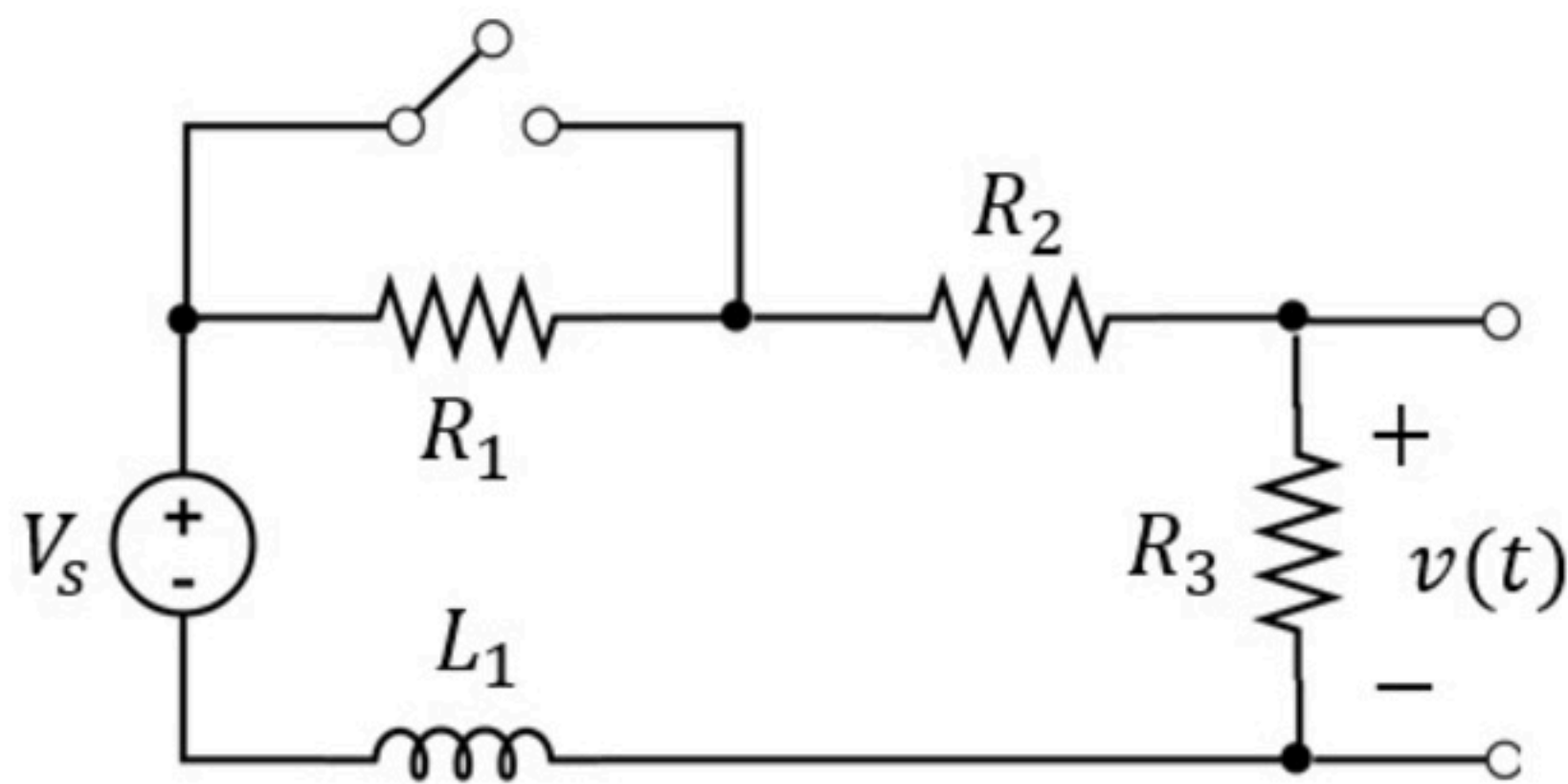

Given Variables:

V_s : 48 V

R_3 : 12 kohm

Calculate the following:

R_1 (ohm) :

24000



R_2 (ohm) :

12000



L_1 (H) :

0.048



Hint: Consider $v(\infty)$ first. Mind the units.