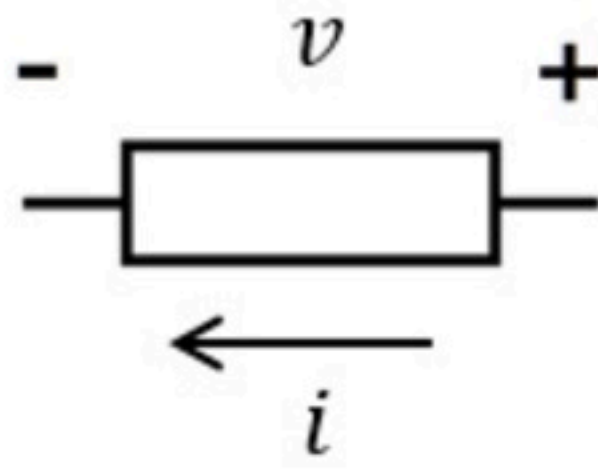



# Basic Concepts 011

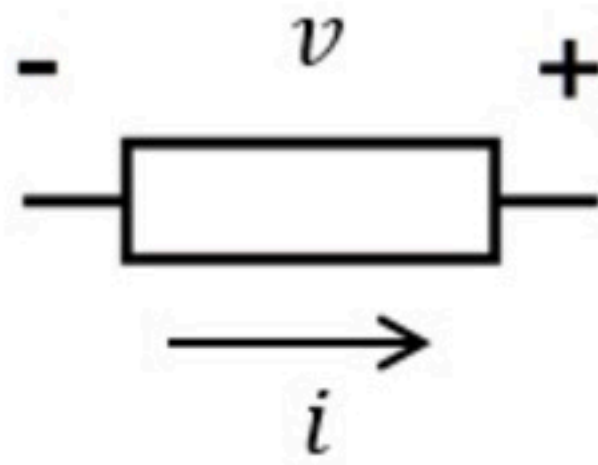Problem has been graded.


Find the power  $P_1$  supplied by this element:



Find the power  $P_2$  supplied by this element:



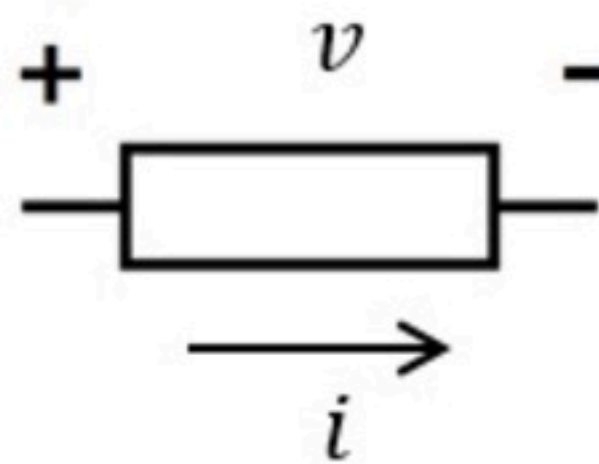Find the power  $P_3$  received by this element:



Given Variables:

$v$  : -5 V

$i$  : 4 A

Calculate the following:

$P_1$  (W) :

$P_2$  (W) :

$P_3$  (W) :

Hint: Convert first to passive sign convention