
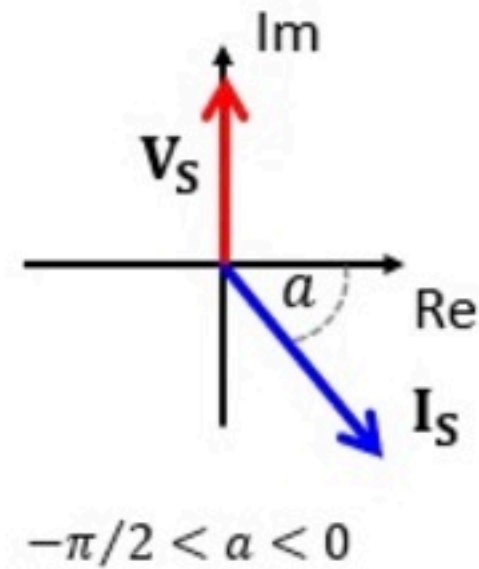


Phasors 019

0 of 5 attempts made

The AC circuit below has $\omega = W_1$ and is in steady state. The phasor diagram shows the phasors of v_S and i_S . You are given the angle a , and vector lengths $|\mathbf{I}_S| = A_1$ and $|\mathbf{V}_S| = A_2\sqrt{b}$. The diagram is not necessarily drawn to scale (but \mathbf{V}_S is along the imaginary axis). The element in the center (rectangular box) is either an inductor or a capacitor but you are not told which.

- At what time does v_R reach its maximum value? Enter $k = t_0 \cdot \frac{12}{\pi}$, where t_0 is the first time that the maximum is reached, for $t_0 \geq 0$. (Hint: convert a to radians first)
- We select the mystery element such that $|\mathbf{I}_a|$ is minimized (note that this is the current through the voltage source). What is the mystery element type (enter 1 for capacitor, 2 for inductor)? What is its value X (i.e., either the capacitance or the inductance value, in F or H respectively)?

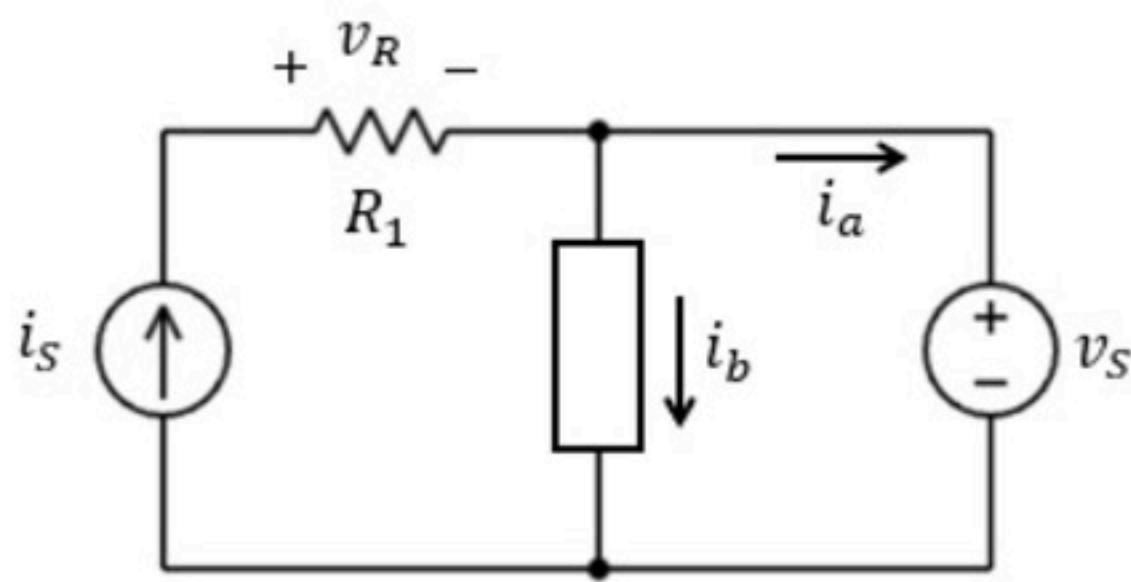

Given Variables:

W1 : 4 rad/s

a : -30 degrees

A1 : 1 A

A2 : 10 V

b : 3

R1 : 1 ohm

Calculate the following:

k (s) :

0.5



Type :

2





X :

5



The AC circuit below has $\omega = \omega_1$ and is in steady state. The phasor diagram shows the phasors of v_s and i_s . You are given the angle α , and vector lengths $|I_s| = A_1$ and $|V_s| = A_2\sqrt{b}$. The diagram is not necessarily drawn to scale (but V_s is along the imaginary axis). The element in the center (rectangular box) is either an inductor or a capacitor but you are not told which.

- At what time does v_R reach its maximum value? Enter $k = t_0 \cdot \frac{12}{\pi}$, where t_0 is the first time that the maximum is reached, for $t_0 \geq 0$. (Hint: convert α to radians first)
- We select the mystery element such that $|I_a|$ is minimized (note that this is the current through the voltage source). What is the mystery element type (enter 1 for capacitor, 2 for inductor)? What is its value X (i.e., either the capacitance or the inductance value, in F or H respectively)?

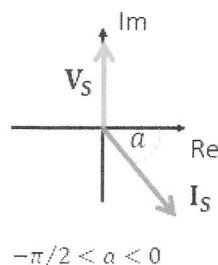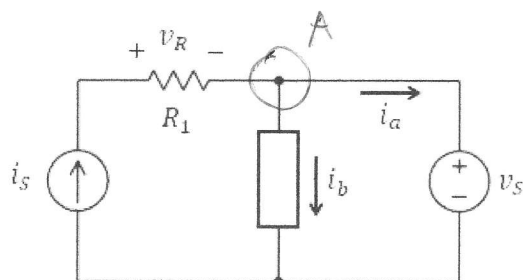

$$\begin{aligned}\omega_1 &= 2 \text{ rad/s} \\ \alpha &= -30^\circ \\ A_1 &= 2 \text{ A} \\ A_2 &= 10 \text{ V} \\ b &= 3 \\ R_1 &= 1 \Omega\end{aligned}$$

$$(a) V_R = R_1 I_s = R_1 \cdot A_1 e^{j\alpha} = 2 e^{-j30^\circ}$$



$$V_{R_{\max}} = |V_R| \quad V_R(t) = 2 \cos(2t - 30^\circ) \quad \text{MAX WHEN } \cos(\theta) = 1$$

$$\theta = 0 \Rightarrow 2t_0 - \frac{\pi}{6} = 0 \Rightarrow t_0 = \frac{\pi}{12} \Rightarrow k = t_0 \cdot \frac{12}{\pi} = 1 \quad \boxed{k=1}$$


$$(b) \text{ KCL @ A: } I_s = I_B + I_A$$

If the mystery element is a capacitor or inductor: I_b is perpendicular to V_s

Let's look at different options

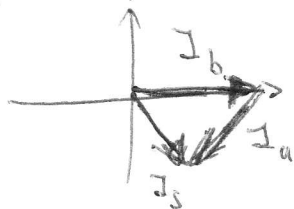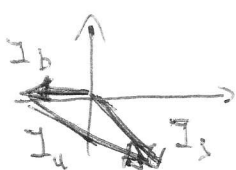

etc. \leadsto

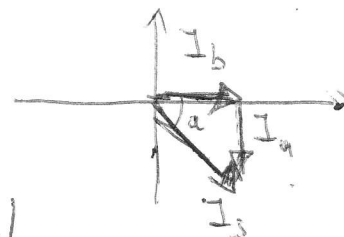

$$\cos(-\alpha) = \frac{|I_b|}{|I_s|} \Rightarrow \cos\left(\frac{\pi}{6}\right) = \frac{\sqrt{3}}{2} = \frac{|I_b|}{2}$$

$$|I_b| = \sqrt{3} \quad \text{on the real axis} \Rightarrow I_b = \sqrt{3}$$

$$\text{also: } V_s = Z \cdot I_b \Rightarrow Z = \frac{V_s}{I_b} = \frac{10\sqrt{3}}{\sqrt{3}} j = 10j$$

$$\begin{aligned}\text{This must be an inductor: } Z &= j\omega L = 10j \\ \Rightarrow \omega L &= 10 \Rightarrow L = \frac{10}{2} = 5 \text{ H} \\ \boxed{X=5}\end{aligned}$$