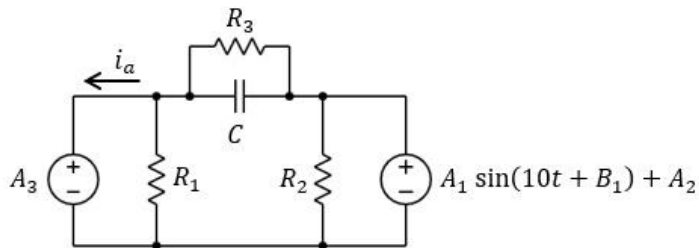


## Q1

Find steady state current  $i_a(t)$ .





$R_1$ :  $3\ \Omega$   
 $R_2$ :  $2\ \Omega$   
 $R_3$ :  $2\ \Omega$   
 $C$ :  $50\ \text{mF}$   
 $A_1$ :  $2\ \text{V}$   
 $B_1$ :  $-20\ \text{degrees}$   
 $A_2$ :  $3\ \text{V}$   
 $A_3$ :  $3\ \text{V}$

## Q2

The AC circuit below has  $\omega = 10\ \text{rad/s}$  and is in steady state. The phasor diagram shows the phasors of  $v_s$  and  $i_a$ . You are given  $|I_a|$  and  $|V_s|$ . The diagram is not necessarily drawn to scale (but  $V_s$  is along the imaginary axis and  $I_a$  is in the quadrant it is depicted).

The element on right (rectangular box) is either an inductor or a capacitor but you are not told which.

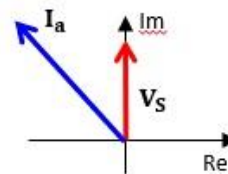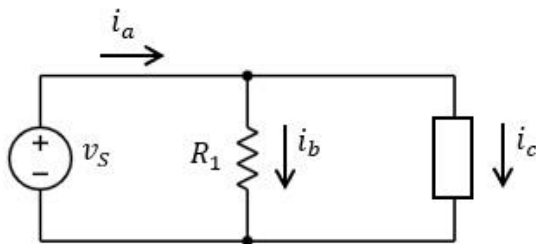- At what time  $t_0$  does the waveform of  $i_b$  reach its maximum value? (if there are multiple such times, giving one of them is sufficient).
- What is the mystery element (capacitor or inductor) and what is its value?



$|I_a|$ :  $5\ \text{A}$   
 $|V_s|$ :  $8\ \text{V}$   
 $R_1$ :  $2\ \Omega$