

ECE 35, Fall 2017

Final - Section A

Last name

First + middle  
name(s)


PID

**Instructions:**


- Read each problem completely and thoroughly before beginning.
- All calculations should be done in your blue book. It should be clear what question they belong to. Answers without supporting calculations will receive zero credit.
- Write clearly and make sure your answer is structured properly. We will not hunt for your work or answers.
- Write your final answers in the answer boxes on these question pages. Make sure you list units!

(1) Answer the questions below.


(a) What is the current  $i_1$ ?

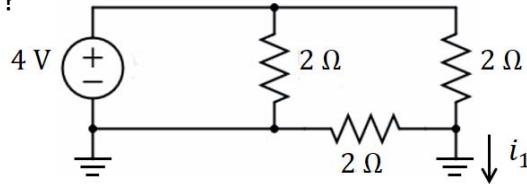

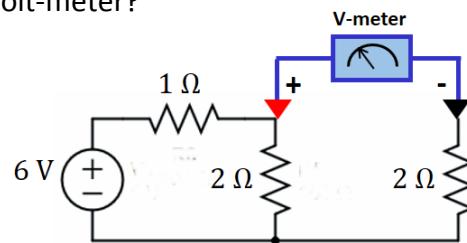
(b) What is the reading from the volt-meter?



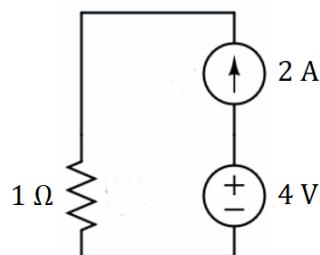
(c) What is the power supplied by the current source?




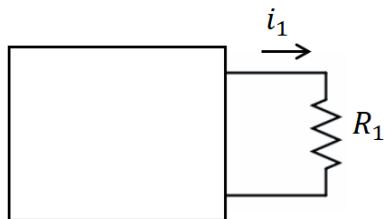
- (d) When  $R_1 = 1 \Omega$ , the current  $i_1 = 4 \text{ A}$ . When  $R_1 = 2 \Omega$ , the current  $i_1 = 3 \text{ A}$ .  
 When is the current  $i_1$  when  $R_1 = 3 \Omega$ ?



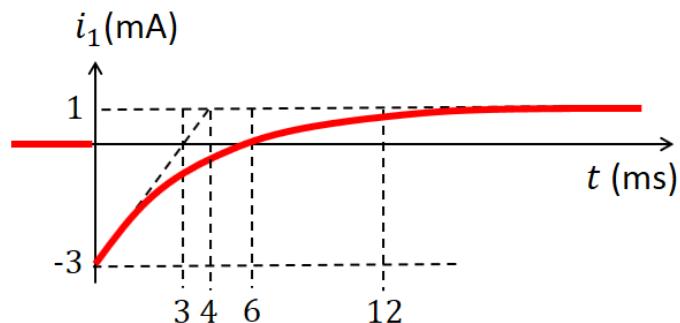
- (e) The graph below shows the current in a first order RL circuit. What is the equation of  $i_1(t)$  for  $t > 0$ ?



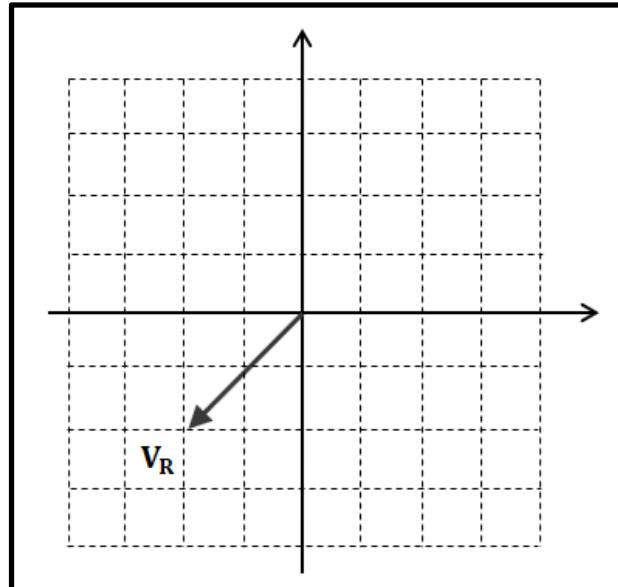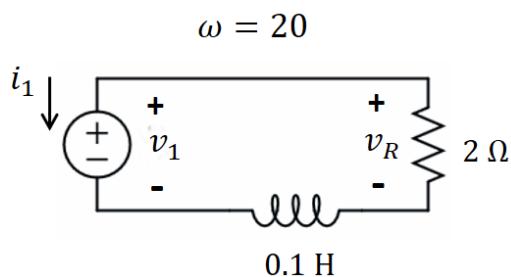- (f) With the phasor  $\mathbf{V}_R$  given on right, draw the phasors  $\mathbf{V}_1$  and  $\mathbf{I}_1$  in the same diagram. You can draw the same scale for A and V (i.e., a 1 A current phasor has the same length as a 1 V voltage phasor).




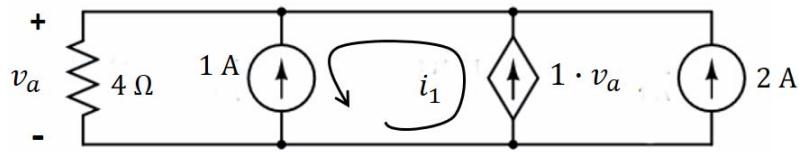(2) What is the value of mesh current  $i_1$ ?




(3) (a) For the circuit below, what is the value of  $i_x$ ?

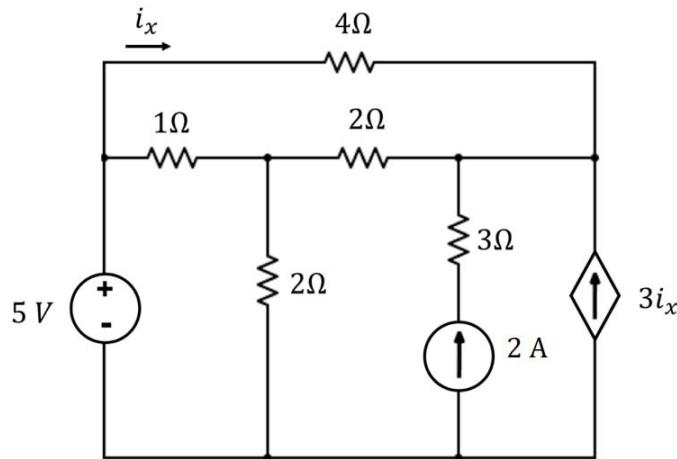(b) What is the power supplied by the dependent source?



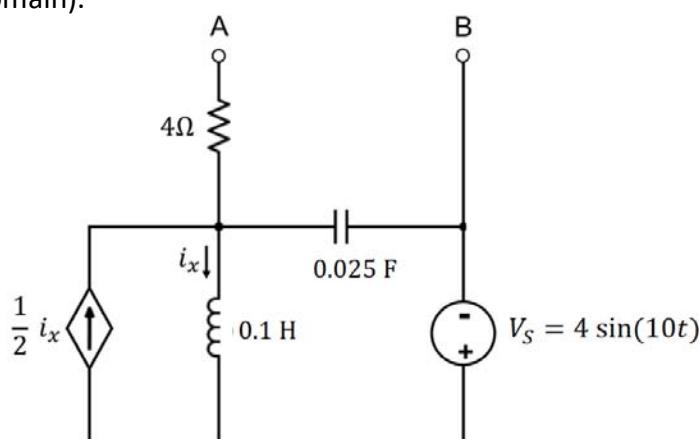(4) What is the Norton equivalent current source  $I_N$  (for the Norton equivalent model between A and B). Write your final answer in the time domain (don't leave it in the phasor domain).



- (5) Consider the circuit below. For  $t < 0$ , the switch is closed and the system has reached steady state. At  $t = 0$ , the switch opens and it remains open.

We measure that for  $t > 0$ ,  $v_C(t) = 2 + 8 e^{-\frac{t}{12}}$ .

(a) What was  $v_C$  at time  $t = 0^-$  (just before the switch was opened)?  $v_C(0^-)$


(b) Find  $V_S$ ,  $R$  and  $C$ .

$V_S$

$R$

$C$

$t = 0$

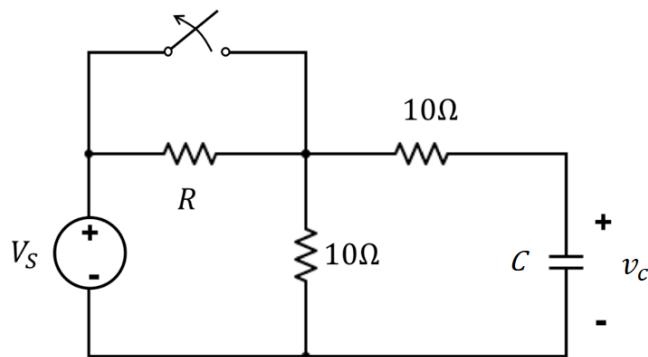

- (6) Consider the circuit below. At  $t < 0$ , the switch is open.

At  $t = 0$ , the switch closes and it remains closed.


We are given the capacitor voltage just before the switch closes:  $v_a(0^-) = V_1$  and  $v_b(0^-) = V_2$ .

$v_a$

(a) What are the capacitor voltages  $v_a$  and  $v_b$  at time  $t = \infty$ ?

$v_b$

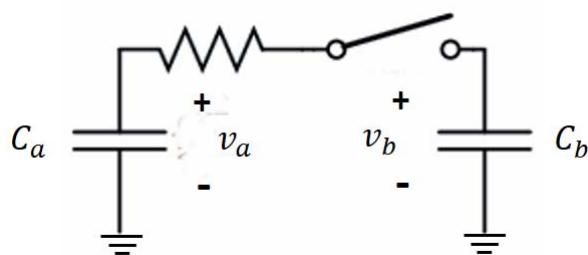(b) Find a concise expression of the total energy converted to heat during the transition.




(7) Consider the circuit below, where a load is connected to a power distribution network (consisting of a resistor, an inductor and an AC voltage source). The load itself consists of a resistor  $R_1$  in parallel with a mystery element  $Z_1$ , where  $Z_1$  is either a capacitor or an inductor. The goal is to maximize the average power received by the load.

(a) In the mystery element a capacitor or an inductor?

(b) What is the value of the resistor  $R_1$ ?

What is the value of the capacitor or inductor that makes up  $Z_1$ ?

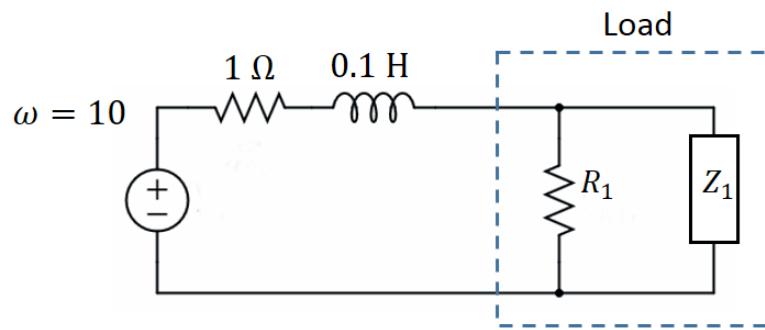(c) If  $Z_1$  is removed from the circuit and  $R_1$  is chosen to be  $1 \Omega$ . If the voltage source is  $v_S(t) = 2 \cos\left(10t + \frac{\pi}{2}\right)$ , what is the complex power of the inductor?



ECE 35, Fall 2017  
Final - Section B


Last name	
First + middle name(s)	
<b>PID</b>	

**Instructions:**


- Read each problem completely and thoroughly before beginning.
- All calculations should be done in your blue book. It should be clear what question they belong to. Answers without supporting calculations will receive zero credit.
- Write clearly and make sure your answer is structured properly. We will not hunt for your work or answers.
- Write your final answers in the answer boxes on these question pages. Make sure you list units!

(1) Answer the questions below.


(a) What is the current  $i_1$ ?

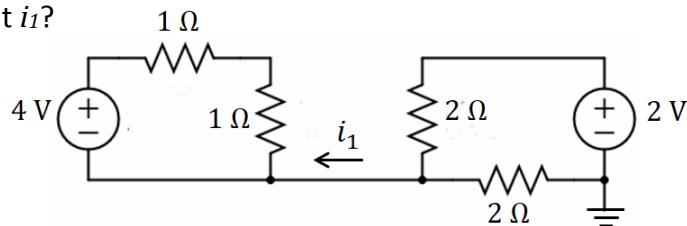





(b) What is the voltage  $v_1$ ?

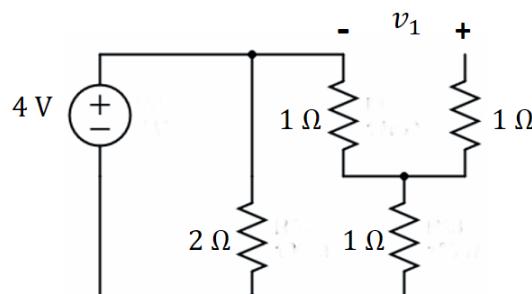

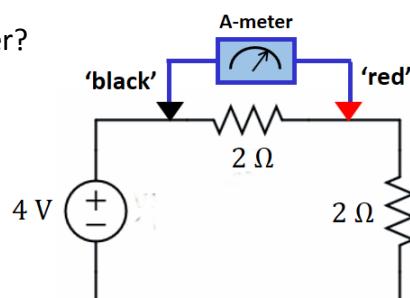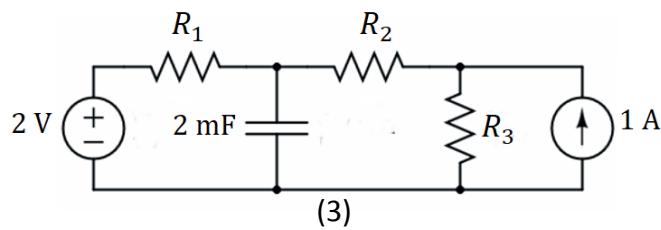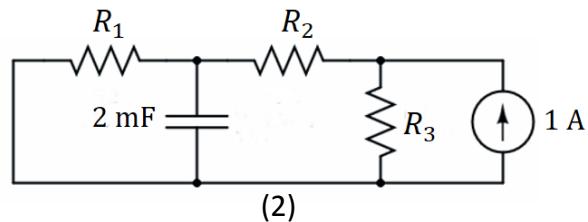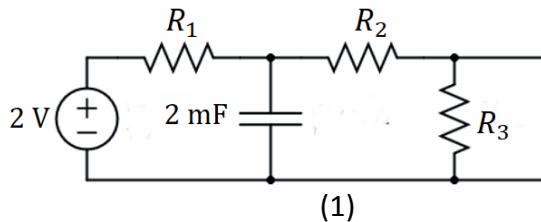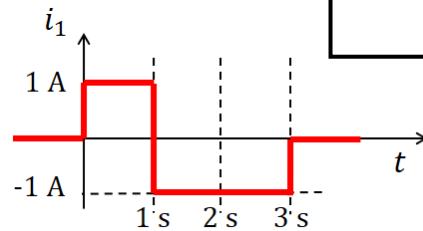
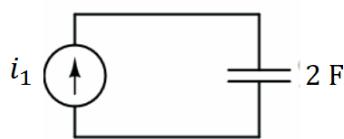

(c) What is the reading from the ammeter?




- (d) The energy stored in the capacitor in scenario (1) is 1 mJ and in scenario (2) it is 4 mJ. What is the energy stored in scenario (3)?



- (e) Assume the capacitor is discharged at time  $t = 0$ . During what time period(s) does the capacitor receive power? For example, write your answer as  $(t < 1 \text{ s})$  and  $(1 \text{ s} < t < 2 \text{ s})$ .




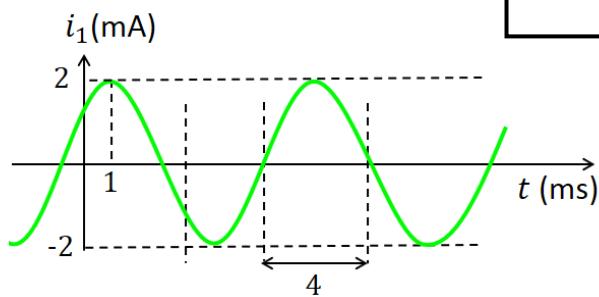- (f) What is the phasor  $\mathbf{I}_1$  of this current waveform? Write the phasor in polar coordinates.




(2) (a) For the circuit below, what is the value of  $i_x$ ?

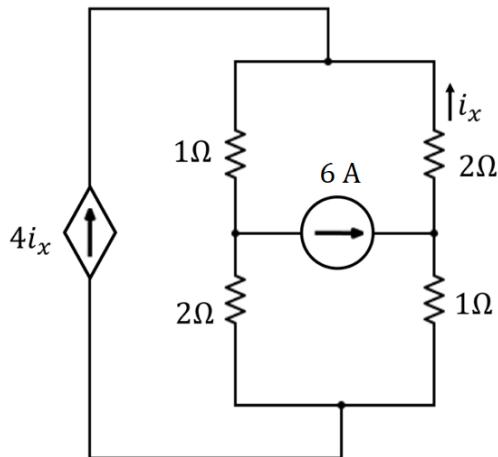(b) What is the power supplied by the dependent source?



(3) (a) For the circuit below, find the Thevenin equivalent model as seen between A and B, when  $V_1 = 4 \text{ V}$  and  $R_1 = 0 \Omega$ . Draw the model in the answer box with the appropriate values.

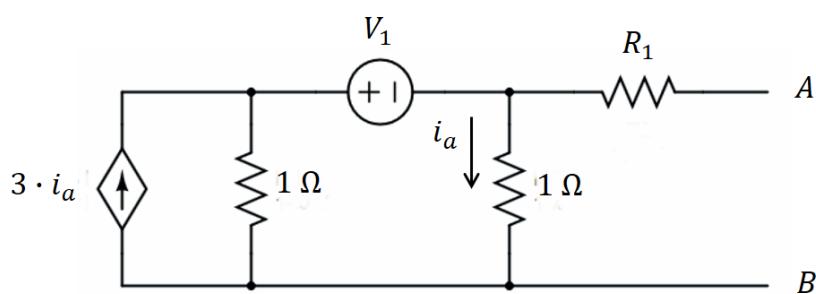(b) What is the Thevenin equivalent resistance when I make the following changes to circuit:  $V_1 = 8 \text{ V}$  and  $R_1 = 17 \Omega$ ?



- (4) Consider the circuit below. For  $t < 0$ , the switch is open and the system has reached steady state. At  $t = 0$ , the switch closes and it remains closed.

Find  $v_C(0^-)$  and  $v_C(0^+)$ .




Find  $i_C(0^-)$  and  $i_C(0^+)$ .




Find the expression for the current  $i_R(t)$  for  $t > 0$ .

$$i_R(t) =$$

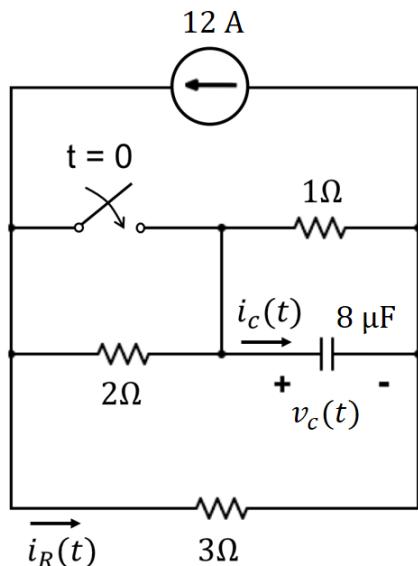

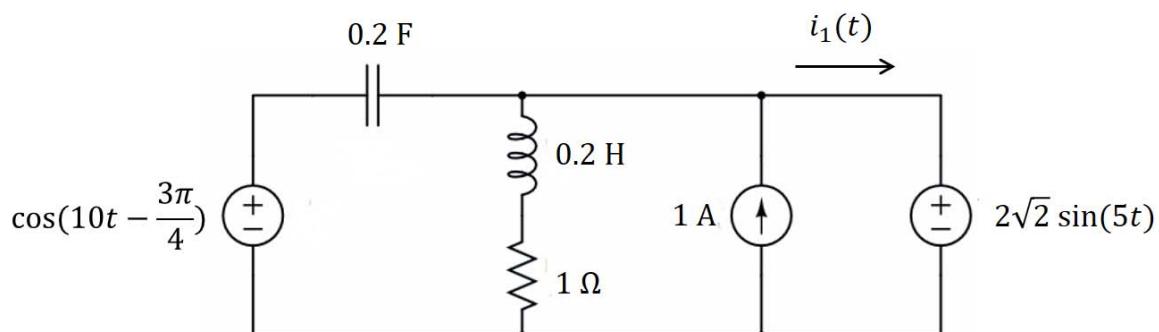- (5) For the circuit below, what is  $i_1(t)$ ? Express your answer in the time domain.



(6) (a) What is the average power received by the inductor?

(b) What is the complex power received by the combination of the resistor and the capacitor?


(c) Someone modified the values of the resistor, capacitor and inductor. With these new elements in the circuit (and with the same source), the total complex power received by all elements combined is  $S = 1 + j$

What element (resistor, capacitor or inductor) do you need to place in parallel with the source to achieve a total complex power of  $S = 1$ ?


Type of element:

What is the value of that element?

Value of the element:

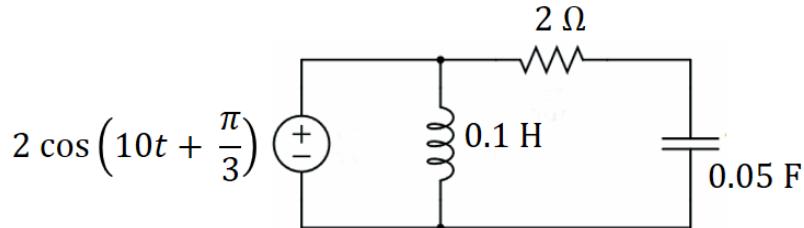

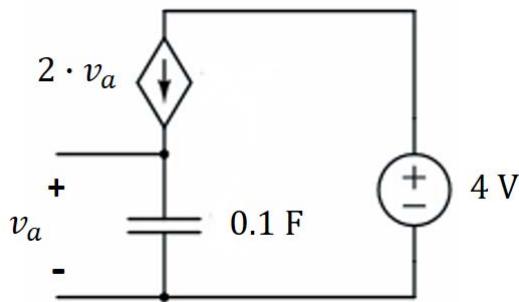(7) For the circuit below, what is the expression for  $v_a(t)$ , for  $t > 0$ ? At  $t = 0$ , the capacitor voltage is 1 V.



ECE 35, Fall 2018  
Final - Section B

Sequence  
number

Grade

/ 50

Last name

First + middle  
name(s)


PID

**Instructions:**

- Do not look at the questions or start writing until it is announced you can do so.
- Read each problem completely and thoroughly before beginning.
- All calculations must be done in your blue book. It should be clear which question they belong to. Answers without supporting calculations will receive zero credit. If you are using intuition, write a short explanation.
- Write clearly and make sure your answer is structured properly. We will not hunt for your work or answers.
- Write your final answers in the answer boxes on these question pages. Make sure you list units!
- You must follow the Final Exam Procedures that were posted on TritonEd. If you are unsure of anything, ask. As a reminder:
  - Your phone should be turned off and put inside your bag in the front of the room (or on the table in the front). If you are found to have a phone (or other communication device) on you during the exam, your exam will not be graded.
  - Calculators are not allowed.
  - This is a closed book exam.



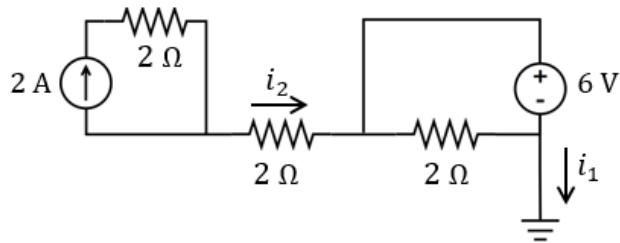
(1) (a) Find the currents  $i_1$  and  $i_2$ . (2 points)



$$i_1$$

$$i_2$$

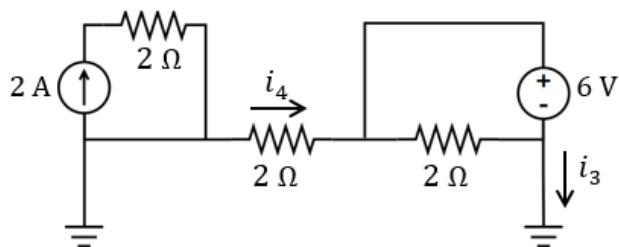
(b) Find the currents  $i_3$  and  $i_4$ . (2 points)



$$i_3$$


$$i_4$$

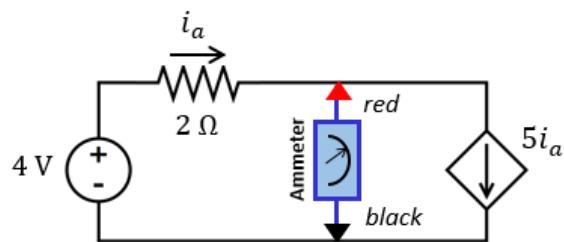(2) (a) What is the ammeter reading? (2 points)



$$i_a$$

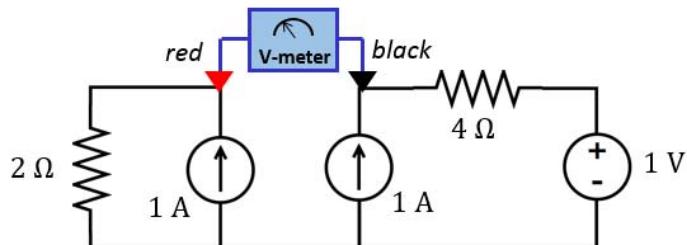(b) What is the volt-meter reading? (2 points)



$$V$$

(c) Find the Thevenin equivalent model between *a* and *b* for the circuit shown in Fig. A.

(3 points)

To help you find this model, someone did an experiment for you (shown in Fig. B): they attached a  $1\ \Omega$  resistor and measured a current of 1 A with the ammeter.


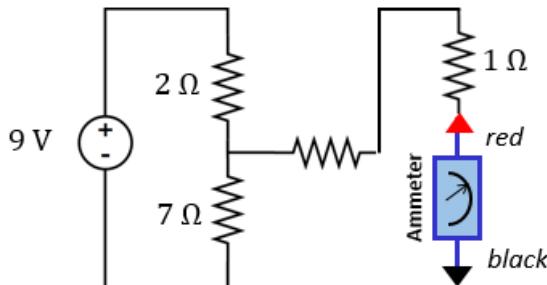




Fig. B

- (3) (a) The phasor diagram shows the currents  $\mathbf{I}_R$ ,  $\mathbf{I}_L$  and  $\mathbf{I}_C$ . Each phasor has a length of 4 A. Find  $i_R$  and  $i_C$  at time  $t = 2$  s. (3 points)

$$i_R(2)$$



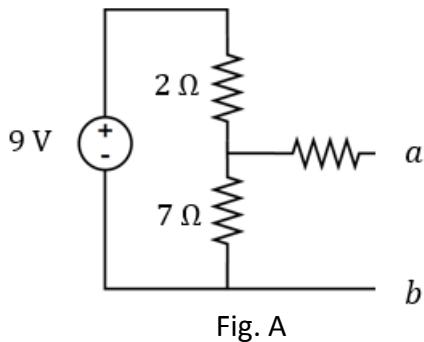


$$i_C(2)$$

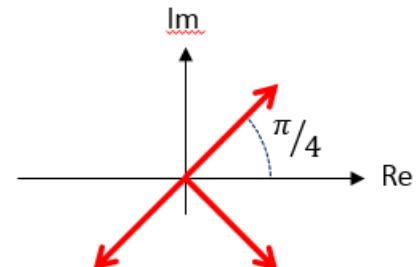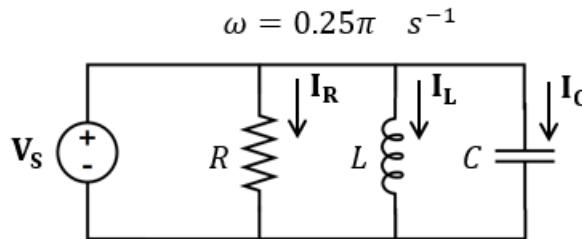


(b) Find  $I_{RMS}$  of  $i_1(t)$ . (2 points)

Find  $V_m$  (i.e., the magnitude of  $v_2$ ) such that the average power received by the  $2 \Omega$  resistor in Fig. B is the same as the average power received by the  $2 \Omega$  resistor in Fig. A. (2 points)

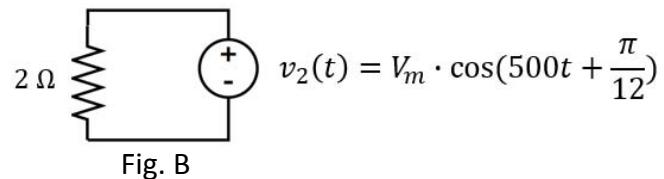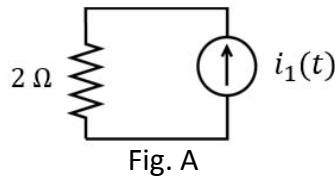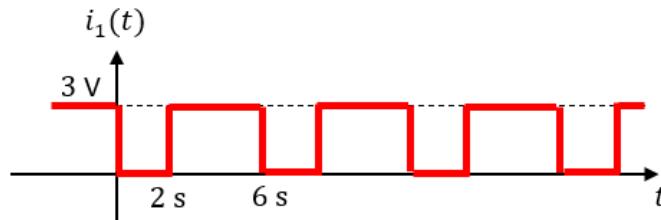(c) Find the equation of the time waveform  $v_1(t)$ . (3 points)


$v_1(t)$

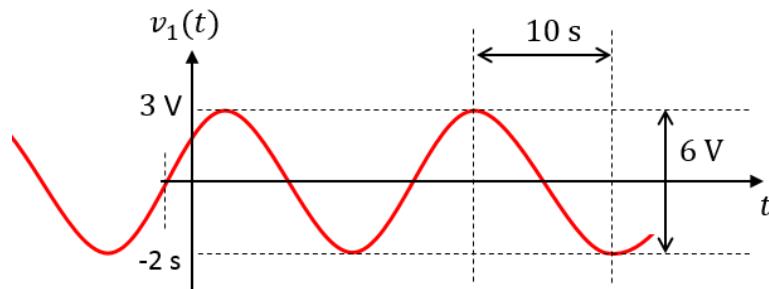

(4) (a) For the circuit below, find  $i_a$ . (3 points)

 $i_a$  

(b) What is the power  $P$  supplied by the dependent source? (3 points)

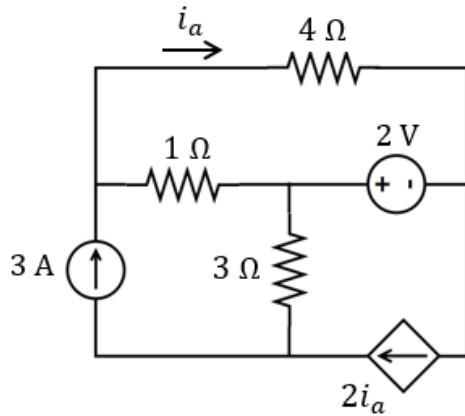 $P$  


(5) For  $t < 1$  s, the switch is closed and you may assume the system has reached steady state.


The switch opens at time  $t = 1$  s.

(a) Find  $i_1(1^-)$ . (1 point)

 $i_1(1^-)$  

(b) Find  $i_1(t)$  for  $t > 1$  s. (6 points)

$i_1(t)$

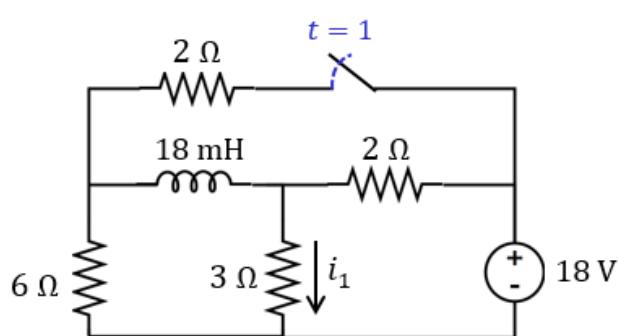


(6) (a) Find the complex power  $\mathbf{S}$  received by the inductor. (4 points)

- (b) What load impedance  $\mathbf{Z}_L$  should be attached between a and b to get maximum average power received by  $\mathbf{Z}_L$ ? You can choose to give your answer in cartesian or polar form.  
(4 points)

$\mathbf{S}$

$\mathbf{Z}_L$

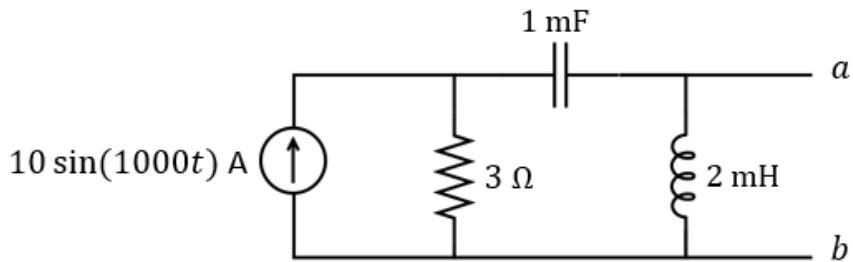

(7) For  $t < t_0$ , the switch is in position A and you may assume the system is in steady state.

The switch moves to position B at time  $t = t_0 = \frac{\pi}{3000}$ .

- (a) Find the capacitor current  $i_C$  at time  $t = t_0^-$  (i.e. with the switch in position A, just before it moves to position B).  
(1 points)


$i_C(t_0^-)$

- (b) Find the inductor current  $i_L$  at time  $t = t_0^+$  (i.e. immediately after the switch moves to position B).  
(3 points)

$i_L(t_0^+)$

- (c) Find the capacitor current  $i_C$  at time  $t = t_0^+$  (i.e. immediately after the switch moves to position B).  
(4 points)

$i_C(t_0^+)$

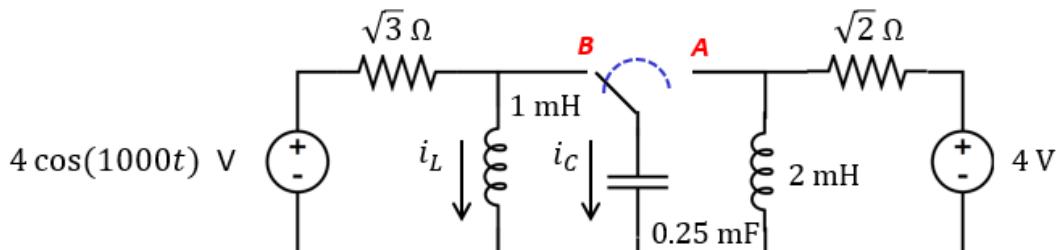

ECE 35, Fall 2019  
Final – Section A

Sequence  
number

Grade

/ 50

Last name

First + middle  
name(s)

PID

**Instructions:**

- Do not look at the questions or start writing until it is announced you can do so.
- Read each problem completely and thoroughly before beginning.
- All calculations must be done in your blue book. It should be clear which question they belong to. Answers without supporting calculations will receive zero credit. If you are using intuition, write a short explanation.
- Write clearly and make sure your answer is structured properly. We will not hunt for your work or answers.
- Write your final answers in the answer boxes on these question pages. Make sure you list units!
- You must follow the Final Exam Procedures that were posted on TritonEd. If you are unsure of anything, ask. As a reminder:
  - Your phone should be turned off and put inside your bag in the front of the room (or on the table in the front). If you are found to have a phone (or other communication device) on you during the exam, your exam will not be graded.
  - Calculators are not allowed.
  - This is a closed book exam.




(1) Consider the circuit below.

- (a) Find the Thevenin equivalent model between A and B. (8 points)

- (b) If we were to place a  $2/3 \Omega$  resistor between A and B in the circuit below, what is the current  $i_R$  through that resistor (measured from A to B)? (1 point)

$i_R$

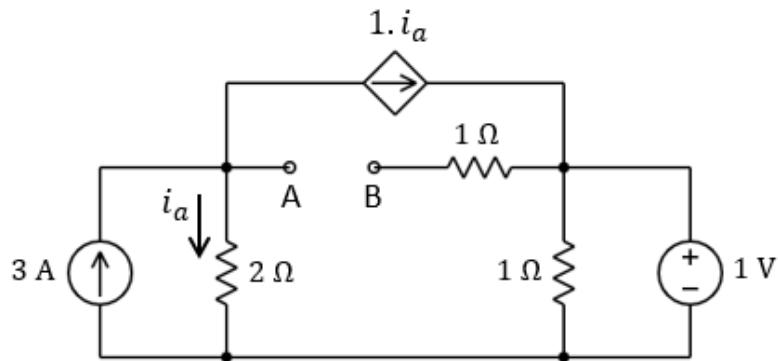

(2) Consider the circuit below. For  $t < 0$  s, you may assume the system has reached steady state.


(a) Find  $v_a(t)$  for  $t > 0$  s.

(8 points)

$v_a(t)$


(b) Sketch the waveform  $v_a(t)$  for  $t > 0$  s. Include where you can observe the time constant.

(2 points)

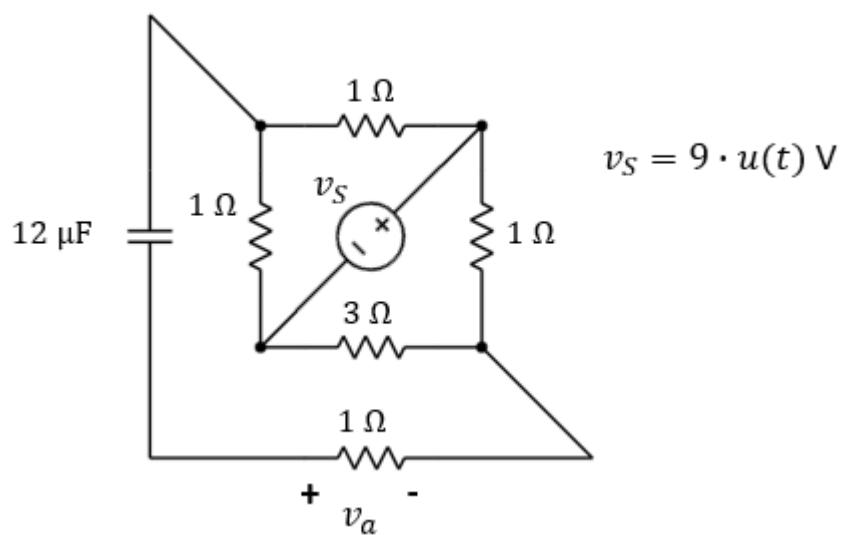

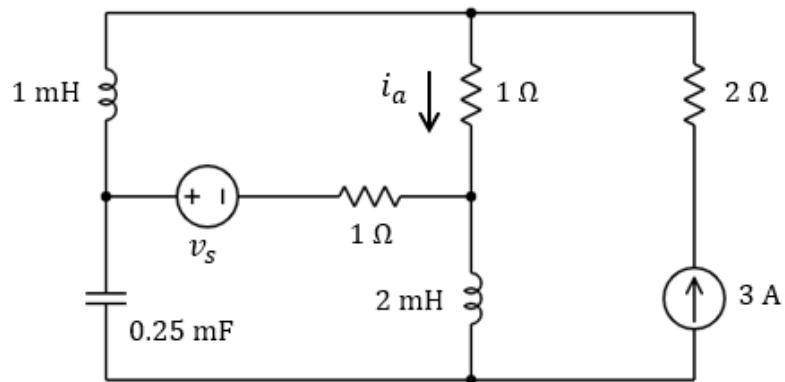(3) Consider the circuit below. The system is in steady state. Find  $i_a(t)$ . (9 points)

$$v_s = 18 \cos\left(1000t - \frac{\pi}{2}\right) \text{ V}$$



(4) Consider the circuit below. The system is in steady state and represented in phasor form.

(a) Find the mesh currents  $\mathbf{I}_1$ ,  $\mathbf{I}_2$  and  $\mathbf{I}_3$  (expressed in polar form). (8 points)


$$\mathbf{I}_1 \quad \boxed{\quad}$$

$$\mathbf{I}_2 \quad \boxed{\quad}$$

$$\mathbf{I}_3 \quad \boxed{\quad}$$

(b) Find the complex power supplied by  $\mathbf{V}_S$ . (2 points)

$$\mathbf{S} \quad \boxed{\quad}$$

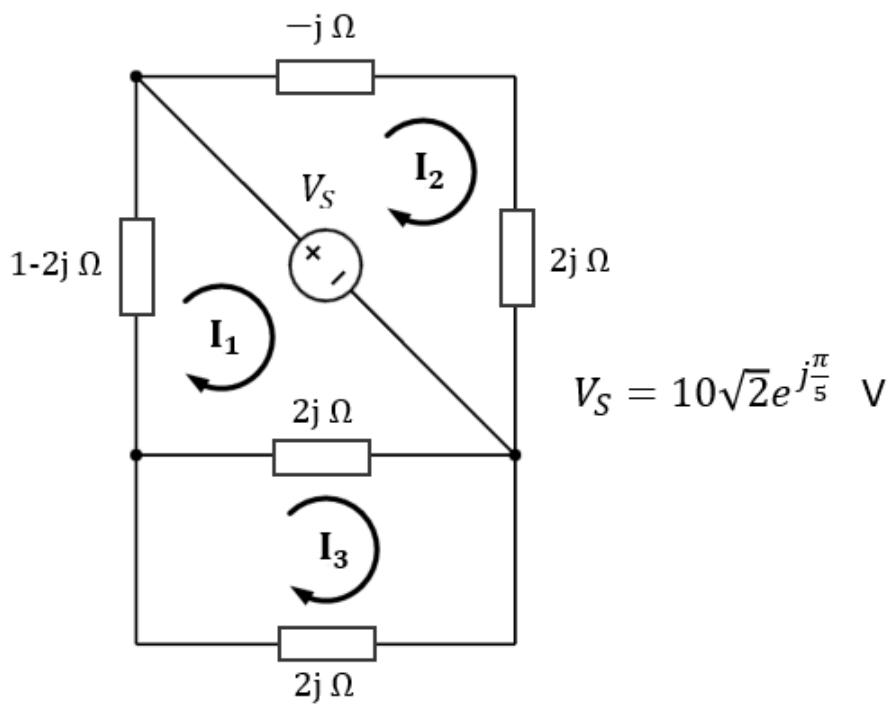

(5) Consider the circuit below. The system is in steady state and represented in phasor form. The ammeter and volt-meter are both ideal.

- (a) Assume the load  $Z_L = 2j \Omega$ . What is the reading X of the ammeter and the reading Y of the volt-meter? (8 points)

X   
(ammeter reading)


Y   
(voltmeter reading)

- (b) We now replace the load  $Z_L$  with a new value such that the average power received by this load is maximized. What is this new value of  $Z_L$ ? (2 points)

$Z_L$

- (c) Find the average power received by the load calculated in part (b). (2 points)

P

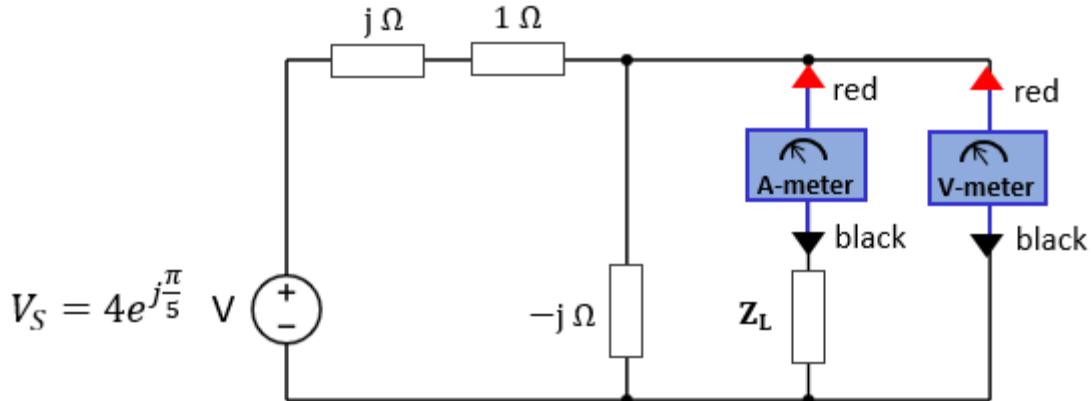

## ECE35 Equation Sheet

**Basics:**  $i \triangleq \frac{dq}{dt}$        $v_{ab} \triangleq \frac{dw}{dq}$        $R = \rho \frac{l}{A}$

**Capacitors:**  $C = \epsilon \cdot \frac{A}{d}$        $Q = C \cdot v$        $w_C = \frac{1}{2} C v^2$

**Inductors:**  $L = \mu \cdot \frac{N^2 A}{l}$        $B \sim i$        $w_L = \frac{1}{2} L i^2$

**AC power:**  $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \quad X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$

<b>Trigonometry:</b>	$\sin(-\alpha) = -\sin(\alpha)$	$\cos(-\alpha) = \cos(\alpha)$
	$\sin(\pi - \alpha) = \sin(\alpha)$	$\cos(\pi - \alpha) = -\cos(\alpha)$
	$\sin\left(\frac{\pi}{2} - \alpha\right) = \cos(\alpha)$	$\cos\left(\frac{\pi}{2} - \alpha\right) = \sin(\alpha)$
	$\sin\left(\alpha - \frac{\pi}{2}\right) = -\cos(\alpha)$	$\cos\left(\alpha - \frac{\pi}{2}\right) = \sin(\alpha)$
	$\sin(2\alpha) = 2 \sin(\alpha) \cos(\alpha)$	$\cos(2\alpha) = \cos^2(\alpha) - \sin^2(\alpha)$

$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$
$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$
$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$
$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$
$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$

$\alpha:$	0	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$
$\sin(\alpha):$	0	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	1
$\tan(\alpha):$	0	$\frac{\sqrt{3}}{3}$	1	$\sqrt{3}$	$\infty$

ECE 35, Fall 2019  
Final – Section B

Sequence  
number

Grade

/ 50

Last name

First + middle  
name(s)

PID

**Instructions:**

- Do not look at the questions or start writing until it is announced you can do so.
- Read each problem completely and thoroughly before beginning.
- All calculations must be done in your blue book. It should be clear which question they belong to. Answers without supporting calculations will receive zero credit. If you are using intuition, write a short explanation.
- Write clearly and make sure your answer is structured properly. We will not hunt for your work or answers.
- Write your final answers in the answer boxes on these question pages. Make sure you list units!
- You must follow the Final Exam Procedures that were posted on TritonEd. If you are unsure of anything, ask. As a reminder:
  - Your phone should be turned off and put inside your bag in the front of the room (or on the table in the front). If you are found to have a phone (or other communication device) on you during the exam, your exam will not be graded.
  - Calculators are not allowed.
  - This is a closed book exam.




(1) Consider the circuit below.

- (a) Find the Thevenin equivalent model between A and B. (8 points)

- (b) If we were to place a  $2/3 \Omega$  resistor between A and B in the circuit below, what is the current  $i_R$  through that resistor (measured from A to B)? (1 point)

$$i_R \quad \boxed{\hspace{2cm}}$$

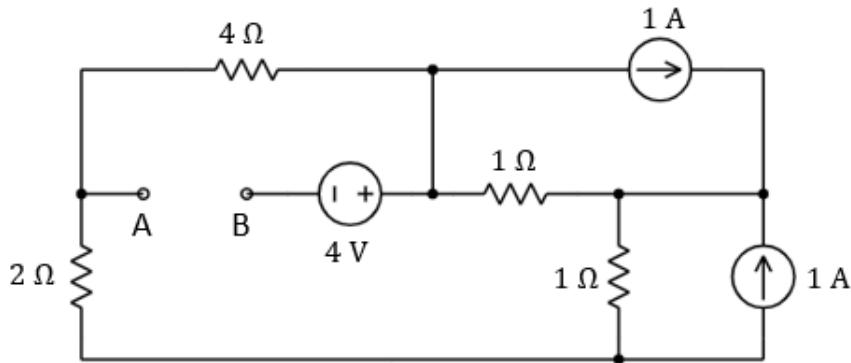

(2) Consider the circuit below. For  $t < 0$  s, you may assume the system has reached steady state.


(a) Find  $v_a(t)$  for  $t > 0$  s.

(8 points)


$$v_a(t)$$

(b) Sketch the waveform  $v_a(t)$  for  $t > 0$  s. Include where you can observe the time constant.

(2 points)

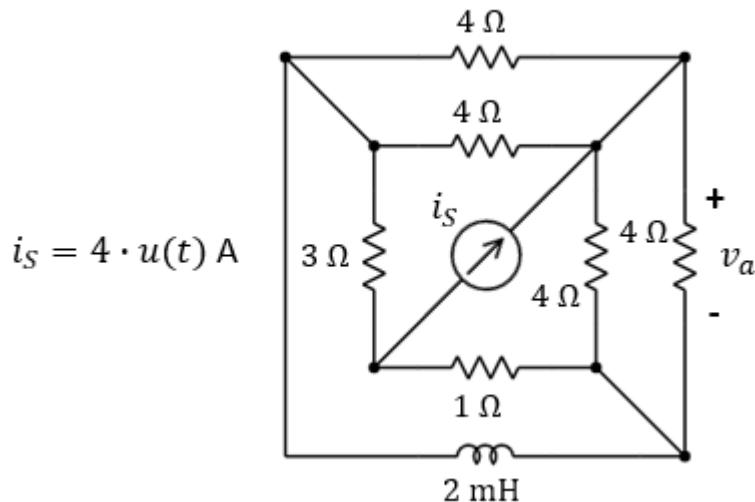

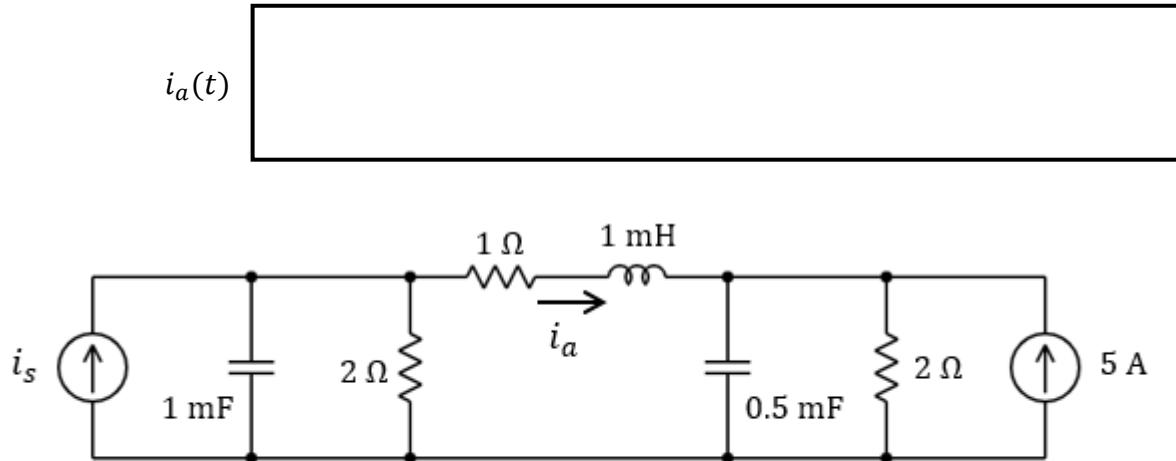(3) Consider the circuit below. The system is in steady state. Find  $i_a(t)$ . (9 points)



$$i_s = 20 \cos\left(1000t - \frac{\pi}{2}\right) \text{ A}$$

(4) Consider the circuit below. The system is in steady state and represented in phasor form.

(a) Find the mesh currents  $\mathbf{I}_1$ ,  $\mathbf{I}_2$  and  $\mathbf{I}_3$  (expressed in polar form). (8 points)


$\mathbf{I}_1$

$\mathbf{I}_2$

$\mathbf{I}_3$

(b) Find the complex power supplied by  $\mathbf{V}_S$ . (2 points)

$\mathbf{S}$

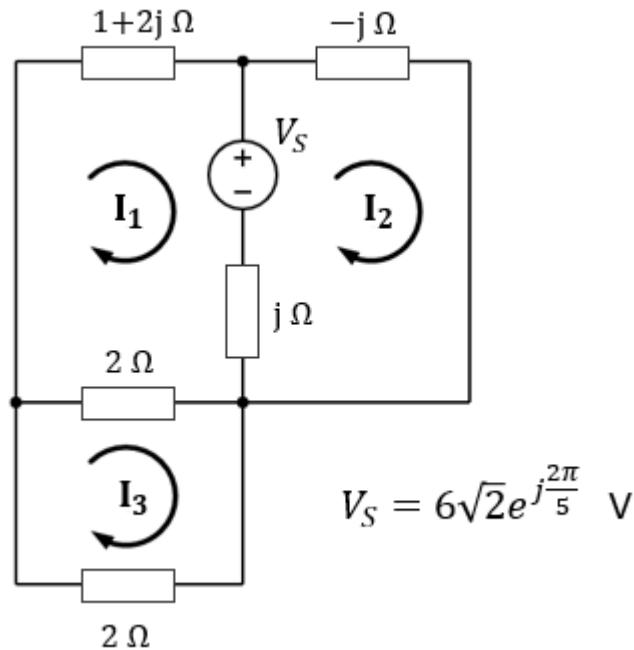

(5) Consider the circuit below. The system is in steady state and represented in phasor form. The ammeter and volt-meter are both ideal.

- (a) Assume the load  $Z_L = -j \Omega$ . What is the reading X of the ammeter and the reading Y of the volt-meter? (8 points)

X   
(ammeter reading)


Y   
(voltmeter reading)

- (b) We now replace the load  $Z_L$  with a new value such that the average power received by this load is maximized. What is this new value of  $Z_L$ ? (2 points)

$Z_L$

- (c) Find the average power received by the load calculated in part (b). (2 points)

P

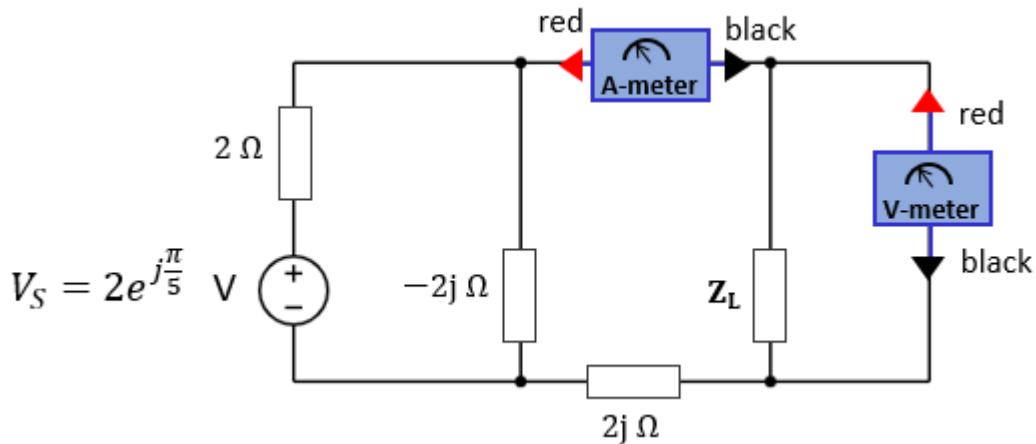

## ECE35 Equation Sheet

**Basics:**  $i \triangleq \frac{dq}{dt}$        $v_{ab} \triangleq \frac{dw}{dq}$        $R = \rho \frac{l}{A}$

**Capacitors:**  $C = \epsilon \cdot \frac{A}{d}$        $Q = C \cdot v$        $w_C = \frac{1}{2} C v^2$

**Inductors:**  $L = \mu \cdot \frac{N^2 A}{l}$        $B \sim i$        $w_L = \frac{1}{2} L i^2$

**AC power:**  $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \quad X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$


<b>Trigonometry:</b>	$\sin(-\alpha) = -\sin(\alpha)$	$\cos(-\alpha) = \cos(\alpha)$
	$\sin(\pi - \alpha) = \sin(\alpha)$	$\cos(\pi - \alpha) = -\cos(\alpha)$
	$\sin\left(\frac{\pi}{2} - \alpha\right) = \cos(\alpha)$	$\cos\left(\frac{\pi}{2} - \alpha\right) = \sin(\alpha)$
	$\sin\left(\alpha - \frac{\pi}{2}\right) = -\cos(\alpha)$	$\cos\left(\alpha - \frac{\pi}{2}\right) = \sin(\alpha)$
	$\sin(2\alpha) = 2 \sin(\alpha) \cos(\alpha)$	$\cos(2\alpha) = \cos^2(\alpha) - \sin^2(\alpha)$

$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$
$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$
$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$
$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$
$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$

$\alpha:$	0	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$
$\sin(\alpha):$	0	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	1
$\tan(\alpha):$	0	$\frac{\sqrt{3}}{3}$	1	$\sqrt{3}$	$\infty$


## Practice Final

### Problem 1

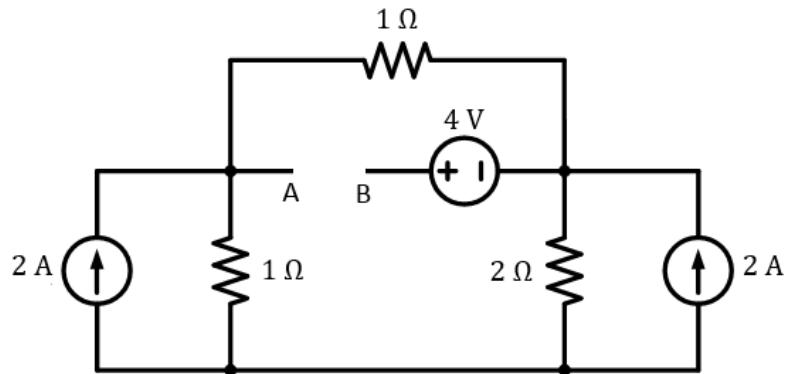


- Find the Thevenin equivalent model between A and B.
- If we were to place a  $1.5 \Omega$  resistor between A and B in the circuit above, what is the current through that resistor (measured from A to B)?

### Problem 2

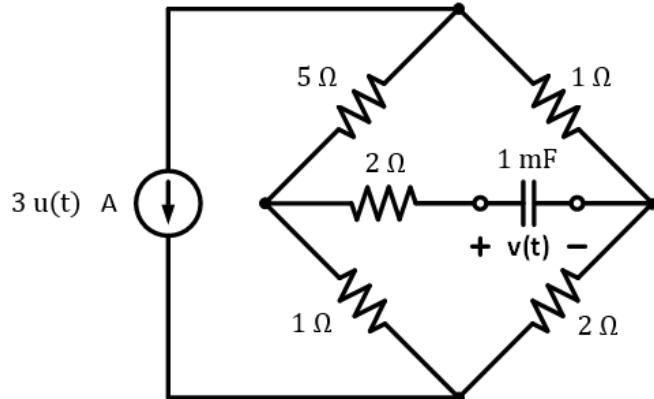


- Find  $v(t)$  for  $t \geq 0$ .
- Sketch the waveform of  $v(t)$  for  $t \geq 0$ .

**Problem 3**

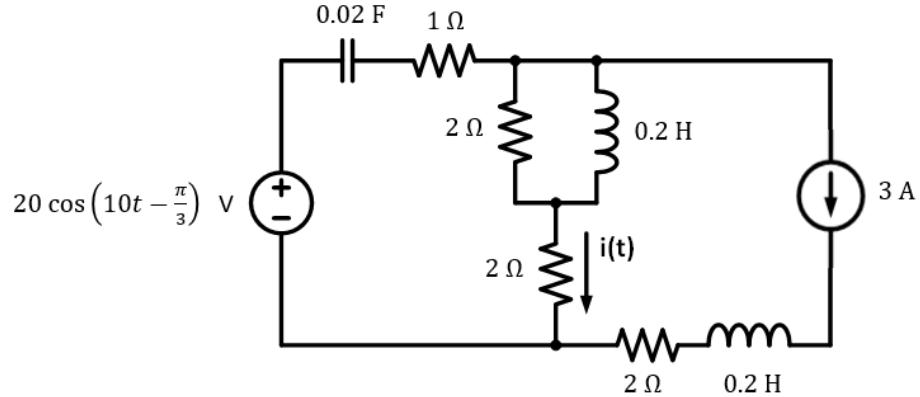


Find the steady-state response of  $i(t)$ .

**Problem 4**

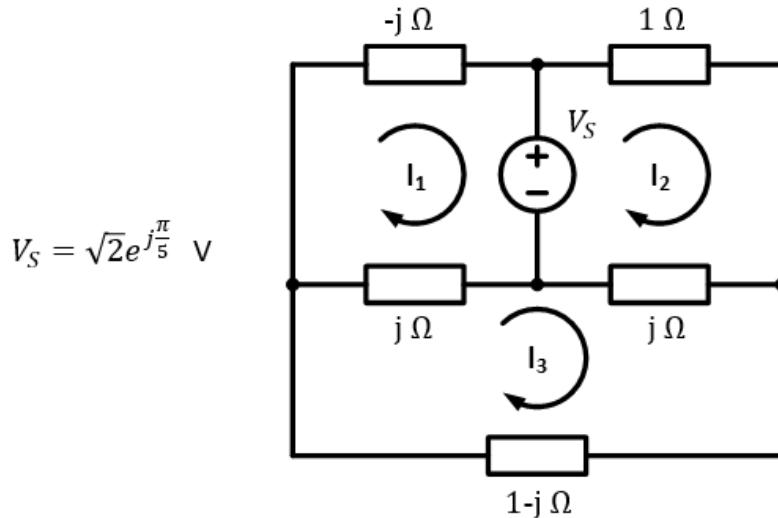

- Find the values of the mesh current phasors,  $I_1$ ,  $I_2$ , and  $I_3$  (in polar form).
- Find the complex power supplied by  $V_S$ .

**Problem 5**

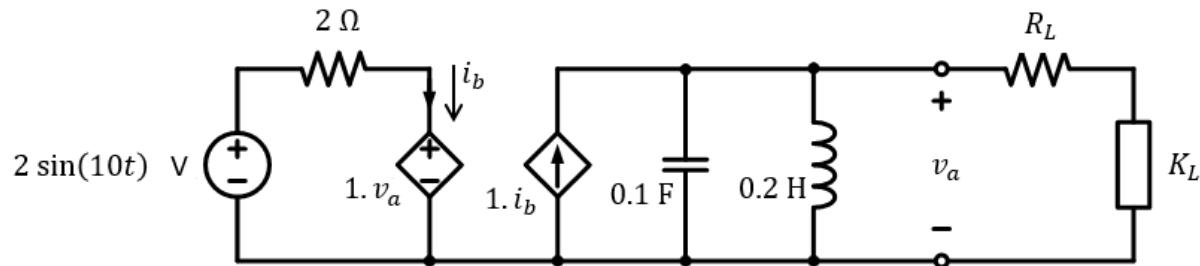


A load ( $R_L + K_L$ ) is connected to a power distribution network consisting of a resistor, inductor, capacitor and AC voltage source. The load itself includes a resistor  $R_L$  in series with a mystery element  $K_L$ , where  $K_L$  is either a capacitor or an inductor. The goal is to maximize the average power delivered to the load.


- Determine the values of  $R_L$  and  $K_L$  for the circuit that cause maximum power transfer to the load.
- Determine the mystery element (a capacitor or an inductor; and its value).
- Calculate the maximum power transferred to the load.

**Q1**

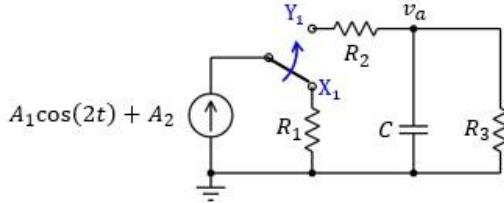
- (a) For  $t < \frac{\pi}{6}$  s, the switch is in position  $X_1$ , and at time  $t = 0$  s the capacitor is fully discharged. At time  $t = \frac{\pi}{6}$  s, the switch moves from position  $X_1$  to position  $Y_1$ . Find the steady state node voltage waveform  $v_a(t)$ .



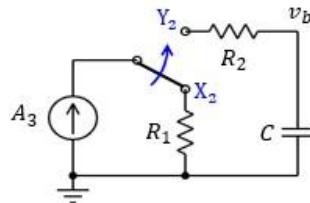
- (b) For  $t < \frac{\pi}{6}$  s, the switch is in position  $X_2$ , and at time  $t = 0$  s the capacitor is fully discharged. At time  $t = \frac{\pi}{6}$  s, the switch moves from position  $X_2$  to position  $Y_2$ . Find the node voltage  $v_b(\pi)$ , i.e., at time  $t = \pi$  s.



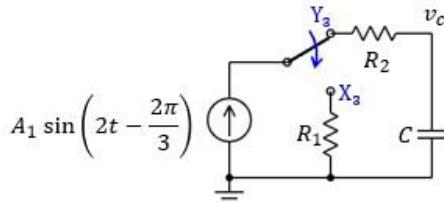- (c) For  $t < \frac{\pi}{6}$  s, the switch is in position  $Y_3$ , and you may assume the system has reached steady state. At time  $t = \frac{\pi}{6}$  s, the switch moves from position  $Y_3$  to position  $X_3$ . Find the node voltage  $v_c(\pi)$ .



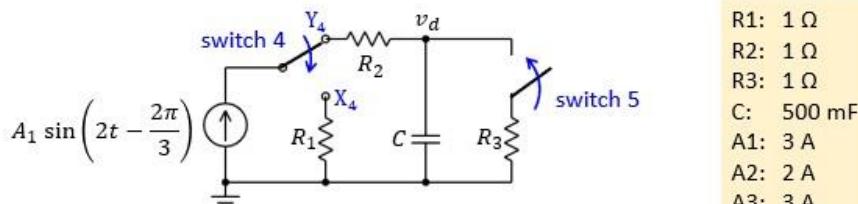- (d) For  $t < \frac{\pi}{6}$  s, switch 4 is in position  $Y_4$  and switch 5 is open, and you may assume the system has reached steady state. At time  $t = \frac{\pi}{6}$  s, switch 4 moves from position  $Y_4$  to position  $X_4$  and switch 5 closes. Find the node voltage  $v_d(\pi)$ .





## Q2

The AC circuit below has  $\omega = 10 \text{ rad/s}$  and is in steady state. The phasor diagram shows the phasors of  $i_S$  and  $v_L$ . You are given the angles  $\alpha$  (between  $I_S$  and the x-axis),  $\beta$  (between  $V_L$  and the x-axis),  $|I_S|$  and  $|V_L|$ . The diagram is not necessarily drawn to scale.

The element represented by the rectangular box is either an inductor or a capacitor but you are not told which.

- Find the complex power  $S_L$  received by the inductor.
- Find the complex power  $S_S$  supplied by the current source.
- Find the complex power  $S_M$  received by the mystery element.
- What is the mystery element (capacitor or inductor)?  
(You do not need to find its value, but your answer needs to be motivated)


$ I_S :$	3 A
alpha:	20 degrees
$ V_L :$	4 V
Beta:	80 degrees
R1:	2 $\Omega$
L:	200 mH

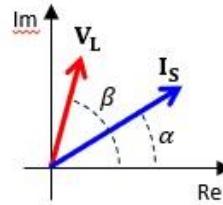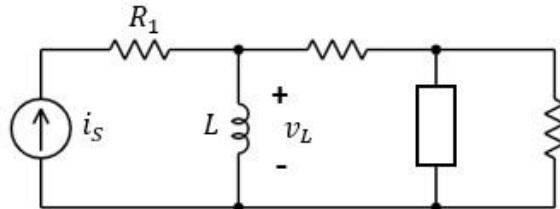
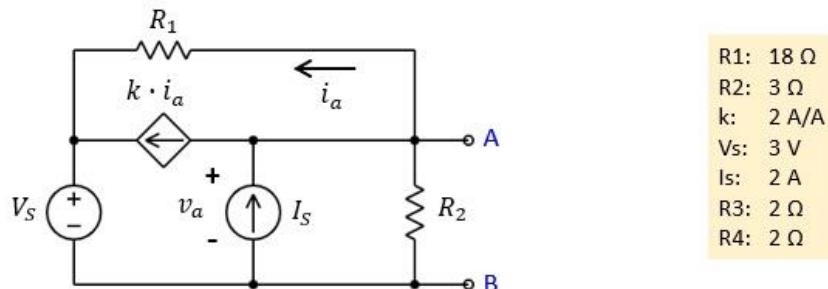
## Q3


Consider the circuit below.

- Find the voltage  $v_a$ .
- Draw the Thevenin model for the circuit between A and B  
(make sure you label A and B in your drawing).



R1:	18 $\Omega$
R2:	3 $\Omega$
k:	2 A/A
V_s:	3 V
I_s:	2 A
R3:	2 $\Omega$
R4:	2 $\Omega$

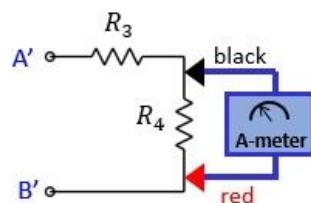
- Connect the circuit on the right to the one on top (A' connected to A and B' connected to B). What is the reading X of the ideal ammeter?



#### Q4

For  $t < 2$  s, the switch is closed, and you may assume the system has reached steady state. The switch opens at time  $t = 2$  s.

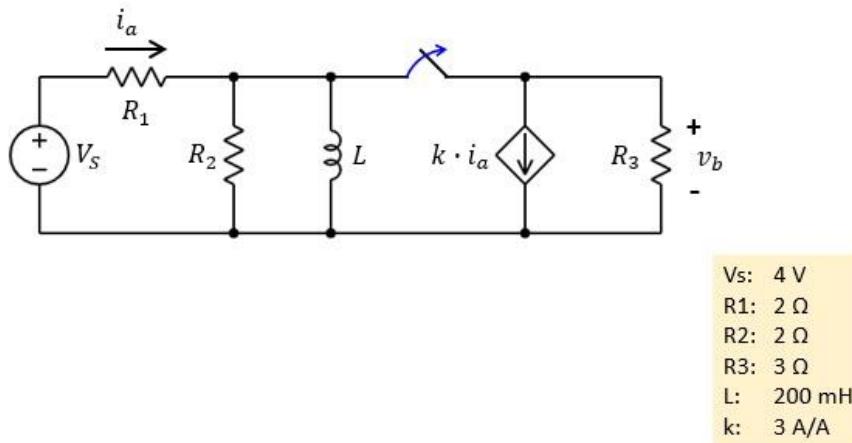- (a) Find  $v_b(t)$  for  $t > 2$  s.
- (b) What is the instantaneous power received by the inductor at time  $t = 2^+$  s.




#### Q5

The circuit below is an AC circuit and is in steady state. The three independent sources all have  $\omega = 10$  rad/s.

You measure the waveform  $i_a(t) = A_1 \cos(10t + B_1)$ .

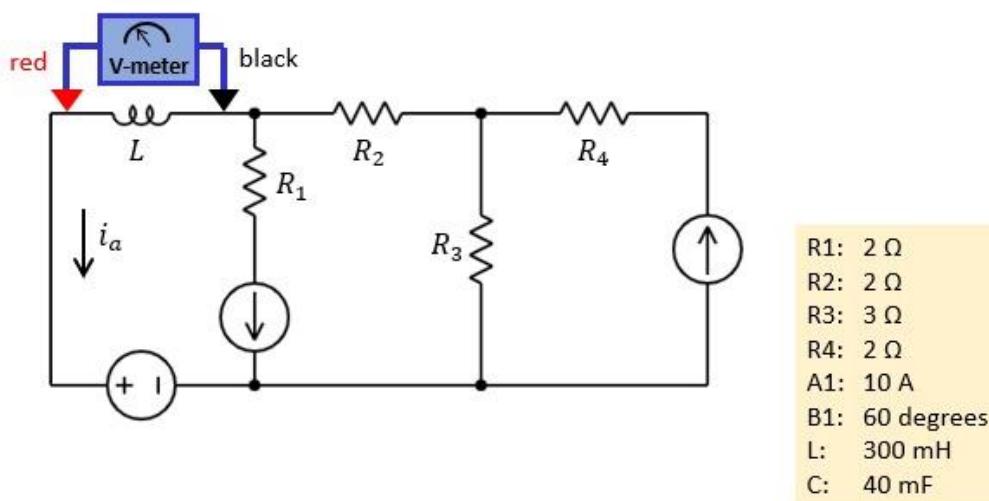Now the circuit is changed: the inductor **L** is replaced by capacitor **C**. In this changed circuit, what will be the reading of the ideal voltmeter?



ECE 35, Fall 2021  
Final – Section A

Your sequence number 

Grade   
  
 / 45

Last name	<input type="text"/>
First + middle name(s)	<input type="text"/>
PID	<input type="text"/>


**Instructions:**

- Do not look at the questions or start writing until it is announced you can do so.
- Make sure you write your PID on EACH page.
- Read each problem completely and thoroughly before beginning.
- Answers without supporting calculations will receive zero credit. If you are using intuition, write a short explanation.
- All calculations must be done on these pages. It should be clear which question they belong to. Use the front for your actual work and the back as scratch paper.
- Write clearly and make sure your answer is structured properly. We will not hunt for your work or answers.
- Write your final answers in the answer boxes. Make sure you list units.
- You must follow the Final Exam Procedures that were posted on Canvas. If you are unsure of anything, ask. As a reminder:
  - Your phone should be turned off and put inside your bag
  - Calculators are not allowed.
  - This is a closed book exam.
  - Follow the Academic Integrity standards.



- (1) (4 points) Consider the circuit below.  
What is the reading  $X$  of the voltmeter?

$X$

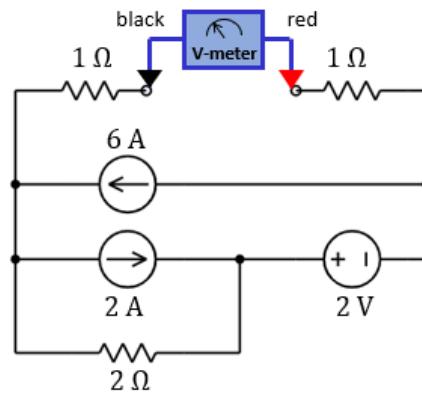

(2) (7 points) Consider the circuit below.

(a) Find the current  $i_b$ .


$i_b$

(b) Find the power  $P_1$  received by the independent source.

$P_1$

(c) Find the power  $P_2$  supplied by the dependent source.


$P_2$

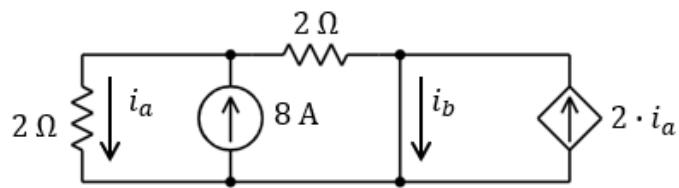


(3) (7 points)

- (a) Consider the circuit below. What is the Thevenin equivalent resistance between A and B?

$$R_{TH}$$

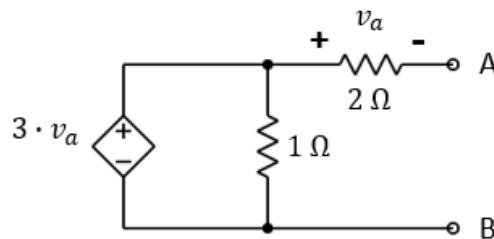

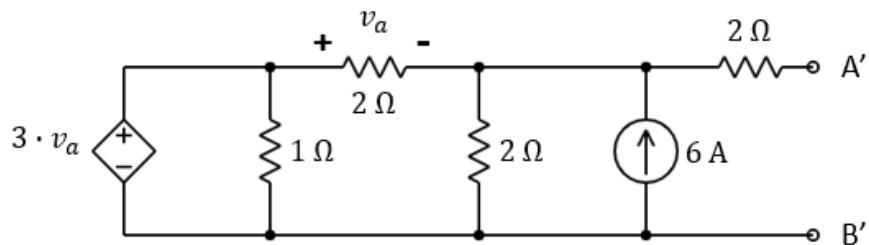- (b) Consider the circuit below (which contains the circuit above). Draw the Norton equivalent model between A' and B' (make sure you label A' and B').



(4) (10 points) Consider the circuit below. For  $t < 2$  s, the switch is in position 1 and you may assume the system has reached steady state. The switch moves from position 1 to position 2 at  $t = 2$  s and remains in position 2.


Note: make sure you don't mix up  $i_a$  and  $i_b$  in the questions below.


(a) Find the current  $i_a(2^- \text{ s})$ . (i.e., just before the switch moves).  $i_a(2^- \text{ s})$


(b) Find the current  $i_b(2^+ \text{ s})$ . (i.e., just after the switch moves).  $i_b(2^+ \text{ s})$

(c) Find the current  $i_a(7 \text{ s})$ .  $i_a(7 \text{ s})$

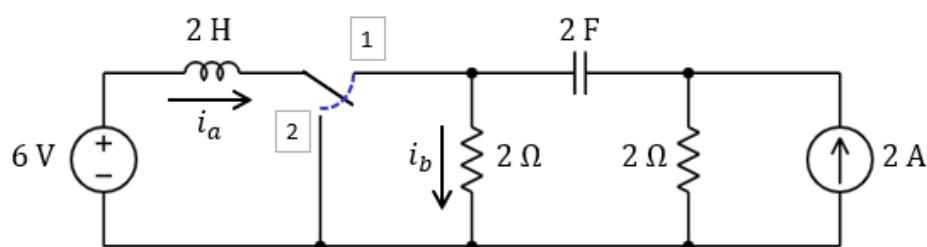(d) Find the current  $i_b(\infty)$ .  $i_b(\infty)$



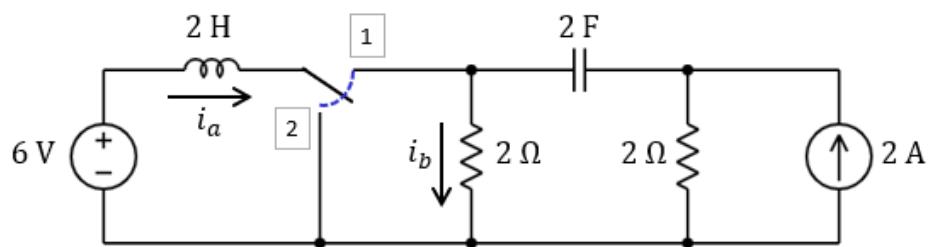

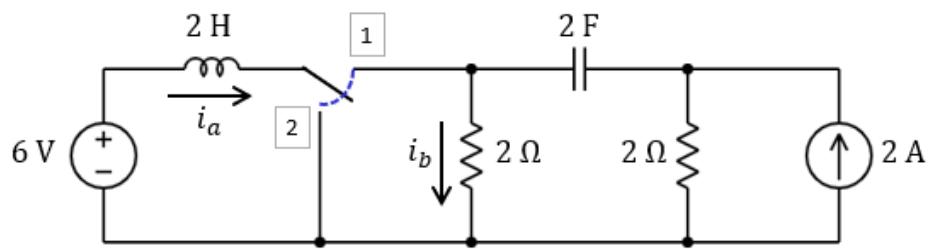



(5) (9 points) Consider the circuit below. For  $t < \frac{\pi}{4}$  ms, the switch is closed and you may assume the system has reached steady state. The source  $i_S$  is an AC source with  $\omega = 4000$  rad/s. Its phasor diagram is shown on the left. The switch opens at  $t = \frac{\pi}{4}$  ms and remains open.


- (a) Find the node voltage  $v_a\left(\frac{\pi^-}{4} \text{ ms}\right)$ . (i.e., just before the switch opens).

$$v_a\left(\frac{\pi^-}{4} \text{ ms}\right)$$

- (b) Find the node voltage  $v_a(\pi \text{ ms})$ .

$$v_a(\pi \text{ ms})$$

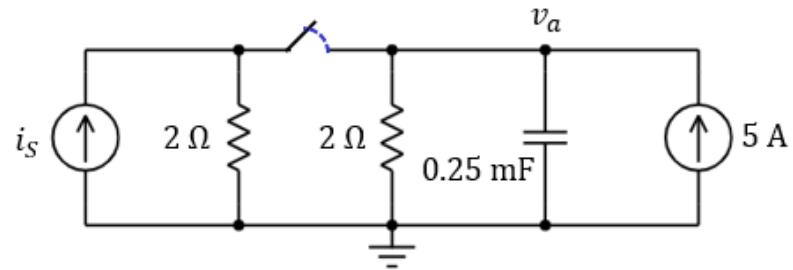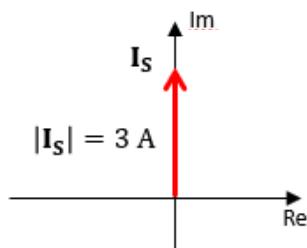

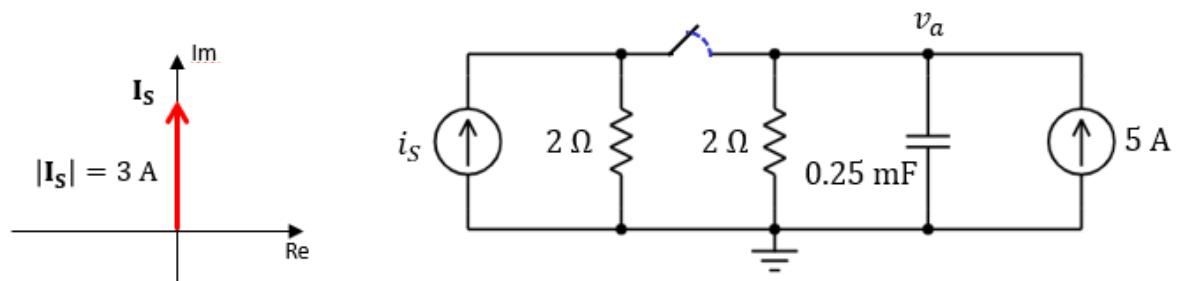

(6) (8 points) The circuit below is in steady state.


- (a) Sketch the phasor of  $v_a$  (make sure the magnitude and phase are labeled).


- (b) Find average power  $P_R$  received by the resistor.

$P_R$

- (c) If the reactive power received by all capacitors and inductors combined is **21.6 VAR**, what is the complex power  $S$  supplied by the independent source?

$S$

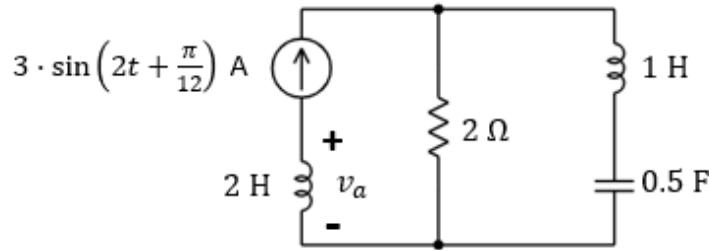

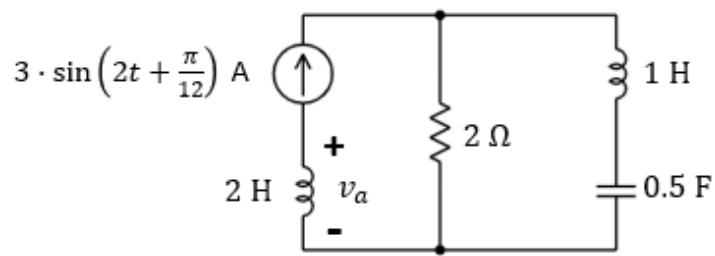

**ECE35 Equation Sheet**

**Basics:**  $i \triangleq \frac{dq}{dt}$        $v_{ab} \triangleq \frac{dw}{dq}$        $R = \rho \frac{l}{A}$

**Capacitors:**  $C = \epsilon \cdot \frac{A}{d}$        $Q = C \cdot v$        $w_C = \frac{1}{2} C v^2$

**Inductors:**  $L = \mu \cdot \frac{N^2 A}{l}$        $B \sim i$        $w_L = \frac{1}{2} L i^2$

**AC power:**  $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$   
 $P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$        $Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i)$        $X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$

**Trigonometry:**  $\sin(-\alpha) = -\sin(\alpha)$        $\cos(-\alpha) = \cos(\alpha)$   
 $\sin(\pi - \alpha) = \sin(\alpha)$        $\cos(\pi - \alpha) = -\cos(\alpha)$   
 $\sin\left(\frac{\pi}{2} - \alpha\right) = \cos(\alpha)$        $\cos\left(\frac{\pi}{2} - \alpha\right) = \sin(\alpha)$   
 $\sin\left(\alpha - \frac{\pi}{2}\right) = -\cos(\alpha)$        $\cos\left(\alpha - \frac{\pi}{2}\right) = \sin(\alpha)$   
 $\sin(2\alpha) = 2 \sin(\alpha) \cos(\alpha)$        $\cos(2\alpha) = \cos^2(\alpha) - \sin^2(\alpha)$

$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$		$\alpha:$	$0$	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$
$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$							
$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$		$\sin(\alpha):$	$0$	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	$1$
$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$		$\tan(\alpha):$	$0$	$\frac{\sqrt{3}}{3}$	$1$	$\sqrt{3}$	$\infty$
$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$							

ECE 35, Fall 2021  
Final – Section B

Your sequence number 

Grade   
  
 / 45

Last name	<input type="text"/>
First + middle name(s)	<input type="text"/>
PID	<input type="text"/>


**Instructions:**

- Do not look at the questions or start writing until it is announced you can do so.
- Make sure you write your PID on EACH page.
- Read each problem completely and thoroughly before beginning.
- Answers without supporting calculations will receive zero credit. If you are using intuition, write a short explanation.
- All calculations must be done on these pages. It should be clear which question they belong to. Use the front for your actual work and the back as scratch paper.
- Write clearly and make sure your answer is structured properly. We will not hunt for your work or answers.
- Write your final answers in the answer boxes. Make sure you list units.
- You must follow the Final Exam Procedures that were posted on Canvas. If you are unsure of anything, ask. As a reminder:
  - Your phone should be turned off and put inside your bag
  - Calculators are not allowed.
  - This is a closed book exam.
  - Follow the Academic Integrity standards.



- (1) (4 points) Consider the circuit below.  
What is the reading  $X$  of the voltmeter?

$X$

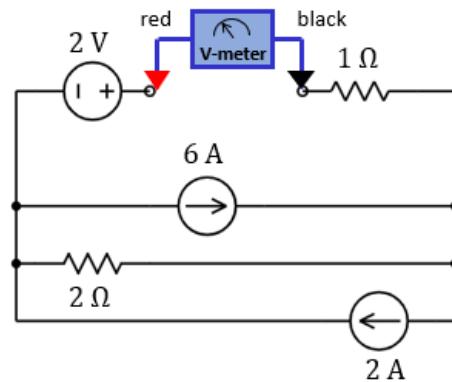

(2) (7 points) Consider the circuit below.

(a) Find the current  $i_b$ .


$i_b$

(b) Find the power  $P_1$  received by the independent source.

$P_1$


(c) Find the power  $P_2$  supplied by the dependent source.

$P_2$

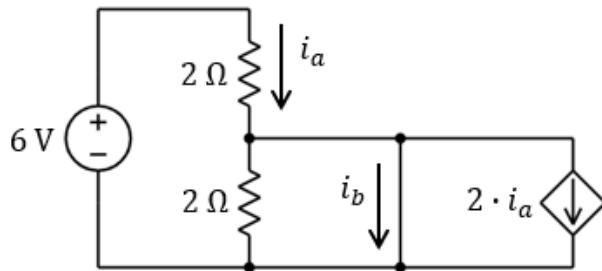


(3) (7 points)

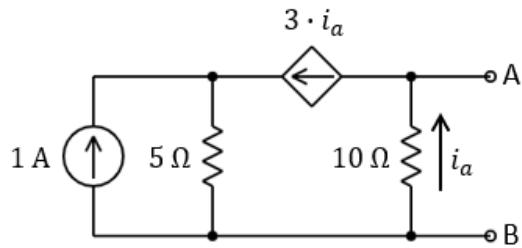- (a) Consider the circuit below. What is the Thevenin equivalent resistance between A and B?



$$R_{TH}$$

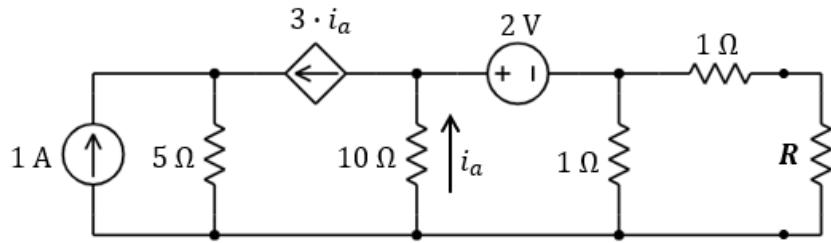- (b) Consider the circuit below (which contains the circuit above). Find the value of resistor  $R$  such that the power received by  $R$  is maximized.



$$R$$

- (4) (10 points) Consider the circuit below. For  $t < 2$  s, the switch is closed and you may assume the system has reached steady state. The switch opens at  $t = 2$  s and remains open.

Note: make sure you don't mix up  $v_a$  and  $v_b$  in the questions below.

- (a) Find the node voltage  $v_a(2^- \text{ s})$ . (i.e., just before the switch opens).

 $v_a(2^- \text{ s})$  


- (b) Find the node voltage  $v_b(2^+ \text{ s})$ . (i.e., just after the switch opens).


 $v_b(2^+ \text{ s})$  


- (c) Find the node voltage  $v_a(10 \text{ s})$ .

 $v_a(10 \text{ s})$  

- (d) Find the node voltage  $v_b(\infty)$ .

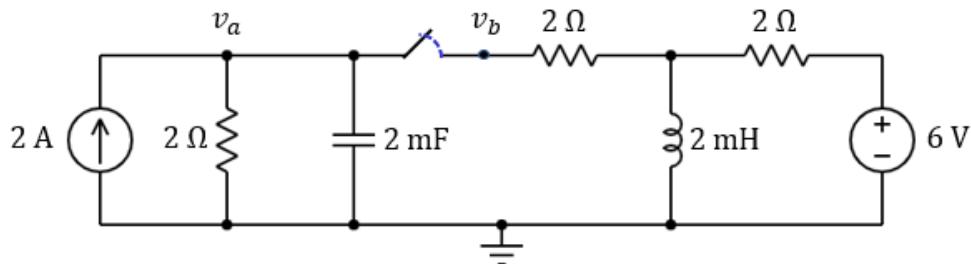 $v_b(\infty)$  

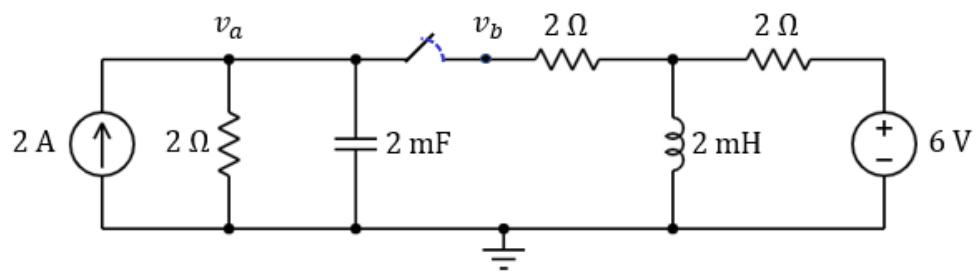

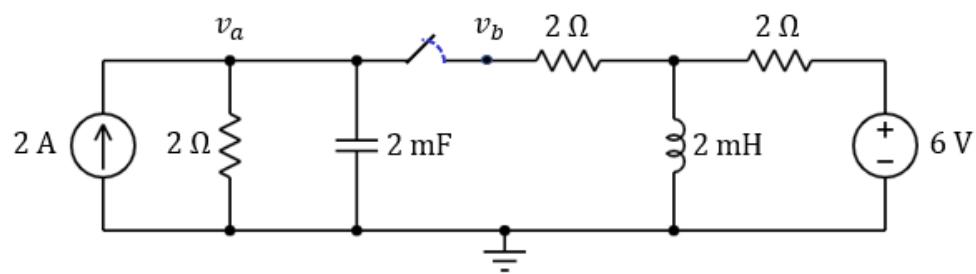


(5) (9 points) Consider the circuit below. For  $t < \frac{\pi}{2}$  s, the switch is in position 1 and you may assume the system has reached steady state. The source  $i_S$  is an AC source with  $\omega = 2$  rad/s. Its phasor diagram is shown on the left. The switch moves from position 1 to position 2 at  $t = \frac{\pi}{2}$  s and remains in position 2.


- (a) Find the current  $i_a\left(\frac{\pi}{2}^- \text{ s}\right)$ . (i.e., just before the switch moves).

$$i_a\left(\frac{\pi}{2}^- \text{ s}\right)$$

- (b) Find the current  $i_a(2\pi \text{ s})$ .

$$i_a(2\pi \text{ s})$$

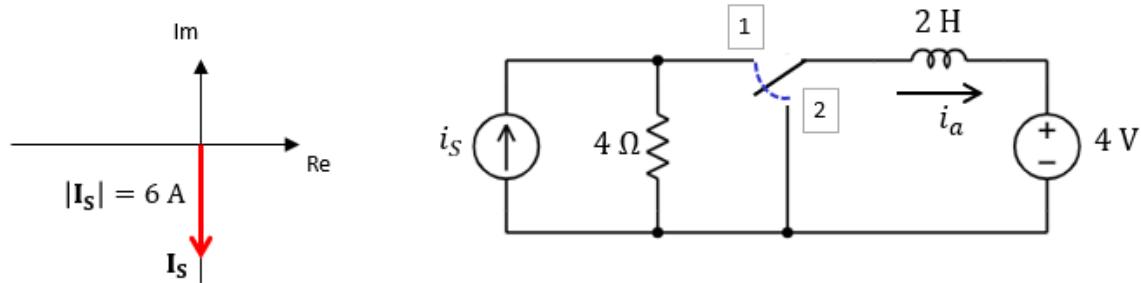

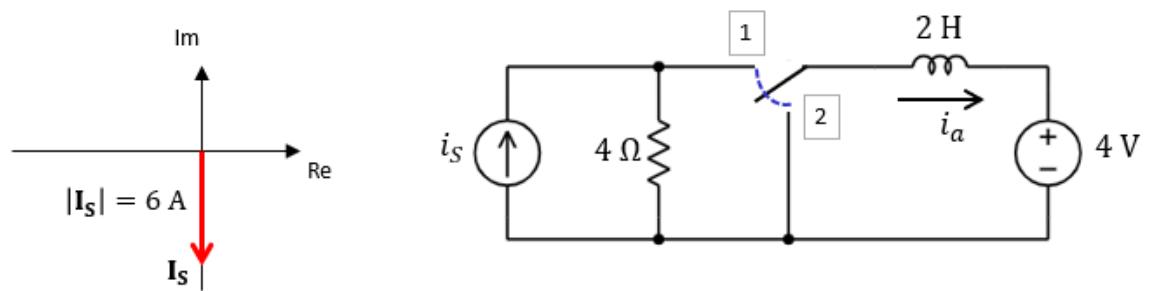

(6) (8 points) The circuit below is in steady state.

- (a) Sketch the phasor of  $i_a$  (make sure the magnitude and phase are labeled).

- (b) Find complex power  $S_L$  received by the inductor.


$S_L$

- (c) If the complex power supplied by the independent source is **0.2 - 0.4j VA**, what is the total complex power  $S$  received by both capacitors ( $S_{C1} + S_{C2}$ ) and the average power  $P_R$  received by the resistor?


$S_{C1} + S_{C2}$

$P_R$
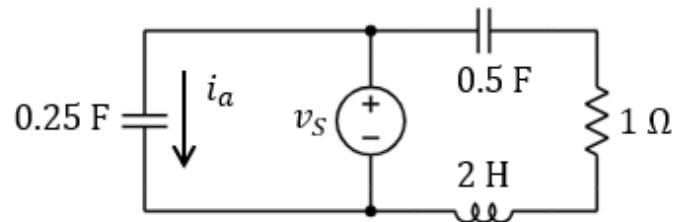
$$v_S = 2 \cdot \sin\left(2t + \frac{\pi}{12}\right) \text{ V}$$


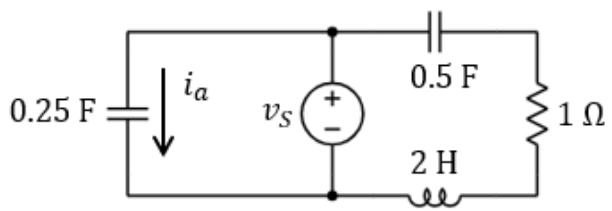
$$v_S = 2 \cdot \sin\left(2t + \frac{\pi}{12}\right) \text{ V}$$



**ECE35 Equation Sheet**

**Basics:**  $i \triangleq \frac{dq}{dt}$        $v_{ab} \triangleq \frac{dw}{dq}$        $R = \rho \frac{l}{A}$

**Capacitors:**  $C = \epsilon \cdot \frac{A}{d}$        $Q = C \cdot v$        $w_C = \frac{1}{2} C v^2$

**Inductors:**  $L = \mu \cdot \frac{N^2 A}{l}$        $B \sim i$        $w_L = \frac{1}{2} L i^2$

**AC power:**  $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$   
 $P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$        $Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i)$        $X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$

**Trigonometry:**  $\sin(-\alpha) = -\sin(\alpha)$        $\cos(-\alpha) = \cos(\alpha)$   
 $\sin(\pi - \alpha) = \sin(\alpha)$        $\cos(\pi - \alpha) = -\cos(\alpha)$   
 $\sin\left(\frac{\pi}{2} - \alpha\right) = \cos(\alpha)$        $\cos\left(\frac{\pi}{2} - \alpha\right) = \sin(\alpha)$   
 $\sin\left(\alpha - \frac{\pi}{2}\right) = -\cos(\alpha)$        $\cos\left(\alpha - \frac{\pi}{2}\right) = \sin(\alpha)$   
 $\sin(2\alpha) = 2 \sin(\alpha) \cos(\alpha)$        $\cos(2\alpha) = \cos^2(\alpha) - \sin^2(\alpha)$

$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$		$\alpha:$	$0$	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$
$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$							
$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$		$\sin(\alpha):$	$0$	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	$1$
$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$		$\tan(\alpha):$	$0$	$\frac{\sqrt{3}}{3}$	$1$	$\sqrt{3}$	$\infty$
$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$							

ECE 35, Fall 2022 – Section A  
Final

Your sequence number

Grade

/ 31

Last name	
First + middle name(s)	
PID	

**Instructions:**

- Do not look at the questions or start writing until it is announced that you can do so.
- You must follow the Final Exam Procedures that were posted on Canvas. If you are unsure of anything, ask. As a reminder:
  - Your phone should be turned off and put inside your bag
  - Calculators are not allowed.
  - This is a closed book exam.
  - Follow the Academic Integrity standards
- These pages contain the exam questions.
  - Do not write any of your work here except for scratch work. It will not be graded.
  - You need to write your final answer in the answer boxes here. Make sure you list units.
  - Keep these question pages stapled together. The last page is the equation sheet; you may detach this if you want.
  - Make sure you write your PID on EACH page.
  - Read each problem completely and thoroughly before beginning.



(1) (7 points)

- (a) In the circuit below, the ammeter and voltmeter are ideal.

What is the reading  $X$  of the voltmeter?

$X$

What is the reading  $Y$  of the ammeter?


$Y$

What is the voltage  $v_a$ ?

$v_a$


What is the power  $P$  received by the 4 A current source?

$P$

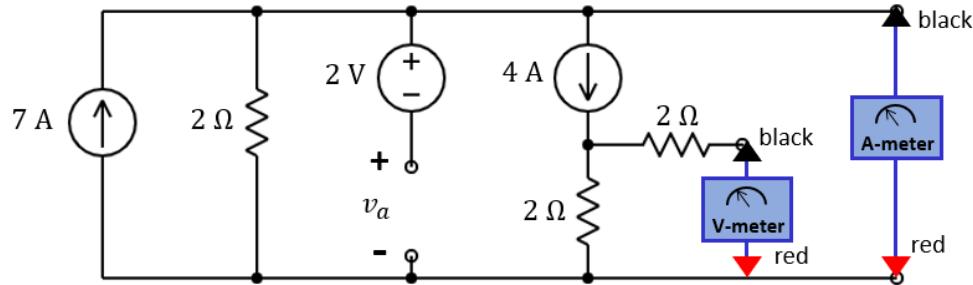

- (b) What is the Thevenin resistance  $R_{th}$  between A and B ?

$R_{th}$

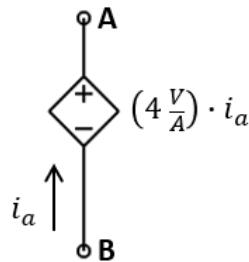

(2) (7 points) For this question, you should make reasonable numerical approximations if needed.


- (a) Consider the circuit below. For  $t < 0$  s, the switch is closed, and the system has reached steady state. At time  $t = 0$  s, the switch opens.

Find the current  $i_a$  at time  $t = 0^-$  s (i.e., immediately before the switch opens).

$i_a(0^-)$

Find the current  $i_a$  at time  $t = 0^+$  s (i.e., immediately after the switch opens).

$i_a(0^+)$

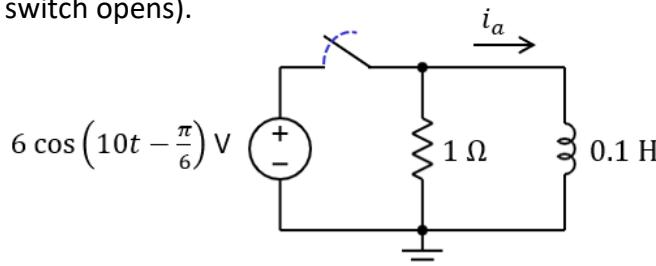

- (b) Consider the circuit below. For  $t < 0$  s, the switch is in position 1, and the system has reached steady state. At time  $t = 0$  s, the switch moves to position 2 (and stays there).

Just before the switch moves,  $i_x$  is 4 A.

Find the current  $i_b$  at time  $t = 0^+$  s (i.e., immediately after the switch moves to position 2).


$i_b(0^+)$

Find the current  $i_b$  at time  $t = 2$  s.

$i_b(2)$

Find the current  $i_b$  at time  $t = \infty$ .

$i_b(\infty)$

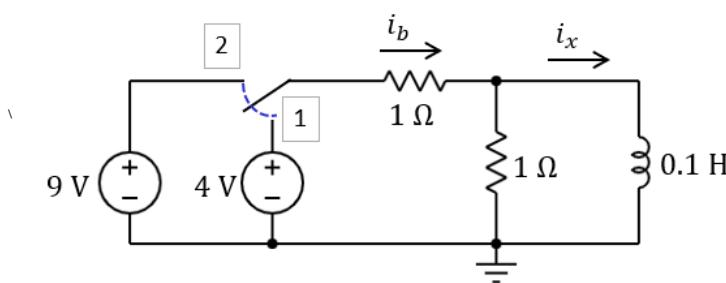


- (c) Consider the circuit below. For  $t < 2$  s, the switch is open, and the system may not have reached steady state. At time  $t = 2$  s, the switch closes. Just after the switch closes,  $i_c$  is 5 A.

Find the current  $i_c$  at time  $t = 4$  s.

$i_c(4)$

Find the current  $i_c$  at time  $t = 6$  s.

$i_c(6)$

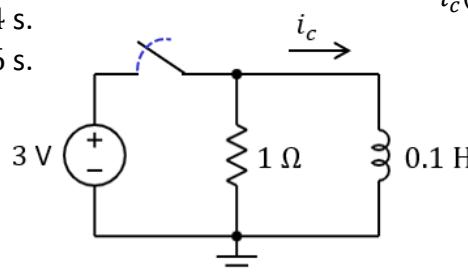

(3) (6 points) Consider the circuit below. You may assume it is in steady-state.

(a) Find the current of current source  $i_{S1}$  at time  $t = \frac{\pi}{20}$  s.


$$i_{S1} \left( \frac{\pi}{20} \text{ s} \right)$$

(b) Find the voltage  $v_a$  at time  $t = \frac{\pi}{20}$  s.

$$v_a \left( \frac{\pi}{20} \text{ s} \right)$$

(c) Find the maximum value of the waveform  $i_a(t)$ .

$$i_{a \max}$$

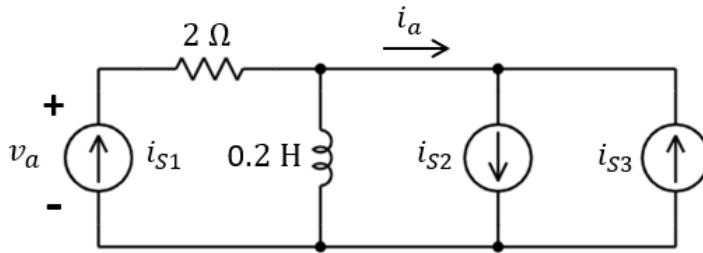

$$i_{S1} = 3 + 5 \cos(10t) \text{ A}$$

$$i_{S2} = 6 \sin\left(20t + \frac{\pi}{4}\right) \text{ A}$$

$$i_{S3} = 3\sqrt{2} \cos(20t) \text{ A}$$

- (4) (6 points) The circuit below represents an AC circuit in steady-state in the phasor domain (for the complex numbers, you may assume units are V, A,  $\Omega$ , etc. as appropriate). The voltage source  $v_S$  is an AC source with  $\omega = 5 \text{ rad/s}$ . Each box represents the impedance of a single circuit element (a resistor, capacitor or inductor).


(a) Find the average power  $P_s$  supplied by the voltage source.

 $P_s$  

(b) Find the average power  $P_1$  received by the element with impedance  $Z_1$ .

 $P_1$  

(c) Find the RMS value of  $i_x$ .

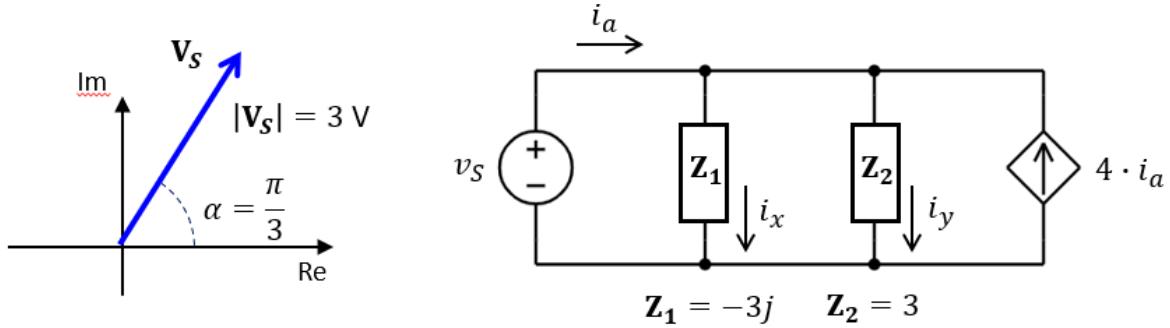 $i_{xRMS}$  


## (5) (5 points)

- (a) Consider the circuit below. You are not given the values of  $k$  and  $V_s$  (but you are told that all sources are DC sources). We are considering the circuit after the switch closes.


- The time constant  $\tau$  associated with  $i_L(t)$  during this transition is  $\tau = 2$  s.
- You also measure that when current  $i_L$  reaches 4 A, the voltage  $v_L$  drops to 0 V.

What is the current  $i_L$  when the system reaches steady state?

Find the Norton equivalent resistance  $R_N$  between A and B if we were to remove the inductor from the circuit.

During the transition (in our original circuit with the inductor in there), when the current  $i_L$  has a value of 1 A, what is the value of the voltage  $v_L$ ?

$i_L$
$R_N$
$v_L$

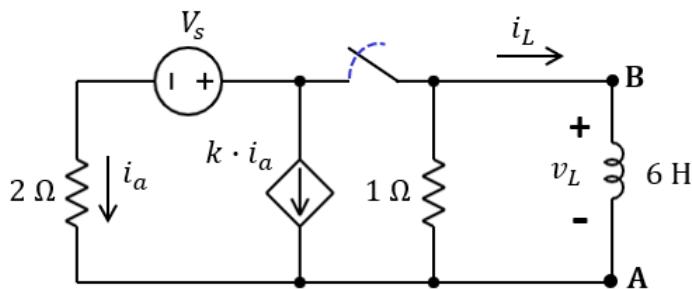


- (b) Consider the circuit below. The unknown values of  $k$  and  $V_s$  are the same as in the circuit above. The switch closes at time  $t = 400$  s (you do not know if the system has reached steady state before the switch closes).

Find the time constant  $\tau_1$  associated with  $v_c(t)$  for  $t > 400$  s.

$\tau_1$
$\tau_2$

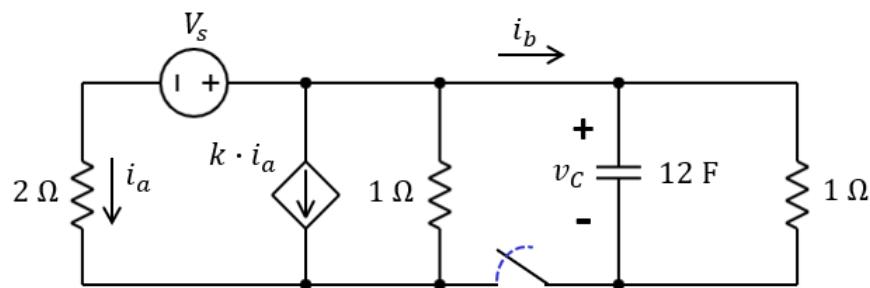Find the time constant  $\tau_2$  associated with  $i_a(t)$  for  $t > 400$  s.



**ECE35 Equation Sheet**

**Basics:**  $i \triangleq \frac{dq}{dt}$        $v_{ab} \triangleq \frac{dw}{dq}$        $R = \rho \frac{l}{A}$

**Capacitors:**  $C = \epsilon \cdot \frac{A}{d}$        $Q = C \cdot v$        $w_C = \frac{1}{2} Cv^2$

**Inductors:**  $L = \mu \cdot \frac{N^2 A}{l}$        $B \sim i$        $w_L = \frac{1}{2} Li^2$

**AC power:**  $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \quad X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$

<b>Trigonometry:</b>	$\sin(-\alpha) = -\sin(\alpha)$	$\cos(-\alpha) = \cos(\alpha)$
	$\sin(\pi - \alpha) = \sin(\alpha)$	$\cos(\pi - \alpha) = -\cos(\alpha)$
	$\sin\left(\frac{\pi}{2} - \alpha\right) = \cos(\alpha)$	$\cos\left(\frac{\pi}{2} - \alpha\right) = \sin(\alpha)$
	$\sin\left(\alpha - \frac{\pi}{2}\right) = -\cos(\alpha)$	$\cos\left(\alpha - \frac{\pi}{2}\right) = \sin(\alpha)$
	$\sin(2\alpha) = 2 \sin(\alpha) \cos(\alpha)$	$\cos(2\alpha) = \cos^2(\alpha) - \sin^2(\alpha)$

$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$	$\alpha:$	0	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$
$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$	$\sin(\alpha):$	0	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	1
$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$	$\tan(\alpha):$	0	$\frac{\sqrt{3}}{3}$	1	$\sqrt{3}$	$\infty$
$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$						
$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$						

ECE 35, Fall 2022 – Section B  
Final

Your sequence number

Grade	
	/ 31

Last name	
First + middle name(s)	
<b>PID</b>	

**Instructions:**

- Do not look at the questions or start writing until it is announced that you can do so.
- You must follow the Final Exam Procedures that were posted on Canvas. If you are unsure of anything, ask. As a reminder:
  - Your phone should be turned off and put inside your bag
  - Calculators are not allowed.
  - This is a closed book exam.
  - Follow the Academic Integrity standards
- These pages contain the exam questions.
  - Do not write any of your work here except for scratch work. It will not be graded.
  - You need to write your final answer in the answer boxes here. Make sure you list units.
  - Keep these question pages stapled together. The last page is the equation sheet; you may detach this if you want.
  - Make sure you write your PID on EACH page.
  - Read each problem completely and thoroughly before beginning.




(1) (7 points)

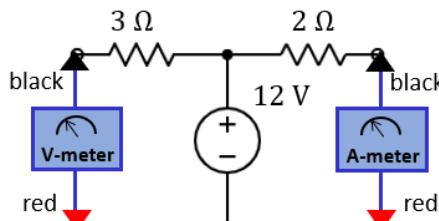(a) The ammeter and voltmeter are ideal.

What is the reading  $X$  of the voltmeter?


What is the reading  $Y$  of the ammeter?



$X$


$Y$

(b) What is the voltage  $v_a$ ?

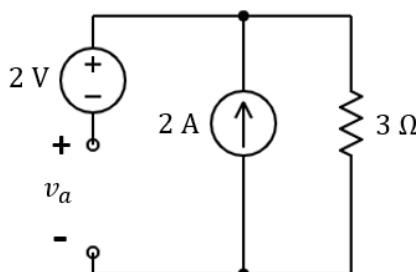

$v_a$

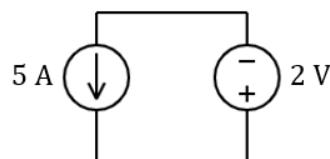
(c) What is the power  $P$  received by the current source?



$P$

(d) What is the voltage  $v_b$ ?


What is the current  $i_a$ ?

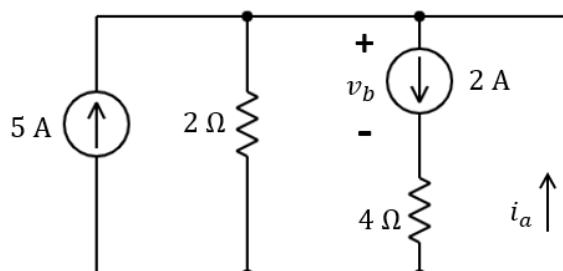

$v_b$

$i_a$

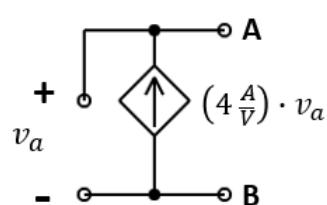
(e) What is the Thevenin resistance  $R_{th}$  between A and B?



$R_{th}$

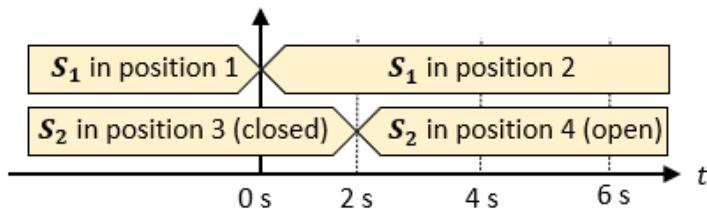- (2) (7 points) For this question, you should make reasonable numerical approximations if needed. Consider the circuit below.

- For  $t < 0$  s, switch  $S_1$  is in position 1, switch  $S_2$  is in position 3, and the system has reached steady state.
- At time  $t = 0$  s, switch  $S_1$  moves from position 1 to position 2 (you may assume that  $i_{S1}$  turns off at that point). Switch  $S_2$  stays in position 3 (closed).
- At time  $t = 2$  s, switch  $S_2$  moves from position 3 to position 4 (open). Switch  $S_1$  stays in position 2.



(a) Find the capacitor voltage  $v_c$  at time  $t = 0^-$  s  
(i.e., immediately before switch  $S_1$  moves).

$$v_c(0^- \text{ s})$$

Find the node voltage  $v_a$  at time  $t = 0^+$  s  
(i.e., immediately after switch  $S_1$  moves).


$$v_a(0^+ \text{ s})$$

(b) Find the node voltage  $v_a$  at time  $t = 2^-$  s.  
(i.e., immediately before switch  $S_2$  moves).

$$v_a(2^- \text{ s})$$

(c) Find the node voltage  $v_a$  at time  $t = 6$  s.

$$v_a(6 \text{ s})$$

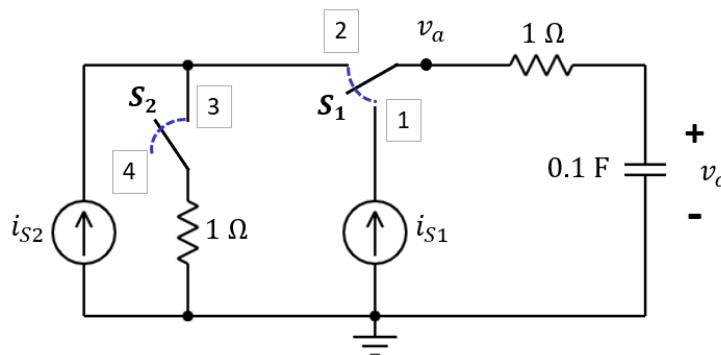

$$i_{S1} = 8 \cos\left(10t - \frac{\pi}{2}\right) \text{ A}$$


$$i_{S2} = 5 \text{ A}$$

(3) (6 points) For all the circuits in this question, you may assume that they are in steady-state.

- (a) Find the phasor of  $v_x(t) = 8 \sin\left(20t + \frac{\pi}{4}\right)$  V. You can write your answer in cartesian or polar coordinates.

 $v_x$ 

- (b) Find the current  $i_b$  at time  $t = \frac{\pi}{10}$  s.

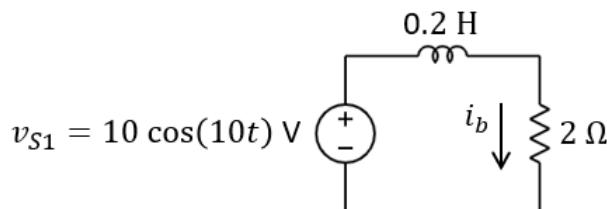
 $i_b \left(\frac{\pi}{10} \text{ s}\right)$ 

- (c) Note the similarity to circuit in part (b).


Find the voltage  $v_{S2}$  of the voltage source at time  $t = \frac{\pi}{10}$  s.

 $v_{S2} \left(\frac{\pi}{10} \text{ s}\right)$ 


Find the current  $i_c$  at time  $t = \frac{\pi}{10}$  s.

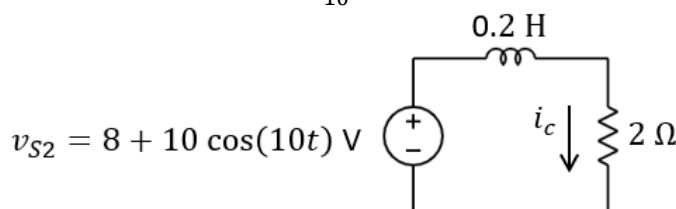 $i_c \left(\frac{\pi}{10} \text{ s}\right)$ 

- (d) Find the current  $i_d$  at time  $t = \frac{\pi}{10}$  s.

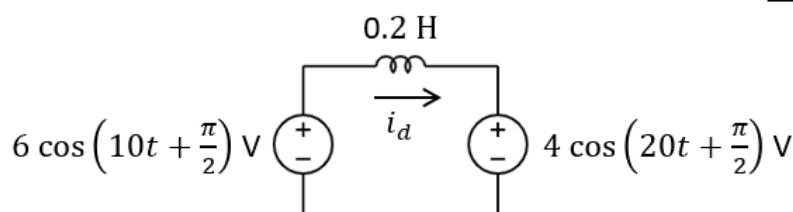 $i_d \left(\frac{\pi}{10} \text{ s}\right)$ 


- (e) Find the maximum value of the waveform  $v_a(t)$ .

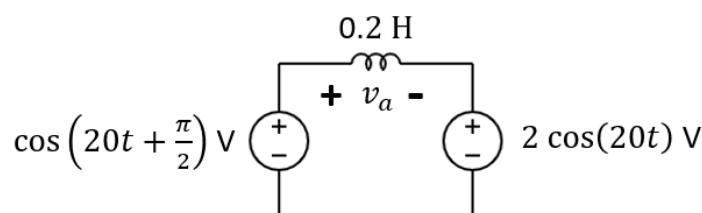 $v_{a \max}$ 

- (4) (6 points) The circuits below represent AC circuits in steady-state in the phasor domain (for the complex numbers, you may assume units are V, A, Ω, etc. as appropriate). The independent current sources are AC sources with  $\omega = 5 \text{ rad/s}$ . Each box represents the impedance of a single circuit element (a resistor, capacitor or inductor).


- (a) Find the phasor  $V_a$ . You can write your answer in cartesian or polar coordinates.

$V_a$

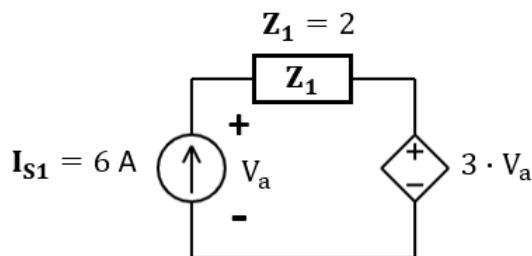

- (b) In the circuit below, we set  $\alpha = \frac{\pi}{2}$  (the figure is clearly not drawn to scale). Find the average power  $P_s$  supplied by the current source  $I_{s2}$ .

$P_s$

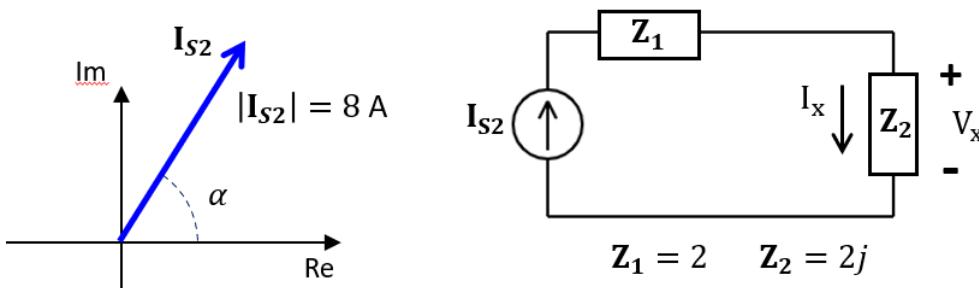

- (c) For the same circuit as in part (b), we change  $\alpha$  to  $\alpha = \frac{\pi}{6}$ .

Find the average power  $P_s$  supplied by the current source  $I_{s2}$ .

$P_s$

Find the average power  $P_1$  received by the element with impedance  $Z_2$ .

$P_2$

Find the magnitude of the phasor  $V_x$ .

$|V_x|$

Find the RMS value of  $i_x$ .

$i_{xRMS}$


(5) (5 points)

- (a) Consider the circuit below. You are not given the values of  $k$  and  $V_s$  (but you are told that all sources are DC sources). We are considering the circuit after the switch closes.

We measure that when the voltage  $v_c$  reaches 6 V, the current  $i_c$  is 2 A. Similarly, when the voltage  $v_c$  becomes 10 V, the current  $i_c$  drops to 0 A.

Find the Norton equivalent resistance  $R_N$  between A and B when we remove the capacitor from the circuit.


$$R_N$$

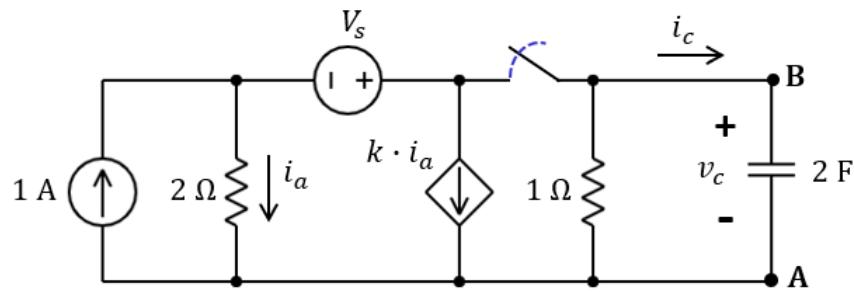

- (b) Consider the circuit below. The unknown values of  $k$  and  $V_s$  are the same as in the circuit above. The switch closes at time  $t = 400 \text{ s}$  (you do not know if the system has reached steady state before the switch closes).

Find the time constant  $\tau$  associated with  $i_a(t)$  for  $t > 400 \text{ s}$ .

$$\tau$$

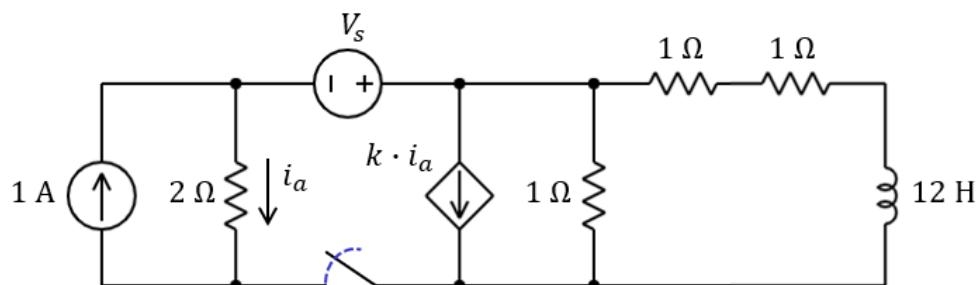

### ECE35 Equation Sheet

**Basics:**  $i \triangleq \frac{dq}{dt}$        $v_{ab} \triangleq \frac{dw}{dq}$        $R = \rho \frac{l}{A}$

**Capacitors:**  $C = \epsilon \cdot \frac{A}{d}$        $Q = C \cdot v$        $w_C = \frac{1}{2} C v^2$

**Inductors:**  $L = \mu \cdot \frac{N^2 A}{l}$        $B \sim i$        $w_L = \frac{1}{2} L i^2$

**AC power:**  $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \quad X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$

<b>Trigonometry:</b> $\sin(-\alpha) = -\sin(\alpha)$	$\cos(-\alpha) = \cos(\alpha)$
$\sin(\pi - \alpha) = \sin(\alpha)$	$\cos(\pi - \alpha) = -\cos(\alpha)$
$\sin\left(\frac{\pi}{2} - \alpha\right) = \cos(\alpha)$	$\cos\left(\frac{\pi}{2} - \alpha\right) = \sin(\alpha)$
$\sin\left(\alpha - \frac{\pi}{2}\right) = -\cos(\alpha)$	$\cos\left(\alpha - \frac{\pi}{2}\right) = \sin(\alpha)$
$\sin(2\alpha) = 2 \sin(\alpha) \cos(\alpha)$	$\cos(2\alpha) = \cos^2(\alpha) - \sin^2(\alpha)$

$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$	$\alpha:$ 0 $\frac{\pi}{6}$ $\frac{\pi}{4}$ $\frac{\pi}{3}$ $\frac{\pi}{2}$
$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$	$\sin(\alpha):$ 0 $\frac{1}{2}$ $\frac{\sqrt{2}}{2}$ $\frac{\sqrt{3}}{2}$ 1
$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$	$\tan(\alpha):$ 0 $\frac{\sqrt{3}}{3}$ 1 $\sqrt{3}$ $\infty$
$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$	
$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$	

# ECE 35, Spring 2020

## Quiz 3

/ 10

Last name

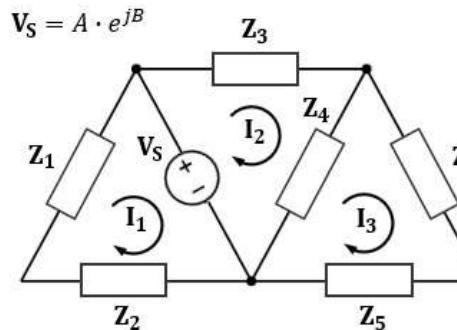

First + middle  
name(s)

**PID**

### (1) (5 points)

Consider the circuit below. The system is in steady state and represented in phasor form.

- Find the mesh currents  $\mathbf{I}_1$ ,  $\mathbf{I}_2$  and  $\mathbf{I}_3$  (expressed in polar form).
- Find the complex power supplied by  $\mathbf{V}_S$ .



A: 6 V  
B: 90 degrees  
Z<sub>1</sub>: 1  
Z<sub>2</sub>: 2  
Z<sub>3</sub>: 1  
Z<sub>4</sub>: 2  
Z<sub>5</sub>: -2j  
Z<sub>6</sub>: 2+2j


### (2) (5 points)

Consider the circuit below. The system is in steady state.

- Find the average power received by resistor  $R$ .
- What load can we place between A and B that would result in maximum average power received by that load? Give your result as two elements in series (with their values).

$$v_s(t) = A_1 \cos(10t) \quad i_s(t) = A_2 \cos(10t)$$

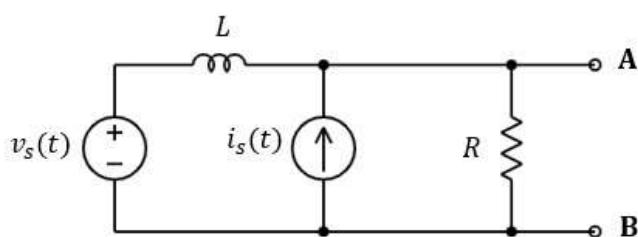
A<sub>1</sub>: 4 V  
A<sub>2</sub>: 3 A  
L: 0.2 H  
R: 2 ohm



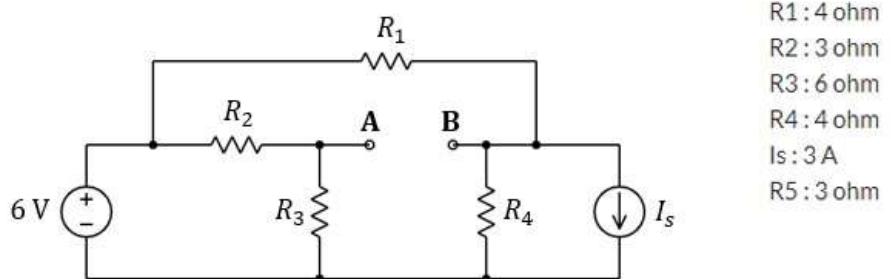(3) (5 points)

Consider the circuit below.


- Find the Thevenin equivalent model between A and B. Make sure to label A and B in your model as well.
- If we were to place a resistor  $R_5$  between A and B, what is the current through that resistor (measured from A to B)?



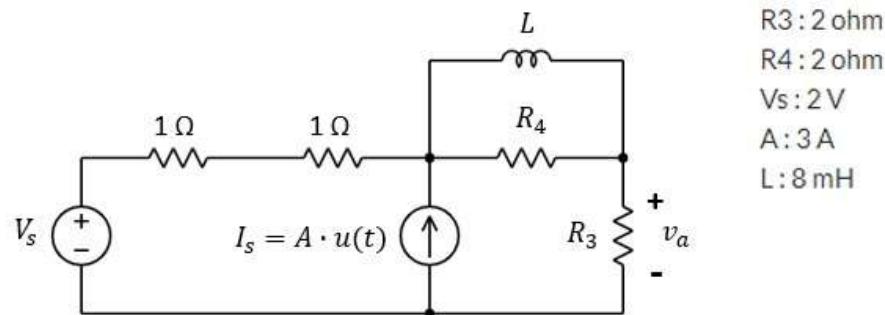(4) (5 points)

Consider the circuit below. For  $t < 0$  s, you may assume the system has reached steady state.

- Find  $v_a(t)$  for  $t > 0$  s.
- Sketch the waveform  $v_a(t)$  for  $t > 0$  s. Include where you can observe the time constant.



**(5) (5 points)**

Consider the circuit below. The system is in steady state.

Find  $i_a(t)$ .

$$i_s(t) = A_1 \cos(2t + B_1) + A_2 \cos(4t + B_2)$$

A1: 2 A


B1: 60 degrees

A2: 4 A

B2: 0 degrees

R1: 9 ohm

k: 3 V/A

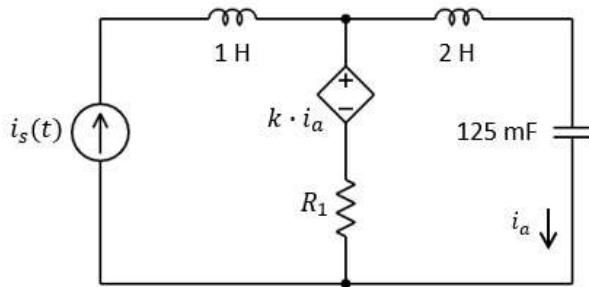

ECE 35, Fall 2019  
Final

Sequence  
number

Grade

/ 45

Last name

First + middle  
name(s)

PID


**Instructions:**

- Do not look at the questions or start writing until it is announced you can do so.
- Read each problem completely and thoroughly before beginning.
- All calculations must be done in your blue book. It should be clear which question they belong to. Answers without supporting calculations will receive zero credit. If you are using intuition, write a short explanation.
- Write clearly and make sure your answer is structured properly. We will not hunt for your work or answers.
- Write your final answers in the answer boxes on these question pages. Make sure you list units!
- You must follow the Final Exam Procedures that were posted on TritonEd. If you are unsure of anything, ask. As a reminder:
  - Your phone should be turned off and put inside your bag in the front of the room (or on the table in the front). If you are found to have a phone (or other communication device) on you during the exam, your exam will not be graded.
  - Calculators are not allowed.
  - This is a closed book exam.




(1) (a) What is the volt-meter reading X? (2 points)

X

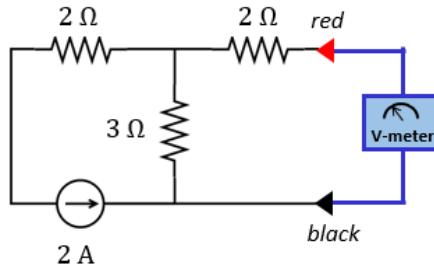


(b) Find **volt-meter** reading X and the **ammeter** reading Y. (2 points)

X   
Y

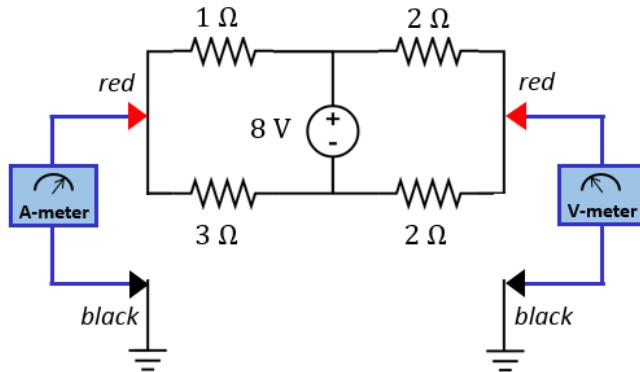

(c) The system is in steady state. Find the current  $i_1$ . (3 points)

$i_1$

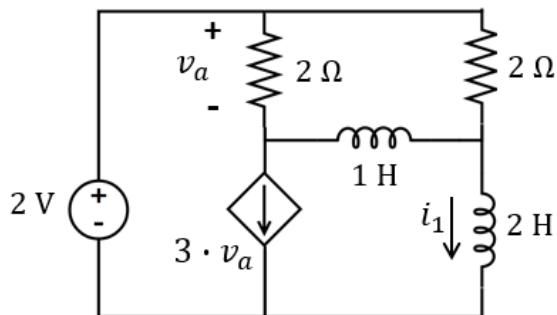

- (2) For  $t < 0$  s, both switches are closed and you may assume the system has reached steady state. Both switches open at time  $t = 0$  s (at exactly the same time).

(a) Find  $v_a(0^-)$ ,  $v_b(0^-)$  and  $v_c(0^-)$ . *(2 points)*

$$v_a(0^-) \quad \boxed{\hspace{2cm}}$$

$$v_b(0^-) \quad \boxed{\hspace{2cm}}$$


$$v_c(0^-) \quad \boxed{\hspace{2cm}}$$

- (b) Find  $v_a(t)$ ,  $v_b(t)$  and  $v_c(t)$  for  $t > 0$  s. Also sketch all three waveforms in your blue book (a rough sketch is fine). *(9 points)*


$$v_a(t) \quad \boxed{\hspace{2cm}}$$

$$v_b(t) \quad \boxed{\hspace{2cm}}$$

$$v_c(t) \quad \boxed{\hspace{2cm}}$$

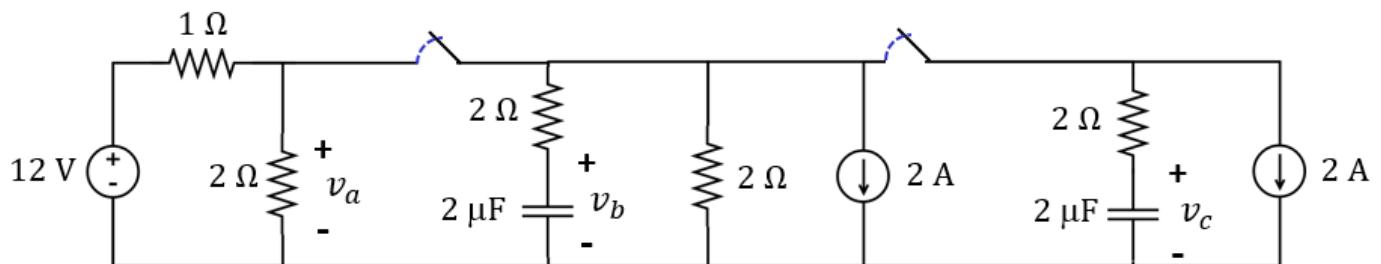

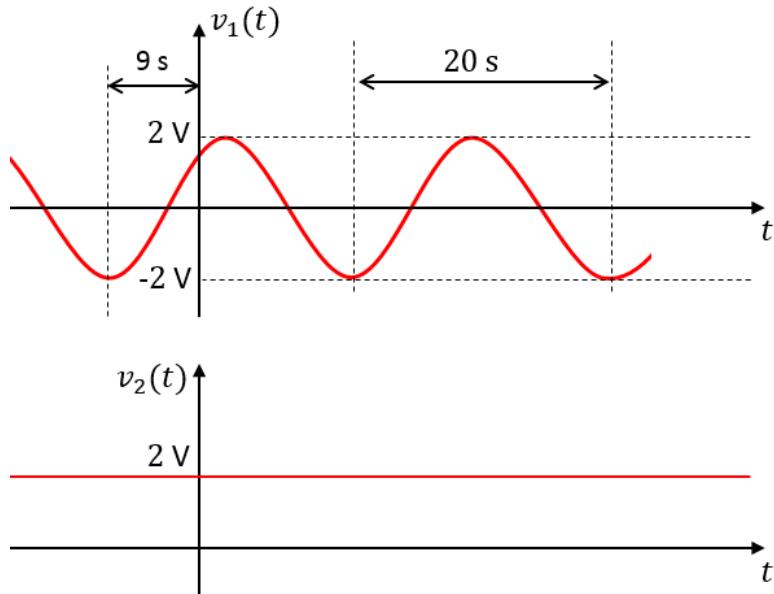- (3) Find the phasors  $\mathbf{V}_1$  and  $\mathbf{V}_2$  for the waveforms below. You can use polar or cartesian notation. (5 points)




$\mathbf{V}_1$	<input type="text"/>
$\mathbf{V}_2$	<input type="text"/>

- (4) (a) For the circuit below, find node voltage  $v_1$ . (4 points)

- (b) Find the power  $P$  supplied by the 3 A current source (i.e., the left current source). (2 points)

$v_1$	<input type="text"/>
$P$	<input type="text"/>

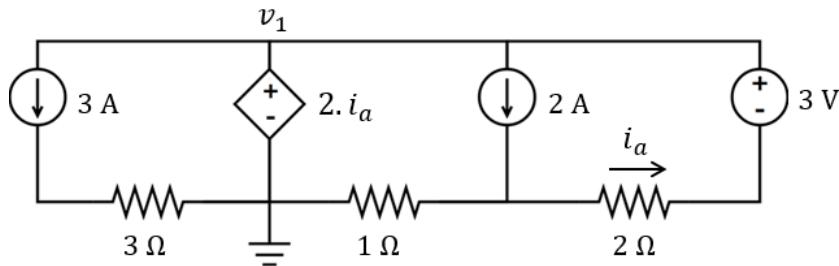


- (5) (a) Consider the figure below. Note that  $k$  of the dependent source is unknown. We make the following measurements:

When  $R_1 = 1 \Omega$ , we find that  $v_1 = 2 \text{ V}$

When  $R_1 = 4 \Omega$ , we find that  $v_1 = 4 \text{ V}$

Find  $v_1$  when  $R_1 = 3 \Omega$ . (4 points)

$$v_1 \boxed{\hspace{1cm}}$$

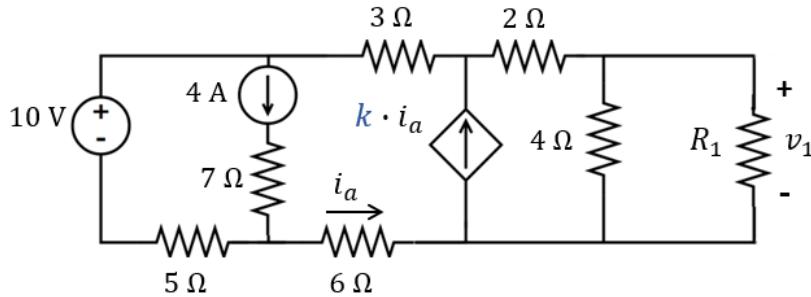


- (b) The circuit below is that of part (a), with a few modifications (marked in red): the current and voltage source have a different value, and an extra inductor, resistor and voltage source are attached (on the right). The value of  $k$  is the same. Furthermore, we set  $R_1 = 2 \Omega$ .

$$v_1 \left( \frac{11\pi}{6} \text{ s} \right) \boxed{\hspace{1cm}}$$

Assume the system is in steady state.

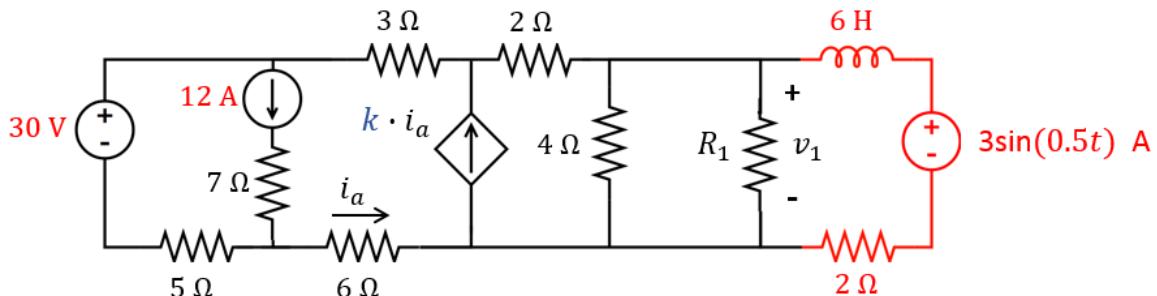Find  $v_1 \left( \frac{11\pi}{6} \text{ s} \right)$ , i.e.,  $v_1$  at time  $t = \frac{11\pi}{6}$  seconds. (5 points)




- (6) (a) Find the average power P and reactive power Q received by the current source. (5 points)

P

Q

- (b) We replace the  $1 \Omega$  resistor with another element (either a resistor, a capacitor or an inductor). The result is that the reactive power Q of the current source is now equal to zero. What is the value X of this new element (so we are looking for the resistance, capacitance or inductance value)? Use the correct units, so we know whether you think it is a resistor, capacitor or inductor (For example,  $X = 9 \Omega$ ). (2 points)

X

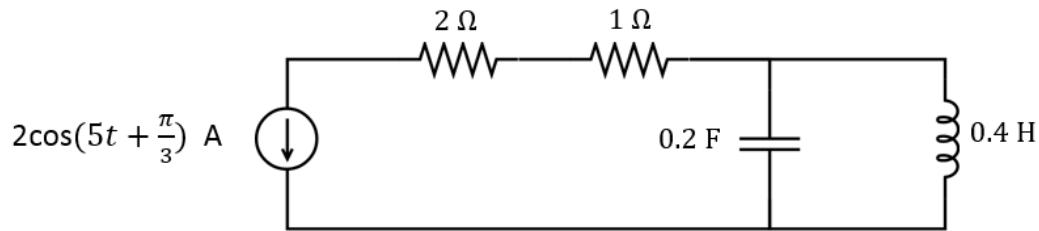

For  $t < 1$  s, the switch is open. The switch closes at  $t = 1$  s and remains closed.


(a) Find  $v_a(0$  s)

(b) Find  $i_a(0$  s)

(c) Find  $v_a(2$  s)

(d) Find  $i_a(2$  s)

R1:	$1\ \Omega$
R2:	$1\ \Omega$
R3:	$2\ \Omega$
V1:	1 V
V2:	2 V
V3:	0 V
I1:	2 A

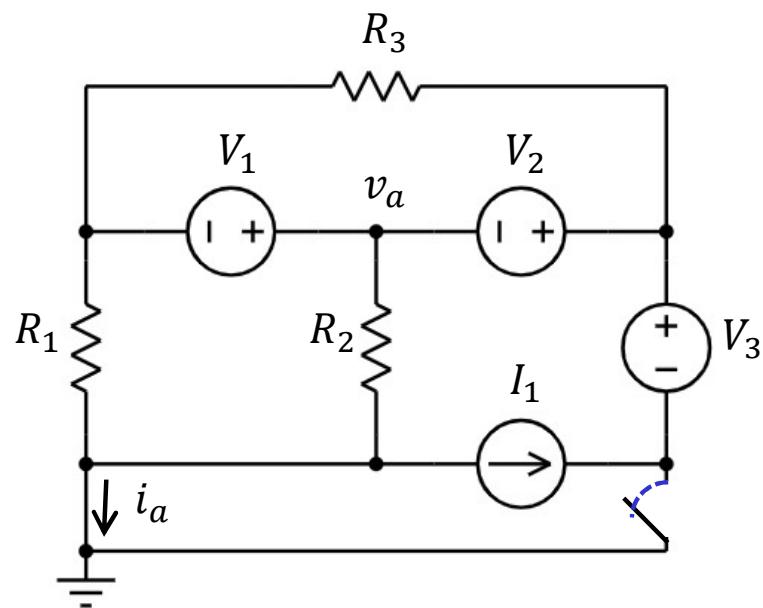



- (a) For the circuit on the right, find the Thevenin equivalent model between A and B. Draw the model and don't forget to label A and B.

R1:	$2 \Omega$
k:	$1 \text{ A/V}$
X:	$4 \text{ V}$
Y:	$1 \text{ V}$

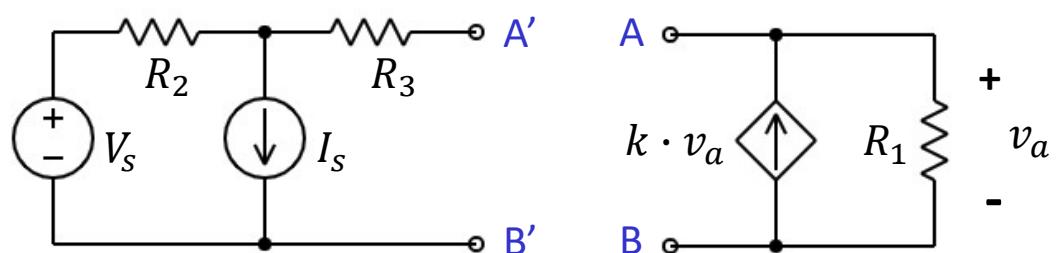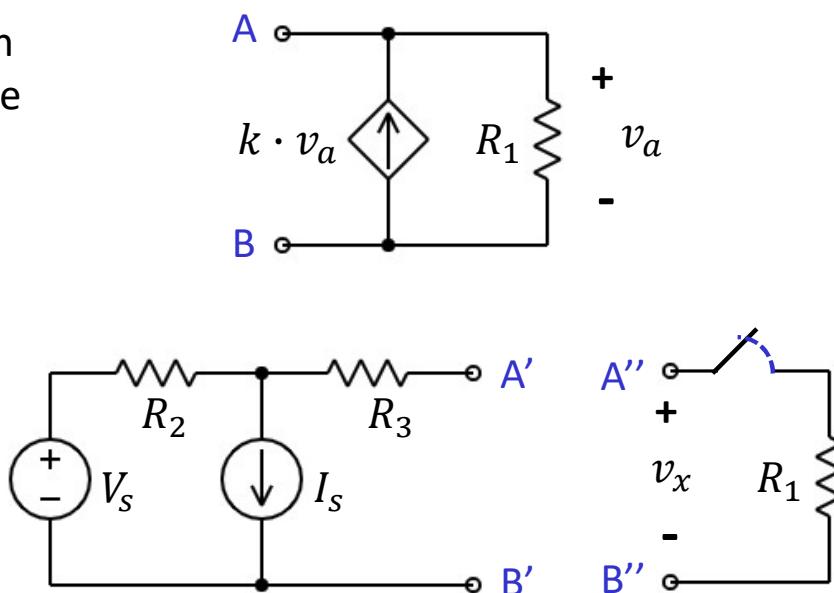- (b) Consider the two circuits on the right (you are not given the values of  $R_2$ ,  $R_3$ ,  $V_s$  or  $I_s$ ). We connect the two circuits together, A' to A'' and B' to B'' and do two measurements. When the switch is open, we measure  $v_x = X$ . When the switch is closed, we measure  $v_x = Y$ .

On the right, the circuit between A' and B' is the same as the one above and the circuit between A and B is the same as the one in part (a).

If we connect them together, A' to A and B' to B, what is value of  $v_a$ ?




For  $t < 0$  s, the switch is closed and you may assume the system has reached steady state. The switch opens at  $t = 0$  s and remains open.

- (a) Find  $i_a(0^-)$  s (i.e., just before the switch opens)
- (b) Find  $v_b(0^+)$  s (i.e., right after the switch opens)
- (c) Find  $i_a(4$  s)
- (d) Find  $v_b(4$  s)

*Note: For any of the parts, you can leave your answers as a function of  $e$ .*

R1:	$4 \Omega$
R2:	$1 \Omega$
R3:	$1 \Omega$
R4:	$3 \Omega$
I <sub>s</sub> :	12 A
k:	2 A/A
C:	4 F
L:	8 H

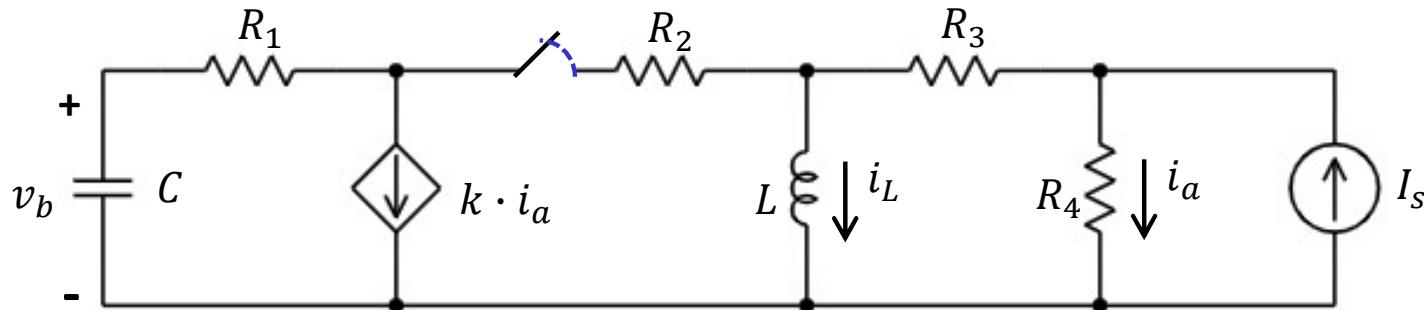


The AC circuit below is in steady state.



- (a) What is the maximum value of the waveform  $i_a(t)$ ?
- (b) Find the complex power  $S$  supplied by the voltage source  $v_1$ .
- (c) Find the average power  $P$  received by that same voltage source  $v_1$ .

R:	$2 \Omega$
C:	$100 \text{ mF}$
L:	$100 \text{ mH}$
k:	$3 \text{ A/A}$
A1:	$10 \text{ V}$
B1:	-15 degrees
T:	$4 \text{ s}$

$$v_1(t) = A_1 \cos(10t + B_1)$$

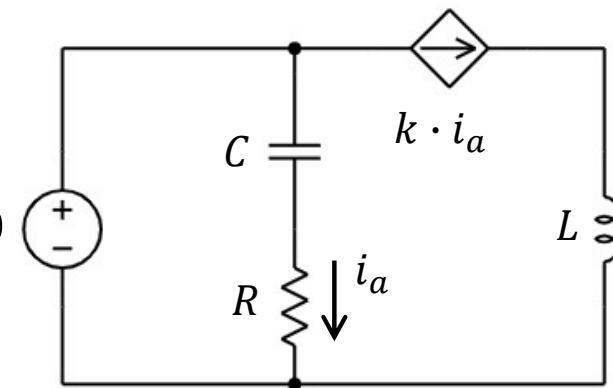

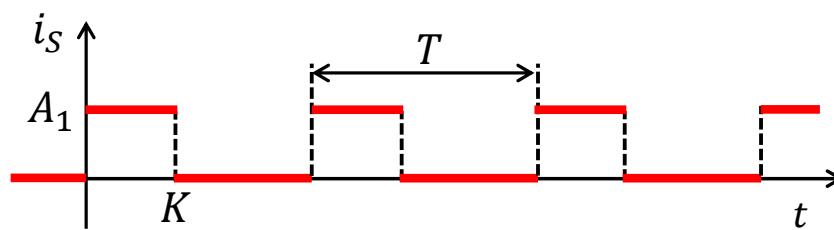
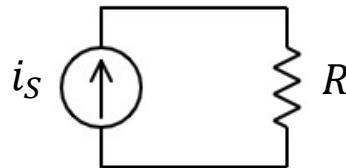
- (d) In the circuit below, the waveform  $i_S(t)$  is periodic with period  $T$ . The resistor  $R$  is the same as in the circuit above. Find the value of  $K$  such that the average power received by the resistor in the circuit below is the same as by the resistor in the circuit above.



In the circuit,  $v_1$  and  $v_2$  are AC sources with  $\omega = 100 \text{ rad/s}$ . The phasor diagram shows the phasors of  $v_1$  and  $v_2$ . It is not drawn to scale. You may assume the system is in steady state.

$V_3$  is a DC source.

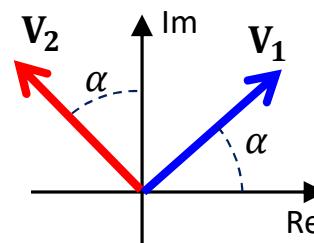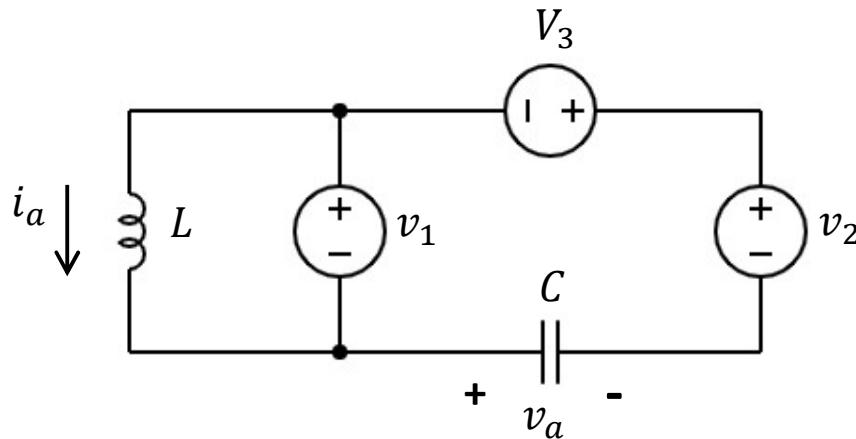- (a) What is  $v_2 \left( \frac{T}{4} \right)$  where  $T$  is the period of the waveform ?
- (b) What is the waveform  $i_a(t)$ ?
- (c) What is the maximum value of the waveform  $v_a(t)$ ?



$ V_1 :$	2 V
$ V_2 :$	3 V
alpha:	30 degrees
$V_3:$	3 V
C:	10 mF
L:	25 mH

# ECE 35, Winter 2022

## Final

Your sequence number 

Grade	Last name
<input type="text"/> / 45	First + middle name(s)
	PID

### Instructions:

- Do not look at the questions or start writing until it is announced you can do so.
- Make sure you write your PID on EACH page.
- We will only look at the work that is within the dotted box on each page. You can use pages that were part of earlier questions if there is still space. There are also two extra pages at the end that you can use as overflow for any of the questions. Always clearly mark where we can find the work for each question.
- You can use the backside of the pages as scratch paper, but we will not look at this for grading purposes.
- Read each problem completely and thoroughly before beginning.
- Answers without supporting calculations will receive zero credit. If you are using intuition, write a short explanation. Write clearly and make sure your answer is structured properly. We will not hunt for your work or answers.
- Write your final answers in the answer boxes. Make sure you list units.
- The last page of the exam is the equation sheet. You may detach this if you want.
- You must follow the Final Exam Procedures that were posted on Canvas. If you are unsure of anything, ask. As a reminder:
  - Your phone should be turned off and put inside your bag
  - Calculators are not allowed.
  - This is a closed book exam.
  - Follow the Academic Integrity standards.




- (1) (5 points) In the circuit below, the two meters are digital multimeters (DMMs), with one set to the ammeter setting and the other to the voltmeter setting. You can assume the DMMs act as ideal meters in either setting.

(a) What is the reading  $X_1$  of the DMM in the ammeter setting?

$X_1$

(b) What is the reading  $Y_1$  of the DMM in the voltmeter setting?

$Y_1$

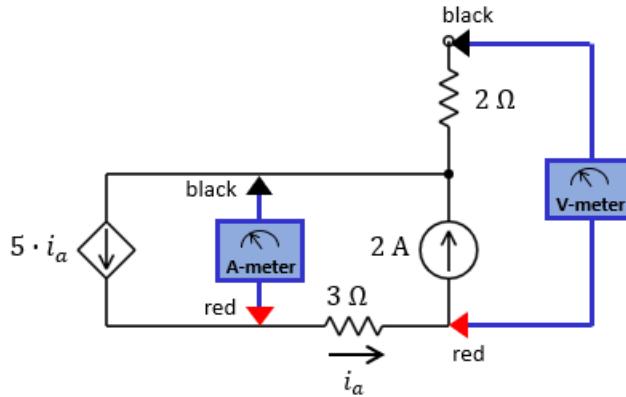

Next, we change the settings of the DMMs, such that the one that was in the voltmeter setting is now in the ammeter setting and vice versa.

(c) What is the reading  $X_2$  of the DMM that is now in the ammeter setting?

$X_2$

(d) What is the reading  $Y_2$  of the DMM that is now in the voltmeter setting?

$Y_2$



**PID**

- (2) (5 points) Consider the circuit below. The current source  $I_S$  changes as indicated in the graph. At time  $t = 3^-$ s (just before the current  $I_S$  changes), the system is not in steady state, but you are told that  $i_a = 9$  A.

(a) Find the current  $i_a$  at time  $t = 3^+$ s (i.e., right after the current  $I_S$  changes)

 $i_a(3^+s)$  

(b) Find the current  $i_a$  at time  $t = \infty$  s.

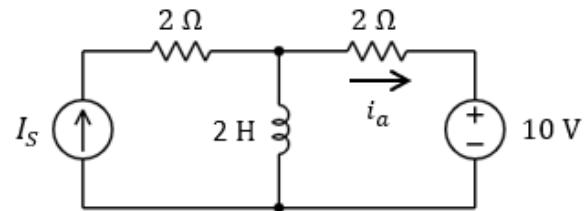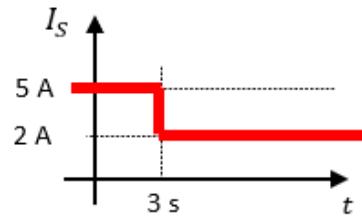 $i_a(\infty)$  

**PID**

(3) (8 points) Consider the circuit below. You are told that  $R_1 = 2 \Omega$  and  $k = 2 \frac{V}{A}$ .

(a) What is the power  $P_1$  received by resistor  $R_1$ ?


$P_1$

(b) What is the current  $i_a$ ? (Hint: consider using superposition)

$i_a$

(c) What is the power  $P_2$  supplied by the dependent voltage source?




$P_2$

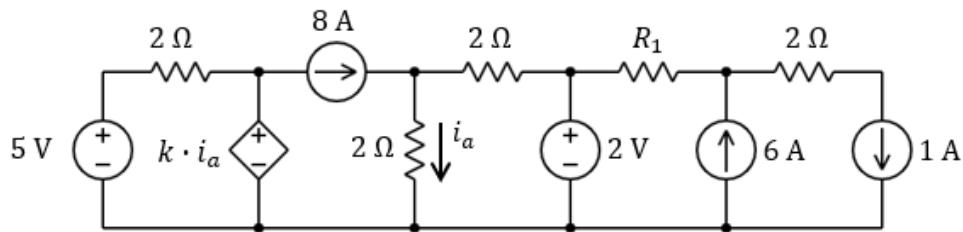

**PID**

**PID**

(4) (7 points)

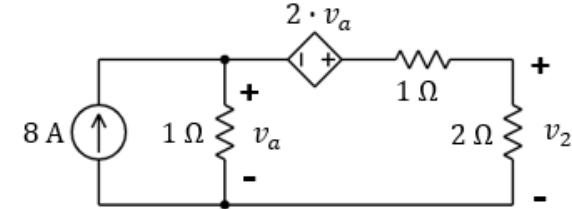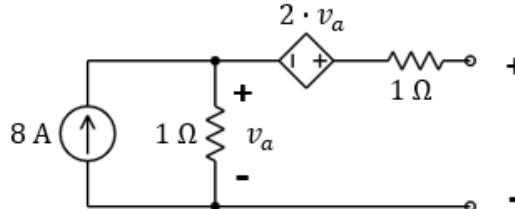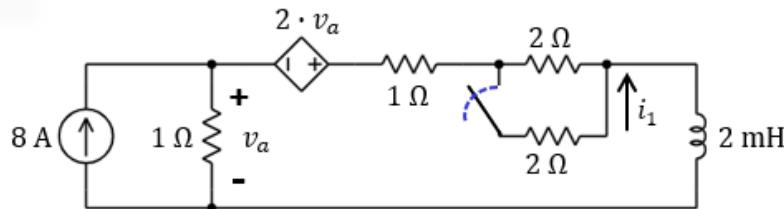(a) For the circuit below on the left, find the voltage  $v_1$ . $v_1$ (b) For the circuit below on the right, find the voltage  $v_2$ . $v_2$ (c) Consider the circuit below. For  $t < 4$  s, the switch is open, and the system has reached steady state. The switch closes at time  $t = 4$  s. Find the time constant  $\tau$  associated with  $i_1(t)$  for  $t > 4$  s. $\tau$ 

**PID**

- (5) (12 points) Consider the circuit below. For  $t < \frac{\pi}{40}$  s, both switches are in position 1 and the system has reached steady state. At time  $t = \frac{\pi}{40}$  s, both switches move from position 1 to position 2 simultaneously.

(a) Find the current  $i_a$  at time  $t = \frac{\pi}{40}^-$  s  
(i.e., immediately before the switches move).

$$i_a\left(\frac{\pi}{40}^-\right)$$

(b) Find the node voltage  $v_a$  at time  $t = \frac{\pi}{40}^-$  s.

$$v_a\left(\frac{\pi}{40}^-\right)$$

(c) Find the node voltage  $v_b$  at time  $t = \frac{\pi}{40}^-$  s.

$$v_b\left(\frac{\pi}{40}^-\right)$$

(d) Find the current  $i_a$  at time  $t = \frac{\pi}{40}^+$  s  
(i.e., immediately after the switches move).


$$i_a\left(\frac{\pi}{40}^+\right)$$

(e) Find the node voltage  $v_a$  at time  $t = \frac{\pi}{40}^+$  s.

$$v_a\left(\frac{\pi}{40}^+\right)$$

(f) Find the node voltage  $v_b$  at time  $t = \frac{\pi}{40}^+$  s.

$$v_b\left(\frac{\pi}{40}^+\right)$$


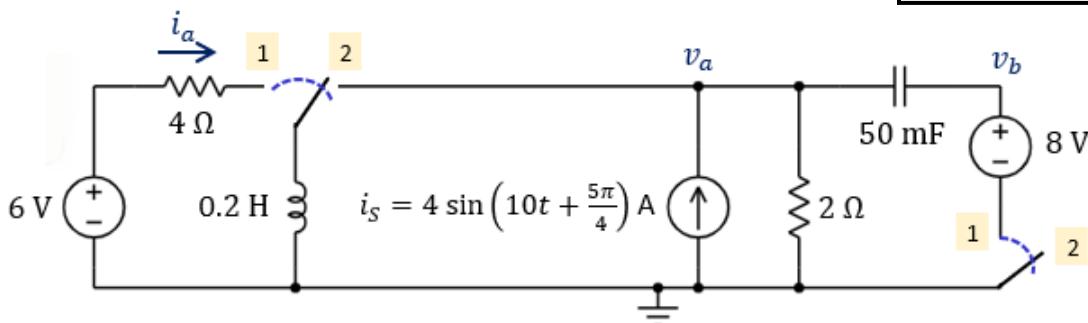


**PID**

**PID**

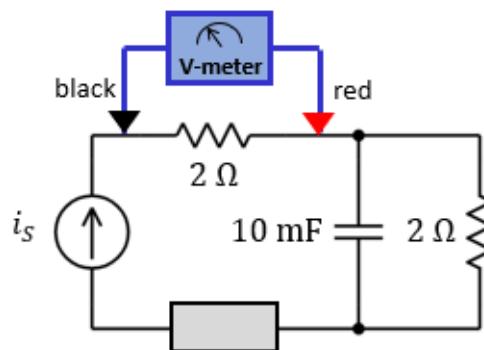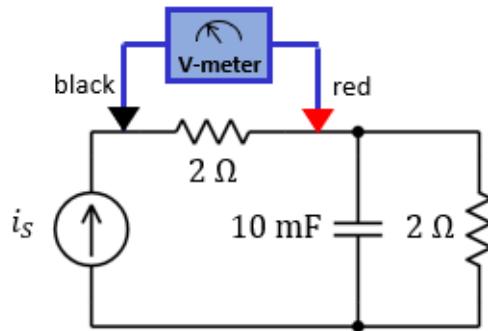(6) (8 points) The circuits below are in steady state.

- Find the complex power received by the capacitor, in the circuit on the left.
- What is the reading  $X$  of the voltmeter, in the circuit on the left?
- I add a new circuit element in series with the current source as illustrated below on the right. As a result, the reactive power supplied by the current source is reduced to zero. What type of element should this new element be and what is its value (i.e., what is its resistance, capacitance or inductance)?



$$i_s = 5 \cos\left(100t + \frac{\pi}{3}\right) \text{ A}$$

**PID**

**PID**

**PID**

**ECE35 Equation Sheet**

**Basics:**  $i \triangleq \frac{dq}{dt}$        $v_{ab} \triangleq \frac{dw}{dq}$        $R = \rho \frac{l}{A}$

**Capacitors:**  $C = \epsilon \cdot \frac{A}{d}$        $Q = C \cdot v$        $w_C = \frac{1}{2} C v^2$

**Inductors:**  $L = \mu \cdot \frac{N^2 A}{l}$        $B \sim i$        $w_L = \frac{1}{2} L i^2$

**AC power:**  $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$   
 $P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$        $Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i)$        $X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$

**Trigonometry:**  $\sin(-\alpha) = -\sin(\alpha)$        $\cos(-\alpha) = \cos(\alpha)$   
 $\sin(\pi - \alpha) = \sin(\alpha)$        $\cos(\pi - \alpha) = -\cos(\alpha)$   
 $\sin\left(\frac{\pi}{2} - \alpha\right) = \cos(\alpha)$        $\cos\left(\frac{\pi}{2} - \alpha\right) = \sin(\alpha)$   
 $\sin\left(\alpha - \frac{\pi}{2}\right) = -\cos(\alpha)$        $\cos\left(\alpha - \frac{\pi}{2}\right) = \sin(\alpha)$   
 $\sin(2\alpha) = 2 \sin(\alpha) \cos(\alpha)$        $\cos(2\alpha) = \cos^2(\alpha) - \sin^2(\alpha)$

$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$		$\alpha:$	$0$	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$
$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$							
$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$		$\sin(\alpha):$	$0$	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	$1$
$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$		$\tan(\alpha):$	$0$	$\frac{\sqrt{3}}{3}$	$1$	$\sqrt{3}$	$\infty$
$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$							