


First order circuits 001

Problem has been graded.

Given a voltage $v(t)$, find the current $i(t)$.

$$v(t) = A_1 + B_1 \cdot e^{-10t}$$

$$i(t) = A_2 + B_2 \cdot e^{-10t}$$

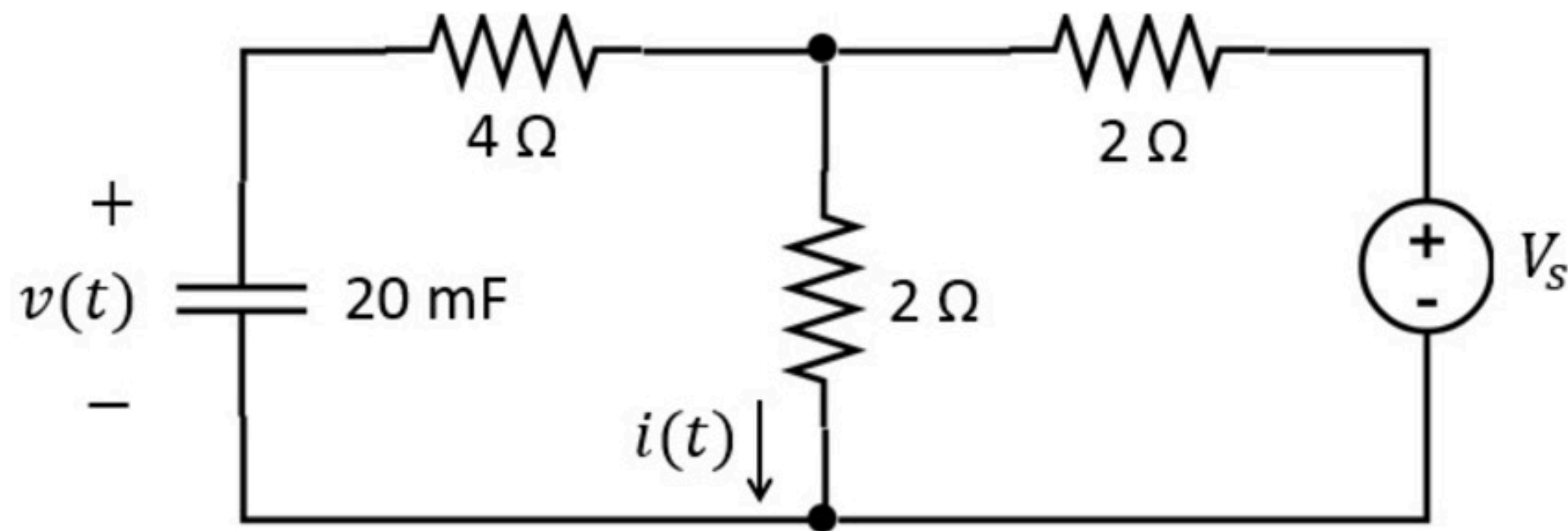

Given Variables:

A_1 : 10 V

B_1 : 10 V

V_s : 20 V

Calculate the following:

A_2 (A) :

5



B_2 (A) :

1



Given a voltage $v(t)$, find the current $i(t)$.


$$v(t) = A_1 + B_1 \cdot e^{-10t}$$

$$i(t) = A_2 + B_2 \cdot e^{-10t}$$

$$A_1 : 10 \text{ V}$$

$$B_1 : 10 \text{ V}$$

$$V_s : 20 \text{ V}$$

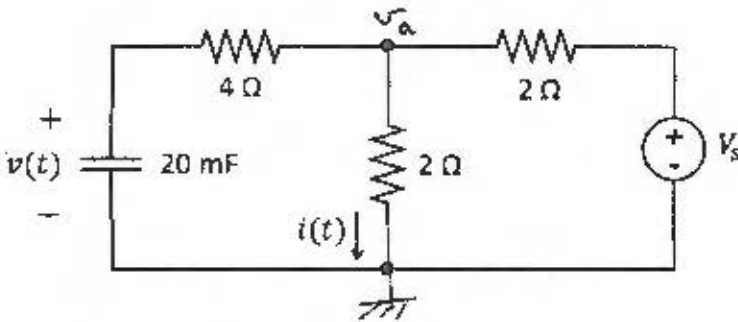

NODAL

$$\frac{v_a - v}{4} + \frac{v_a - V_s}{2} + \frac{v_a}{2} = 0$$

$$v_a - v + 2(v_a - V_s) + 2v_a = 0$$

$$5v_a = v + 2V_s$$

$$v_a = \frac{v}{5} + \frac{2V_s}{5}$$

$$i = \frac{v_a}{2} = \frac{v}{10} + \frac{V_s}{5} = 1 + e^{-10t} + 4$$


$$A_2 = 5 \text{ A}$$

$$B_2 = 1 \text{ A}$$

First order circuits 002

Unlimited Attempts.

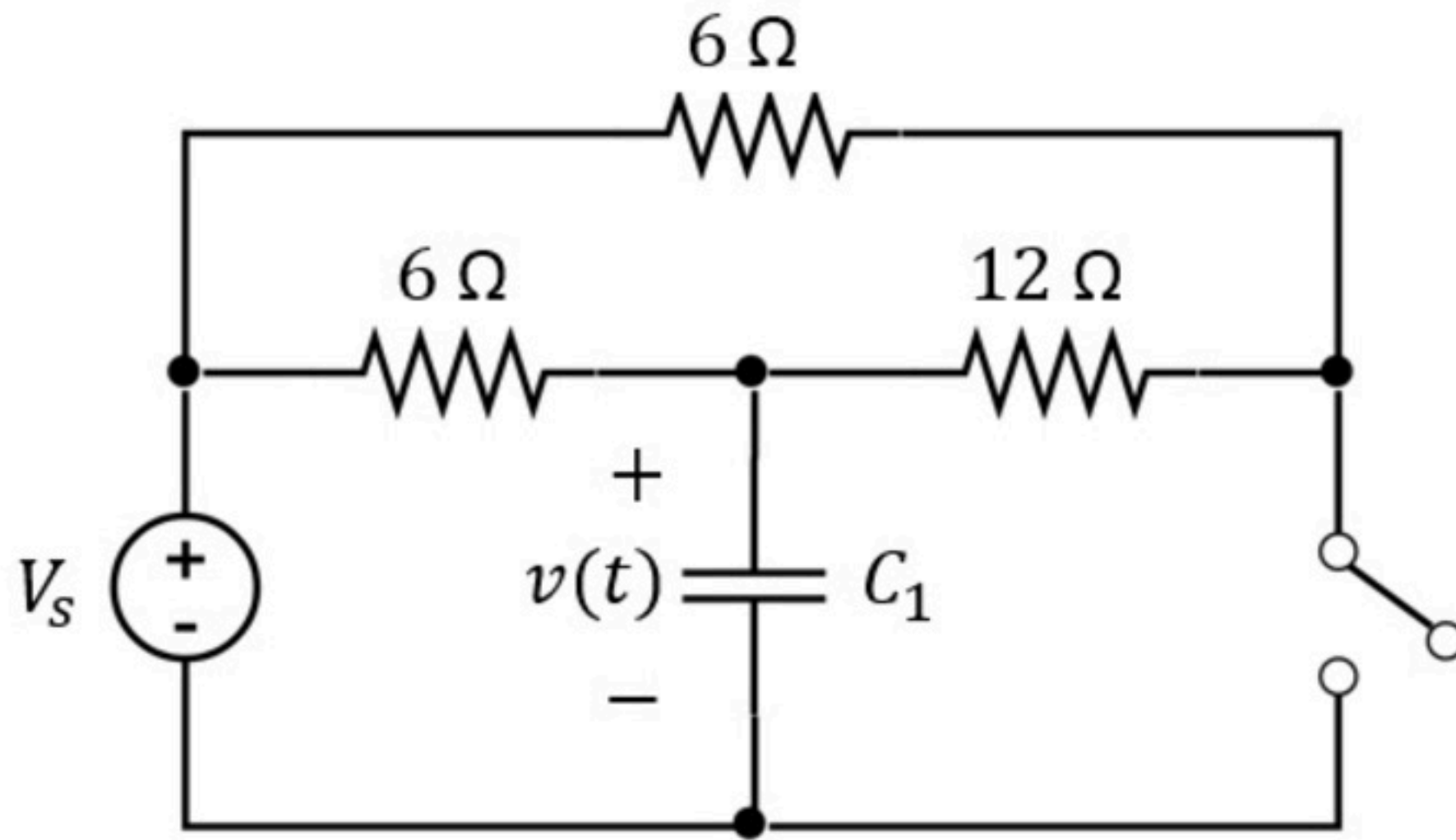- Find the time constant τ_1 and the steady state capacitor voltage $v_1 = v(\infty)$ when the switch is open.
- Find the time constant τ_2 and the steady state capacitor voltage $v_2 = v(\infty)$ when the switch is closed.



Given Variables:

V_s : 30 V

C_1 : 8 nF

Calculate the following:

τ_1 (ns) :

36



v_1 (V) :

30



τ_2 (ns) :

32



v_2 (V) :

20






Hint: The circuit is different in the two cases

- a) Find the time constant τ_1 and the steady state capacitor voltage $v_1 = v(\infty)$ when the switch is open.
- b) Find the time constant τ_2 and the steady state capacitor voltage $v_2 = v(\infty)$ when the switch is closed.


$V_s : 60 \text{ V}$

$C_1 : 6 \text{ nF}$

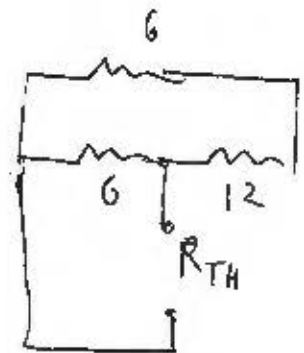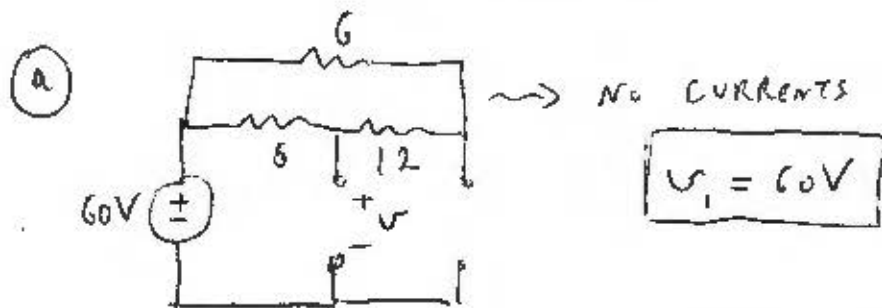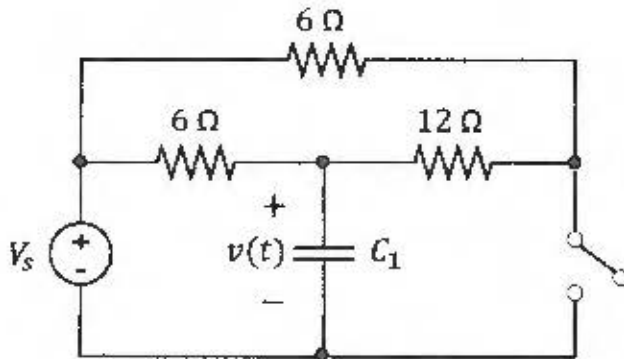



$$\tau_1 = R_{TH} \cdot C_1 \Rightarrow \tau_1 = 27 \text{ ns}$$
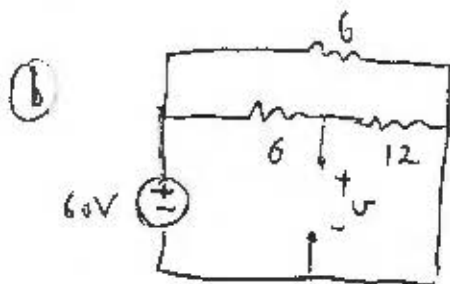
$$R_{TH} = 6 // 18 = \frac{9}{2} \Omega$$



$$v = 60 \cdot \frac{12}{6+12} = 40$$

$$v_2 = 40 \text{ V}$$

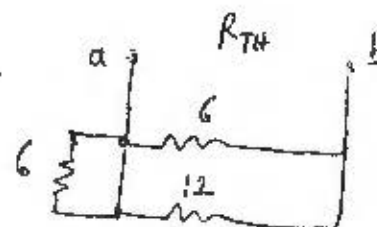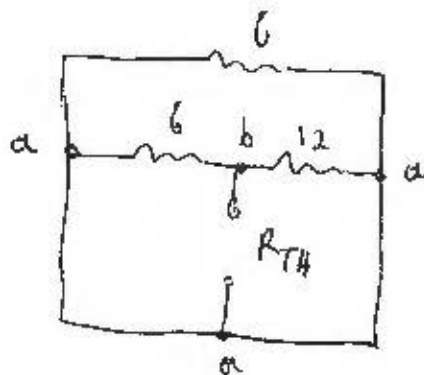

$$R_{TH} = 6 // 12 = 4 \Omega$$


$$\tau_2 = R_{TH} \cdot C_1 \Rightarrow \tau_2 = 24 \text{ ns}$$

First order circuits 003

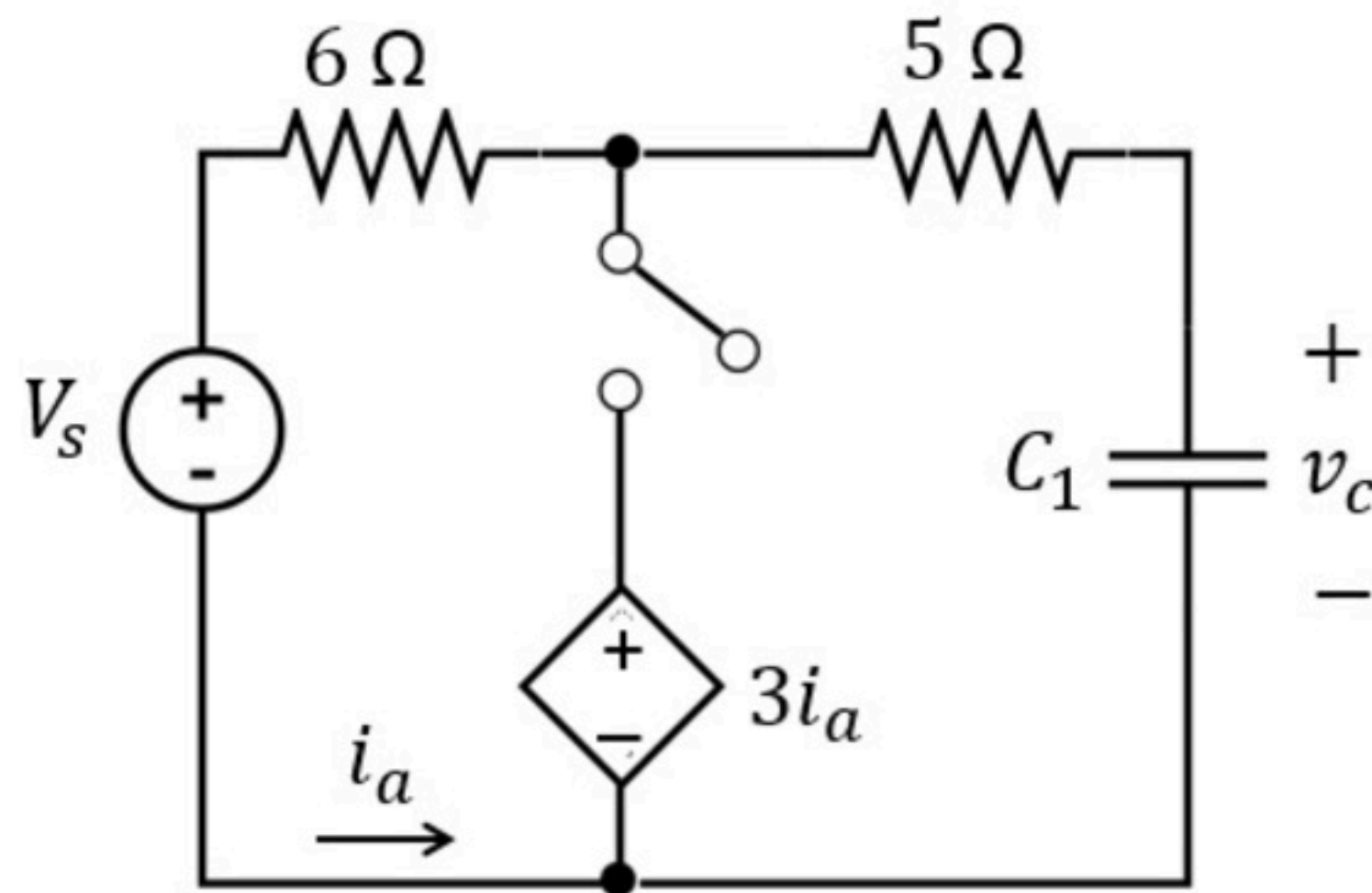Problem has been graded.

The switch has been open for a long time before it closes at time $t = 0$.

Find the capacitor voltage $v_c = A + B \cdot e^{-t/\tau}$ for $t > 0$.



Given Variables:

V_s : 15 V

C_1 : 0.1 nF

Calculate the following:

A (V) :

-15

✓

B (V) :

30

✓

τ (ns) :

0.5

✓


Hint: First find the capacitor voltage at $t = 0^-$. Note where A and B are.

The switch has been open for a long time before it closes at time $t = 0$.


Find the capacitor voltage $v_c = A + B \cdot e^{-t/\tau}$ for $t > 0$.

$V_s : 30 \text{ V}$

$C_1 : 0.2 \text{ nF}$

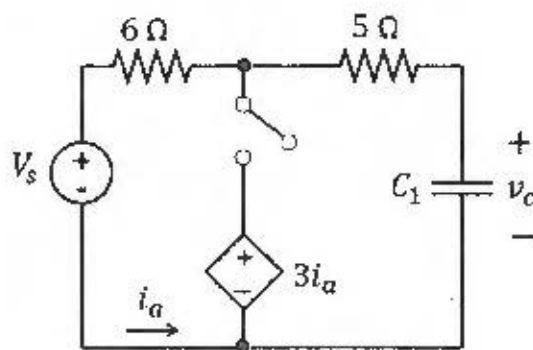

(a) $t = 0^-$

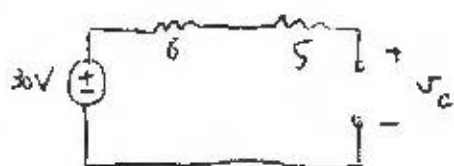


$$v_c(0^-) = 30 \text{ V}$$

\Downarrow

$$(b) v_c(0^+) = 30 \text{ V}$$

(c) $t = \infty$

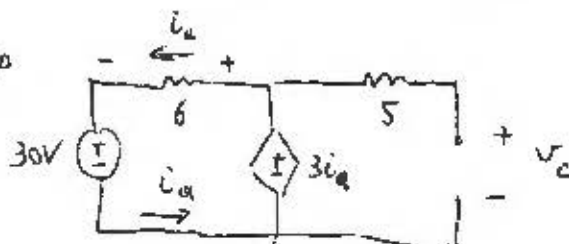


$$30 + 6i_a - 3i_a = 0$$

$$3i_a = -30$$

$$i_a = -10 \text{ A}$$

$$\Rightarrow v_c(\infty) = 3i_a = -30 \text{ V}$$


(d)

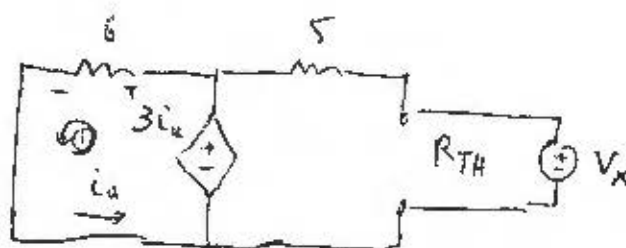

$$\text{KVL } \textcircled{1}: 3i_a - 6i_a = 0$$

$$\Rightarrow i_a = 0$$

\Rightarrow

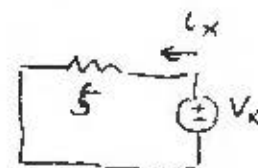

$$\frac{V_x}{5} = i_x \Rightarrow R_{TH} = 5 \Omega$$

$$\tau = RC = 1 \text{ ns}$$

$$A = v_c(\infty) \Rightarrow A = -30 \text{ V}$$

$$A + B = v_c(0^+) \Rightarrow B = 60 \text{ V}$$


First order circuits 004

Problem has been graded.

The switch closes at time $t = 0$.

Find the current i_L for $t > 0$:

$$i_L(t) = A \cdot e^{-t/\tau} + B$$

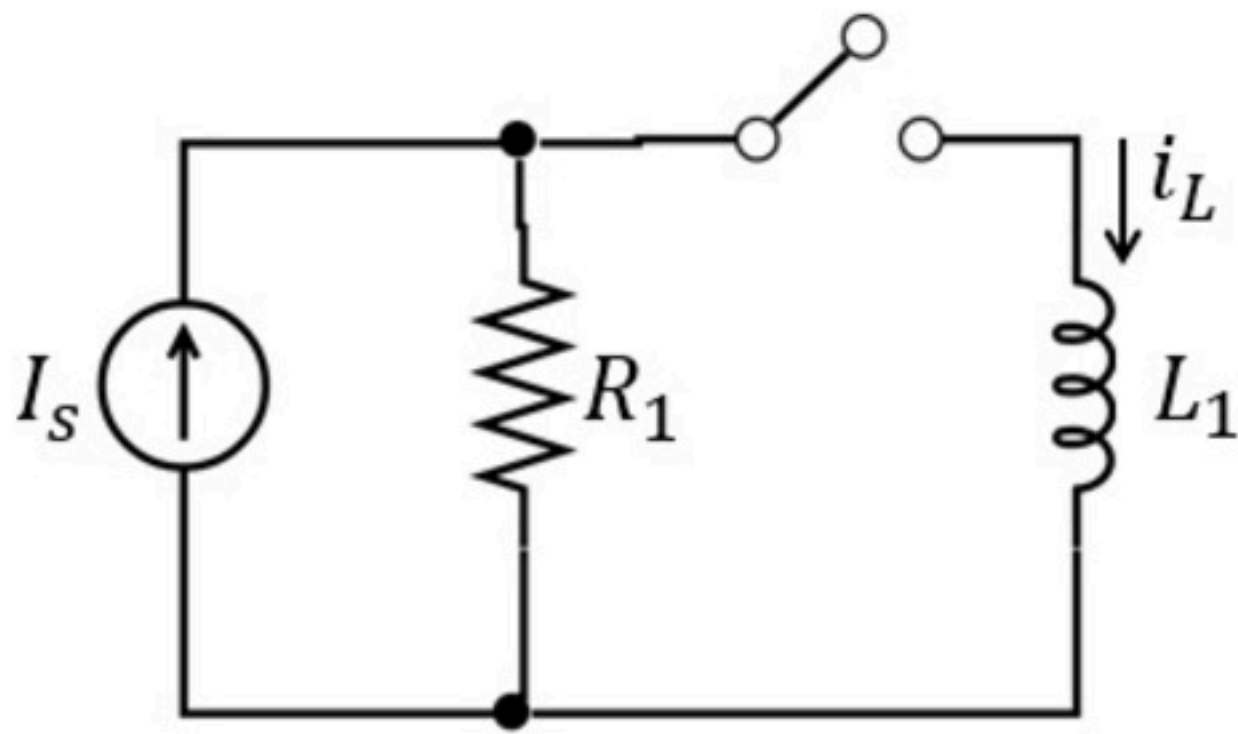

Given Variables:

I_S : 2 A

R_1 : 10 kohm

L_1 : 10 mH

Calculate the following:

A (A) :

-2



B (A) :

2



τ (ms) :

0.001



Hint: What is the current i_L for $t < 0$?

The switch closes at time $t = 0$.


Find the current i_L for $t > 0$:

$$i_L(t) = A \cdot e^{-t/\tau} + B$$

$I_s : 2 \text{ A}$

$R_1 : 3 \text{ kohm}$

$L_1 : 30 \text{ mH}$

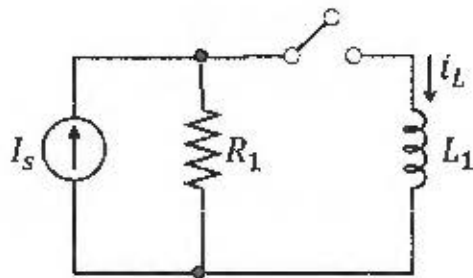


(a) $t = 0^- : i_L = 0$

(b) $t = 0^+ : i_L(0^+) = i_L(0^-) = 0 \text{ A}$

(c) $t = \infty :$



(d)

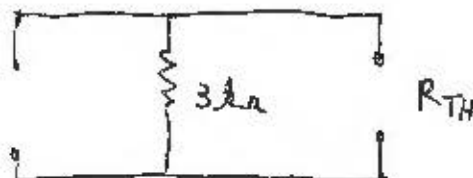

$$R_{TH} = 3 \text{ k}\Omega$$

$$\tau = \frac{L_1}{R_{TH}} = \frac{30 \cdot 10^{-3}}{3 \cdot 10^3} = 10 \cdot 10^{-6} \text{ s}$$

$$\tau = 0.01 \text{ ms}$$

$$B = i_L(\infty) = 2 \text{ A} \Rightarrow B = 2 \text{ A}$$

$$A + B = i_L(0^+) = 0 \text{ A} \Rightarrow A = -2 \text{ A}$$


$$i_L(t) = 2 - 2 e^{-\frac{t}{0.01 \text{ ms}}} \text{ A}$$

$$i_L(t) = 2 \left(1 - e^{-\frac{t}{0.01 \text{ ms}}} \right) \text{ A}$$

First order circuits 005

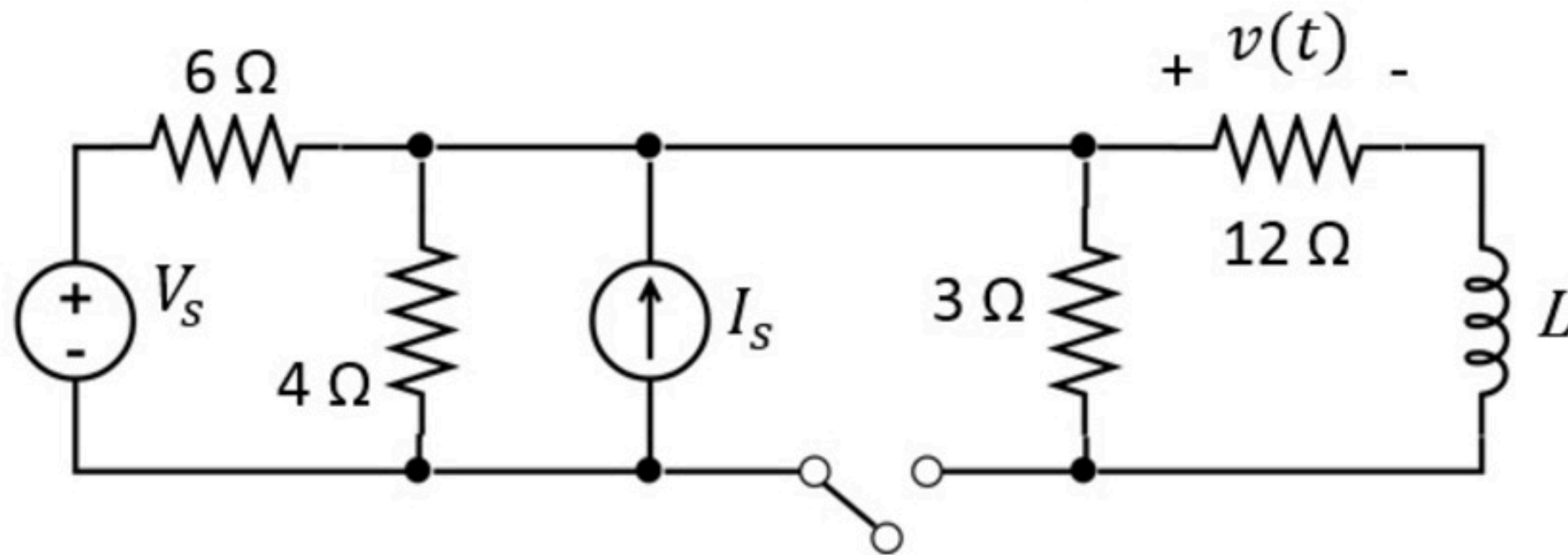Problem has been graded.

The switch has been closed for a long time before it opens at $t = 0$. After the switch opens, find the resistor voltage $v(t) = A \cdot e^{-t/\tau} + B$.



Given Variables:

V_s : 28 V

I_s : 2 A

L : 1.5 mH

Calculate the following:

A (V) :

8

✓

B (V) :

0

✓

τ (ms) :

0.1

✓



Hint: What is the current i_L for $t < 0$?

The switch has been closed for a long time before it opens at $t = 0$. After the switch opens, find the resistor voltage $v(t) = A \cdot e^{-t/\tau} + B$.

$$V_s : 12 \text{ V}$$

$$I_s : 8 \text{ A}$$

$$L : 15 \text{ mH}$$

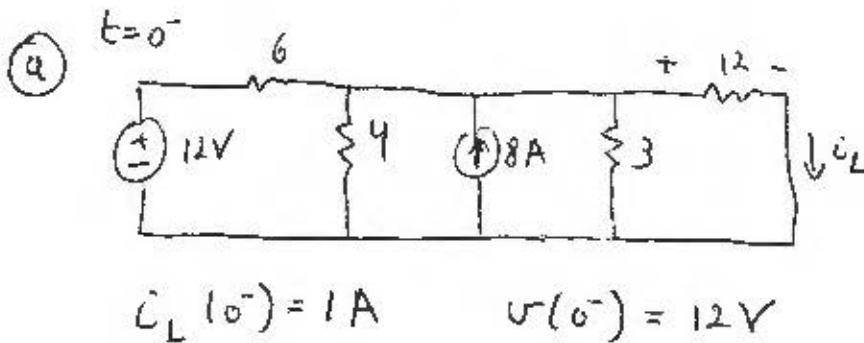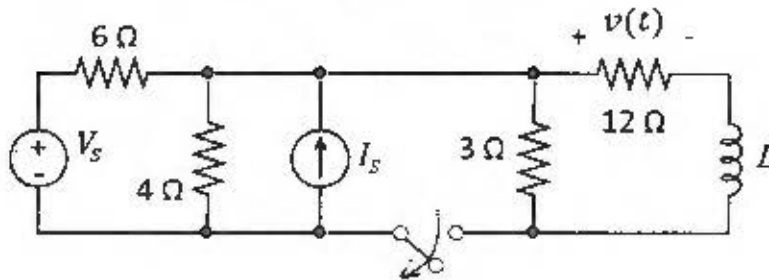


SUPERPOSITION

$$i_{L1} = \frac{12}{6 + 4 \parallel 3 \parallel 12} \cdot \frac{4 \parallel 3}{4 \parallel 3 + 12} = \frac{1}{5} \text{ A}$$


$$i_{L2} = \frac{6 \parallel 4 \parallel 3}{6 \parallel 4 \parallel 3 + 12} \cdot 8 = \frac{4}{5} \text{ A}$$

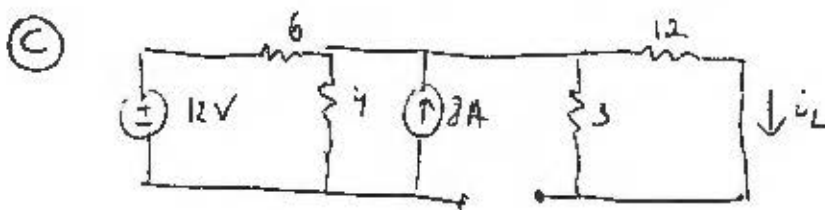b) $t = 0^+ : i_L(0^+) = 1 \text{ A} \Rightarrow v(0^+) = 12 \text{ V}$



$$i_L(\infty) = 0 \text{ A}$$

$$v(\infty) = 0 \text{ V}$$

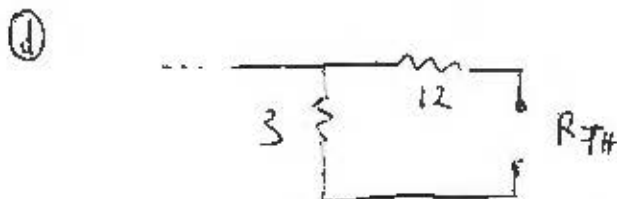

$$R_{TH} = 15 \Omega$$

$$\tau = \frac{L}{R_{TH}} = \frac{15 \cdot 10^{-3}}{15} = 10^{-3} \text{ s}$$

$$\tau = 1 \text{ ms}$$

$$B = v(\infty) \Rightarrow B = 0 \text{ V}$$

$$A + B = v(0^+) \Rightarrow A = 12 \text{ V}$$


First order circuits 006

Problem has been graded.

When $t < 0$, $i_s = I_0$

When $t > 0$, $i_s = I_1$

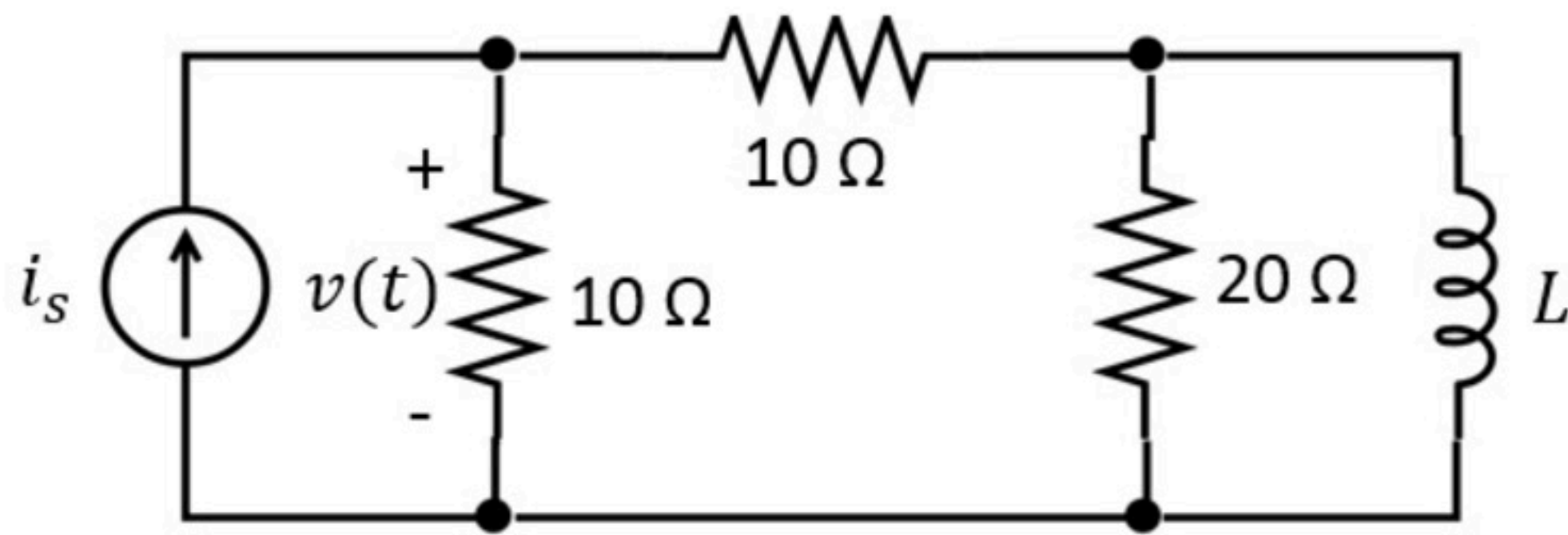Find $v(t) = A \cdot e^{-t/\tau} + B$ for $t > 0$



Given Variables:

$I_0 : 2\text{ A}$

$I_1 : 10\text{ A}$

$L : 0.25\ \mu\text{H}$

Calculate the following:

A (V) :

20

✓

B (V) :

50

✓

τ (ns) :

25

✓

Hint: What is the inductor current for $t < 0$?

When $t < 0$, $i_s = I_0$


$$I_0 = 4 \text{ A}$$

When $t > 0$, $i_s = I_1$


$$I_1 = 6 \text{ A}$$

Find $v(t) = A \cdot e^{-t/\tau} + B$ for $t > 0$

$$L = 0.25 \text{ uH}$$

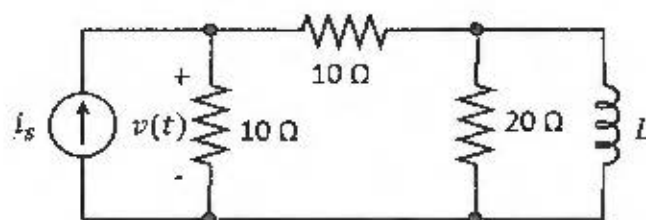


(a) $t = 0^-$

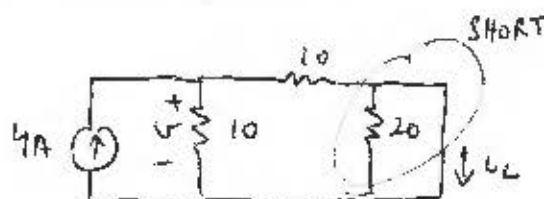

$$v(0^-) = (4 \text{ A}) \cdot (10 // 10) = 20 \text{ V}$$

$$i_L(0^-) = (4 \text{ A}) \cdot \frac{10}{10 + 10} = 2 \text{ A}$$

(b) $t = 0^+$

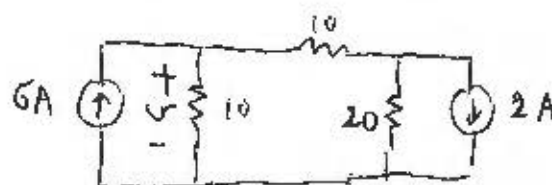

$$i_L(0^+) = 2 \text{ A}$$


SUPERPOSITION

$$v_1 = 6 \cdot (10 // 30) = 6 \cdot \frac{30}{4} = 45 \text{ V}$$

$$v_2 = (-2) \cdot (20 // 20) \cdot \frac{1}{2} = -10 \text{ V}$$


$$v(0^+) = v_1 + v_2 = 35 \text{ V}$$

(c) $t = \infty$

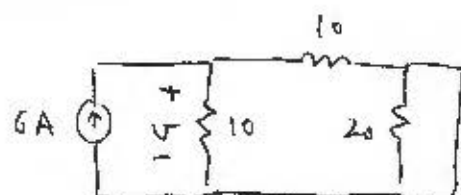

$$v(\infty) = 6 \cdot (10 // 10) = 30 \text{ V}$$

(d)

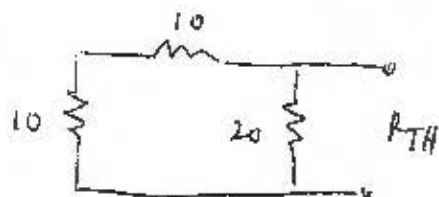

$$R_{TH} = 20 // 20 = 10 \Omega$$

$$\tau = \frac{L}{R_{TH}} = \frac{0.25 \cdot 10^{-6}}{10} = 25 \cdot 10^{-9}$$

$$\tau = 25 \text{ ns}$$

$$B = v(\infty) \Rightarrow$$

$$B = 30 \text{ V}$$

$$A + B = v(0^+) \Rightarrow$$

$$A = 5 \text{ V}$$


First order circuits 007

Problem has been graded.

The switch closes at time $t = 0$ and we measure

$$v(t) = 24 - 12e^{-t/2\mu s} \text{ V} \quad \text{for } t > 0$$

Find the values of R_1 , R_2 , and L_1 .

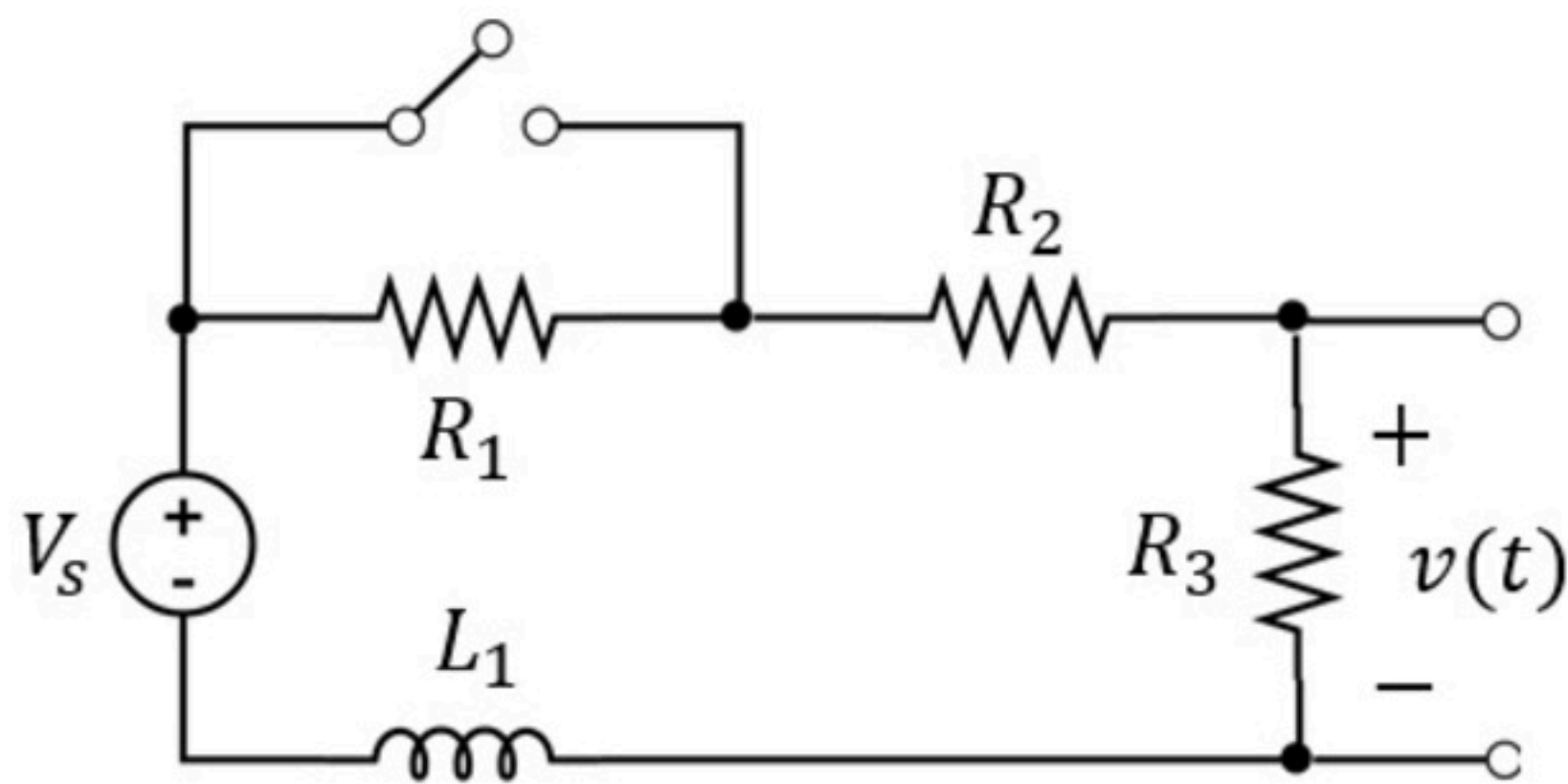

Given Variables:

V_s : 48 V

R_3 : 12 kohm

Calculate the following:

R_1 (ohm) :

24000



R_2 (ohm) :

12000



L_1 (H) :

0.048



Hint: Consider $v(\infty)$ first. Mind the units.


The switch closes at time $t = 0$ and we measure

$$v(t) = 24 - 12e^{-t/2\mu s} \text{ V for } t > 0$$

Find the values of R_1 , R_2 , and L_1 .


$$V_s : 36 \text{ V}$$

$$R_3 : 2 \text{ kohm}$$

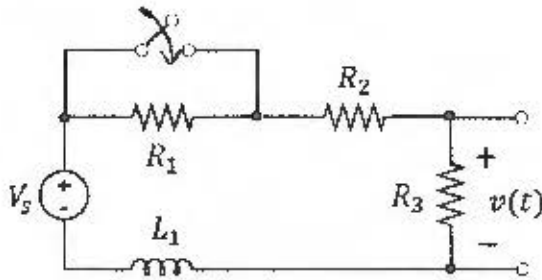

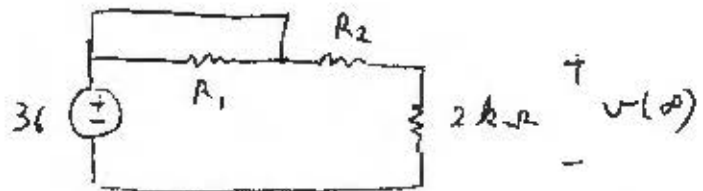
a) $t = \infty : v(\infty) = 24 \text{ V}$

$$v(\infty) = 36 \cdot \frac{2k}{2k + R_2}$$



$$\Rightarrow 24R_2 = 36 \cdot 2k - 24 \cdot 2k \Rightarrow R_2 = 1k\Omega \Rightarrow \boxed{R_2 = 1000\Omega}$$

b)

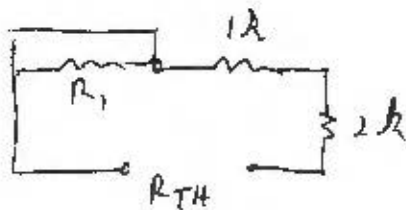


$$R_{TH} = 3k\Omega$$

$$\tau = 2 \cdot 10^{-6} \text{ s} = \frac{L_1}{R_{TH}}$$

$$\Rightarrow L_1 = \tau \cdot R_{TH} = 2 \cdot 10^{-6} \cdot 3 \cdot 10^3 = 6 \cdot 10^{-3}$$

$$\boxed{L_1 = 0.006 \text{ H}}$$


c) $t = 0^+ : v(0^+) = 12 \text{ V}$

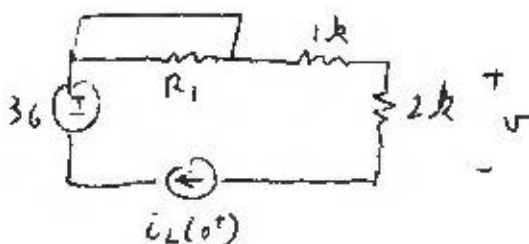

$$v(0^+) = i_L(0^+) \cdot 2k$$

$$\Rightarrow i_L(0^+) = \frac{12}{2k} = 6 \text{ mA}$$

d) $t = 0^- :$

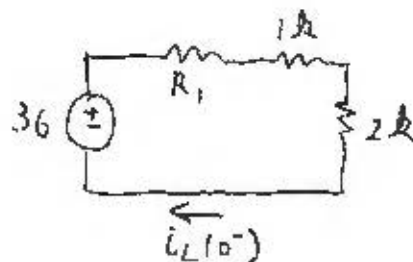

$$i_L(0^-) = i_L(0^+) = 6 \cdot 10^{-3}$$

$$= \frac{36}{R_1 + 1k + 2k}$$

$$R_1 = \frac{36}{6 \cdot 10^{-3}} - 1k - 2k \quad R_1 = 3k$$

$$\boxed{R_1 = 3000\Omega}$$

First order circuits 008


Unlimited Attempts.

When $t < 0$, $v_s = V_0$

When $t > 0$, $v_s = V_1$

Find $i(t) = A_1 + B_1 \cdot e^{-t/\tau_1}$ for $t > 0$

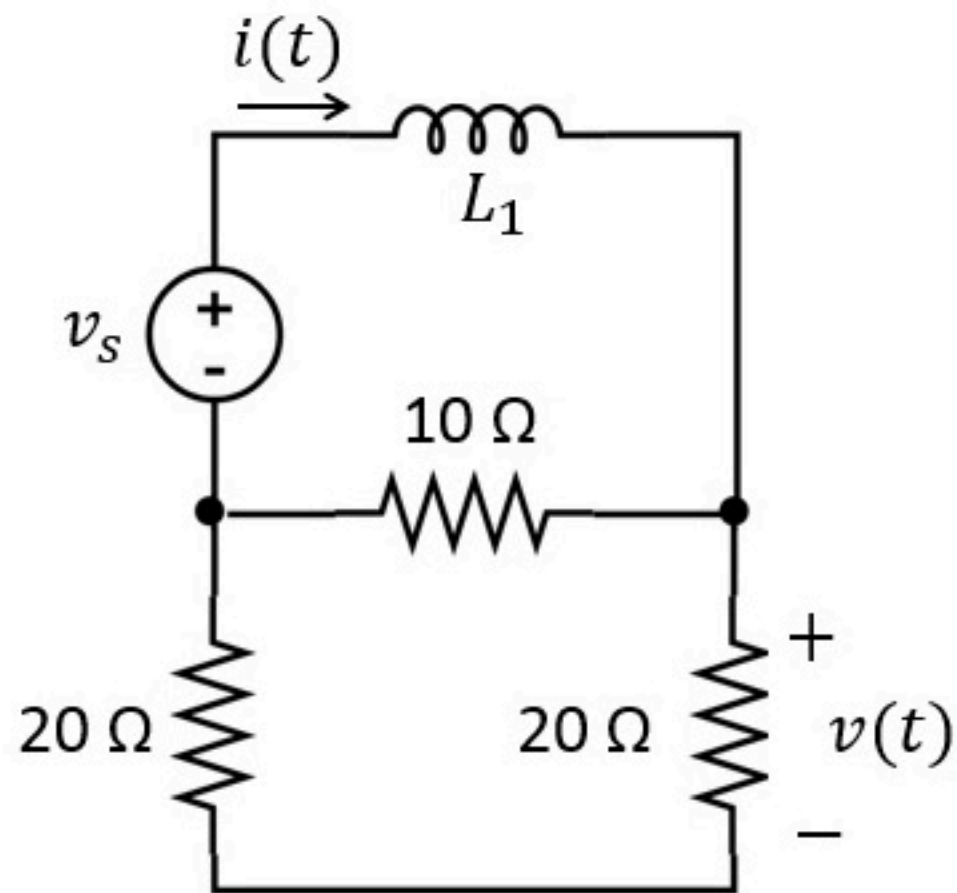and $v(t) = A_2 + B_2 \cdot e^{-t/\tau_2}$ for $t > 0$



Given Variables:

$V_0 : 24\text{ V}$

$V_1 : 32\text{ V}$

$L_1 : 4\text{ mH}$

Calculate the following:

$A_1\text{ (A)} :$

4

✓

$B_1\text{ (A)} :$

-1

✓

$\tau_1\text{ (ms)} :$

0.5

✓

$A_2\text{ (V)} :$

16

✓

$B_2\text{ (V)} :$

-4

✓

$\tau_2\text{ (ms)} :$

0.5

✓

Hint: What is the current i_L for $t < 0$? Note where A and B are.

When $t < 0$, $v_s = V_0$

When $t > 0$, $v_s = V_1$


Find $i(t) = A_1 + B_1 \cdot e^{-t/\tau_1}$ for $t > 0$

and $v(t) = A_2 + B_2 \cdot e^{-t/\tau_2}$ for $t > 0$


$V_0 = 40 \text{ V}$

$V_1 = 64 \text{ V}$

$L_1 = 2 \text{ mH}$

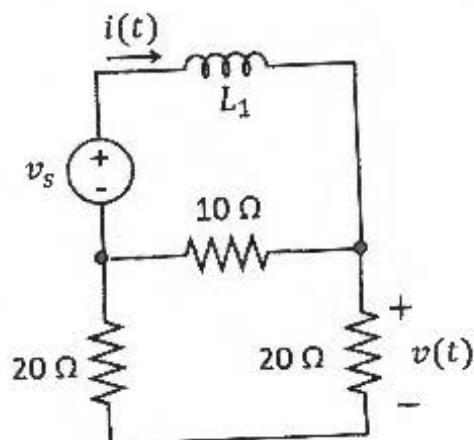


(a) $t = 0^-$

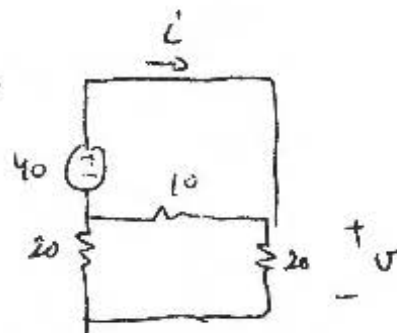

$$i(0^-) = \frac{40}{10 \parallel 20} = \frac{40}{8} = 5 \text{ A}$$

$$v(0^-) = 40 \cdot \frac{20}{20+20} = 20 \text{ V}$$


(b) $t = 0^+$

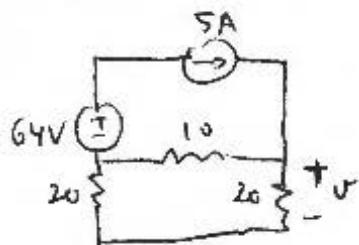

$$i(0^+) = 5 \text{ A}$$

$$v(0^+) = (5 \text{ A}) \cdot (10 \parallel 20) \cdot \frac{20}{20+20} = 20 \text{ V}$$


(c) $t = \infty$

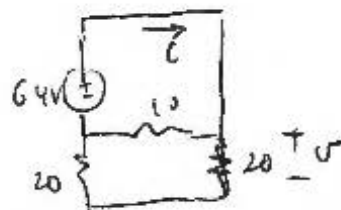

$$i(\infty) = \frac{64}{10 \parallel 20} = 8 \text{ A}$$

$$v(\infty) = 64 \cdot \frac{20}{20+20} = 32 \text{ V}$$

(d)

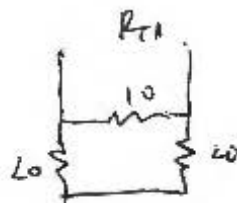

$$R_{TH} = 10 \parallel 20 = 8 \Omega$$

$$\tau = \frac{L_1}{R_{TH}} = \frac{2 \cdot 10^{-3}}{8} = 0.25 \cdot 10^{-3}$$

$$A_1 = i(\infty) \Rightarrow \boxed{A_1 = 8 \text{ A}}$$

$$A_2 = v(\infty) \Rightarrow \boxed{A_2 = 32 \text{ V}}$$

$$B_1 + A_1 = i(0^+) \Rightarrow \boxed{B_1 = -3 \text{ A}}$$

$$B_2 + A_2 = v(0^+) \Rightarrow \boxed{B_2 = -12 \text{ V}}$$

$$\boxed{\tau_1 = \tau_2 = 0.25 \text{ ms}}$$


First order circuits 009

Problem has been graded.

For $t < 0$, the switch has been in position A for a long time. At time $t = 0$, it moves from A to B .

Find the time t_1 it takes to reduce the capacitor voltage to 37% of its initial voltage ($\frac{1}{e} \approx .37$).

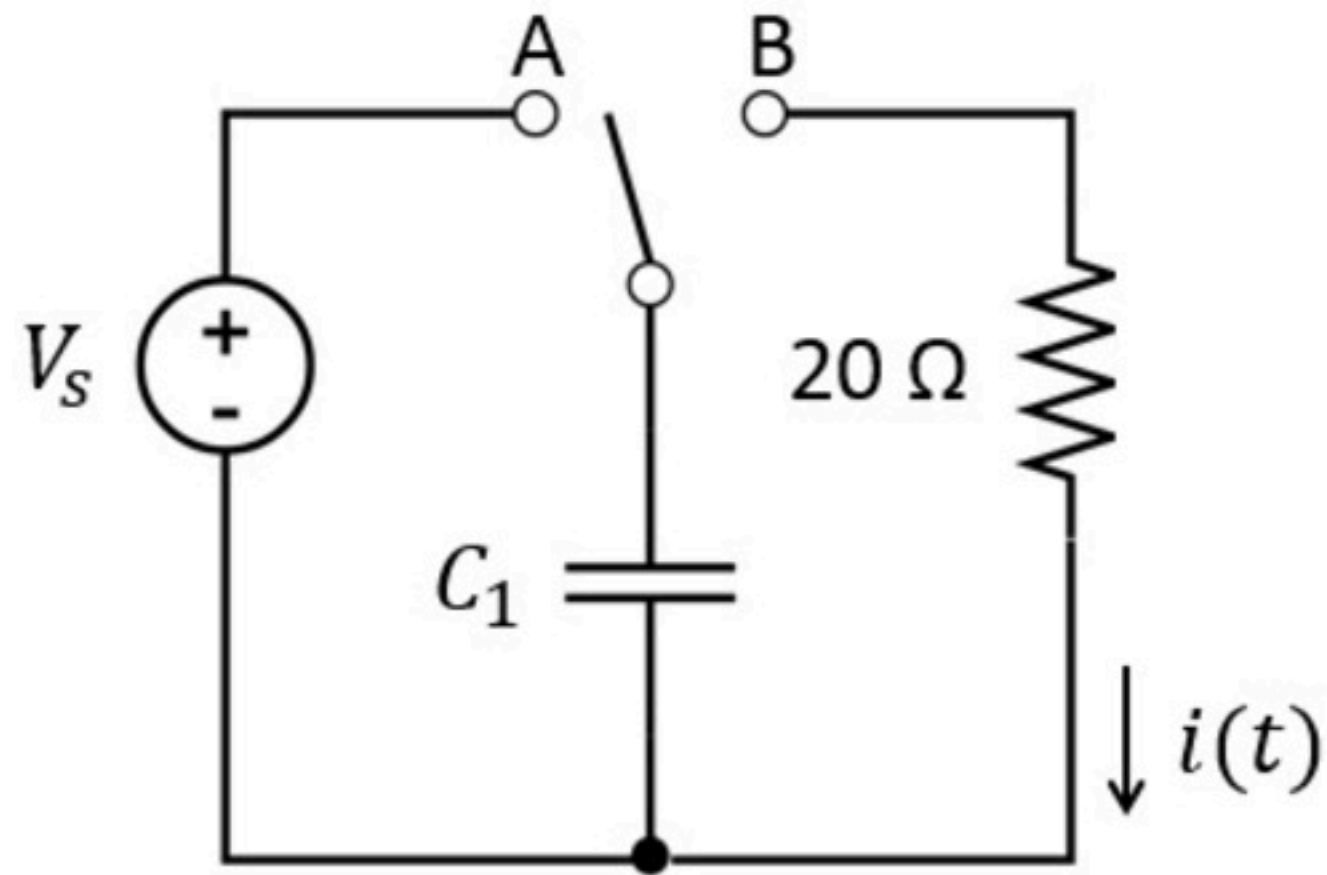What is the total energy E received by the resistor from the moment the switch is flipped until the capacitor is completely discharged?



Given Variables:

$V_s : 12\text{ V}$

$C_1 : 2\ \mu\text{F}$

Calculate the following:

$t_1\text{ (ms)} :$

0.04

✓

$E\text{ (mJ)} :$

0.144

✓

Hint: To calculate E , consider where the energy is coming from. Verify by integrating the $P(t)$.


For $t < 0$, the switch has been in position A for a long time. At time $t = 0$, it moves from A to B.

$$V_s : 2 \text{ V}$$

$$C_1 : 2 \text{ }\mu\text{F}$$

Find the time t_1 it takes to reduce the capacitor voltage to 37% of its initial voltage ($\frac{1}{e} \approx .37$).

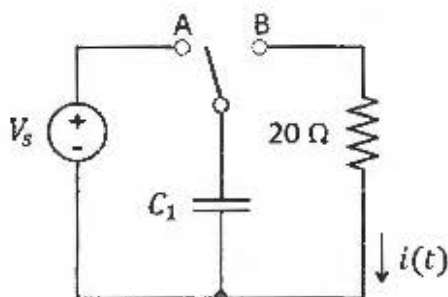What is the total energy E received by the resistor from the moment the switch is flipped until the capacitor is completely discharged?



1

(a) $t = 0^-$: $V_C(0^-) = 2 \text{ V}$

(b) $t = 0^+$: $V_C(0^+) = 2 \text{ V}$

(c) $t = \infty$: $V_C(\infty) = 0 \text{ V}$

(d) $R_{TH} = 20 \text{ }\Omega$

$$\tau = R_{TH} \cdot C = 40 \text{ }\mu\text{s}$$

$$\Rightarrow V_C(t) = 2 e^{-\frac{t}{\tau}}$$

$$V_C(t_1) = \frac{1}{e} \cdot V_C(0^+) = \frac{2}{e}$$

$$\Rightarrow 2 e^{-\frac{t_1}{\tau}} = 2 e^{-1} \Rightarrow \frac{t_1}{\tau} = 1 \Rightarrow t_1 = \tau = 40 \text{ }\mu\text{s}$$

$$t_1 = 0.04 \text{ ms}$$

2 $E_{rec.} = E_{supplied} \Rightarrow$ coming from capacitor

$$E = \frac{1}{2} C V^2 = \frac{1}{2} 2 \cdot 10^{-6} 2^2 = 4 \text{ }\mu\text{J}$$

$$E = 0.004 \text{ mJ}$$

OR $i(t) = A e^{-\frac{t}{\tau}} + B = 0.1 e^{-\frac{t}{\tau}}$

$$i(0^+) = \frac{2 \text{ V}}{20 \text{ }\Omega} = 0.1 \text{ A}$$

$$i(\infty) = 0$$

$$\begin{aligned} E &= \int P = \int_0^{\infty} i^2 R = 20 \cdot (0.1)^2 \int_0^{\infty} e^{-\frac{2t}{\tau}} dt \\ &= -0.2 \cdot \frac{\tau}{2} e^{-\frac{2t}{\tau}} \Big|_0^{\infty} \\ &= 0.1 \tau \Rightarrow E = 4 \text{ }\mu\text{J} \end{aligned}$$


PP First order circuits 011

Unlimited Attempts.

The voltage source behaves as shown (and assume it has been zero for a long time for $t < 0$).

Find $v_1(t) = D$ for $t = 0^-$
 $= A_1 \cdot e^{-t/\tau_1} + B_1$ for $0 < t < 2$ s
 $= A_2 \cdot e^{-(t-2)/\tau_2} + B_2$ for $2 \leq t$

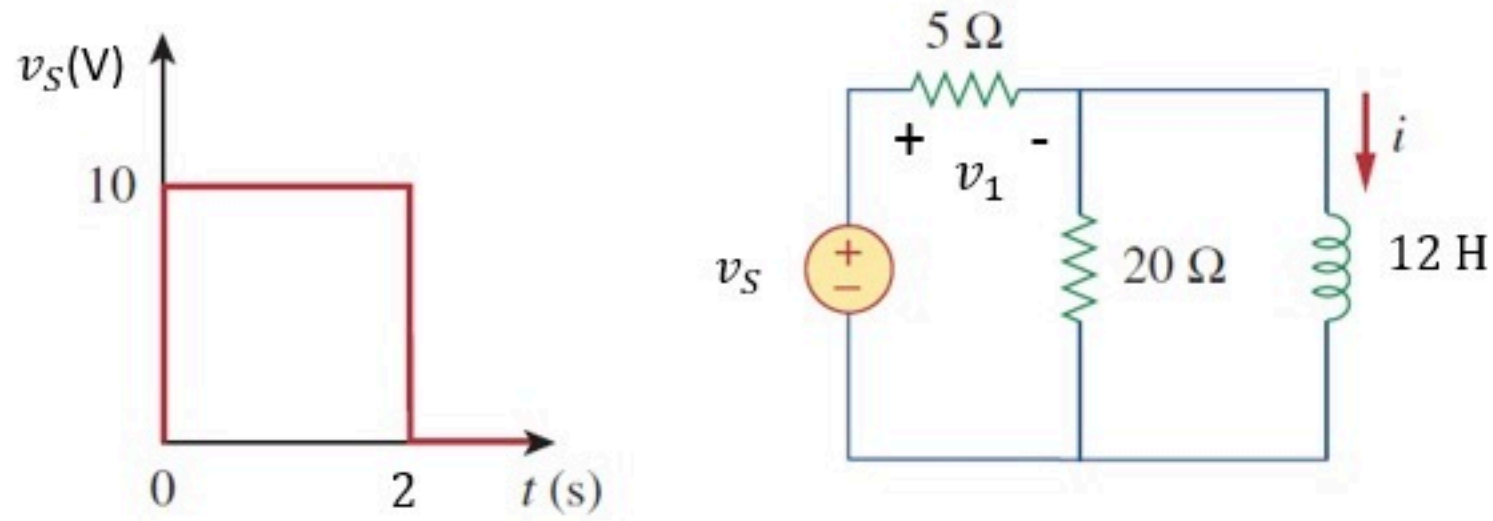Note, for your calculations, use: $e^{-1/1.5} \approx 0.5$



Given Variables:

...

Calculate the following:

D (V) :

0

✓

A1 (V) :

-8

✓

B1 (V) :

10

✓

tau1 (s) :

3

✓

A2 (V) :

4

✓

B2 (V) :

0


✓

tau2 (s) :

3


✓

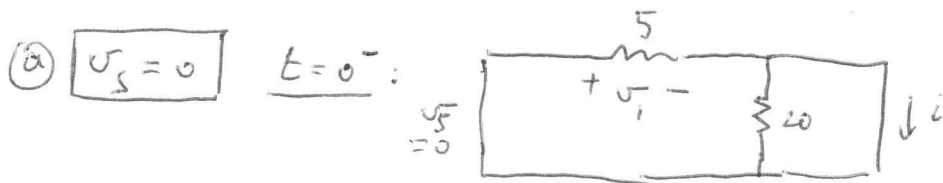Hint: Find the result of the first transition first.




$$V_1(0^-) = 0V$$

$$i(0^-) = 0A \quad \boxed{D = 0V}$$

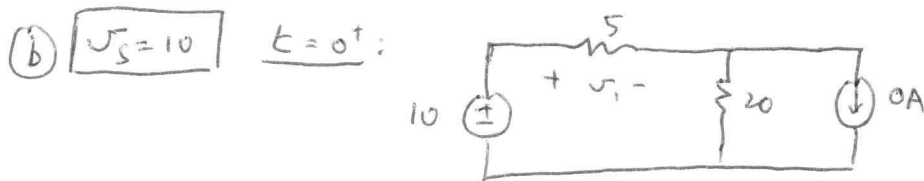

$$i(0^+) = 0A \rightarrow \text{open}$$
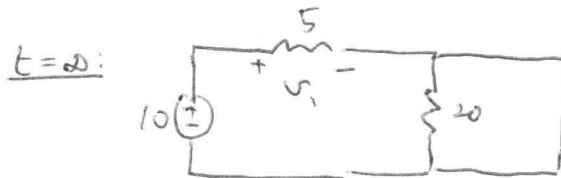
$$V_1(0^+) = \frac{10 \cdot 5}{5+20} = 2V$$



$$i(\infty) = \frac{10}{5} = 2A$$

$$V_1(\infty) = 10V$$

R_{TH} : $R_{TH} = 5 \parallel 20 = 4\Omega \Rightarrow \tau = \frac{L}{R} = \frac{12}{4} = 3s$

$$V_1(t) = -8e^{-\frac{t}{3}} + 10, \quad 0 < t < 2$$


$$i(t) = -2e^{-\frac{t}{3}} + 2, \quad 0 < t < 2$$

$$\boxed{A_1 = -8V}$$

$$\boxed{B_1 = 10V}$$


$$\boxed{\tau_1 = 3s}$$

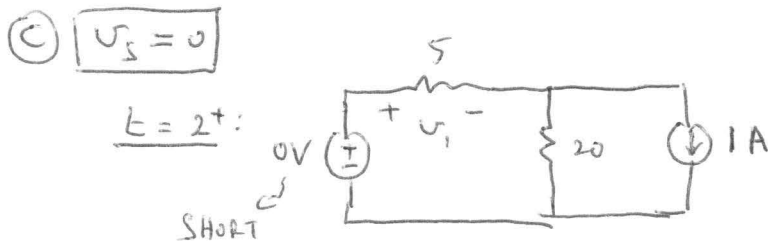$t = 2^-$: $i(2^-) = -2e^{-\frac{2}{3}} + 2 = -2e^{-\frac{1}{1.5}} + 2 = -2 \cdot \frac{1}{2} + 2 = 1A$



$$i(2^+) = i(2^-) = 1A$$
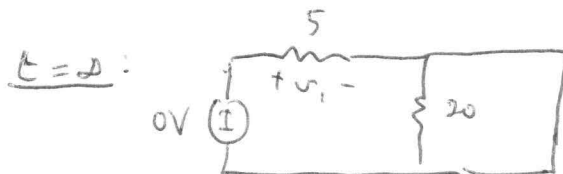
$$V_1 = 1 \cdot (5 \parallel 20) = 1 \cdot 4 = 4V$$



$$i(\infty) = 0$$

$$V_1(\infty) = 0V$$

~~RECALCULATE~~
 R_{TH} : SAME AS BEFORE $\Rightarrow \tau = 3s$

$$V_1(t) = 4e^{-\frac{t}{3}} + 0$$

$$\boxed{A_2 = 4V}$$

$$\boxed{B_2 = 0V}$$

$$\boxed{\tau_2 = 3s}$$

Second order circuits 001

Problem has been graded.


The switch opens at time $t = 2$ s. Before the switch opens, the system has reached steady state.

Find these voltages and currents (i.e., just before the switch opens):

$$i_{L1} = i_L(2^-) \quad v_{L1} = v_L(2^-) \quad i_{C1} = i_C(2^-) \quad v_{C1} = v_C(2^-)$$

Find these voltages and currents (i.e., just after the switch opens):
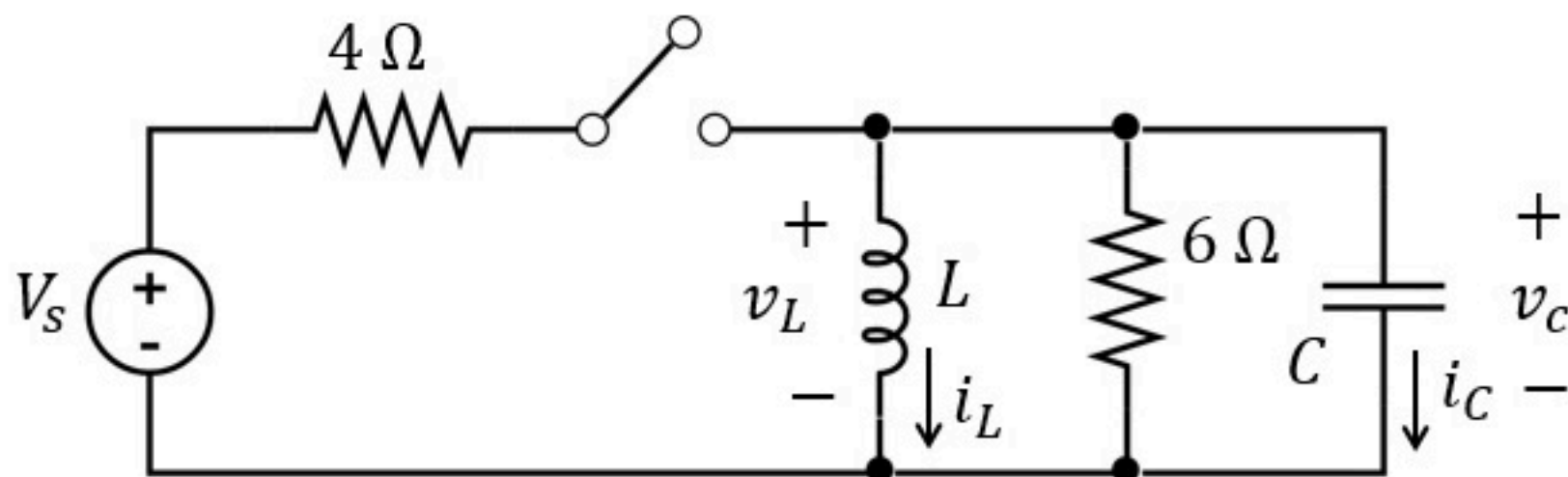
$$i_{L2} = i_L(2^+) \quad v_{L2} = v_L(2^+) \quad i_{C2} = i_C(2^+) \quad v_{C2} = v_C(2^+)$$



Given Variables:

V_s : 8 V

C : 2 nF

L : 2 mH

Calculate the following:

i_{L1} (A) :

2

✓

v_{L1} (V) :

0

✓

i_{C1} (A) :

0

✓

v_{C1} (V) :

0

✓

i_{L2} (A) :

2

✓

v_{L2} (V) :

0

✓

i_{C2} (A) :

-2

✓

v_{C2} (V) :

0

✓

Hint: In steady state, the capacitor and inductor behave as an open and short respectively.

The switch opens at time $t = 2$ s. Before the switch opens, the system has reached steady state.

$$V_s : 20 \text{ V}$$

Find these voltages and currents (i.e., just before the switch opens):


$$C : 2 \text{ nF}$$

$$i_{L1} = i_L(2^-) \quad v_{L1} = v_L(2^-) \quad i_{C1} = i_C(2^-) \quad v_{C1} = v_C(2^-)$$


$$L : 1 \text{ mH}$$

Find these voltages and currents (i.e., just after the switch opens):
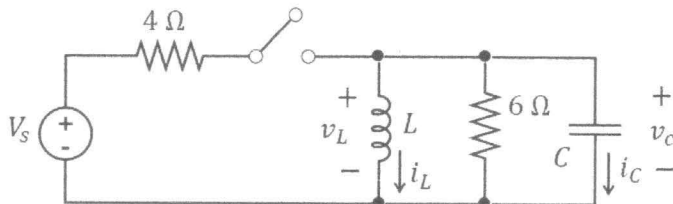
$$i_{L2} = i_L(2^+) \quad v_{L2} = v_L(2^+) \quad i_{C2} = i_C(2^+) \quad v_{C2} = v_C(2^+)$$




(a) $t = 2^-$: SWITCH IS CLOSED

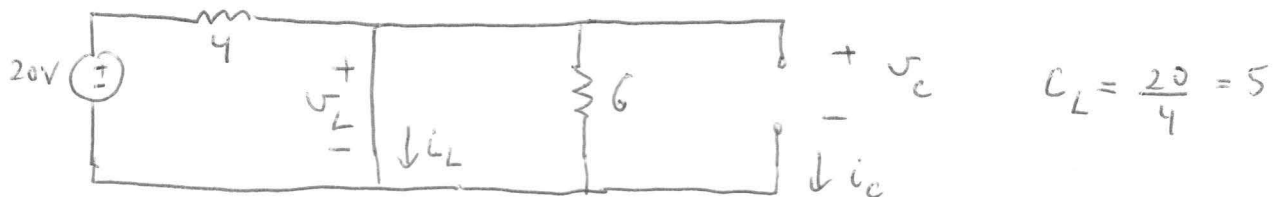

$$v_L(2^-) = 0 \text{ V} \quad i_C(2^-) = 0 \text{ A} \quad v_C(2^-) = 0 \text{ V} \quad i_L(2^-) = 5 \text{ A}$$

(b) $t = 2^+$

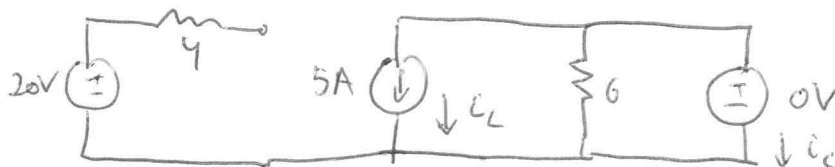

$$i_L(2^+) = 5 \text{ A} \quad v_C(2^+) = 0 \text{ V} \quad v_L(2^+) = 0 \text{ V} \quad i_C(2^+) = -5 \text{ A}$$