

## Quiz 2

/ 12

Last name

First + middle  
name(s)

PID

## Instructions:

- Read each problem completely and thoroughly before beginning
- All calculations need to be done on these sheets
- Write your answers in the answer boxes for each question. Make sure you list units!
- Answers without supporting calculations will receive zero credit

- (1) (a) (3 points) Draw the Thevenin model for the circuit in figure 1 below, between A and B (make sure you label A and B in your drawing).

You are not given the values of  $V_1$ ,  $I_1$  or  $R_1$ . However, you are told that if you attach an ammeter as shown in figure 2, the ammeter reading is **2A**. Also, if you attach a voltage source as shown in figure 3, the current  $i_a$  is **2A**.

Drawing of the Thevenin model

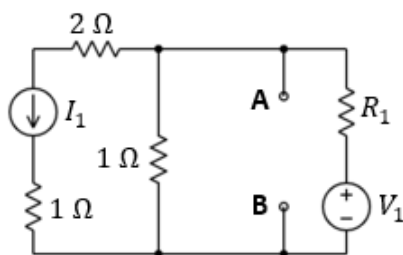


Figure 1

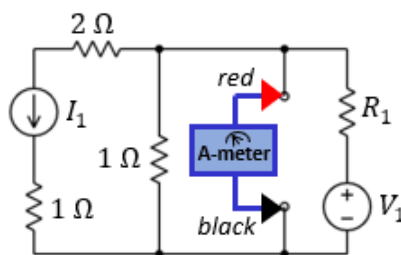


Figure 2

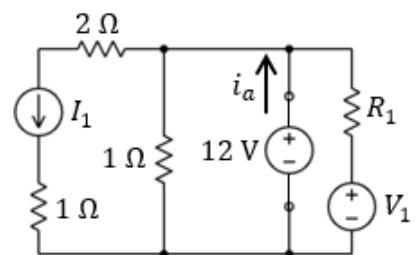


Figure 3

- (b) (3 points) We attach the circuit from figure 4 to the one from figure 1 above (with A' connected to A and B' connected to B).

Find the value of  $k$  such that the power received by the two elements in figure 4 combined is maximized (i.e., the power received by the dependent source and the resistor combined).

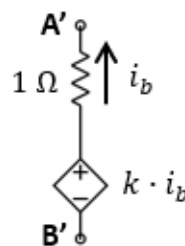


Figure 4

 $k$

Copies of the circuits from the previous page ...

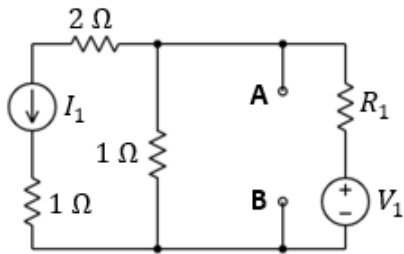


Figure 1

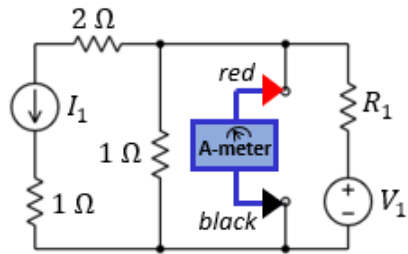


Figure 2

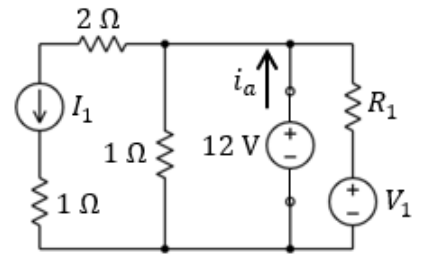


Figure 3

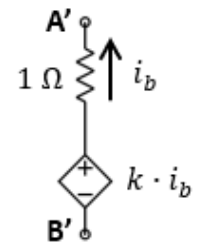


Figure 4

(2) (6 points) For  $t < 2$  s, both switches are closed, and you may assume that the system has reached steady state. Both switches open at time  $t = 2$  s.

(a) Find  $v_1(2^- \text{ s})$ . (i.e., the left node voltage just before the event)  $v_1(2^- \text{ s})$

(b) Find  $v_2(2^- \text{ s})$ . (i.e., the right node voltage just before the event)  $v_2(2^- \text{ s})$


(c) Find  $v_1(2^+ \text{ s})$ . (i.e., the left node voltage just after the event)  $v_1(2^+ \text{ s})$

(d) Find  $v_2(t)$  for  $t > 2$  s.


Write the equation.

(i.e., for the right node voltage)

$v_2(t)$

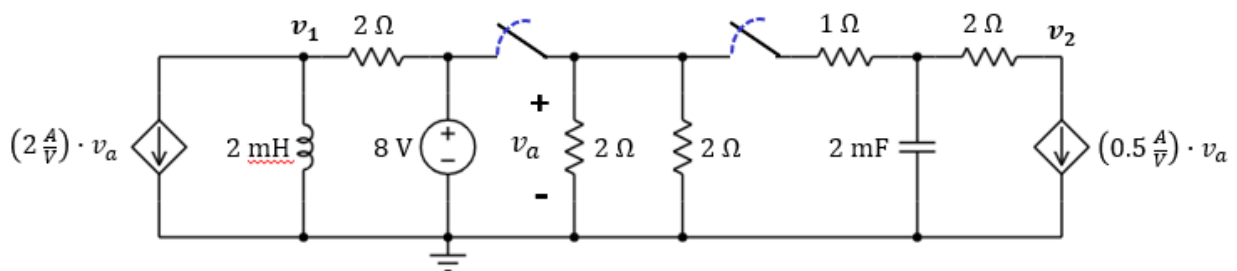

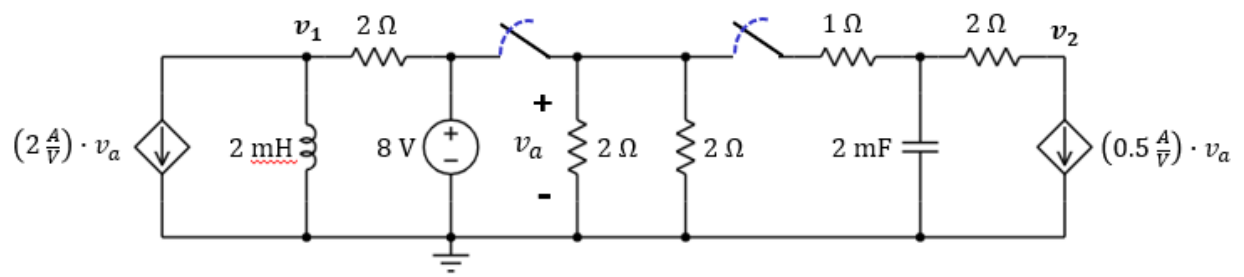Copy of the circuit from the previous page ...



## ECE35 Equation Sheet

**Basics:**  $i \triangleq \frac{dq}{dt}$        $v_{ab} \triangleq \frac{dw}{dq}$        $R = \rho \frac{l}{A}$

**Capacitors:**  $C = \epsilon \cdot \frac{A}{d}$        $Q = C \cdot v$        $w_C = \frac{1}{2} C v^2$

**Inductors:**  $L = \mu \cdot \frac{N^2 A}{l}$        $B \sim i$        $w_L = \frac{1}{2} L i^2$

**AC power:**  $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \quad X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$

**Trigonometry:**

$\sin(-\alpha) = -\sin(\alpha)$	$\cos(-\alpha) = \cos(\alpha)$
$\sin(\pi - \alpha) = \sin(\alpha)$	$\cos(\pi - \alpha) = -\cos(\alpha)$
$\sin\left(\frac{\pi}{2} - \alpha\right) = \cos(\alpha)$	$\cos\left(\frac{\pi}{2} - \alpha\right) = \sin(\alpha)$
$\sin\left(\alpha - \frac{\pi}{2}\right) = -\cos(\alpha)$	$\cos\left(\alpha - \frac{\pi}{2}\right) = \sin(\alpha)$
$\sin(2\alpha) = 2 \sin(\alpha) \cos(\alpha)$	$\cos(2\alpha) = \cos^2(\alpha) - \sin^2(\alpha)$

$$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$$

$$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$$

$$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$$

$$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$$

$$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$$

$\alpha:$	0	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$
$\sin(\alpha):$	0	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	1
$\tan(\alpha):$	0	$\frac{\sqrt{3}}{3}$	1	$\sqrt{3}$	$\infty$