

ECE 65: Components & Circuits Lab

Lecture 8

Diode waveform shaping circuits

Peak detector circuits


Reference notes: sections 2.9

Sedra & Smith (7th Ed): sections 4.4-4.6


Saharnaz Baghdadchi

Course map


2. Diodes

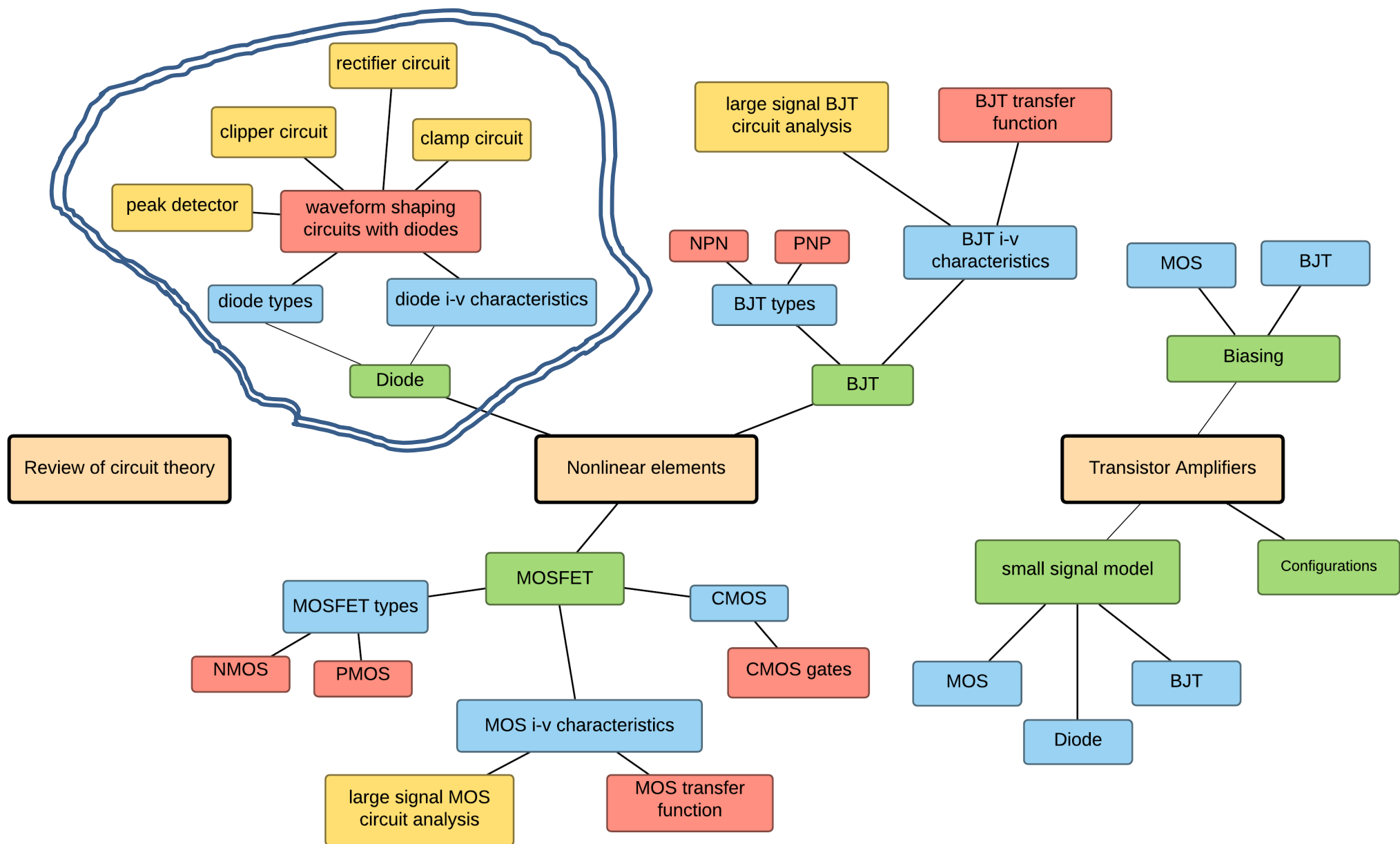


Ideal Peak Detector Circuit

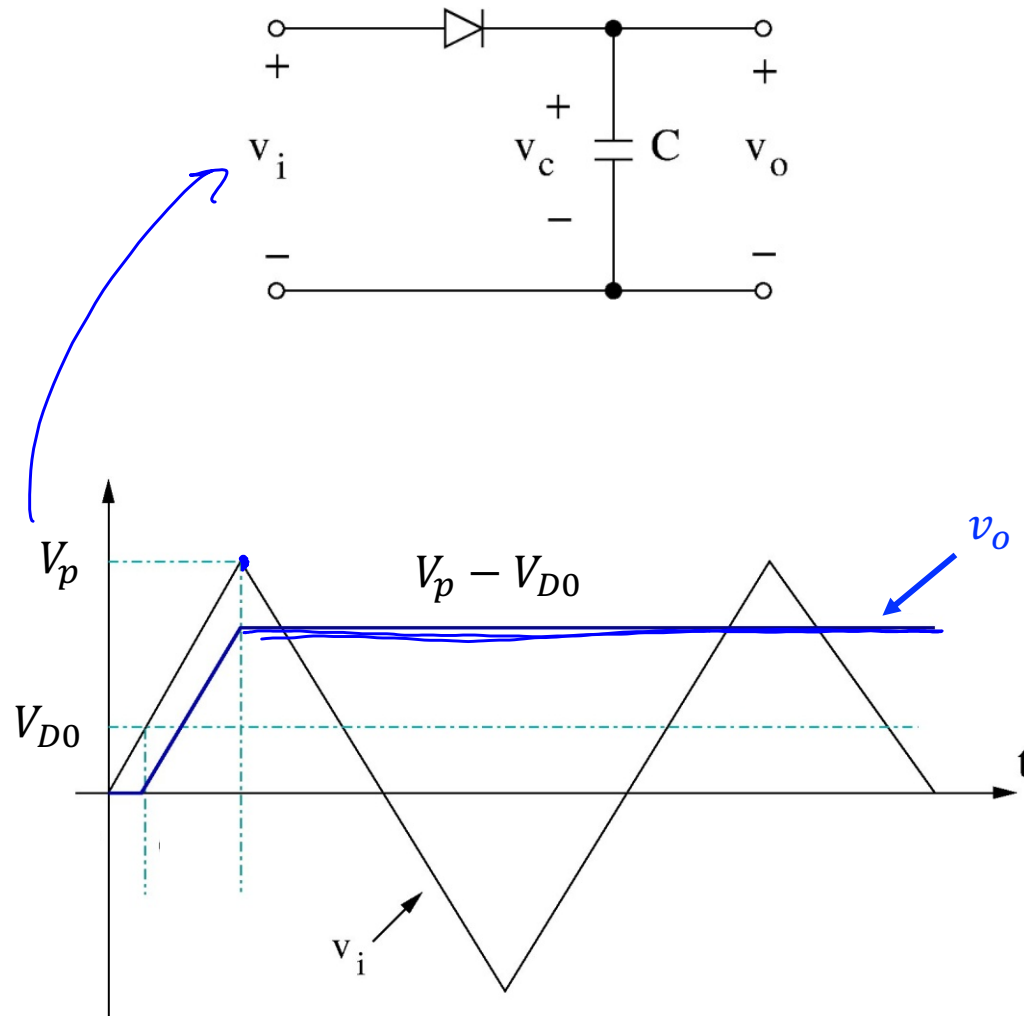

Ideal Peak Detector Circuit

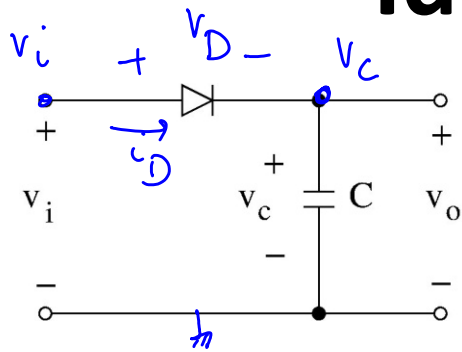


When the Diode is initially OFF:

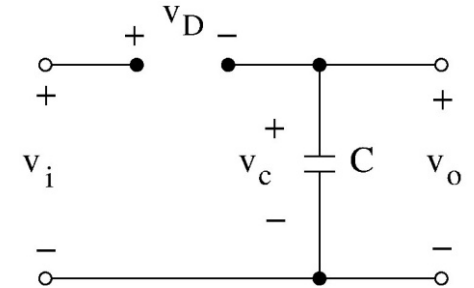


$$V_D = v_i - v_c = v_i$$

$$i_D = 0, V_D < V_{D0}$$


$$\Rightarrow v_i < v_{D0}$$

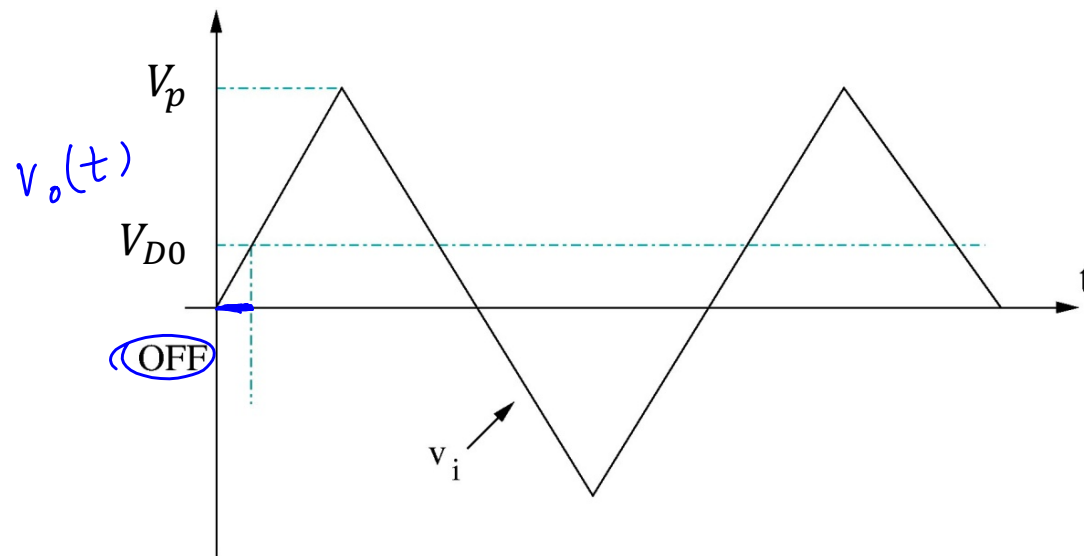

Ideal Peak Detector Circuit

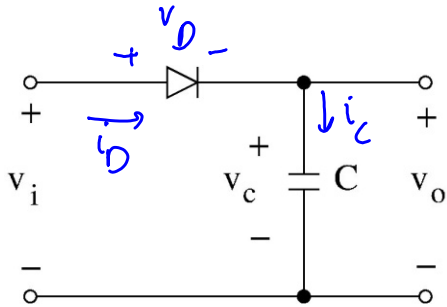

When the Diode is ON:

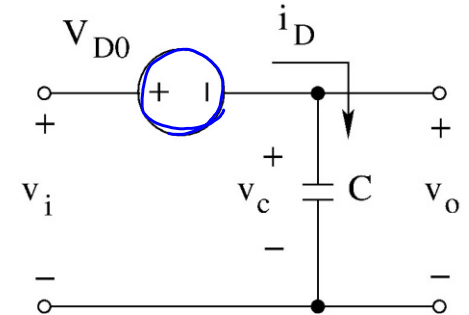


$$V_D = V_{D0}$$

$$i_D \geq 0$$

$$V_o = -V_D + V_i = -V_{D0} + V_i$$


$$i_D = i_C = C \frac{dv_c}{dt} = C \frac{d(v_i - V_{D0})}{dt}$$

$$= C \frac{dv_i}{dt}$$


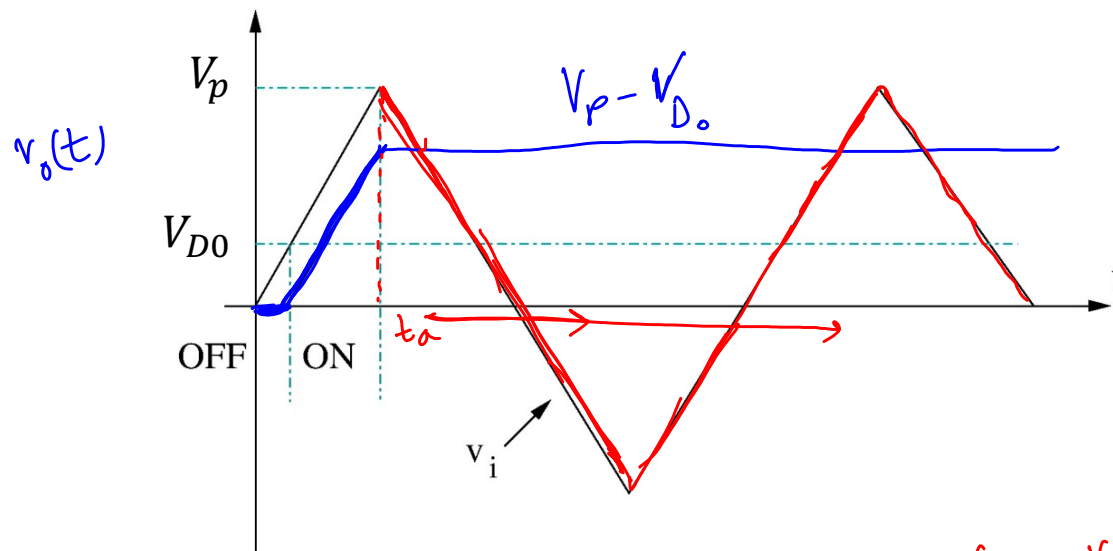


at $t = t_a$, $V_i = V_p$, $V_c = V_p - V_{D0}$, $V_o = V_i - V_c = V_i - (V_p - V_{D0})$


Ideal Peak Detector Circuit

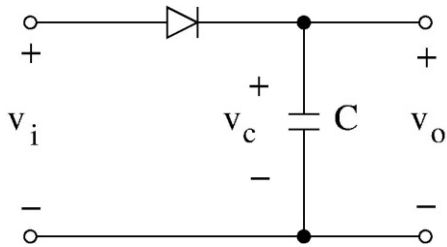

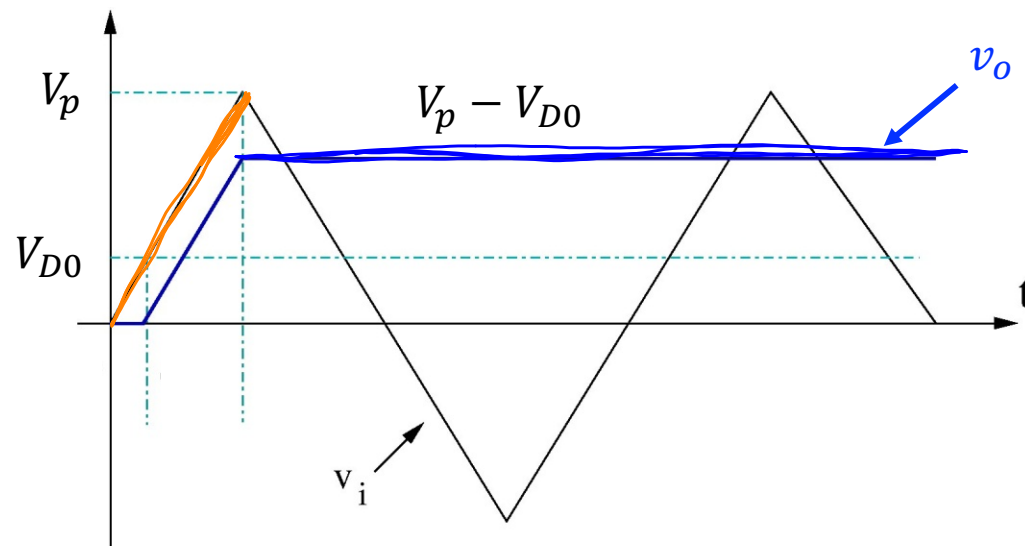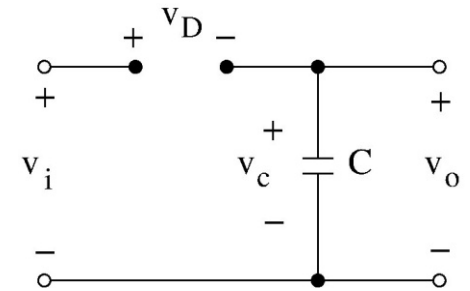After v_i reached its peak value, the diode does not turn ON anymore.




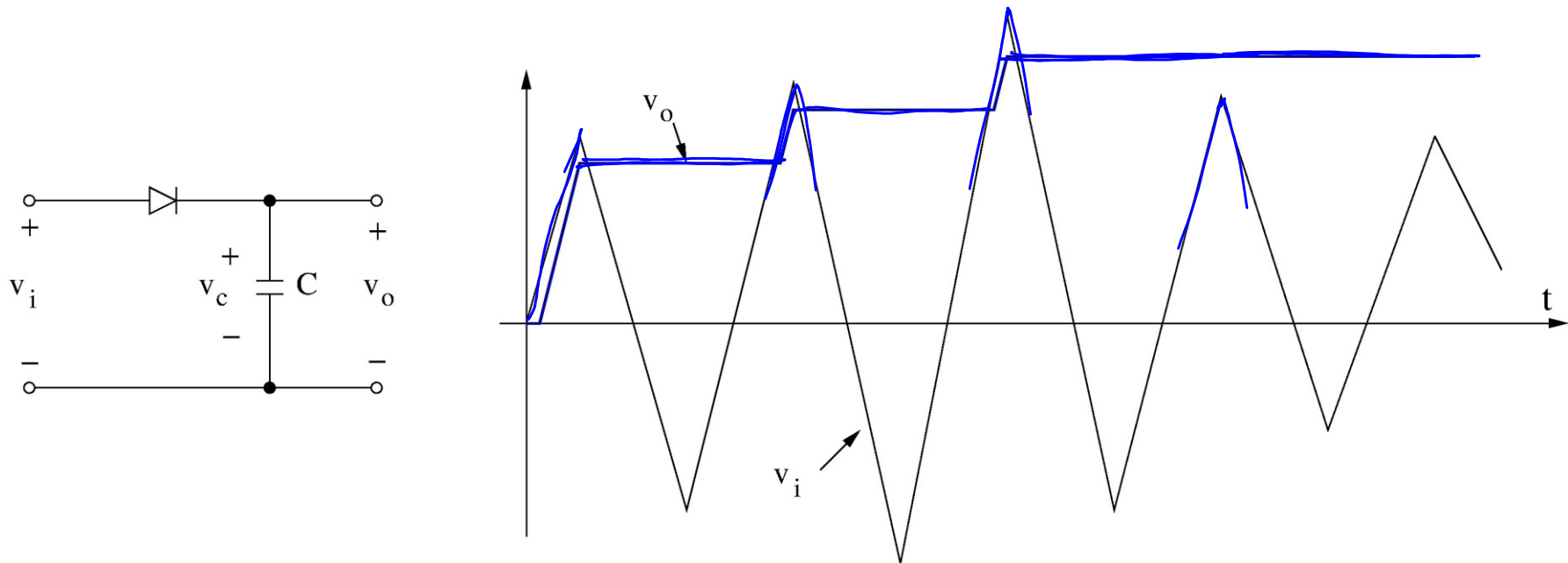
Response of the Ideal Peak Detector (v_i amplitude changes)



v_o is the “peak” value of input waveform ($V_p - V_{D0}$):

Note v_o did not “drop” after the peak was decreased in the 3rd cycle.

Practical Peak Detector Circuit

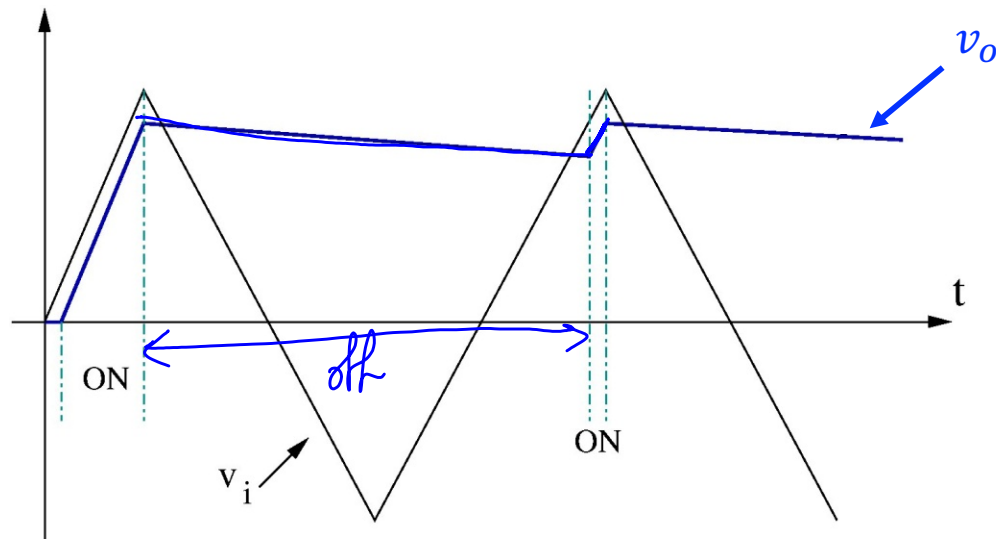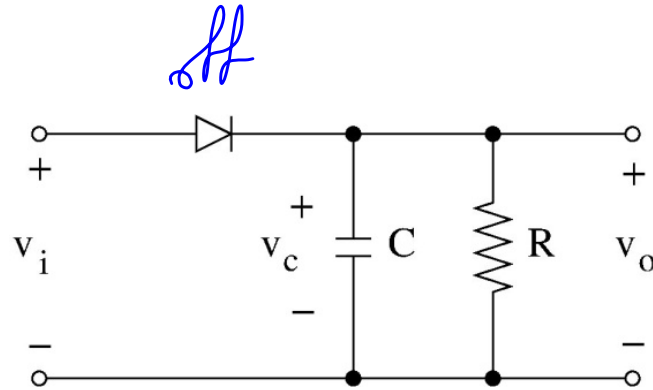

Practical Peak Detector Circuit




Diode OFF: $i_D = 0$ and $v_D < V_{D0}$

Capacitor discharges into the resistor with a time constant of $\tau = RC$

$$v_o = v_c(t) = v_{c0} e^{-(t-t_0)/\tau}$$

$$v_D = v_i - v_c < V_{D0}$$

$$\rightarrow v_i < v_c(t) + V_{D0}$$

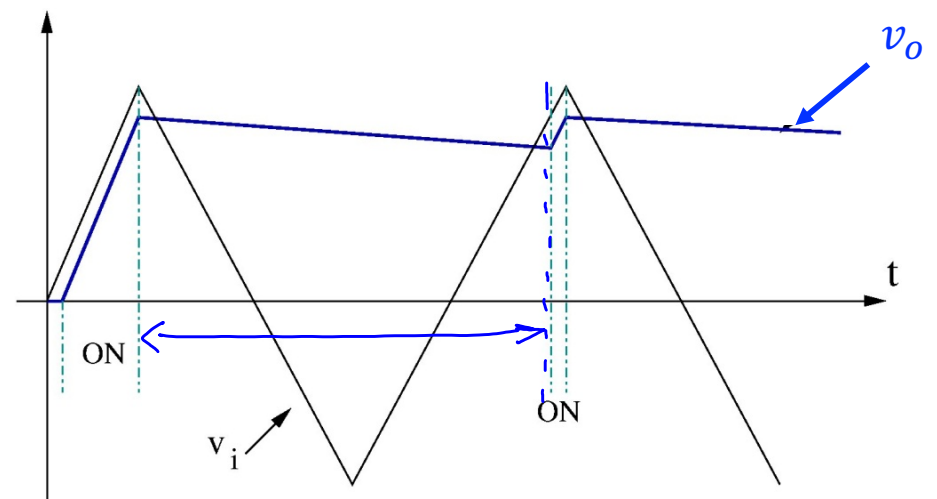
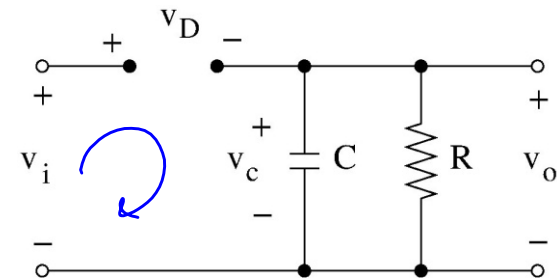
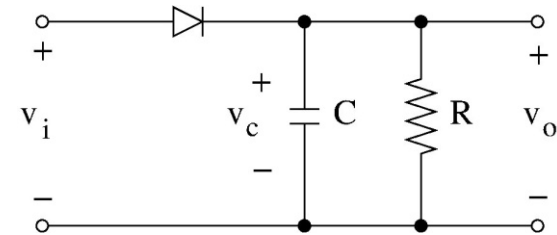


Practical Peak Detector Circuit

Diode ON: $v_D = V_{D0}$ and $i_D \geq 0$

$$v_o = v_C = v_i - V_{D0}$$
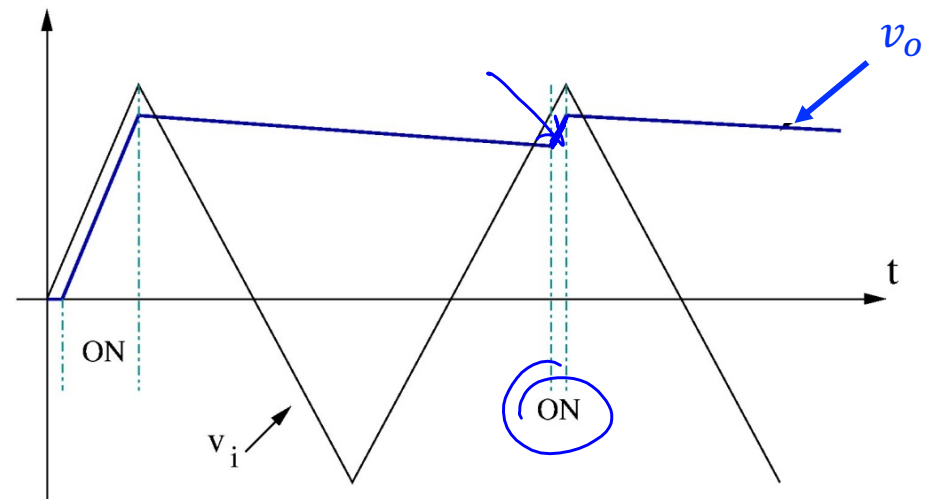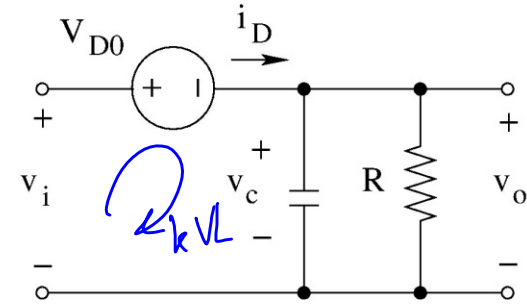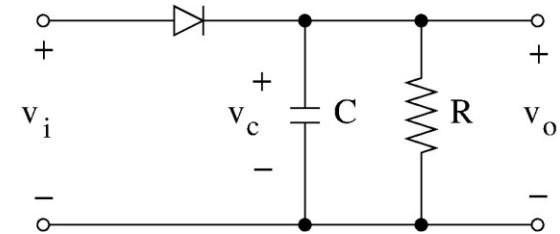
$$i_C = C \frac{dv_C}{dt} = C \frac{d(v_i - V_{D0})}{dt} = C \frac{dv_i}{dt}$$



Response of the Practical Peak Detector

Shape of output signal depends on the ratio of τ/T



“ideal” peak detector: $\tau/T \rightarrow \infty$

“Good” peak detector: $\tau/T \gg 1$

As τ/T decreases, the circuit departs from a peak detector.






For $\tau/T \ll 1$, capacitor discharges very fast and circuit resembles a rectifier circuit

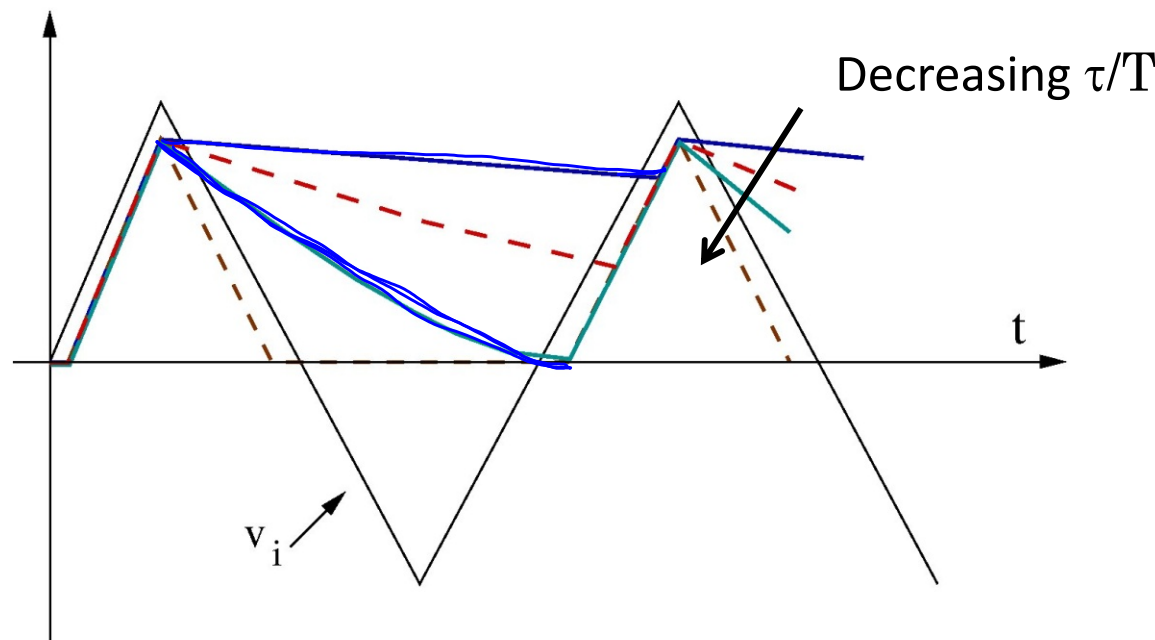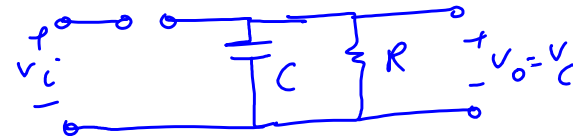τ : time constant $= RC$
 T : period of $v_i(t)$



Lecture 8 reading quiz.

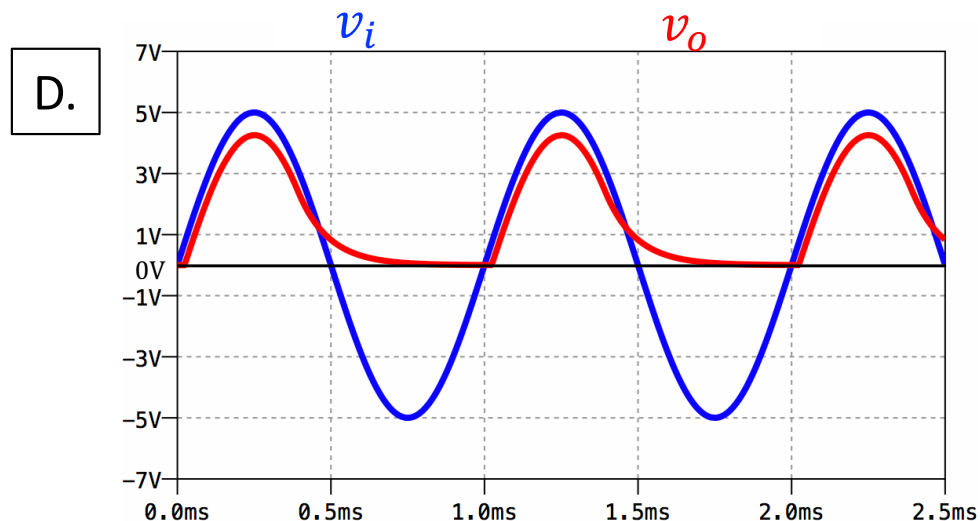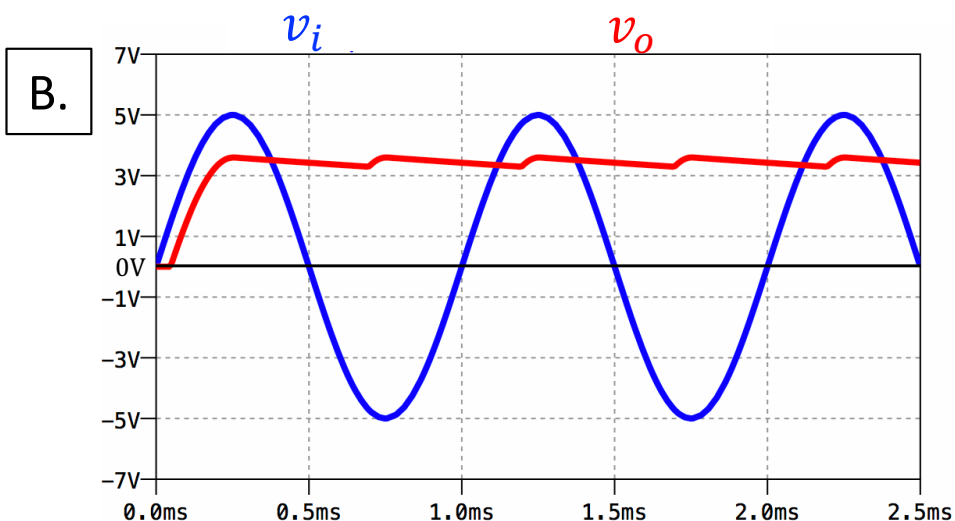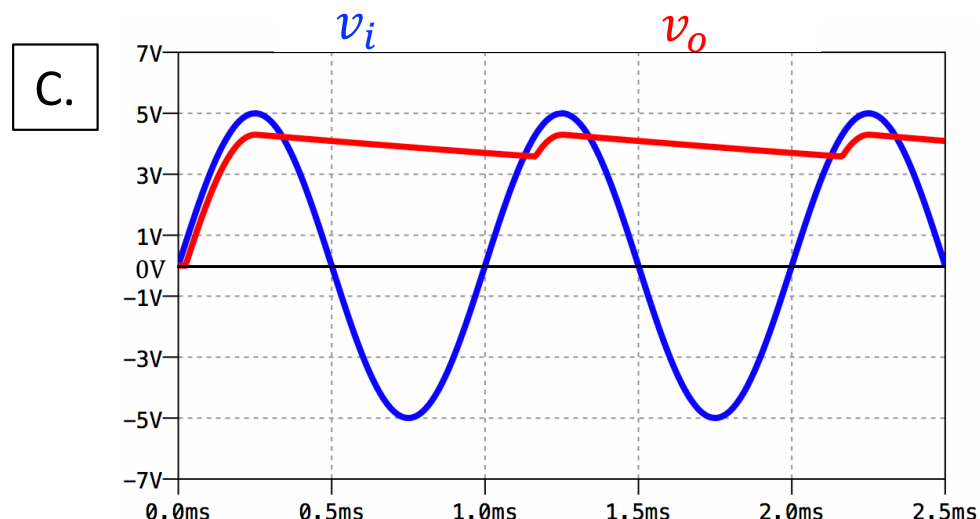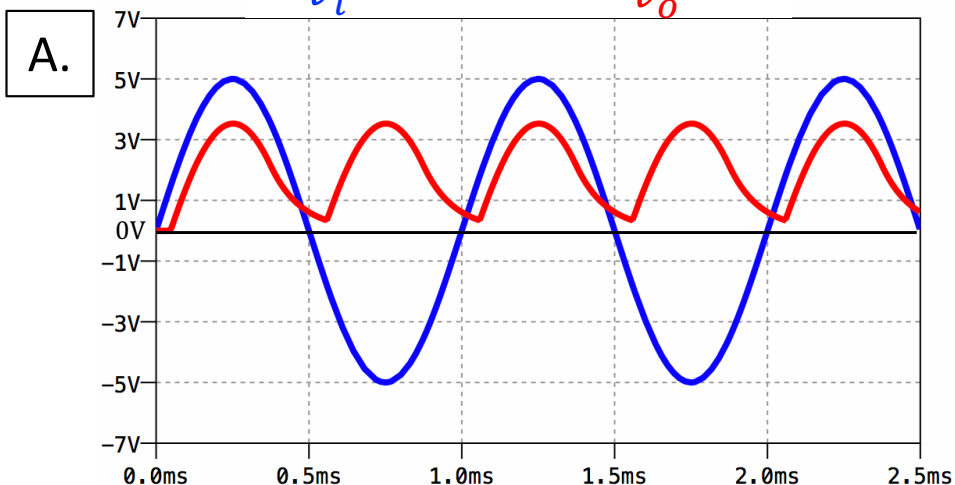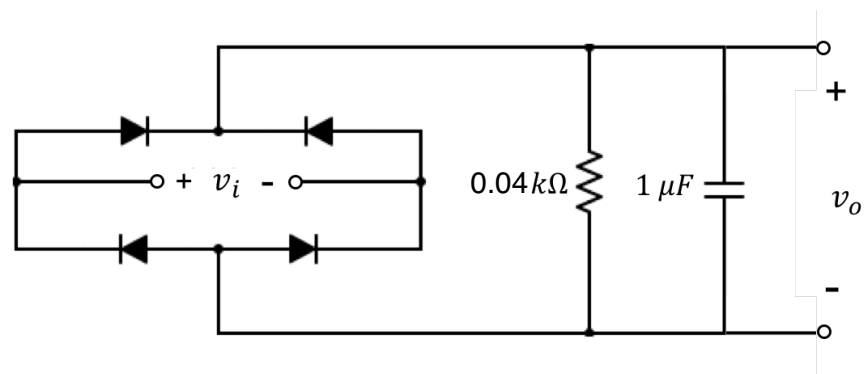
In the following diode circuit, which one of the options could be the input and output voltages for this circuit? $V_{D0} = 0.7\text{ V}$.



Discussion question 1.

In the circuit below, $v_i(t) = 10 \sin(\omega t)$ where $\omega = 1000 \text{ rad/s}$, $v_c(0) = 0$.

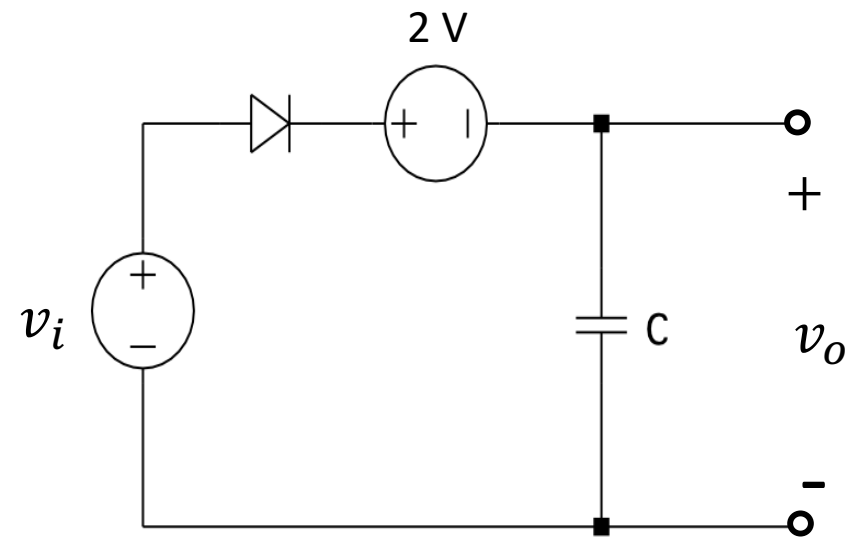$V_{D0} = 0.7 \text{ V}$. What is the value of $v_o(t)$ at $t = 1 \text{ ms}$ and $t = 2 \text{ ms}$? Draw one cycle of the input and output waveforms.




Hints:

Discussion question 1.

In the circuit below, $v_i(t) = 10 \sin(\omega t)$ where $\omega = 1000 \text{ rad/s}$, $v_c(0) = 0$.

$V_{D0} = 0.7 \text{ V}$. What is the value of $v_o(t)$ at $t = 1 \text{ ms}$ and $t = 2 \text{ ms}$? Draw one cycle of the input and output waveforms.

- Find the period of the input sinusoidal waveform.
 $T = 2\pi/\omega$
- Find the minimum amplitude of v_i to turn the diode ON. You should write a KVL in the circuit to get the answer. Note that $V_c(0) = 0$
- The diode will conduct until v_i reaches its peak amplitude. Then, it will disconnect.
- Find the time point at which v_i reaches its peak amplitude and compare it with the given time points, $t = 1 \text{ ms}$ and 2 ms . The relationship between v_{out} and v_i will be different at different time points.

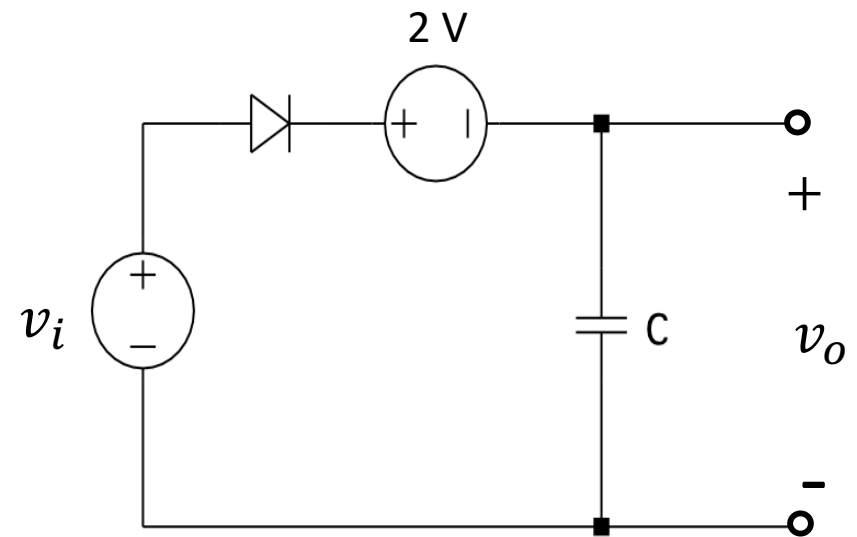

Discussion question 2.

Design a clipper circuit that limits voltages above 6 V. You can use any combination of regular PN junction diodes, Zener diodes or DC sources.

Extra problem for practice

Find v_R and i in the below circuit for $-5\text{ V} \leq v_i \leq 5\text{ V}$.

(Assume Si diodes with $V_{D0} = 0.7\text{ V}$)

