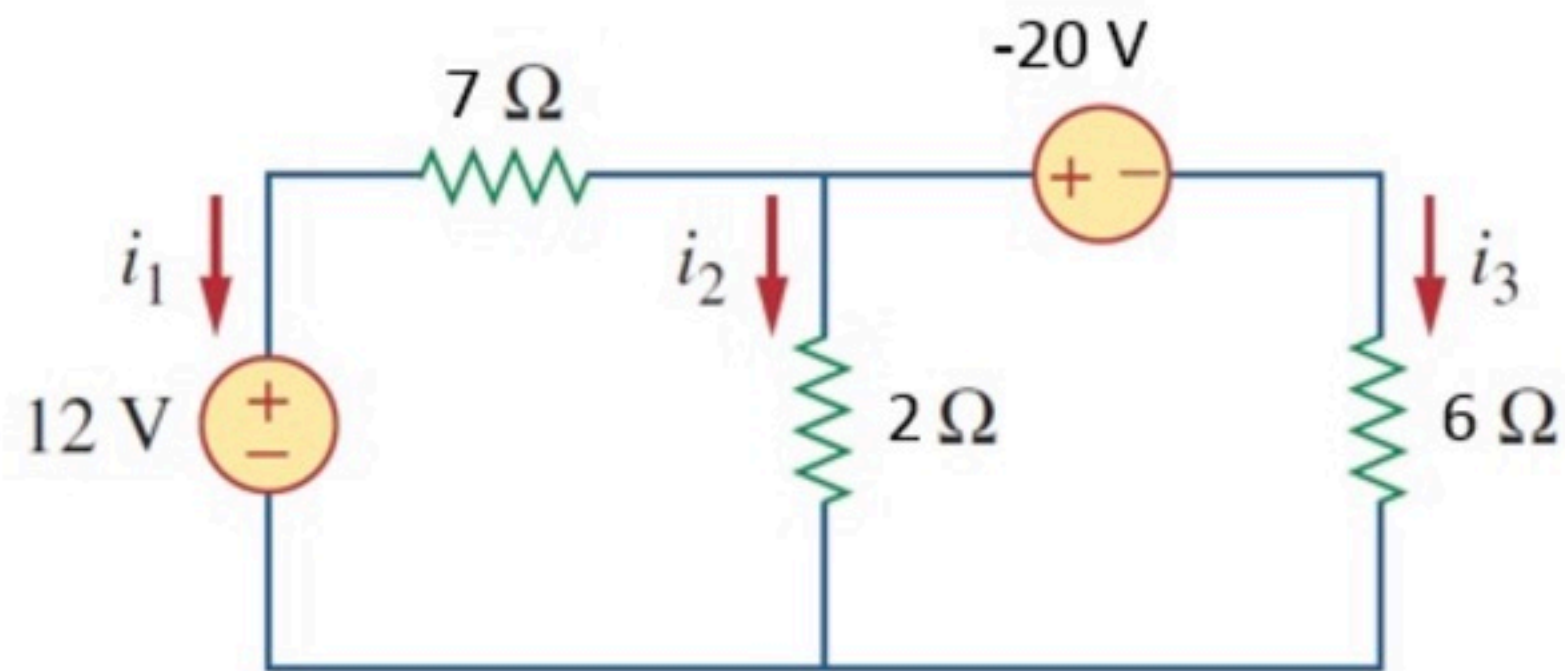


PP Nodal Mesh 011

Problem has been graded.

Find the currents i_1 , i_2 , and i_3 . Solve using mesh analysis.

For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

...

Calculate the following:

i_1 (A) :

-2



i_2 (A) :

-1



i_3 (A) :

3



Hint: Define 2 mesh currents