
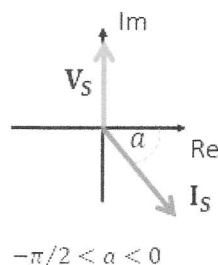


The AC circuit below has  $\omega = \omega_1$  and is in steady state. The phasor diagram shows the phasors of  $v_s$  and  $i_s$ . You are given the angle  $\alpha$ , and vector lengths  $|I_s| = A_1$  and  $|V_s| = A_2\sqrt{b}$ . The diagram is not necessarily drawn to scale (but  $V_s$  is along the imaginary axis). The element in the center (rectangular box) is either an inductor or a capacitor but you are not told which.

- At what time does  $v_R$  reach its maximum value? Enter  $k = t_0 \cdot \frac{12}{\pi}$ , where  $t_0$  is the first time that the maximum is reached, for  $t_0 \geq 0$ . (Hint: convert  $\alpha$  to radians first)
- We select the mystery element such that  $|I_a|$  is minimized (note that this is the current through the voltage source). What is the mystery element type (enter 1 for capacitor, 2 for inductor)? What is its value  $X$  (i.e., either the capacitance or the inductance value, in F or H respectively)?

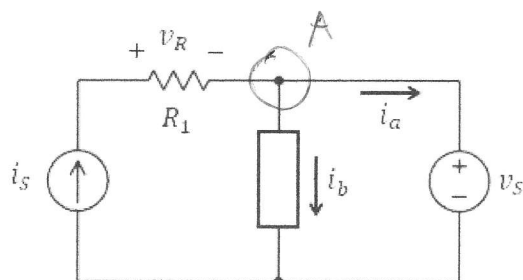

$$\begin{aligned}\omega_1 &= 2 \text{ rad/s} \\ \alpha &= -30^\circ \\ A_1 &= 2 \text{ A} \\ A_2 &= 10 \text{ V} \\ b &= 3 \\ R_1 &= 1 \Omega\end{aligned}$$

$$(a) V_R = R_1 I_s = R_1 \cdot A_1 e^{j\alpha} = 2 e^{-j30^\circ}$$



$$V_{R_{\max}} = |V_R| \quad v_R(t) = 2 \cos(2t - 30^\circ) \quad \text{MAX WHEN } \cos(\theta) = 1$$

$$\theta = 0 \Rightarrow 2t_0 - \frac{\pi}{6} = 0 \Rightarrow t_0 = \frac{\pi}{12} \Rightarrow k = t_0 \cdot \frac{12}{\pi} = 1 \quad \boxed{k=1}$$


$$(b) \text{ KCL @ A: } I_s = I_B + I_A$$

If the mystery element is a capacitor or inductor:  $I_b$  is perpendicular to  $V_s$

Let's look at different options

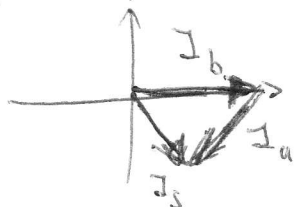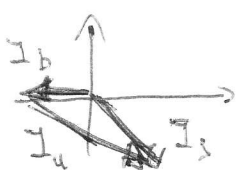

etc.  $\leadsto$

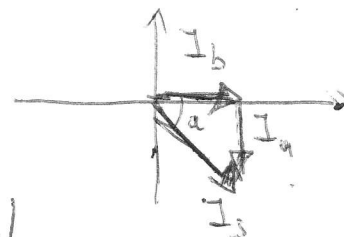

$$\cos(-\alpha) = \frac{|I_b|}{|I_s|} \Rightarrow \cos\left(\frac{\pi}{6}\right) = \frac{\sqrt{3}}{2} = \frac{|I_b|}{2}$$

$$|I_b| = \sqrt{3} \quad \text{on the real axis} \Rightarrow I_b = \sqrt{3}$$

$$\text{also: } V_s = Z \cdot I_b \Rightarrow Z = \frac{V_s}{I_b} = \frac{10\sqrt{3}}{\sqrt{3}} j = 10j$$

$$\begin{aligned}\text{This must be an inductor: } Z &= j\omega L = 10j \\ \Rightarrow \omega L &= 10 \Rightarrow L = \frac{10}{2} = 5 \text{ H} \\ \Rightarrow X &= 5\end{aligned}$$