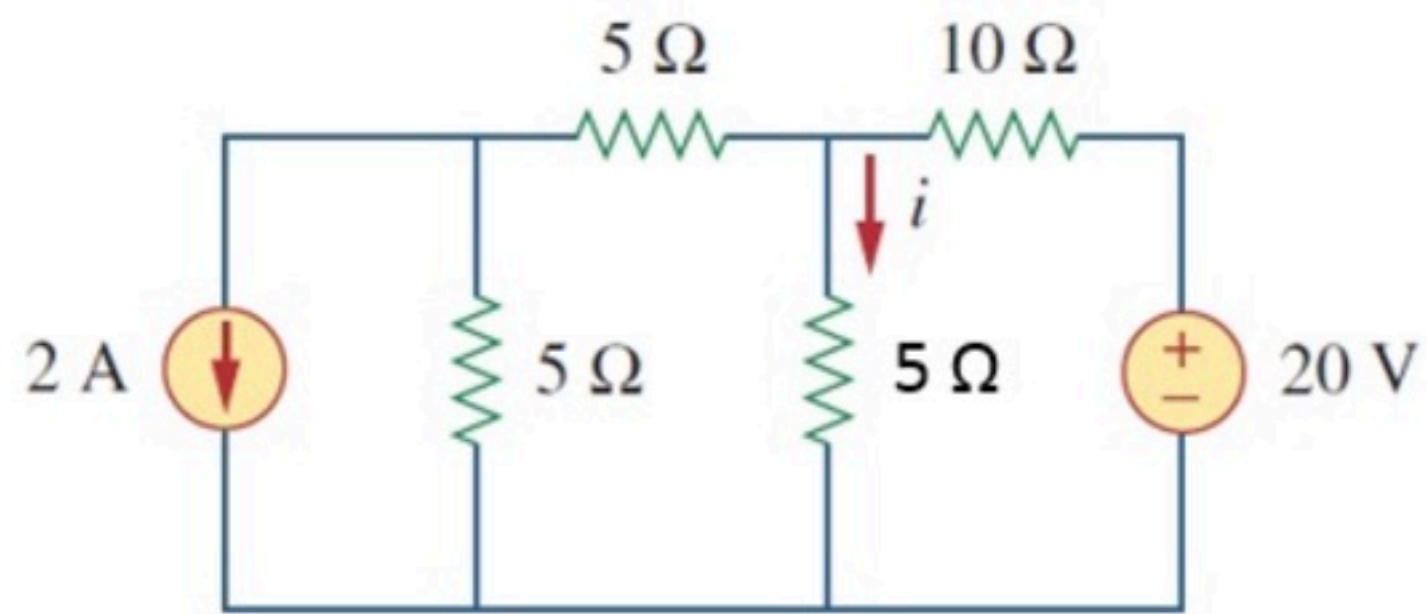


PP Circuit theorems 006

Unlimited Attempts.

Use source transformations to find i .



Given Variables:

...

Calculate the following:

$i\text{ (A)} :$

0.5



Hint: Make sure you use the correct transformations.