


Phasors 001

Problem has been graded.

$$v_1(t) = B \cos(200t + D_1) \quad \text{with } -180^\circ \leq D_1 \leq 180^\circ$$

$$v_2(t) = B \sin(200t + D_2) \quad \text{with } -180^\circ \leq D_2 \leq 180^\circ$$

Find D_1 and D_2 .

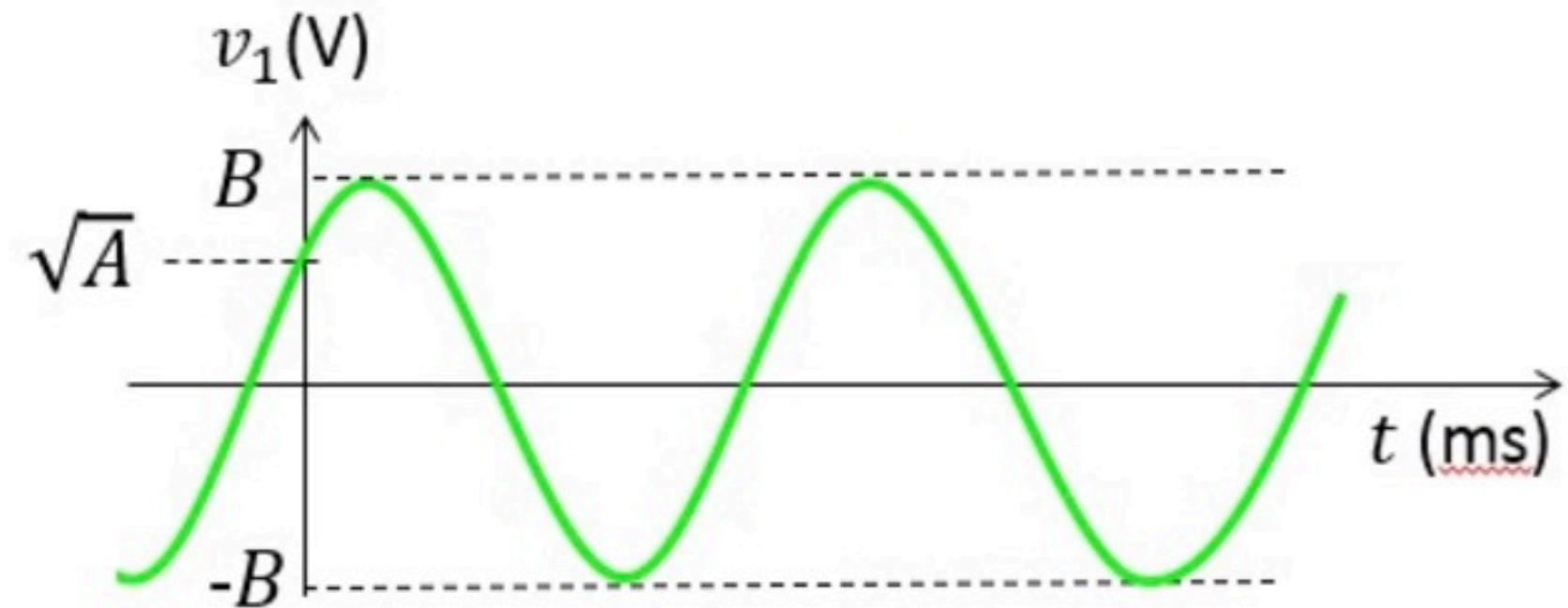

Given Variables:

A : 9 V²

B : 6 V

Calculate the following:

D1 (degrees) :

-60



D2 (degrees) :

150



Hint: Look on the graph to disambiguate.


$$v_1(t) = B \cos(200t + D_1) \quad \text{with } -180^\circ \leq D_1 \leq 180^\circ$$

A : $3\sqrt{2}$


$$v_2(t) = B \sin(200t + D_2) \quad \text{with } -180^\circ \leq D_2 \leq 180^\circ$$

B : 2 V

Find D_1 and D_2 .

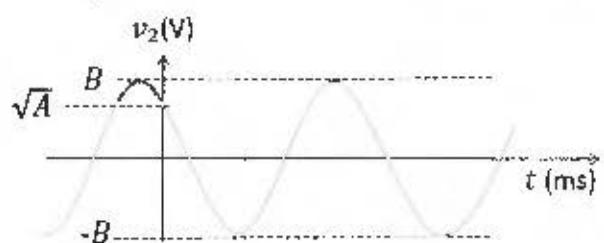

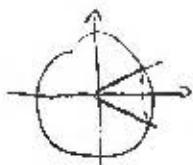① PLUG IN $t=0$: $v_1(0) = 2 \cos(D_1) = \sqrt{3} \Rightarrow \cos(D_1) = \frac{\sqrt{3}}{2}$



$$D_1 = 30^\circ$$

$$\text{or } D_1 = -30^\circ$$

WE KNOW THAT $\cos(\omega(t-t_0)) = \cos(\omega t + \phi)$

$$\phi = -\omega t_0$$

HERE $t_0 > 0 \Rightarrow \phi < 0 \Rightarrow \boxed{D_1 = -30^\circ \text{ degrees}}$

② OPTION 1: WRITE AS $\cos()$ FIRST

$$v_2(t) = B \cos(200t + \alpha) \Rightarrow v_2(0) = 2 \cos(\alpha) = \sqrt{3}$$

$$\Rightarrow \alpha = 30^\circ \text{ or } -30^\circ \quad \text{HERE } t_0 < 0 \Rightarrow \phi > 0 \Rightarrow \alpha = 30^\circ$$

$$v_2(t) = B \cos(200t + 30^\circ) = B \sin(200t + 30^\circ + 90^\circ) \Rightarrow \boxed{D_2 = 120^\circ}$$

OPTION 2: $v_2(0) = 2 \sin(D_2) = \sqrt{3} \Rightarrow \sin(D_2) = \frac{\sqrt{3}}{2}$



$$D_2 = 60^\circ$$

$$\text{or } D_2 = 180^\circ - 60^\circ = 120^\circ$$

LOOK AT THE
GRAPH

SIN() SHIFTED MORE
THAN 90°

$$\Rightarrow \boxed{D_2 = 120^\circ}$$

Phasors 002

Problem has been graded.


Express the current as a time waveform

$$i(t) = A_1 \cdot \cos(2\pi f_1 \cdot t + B_1)$$

with $0 \leq A_1$ and $-180^\circ \leq B_1 \leq 180^\circ$

and as a phasor
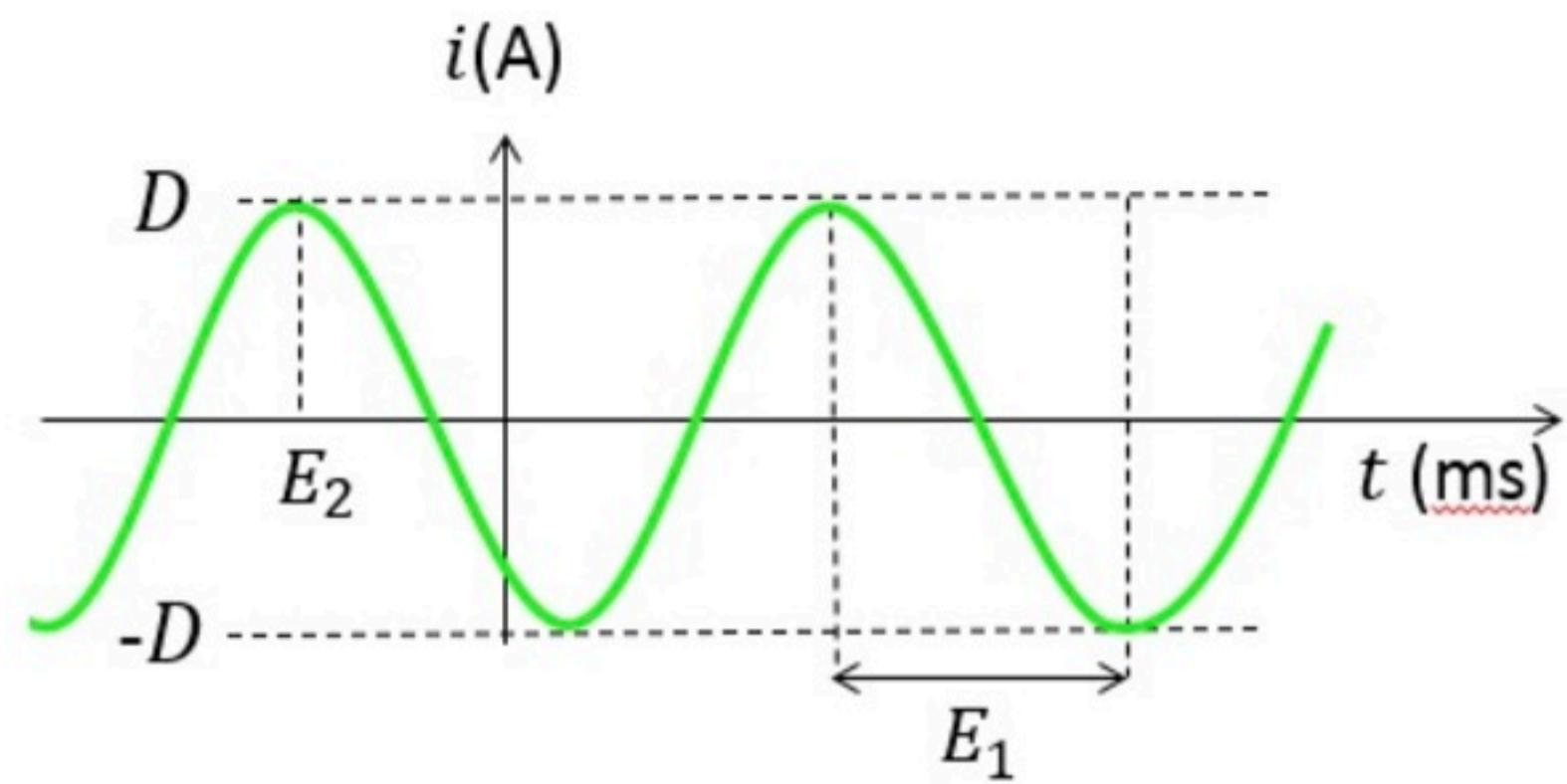
$$\mathbf{I} = A_2 \cdot e^{jB_2} \quad \text{with } 0 \leq A_2 \text{ and } -180^\circ \leq B_2 \leq 180^\circ$$



Given Variables:

D : 5 A

E1 : 1 ms

E2 : -0.7 ms

Calculate the following:

f1 (1/s) :

500



A1 (A) :

5



B1 (degrees) :

126



A2 (A) :

5



B2 (degrees) :

126



Express the current as a time waveform

$$i(t) = A_1 \cdot \cos(2\pi f_1 \cdot t + B_1)$$

with $0 \leq A_1$ and $-180^\circ \leq B_1 \leq 180^\circ$


D : 6 A

and as a phasor

E1 : 2 ms

E2 : -1.7 ms
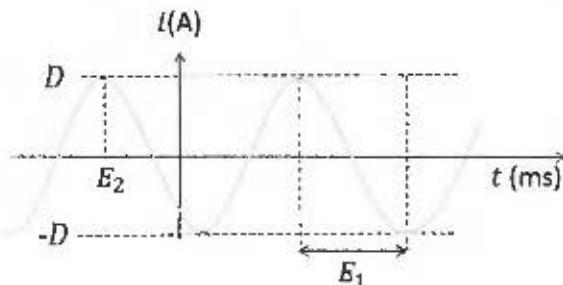
$$I = A_2 \cdot e^{jB_2} \quad \text{with } 0 \leq A_2 \text{ and } -180^\circ \leq B_2 \leq 180^\circ$$



$$T = 2 \cdot E_1 = 4 \text{ ms} \Rightarrow f_1 = \frac{1}{T} = \frac{1000}{4} = 250$$

$$f_1 = 250 \text{ s}^{-1}$$

$$A_1 = A_2 = D \Rightarrow A_1 = 6 \text{ A} \quad A_2 = 6 \text{ A}$$

$$\phi = -\omega t_0 = -\frac{2\pi}{T} \cdot E_2 = -\frac{2\pi}{4} \cdot (-1.7) = \frac{\pi \cdot 1.7}{2} \text{ rad}$$

$$\phi = \frac{180^\circ \cdot 1.7}{2} = 90^\circ \cdot 1.7 = (9 \cdot 17)^\circ = 153^\circ$$

$$B_1 = 153^\circ$$

$$B_2 = 153^\circ$$

Phasors 003

Problem has been graded.

Consider the sinusoids:

$$i_1(t) = 12 \cos(10t + A_1)$$

$$i_2(t) = 12 \sin(10t + A_2)$$

The corresponding phasors are:

$$\mathbf{I}_1 = 12e^{jB_1} \quad \text{with } -180^\circ \leq B_1 \leq 180^\circ$$

$$\mathbf{I}_2 = 12e^{jB_2} \quad \text{with } -180^\circ \leq B_2 \leq 180^\circ$$

Find B_1 and B_2 .

Given Variables:

A1 : 35 degrees

A2 : 45 degrees

Calculate the following:

B1 (degrees) :

35



B2 (degrees) :

-45



Hint: Convert the sine to cosine first.

Consider the sinusoids:

$$i_1(t) = 12 \cos(10t + A_1)$$

A1 : 55 degrees

$$i_2(t) = 12 \sin(10t + A_2)$$

A2 : 20 degrees

The corresponding phasors are:

$$\mathbf{I}_1 = 12e^{jB_1} \quad \text{with } -180^\circ \leq B_1 \leq 180^\circ$$

$$\mathbf{I}_2 = 12e^{jB_2} \quad \text{with } -180^\circ \leq B_2 \leq 180^\circ$$

Find B_1 and B_2 .

$$i_1(t) = 12 \cos(10t + 55^\circ) \Rightarrow \mathbf{I}_1 = 12 e^{j55^\circ}$$

$$B_1 = 55^\circ$$

$$i_2(t) = 12 \sin(10t + 20^\circ)$$

$$= 12 \cos(10t + 20^\circ - 90^\circ)$$

$$= 12 \cos(10t - 70^\circ) \Rightarrow \mathbf{I}_2 = 12 e^{-j70^\circ}$$

$$B_2 = -70^\circ$$


Phasors 004

Problem has been graded.

You are given $v_S = A_1 \cdot \sqrt{2} \cdot \cos(100t + B_1)$

$$v_C = A_2 \cdot \cos(100t + B_2)$$

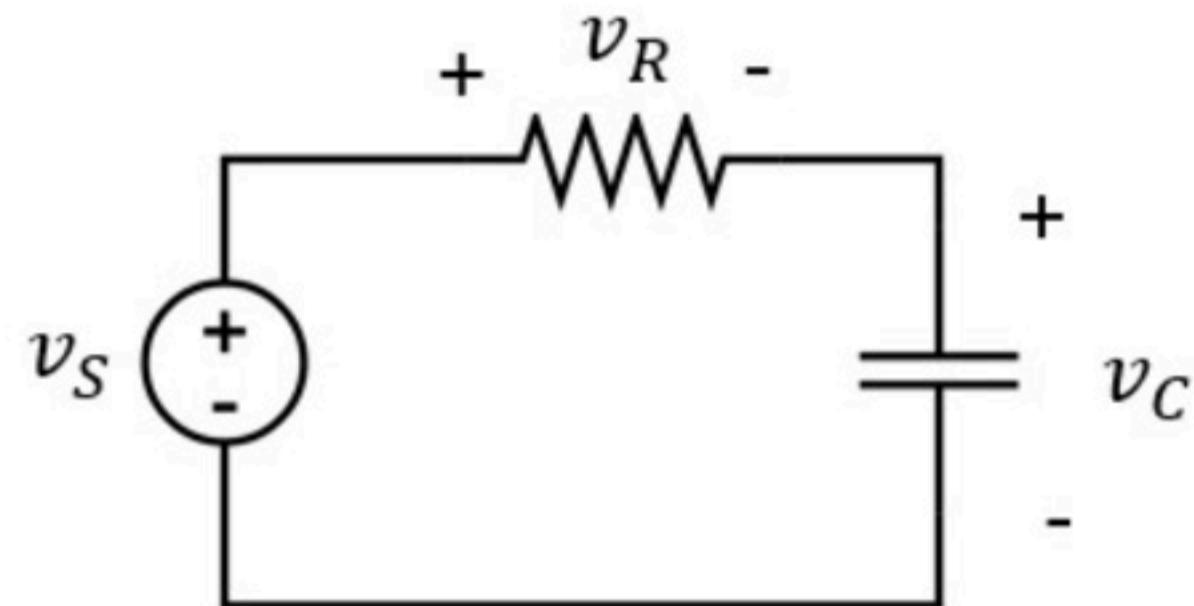Find $v_R = A_3 \cdot \cos(100t + B_3)$ with $-180^\circ \leq B_3 \leq 180^\circ$



Solve without using a calculator.

Given Variables:

A1 : 4 V

B1 : 20 degrees

A2 : 4 V

B2 : -25 degrees

Calculate the following:

A3 (V) :

4



B3 (degrees) :

65



Hint: Convert to phasors. Multiply out the common $\exp(jB)$ factor.

$$\text{You are given } v_s = A_1 \cdot \sqrt{2} \cdot \cos(100t + B_1)$$


$$A1 : 2 \text{ V}$$

$$v_C = A_2 \cdot \cos(100t + B_2)$$

$$B1 : 35 \text{ degrees}$$

$$\text{Find } v_R = A_3 \cdot \cos(100t + B_3) \text{ with } -180^\circ \leq B_3 \leq 180^\circ$$

$$A2 : 2 \text{ V}$$

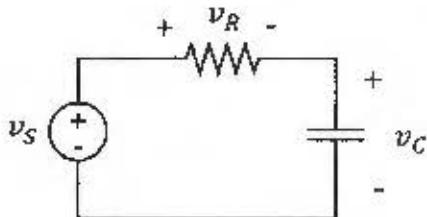

$$B2 : -10 \text{ degrees}$$

Solve without using a calculator.

$$V_s = 2\sqrt{2} e^{j35^\circ} \quad V_c = 2 e^{-j10^\circ}$$

$$\begin{aligned} \text{KVL: } V_R &= V_s - V_c = 2\sqrt{2} e^{j35^\circ} - 2 e^{-j10^\circ} \\ &= 2 e^{j35^\circ} \left(\sqrt{2} - e^{-j45^\circ} \right) \\ &= 2 e^{j35^\circ} \left(\sqrt{2} - \left(\frac{\sqrt{2}}{2} - j \frac{\sqrt{2}}{2} \right) \right) \\ &= 2 e^{j35^\circ} \left(\frac{\sqrt{2}}{2} + j \frac{\sqrt{2}}{2} \right) \\ &= 2 e^{j35^\circ} e^{j45^\circ} \\ &= 2 e^{j80^\circ} \end{aligned}$$

$$\Rightarrow v_R = 2 \cos(100t + 80^\circ)$$

$$A_3 = 2 \text{ V}$$

$$B_3 = 80^\circ$$

Phasors 005

Unlimited Attempts.

Each voltage-current pair below is the voltage across an element and the current through that element, adhering to the passive sign convention (ω is in units of rad/s).

$$v_1(t) = A_1 \cdot \cos(400t + 25^\circ) \quad i_1(t) = B_1 \cdot \sin(400t + 25^\circ)$$

$$v_2(t) = A_2 \cdot \sin(500t + 70^\circ) \quad i_2(t) = B_2 \cdot \sin(500t + 160^\circ)$$

$$v_3(t) = A_3 \cdot \cos(700t + 30^\circ) \quad i_3(t) = B_3 \cdot \sin(700t + 120^\circ)$$

For each element:

- Indicate the type of element. Enter 1 for resistor, 2 for inductor, and 3 for capacitor.
- Find the value of the element. Assume the units are $\text{m}\Omega$, mH or mF respectively.

Given Variables:

A1 : 12 V

B1 : 3 A

A2 : 20 V

B2 : 4 A

A3 : 2 V

B3 : 4 A

Calculate the following:

Type 1 (.) :

2



Value 1 (.) :

10



Type 2 (.) :

3



Value 2 (.) :

0.4



Type 3 (.) :

1



Value 3 (.) :

500



Each voltage-current pair below is the voltage across an element and the current through that element, adhering to the passive sign convention.

$$v_1(t) = A_1 \cdot \cos(400t + 25)$$

$$i_1(t) = B_1 \cdot \sin(400t + 25)$$

$$v_2(t) = A_2 \cdot \sin(500t + 70)$$

$$i_2(t) = B_2 \cdot \sin(500t + 160)$$

$$v_3(t) = A_3 \cdot \cos(700t + 30)$$

$$i_3(t) = B_3 \cdot \sin(700t + 120)$$

$$A1 : 16 V$$

$$B1 : 2 A$$

$$A2 : 32 V$$

$$B2 : 8 A$$

$$A3 : 3 V$$

$$B3 : 30 A$$

For each element:

- a) Indicate the type of element. Enter 1 for resistor, 2 for inductor, and 3 for capacitor.

- b) Find the value of the element. Assume the units are $m\Omega$, mH or mF respectively.

$$\sin(\alpha) = \cos(\alpha - 90^\circ)$$

$$V = Z \cdot I$$

$$Z_L = j\omega L \Rightarrow \angle Z = 90^\circ$$

$$Z_C = \frac{1}{j\omega C} \Rightarrow \angle Z = -90^\circ$$

$$Z_R = R \Rightarrow \angle Z = 0^\circ$$

$$\textcircled{1} \quad V_1 = 16 e^{j25^\circ} \quad I_1 = 2 e^{j(25^\circ - 90^\circ)}$$

$$\angle Z_1 = \angle V_1 - \angle I_1 = 25^\circ - (25^\circ - 90^\circ) = 90^\circ$$

$$|Z_1| = \frac{|V_1|}{|I_1|} = \frac{16}{2} = \omega L \Rightarrow L = \frac{16}{2\pi f} \cdot \frac{1}{400}$$

INDUCTOR

L = 20 mH

$$\textcircled{2} \quad V_2 = 32 e^{j(70^\circ - 90^\circ)} \quad I_2 = 8 e^{j(160^\circ - 90^\circ)}$$

$$\angle Z_2 = \angle V_2 - \angle I_2 = (70^\circ - 90^\circ) - (160^\circ - 90^\circ) = -90^\circ$$

$$|Z_2| = \frac{|V_2|}{|I_2|} = \frac{32}{8} = \frac{1}{\omega C} \Rightarrow C = \frac{1}{500} \cdot \frac{8}{32}$$

CAPACITOR

C = 0.5 mF

$$\textcircled{3} \quad V_3 = 3 e^{j30^\circ} \quad I_3 = 30 e^{j(120^\circ - 90^\circ)}$$

$$\angle Z_3 = \angle V_3 - \angle I_3 = 30^\circ - (120^\circ - 90^\circ) = 0^\circ \Rightarrow$$

RESISTOR

$$|Z_3| = \frac{|V_3|}{|I_3|} = \frac{3}{30} = R \Rightarrow R = \frac{1}{10}$$

R = 100 m\Omega


Phasors 006

Problem has been graded.

Find the steady-state currents $i_1(t)$ and $i_2(t)$.

$$i_1(t) = A_1$$
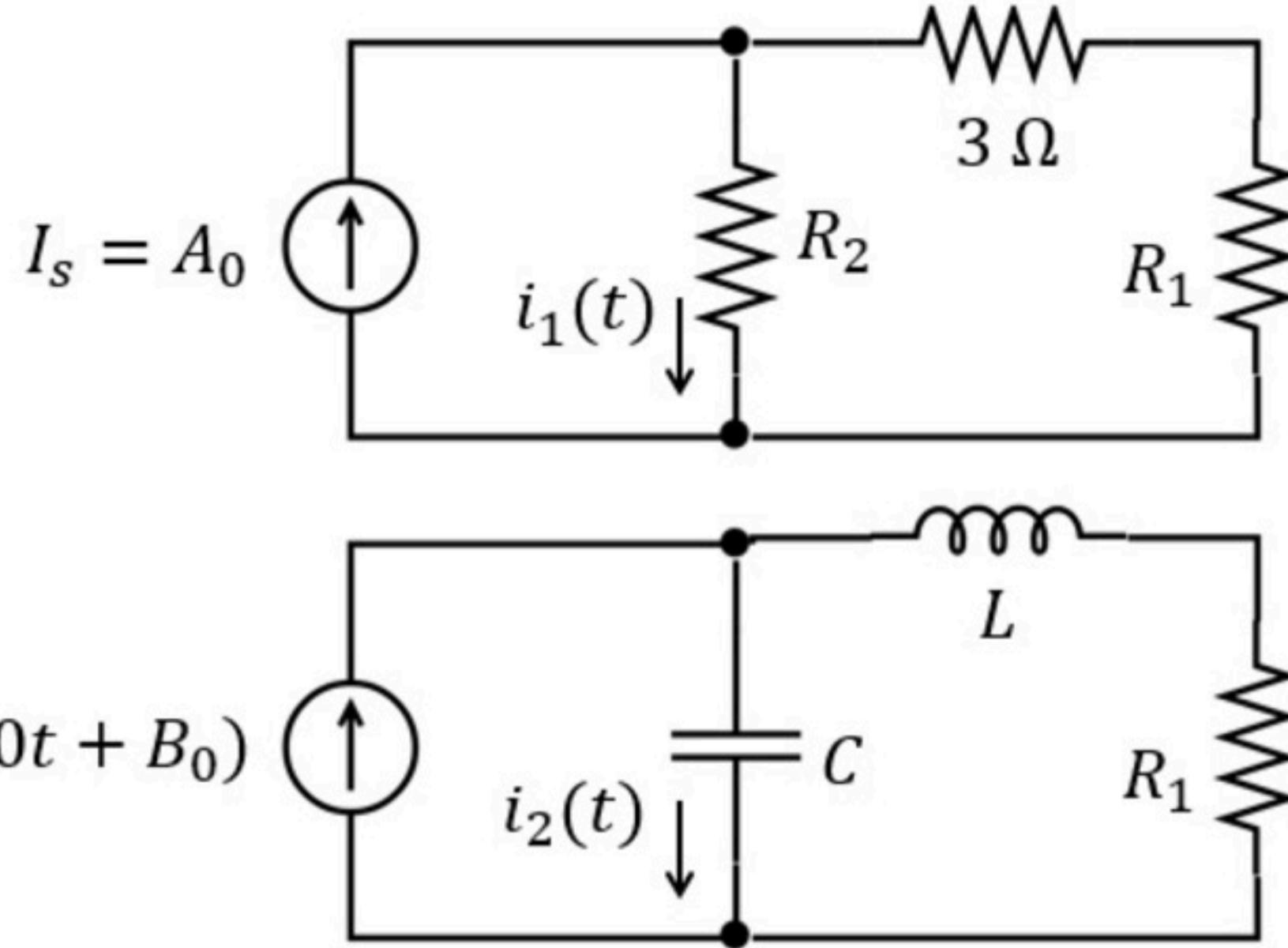
$$i_2(t) = A_2 \cos(1000t + B_2) \quad \text{with } -180^\circ < B_2 \leq 180^\circ$$



Given Variables:

A0 : 2 A

B0 : 25 degrees

C : 200 uF

L : 3 mH

R1 : 6 ohm

R2 : 3 ohm

Calculate the following:

A1 (A) :

1.5



A2 (A) :

1.5



B2 (degrees) :

70



Find the steady-state currents $i_1(t)$ and $i_2(t)$.


A0 : 2 A

$$i_1(t) = A_1$$


B0 : 20 degrees

$$i_2(t) = A_2 \cos(1000t + B_2) \quad \text{with } -180^\circ < B_2 \leq 180^\circ$$

C : 250 μF

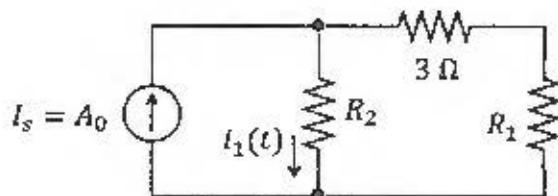

L : 4 mH

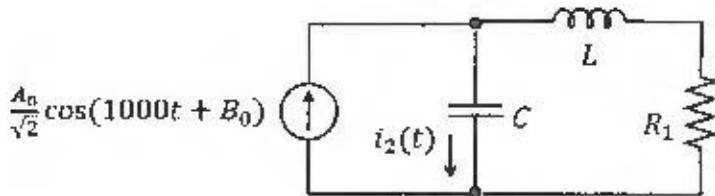


R1 : 4 ohm

R2 : 3 ohm

$$\textcircled{1} \text{ CURRENT DIVIDER. } I_1 = 2 \cdot \frac{3+4}{3+4+3} = \frac{14}{10}$$

$$A_1 = 1.4 \text{ A}$$

\textcircled{2}

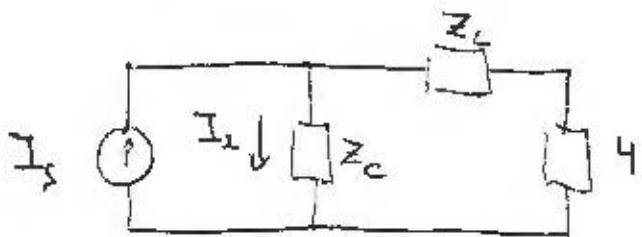

$$Z_L = j\omega L = j 1000 \cdot 4 \cdot 10^{-3} = 4j$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j 1000 \cdot 250 \cdot 10^{-6}} = -4j$$

$$I_s = \frac{2}{\sqrt{2}} \cdot e^{j20^\circ}$$

$$I_2 = I_s \cdot \frac{4j+4}{4j+4-4j} = I_s \cdot \frac{4(1+j)}{4} = \frac{2}{\sqrt{2}} e^{j20^\circ} \sqrt{2} e^{j45^\circ}$$

$$I_2 = 2 e^{j65^\circ}$$

$$i_2(t) = 2 \cos(1000t + 65^\circ)$$

$$A_2 = 2 \text{ A}$$

$$B_2 = 65^\circ$$

Phasors 007


Problem has been graded.

$$v_s(t) = A_1 \sqrt{2} \cdot \cos(W_1 t + B_1)$$

$$i_s(t) = 2 \cdot \cos(W_1 t - 90^\circ) \quad \text{A}$$

Find steady state voltage
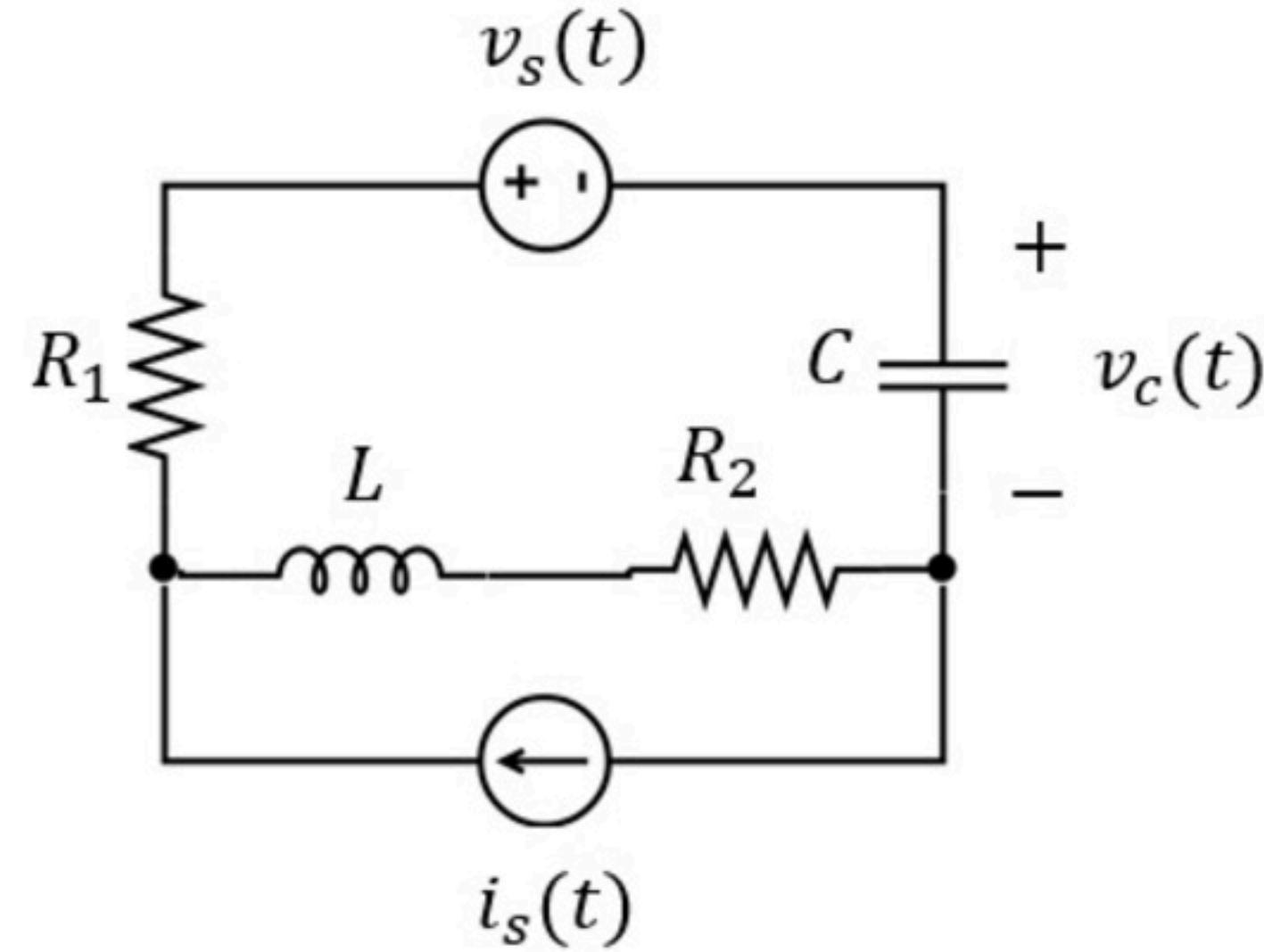
$$v_c(t) = A_2 \sqrt{2} \cdot \cos(W_2 t + B_2) \quad \text{with } -180^\circ < B_2 \leq 180^\circ$$



Given Variables:

A1 : 14 V

B1 : -45 degrees

W1 : 2000 (1/s)

C : 125 uF

L : 2 mH

R1 : 4 ohm

R2 : 4 ohm

Calculate the following:

A2 (V) :

3



B2 (degrees) :

45



W2 (1/s) :

2000



Hint: We do not need to use superposition, but we could if we wanted to.

$$v_s(t) = A_1 \sqrt{2} \cdot \cos(W_1 t + B_1)$$

A1 : 32 V

$$i_s(t) = 2 \cdot \cos(W_1 t - 90^\circ) \quad A$$


B1 : -45 degrees

Find steady state voltage

W1 : 2000 1/s

$$v_c(t) = A_2 \sqrt{2} \cdot \cos(W_2 t + B_2) \quad \text{with } -180^\circ < B_2 \leq 180^\circ$$


C : 125 μF

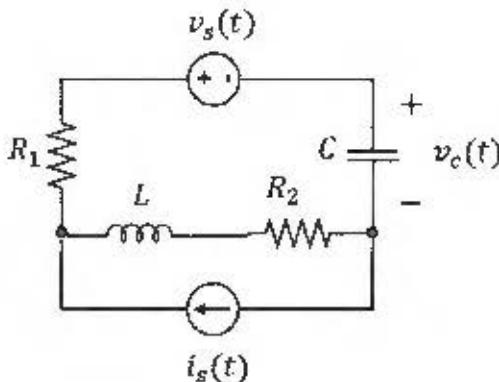

L : 2 mH

R1 : 4 ohm

R2 : 4 ohm

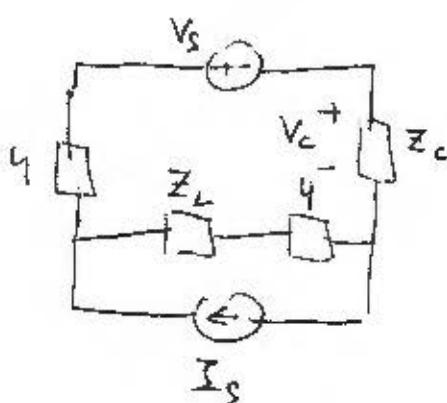

$$Z_C = \frac{1}{j\omega C} = \frac{10^6}{j2000 \cdot 125} = -4j$$

$$Z_L = j\omega L = j2000 \cdot 2 \cdot 10^{-3} = 4j$$

$$V_s = 32\sqrt{2} e^{-j45^\circ} = 32V_1 \left(\frac{\sqrt{2}}{2} - j \frac{\sqrt{2}}{2} \right) \\ = 32 - 32j$$

$$I_s = 2 e^{-j90^\circ} = -2j$$

$$\textcircled{1} \quad \underline{\text{ONLY } V_s} \quad V_{c_1} = -V_s \cdot \frac{Z_C}{Z_C + Z_L + 4 + 4} = \frac{(-32 + 32j) \cdot (-4j)}{-4j + 4j + 4 + 4} = \frac{-32}{8} (-32 + 32j) \\ = 16 + 16j$$

$$\textcircled{2} \quad \underline{\text{ONLY } I_s} : \quad V_{c_2} = I_s \cdot \frac{Z_L + 4}{Z_L + 4 + Z_C + 4} Z_C = (-2j) \frac{4 + 4j}{4 - 4j + 4j + 4} \cdot (-4j) \\ = -\frac{8(4 + 4j)}{8} = -4 - 4j$$

$$\textcircled{3} \quad \underline{\text{SUPERPOSITION}} : \quad V_c = V_{c_1} + V_{c_2} = 16 + 16j = 16\sqrt{2} e^{j45^\circ}$$

$$V_c(t) = 16\sqrt{2} \cos(2000t + 45^\circ)$$

$A_2 = 12V$
$B_2 = 45^\circ$

$W_2 = 2000 \frac{1}{s}$


Phasors 008

Unlimited Attempts.

$$v_s(t) = A_1 \cdot \cos(1000t)$$

Find steady state voltage
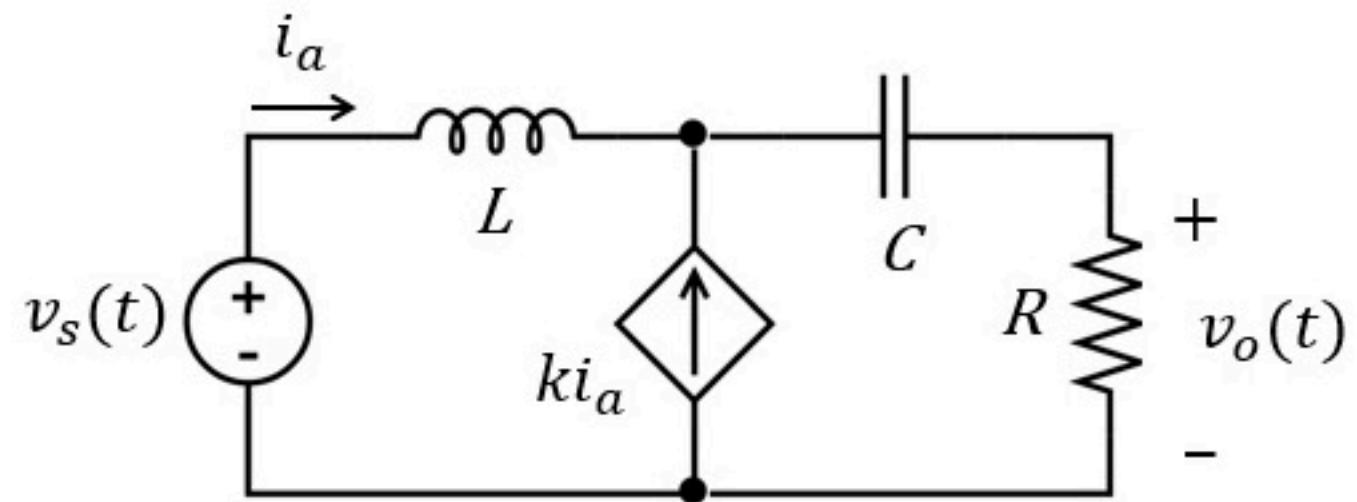
$$v_o(t) = A_2 \sqrt{2} \cdot \cos(1000t + B_2) \quad \text{with } -180^\circ < B_2 \leq 180^\circ$$



Given Variables:

A1 : 5 V

L : 20 mH

C : 20 uF

R : 45 ohm

k : 3 A/A

Calculate the following:

A2 (V) :

2.5



B2 (degrees) :

45



$$v_s(t) = A_1 \cdot \cos(1000t)$$

$$A_1 : 2 \text{ V}$$

Find steady state voltage


$$v_o(t) = A_2 \sqrt{2} \cdot \cos(1000t + B_2) \quad \text{with } -180^\circ < B_2 \leq 180^\circ$$

$$L : 150 \text{ mH}$$


$$C : 20 \mu\text{F}$$

$$R : 25 \text{ ohm}$$

$$k : 1 \text{ A/A}$$

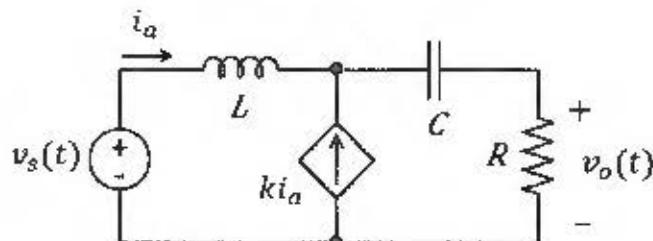

$$I_i = I_a + I_a = 2 I_a$$

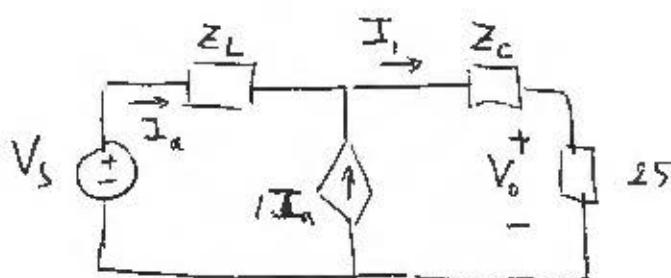

$$Z_L = j\omega L = j 150$$

$$Z_C = \frac{1}{j\omega C} = -j 50$$

$$V_s = 2$$

$$\underline{KVL}: V_s - I_a \cdot Z_L = I_i (Z_C + 25) = 2 I_a (Z_C + 25)$$

$$\Rightarrow I_a = \frac{V_s}{Z_L + 2 Z_C + 50} = \frac{V_s}{150j - 100j + 50} = \frac{V_s}{50 + 50j}$$

$$V_o = I_i \cdot 25 = 2 I_a \cdot 25 = \frac{50 \cdot V_s}{50 + 50j} = \frac{2}{1+j}$$

$$= \frac{2}{\sqrt{2}} e^{-j45^\circ} = \sqrt{2} e^{-j45^\circ}$$

$$v_o(t) = \sqrt{2} \cos(1000t - 45^\circ)$$

$$A_2 = 1 \text{ V}$$

$$B_2 = -45^\circ$$

Phasors 009


0 of 5 attempts made

$$i_s(t) = A_1 \cdot \cos\left(1000t + \frac{\pi}{2}\right) + A_2 \cdot \cos\left(2000t - \frac{\pi}{2}\right)$$

Assume the system is in steady state. Find the current i_a at times

$$t_1 = 4\pi \text{ ms: } i_a(t_1) = B_1$$
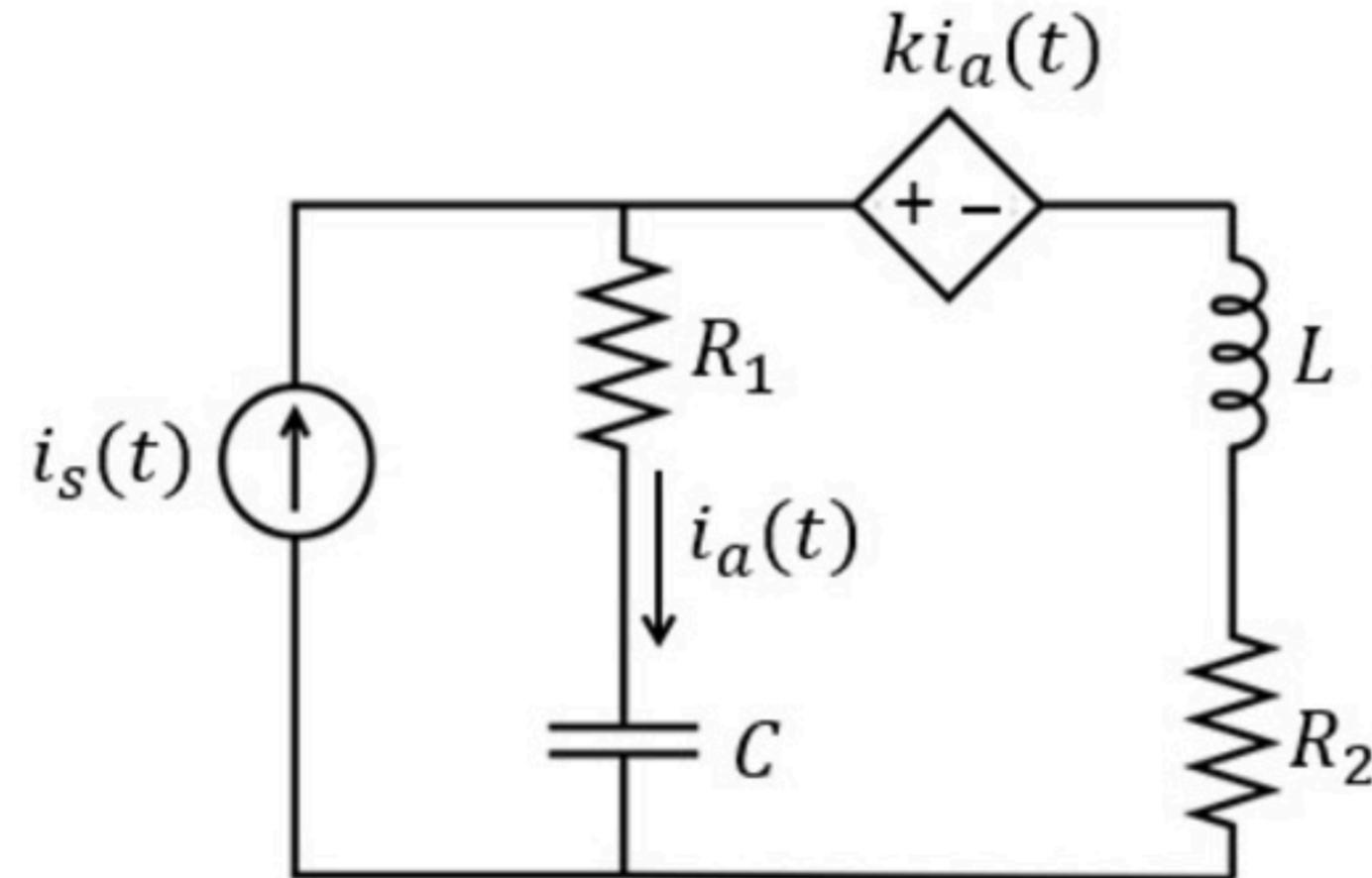
$$t_2 = 5\pi \text{ ms: } i_a(t_2) = B_2$$



Given Variables:

A1 : 1 A

A2 : 1 A

L : 1 mH

C : 250 uF

R1 : 1 ohm

R2 : 2 ohm

k : 4 V/A

Calculate the following:

B1 (A) :

-2.5



B2 (A) :

-1.5



$$i_s(t) = A_1 \cdot \cos(1000t + 90^\circ) + A_2 \cdot \cos(2000t - 90^\circ)$$

A1 : 6 A

Assume the system is in steady state. Find the current i_a at times


A2 : 9 A

$$t_1 = 4\pi \text{ ms}: i_a(t_1) = B_1$$

L : 1 mH

$$t_2 = 5\pi \text{ ms}: i_a(t_2) = B_2$$

C : 250 μF

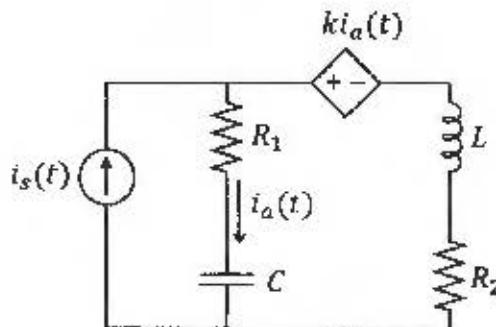

2 DIFFERENT ω !

WE NEED TO
USE SUPERPOSITION

R1 : 8 ohm

R2 : 2 ohm

k : 1 V/A

$$\underline{\omega = 1000}, \quad Z_L = j \cdot 1000 L = j$$


$$Z_C = \frac{1}{j \omega C} = -4j$$

$$I_s = 6 e^{j\frac{\pi}{2}} = 6j$$

$$Z_L = j 2000 L = 2j$$

$$Z_C = \frac{1}{j 2000 C} = -2j$$

$$I_s = 9 e^{-j\frac{\pi}{2}} = -9j$$

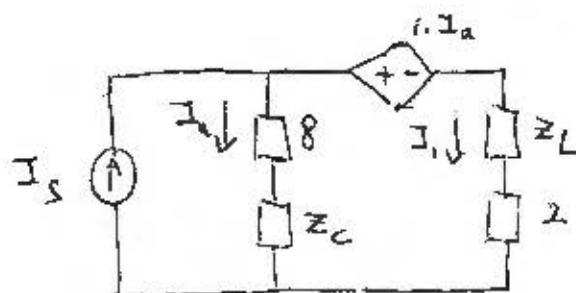

$$\underline{\omega = 2000}$$

$$I_a = I_s - I_a \Rightarrow I_a (8 + Z_C) = 1 \cdot I_a + (I_s - I_a)(2 + Z_L)$$

$$\Rightarrow I_a = I_s - \frac{2 + Z_L}{9 + Z_C + Z_L}$$

$$\textcircled{1} \quad \underline{\omega = 1000}: \quad I_a = 6j \frac{(2+j)}{(9-4j+j)} = \frac{6(-1+2j)}{3(3-j)} \frac{(3+j)}{(3+j)} = \frac{2}{10} (-5+5j) = -1+j$$

$$i_{a1}(t) = \sqrt{2} \cos(1000t + 135^\circ)$$

$$\textcircled{2} \quad \underline{\omega = 2000}: \quad I_a = (-9j) \frac{2+2j}{9+3j-1} = 2(1-j) \Rightarrow i_{a2}(t) = 2\sqrt{2} \cos(2000t - 45^\circ)$$

$$\textcircled{3} \quad i_a(t) = i_{a1}(t) + i_{a2}(t) = \sqrt{2} \cos(1000t + \frac{3\pi}{4}) + 2\sqrt{2} \cos(2000t - \frac{\pi}{4})$$

$$\textcircled{4} \quad E = 4\pi \cdot 10^{-3} \quad i_a = \sqrt{2} \cos(4\pi + \frac{3\pi}{4}) + 2\sqrt{2} \cos(8\pi - \frac{\pi}{4}) = \sqrt{2} \cos(\frac{11\pi}{4}) + 2\sqrt{2} \cos(-\frac{\pi}{4}) \\ = \sqrt{2} \left(-\frac{\sqrt{2}}{2}\right) + 2\sqrt{2} \left(\frac{\sqrt{2}}{2}\right) = -1 + 2 = 1 \quad \boxed{B_1 = 1 \text{ A}}$$

$$E = 5\pi \cdot 10^{-3}, \quad i_a = \sqrt{2} \cos(5\pi + \frac{3\pi}{4}) + 2\sqrt{2} \cos(10\pi - \frac{\pi}{4}) = \sqrt{2} \cos(-\frac{\pi}{4}) + 2\sqrt{2} \cos(-\frac{\pi}{4})$$

$$= \sqrt{2} \left(\frac{\sqrt{2}}{2}\right) + 2\sqrt{2} \left(\frac{\sqrt{2}}{2}\right) = 1 + 2 = 3$$

$$\boxed{B_2 = 3 \text{ A}}$$


Phasors 010

Problem has been graded.

$$v_s(t) = A_1 \cdot \cos(100t) \quad \text{and} \quad i_s(t) = A_2$$

Find $i_a(t) = A_3\sqrt{2} \cdot \cos(100t + B_3) + A_4$

with $-180^\circ < B_3 \leq 180^\circ$

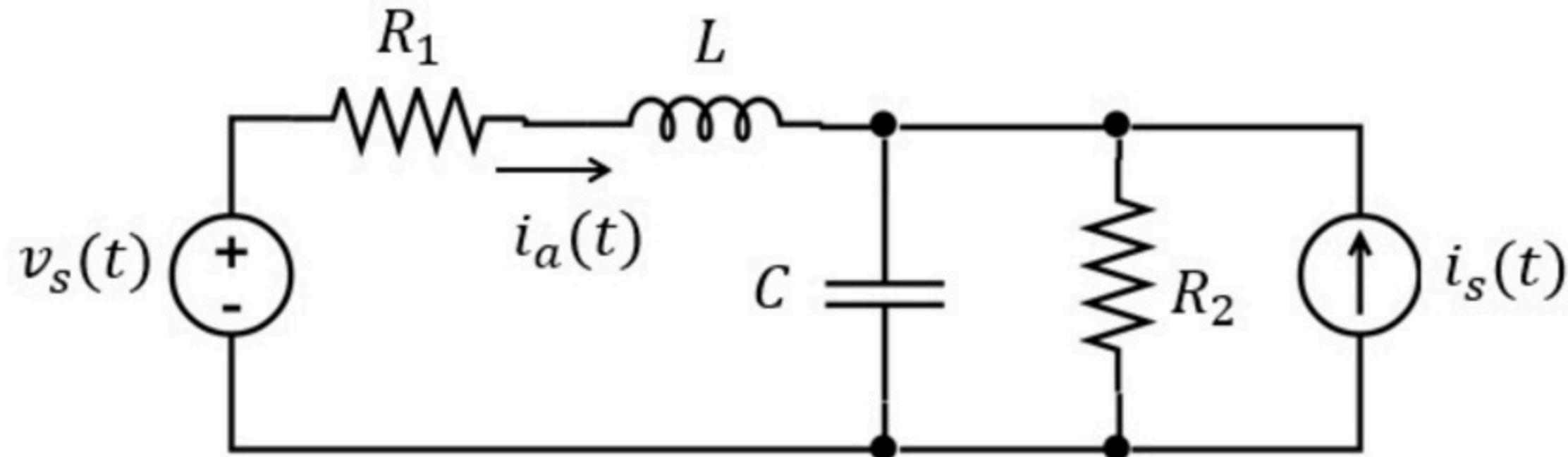

Given Variables:

A1 : 100 V

A2 : 6 A

C : 0.1 mF

L : 1.5 H

R1 : 50 ohm

R2 : 100 ohm

Calculate the following:

A3 (A) :

0.5



B3 (degrees) :

-45



A4 (A) :

-4



Hint: Use superposition

$$v_s(t) = A_1 \cdot \cos(100t) \quad \text{and} \quad i_s(t) = A_2$$

A1 : 100 V

$$\text{Find } i_a(t) = A_3 \sqrt{2} \cdot \cos(100t + B_3) + A_4$$

$$\text{with } -180^\circ < B_3 \leq 180^\circ$$


A2 : 6 A

C : 0.1 mF

L : 1.5 H

R1 : 50 ohm

R2 : 100 ohm

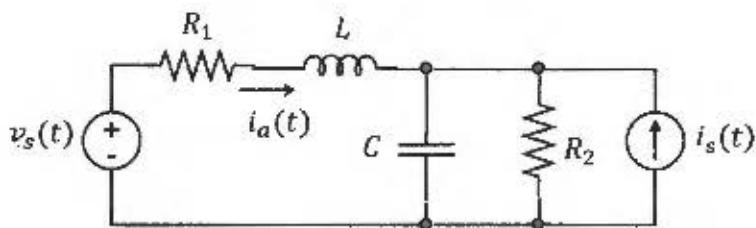


DIFFERENT ω ! WE NEED TO USE SUPERPOSITION

① $i_s(t)$ ONLY : $\omega = 0$ DC \Rightarrow L SHORT / C OPEN



$$E_{u_1} = -\frac{100}{100+50} \cdot 6 = -4 \text{ A}$$

② $v_s(t)$ ONLY : $\omega = 100$

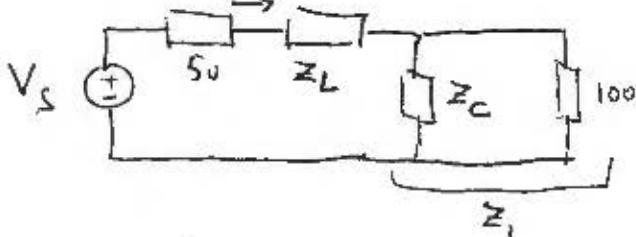

$$Z_L = j 100 L = 150 j$$

$$Z_C = \frac{1}{j 100 C} = -100 j$$

$$V_S = 100$$

$$Z_i = \frac{1}{\frac{1}{50} + \frac{1}{-j 100}} = \frac{100}{1+j} = 50(1-j)$$

$$I_A = \frac{V_S}{Z_i + 50 + Z_L} = \frac{100}{50 - 50j + 50 + 150j} = \frac{100}{100 + 100j} = \frac{\sqrt{2}}{2} e^{-j45^\circ}$$

$$i_{a_2} = \frac{\sqrt{2}}{2} \cos(100t - 45^\circ)$$

$$③ i_a(t) = i_{a_1} + i_{a_2} = \frac{\sqrt{2}}{2} \cos(100t - 45^\circ) - 4$$

$A_3 = 0.5 \text{ A}$

$B_3 = -45^\circ$


$A_4 = -4 \text{ A}$

Phasors 011

Unlimited Attempts.

In the circuit below, $v_s(t) = A_1 \cdot \cos(25 \cdot 10^4 \cdot t)$.

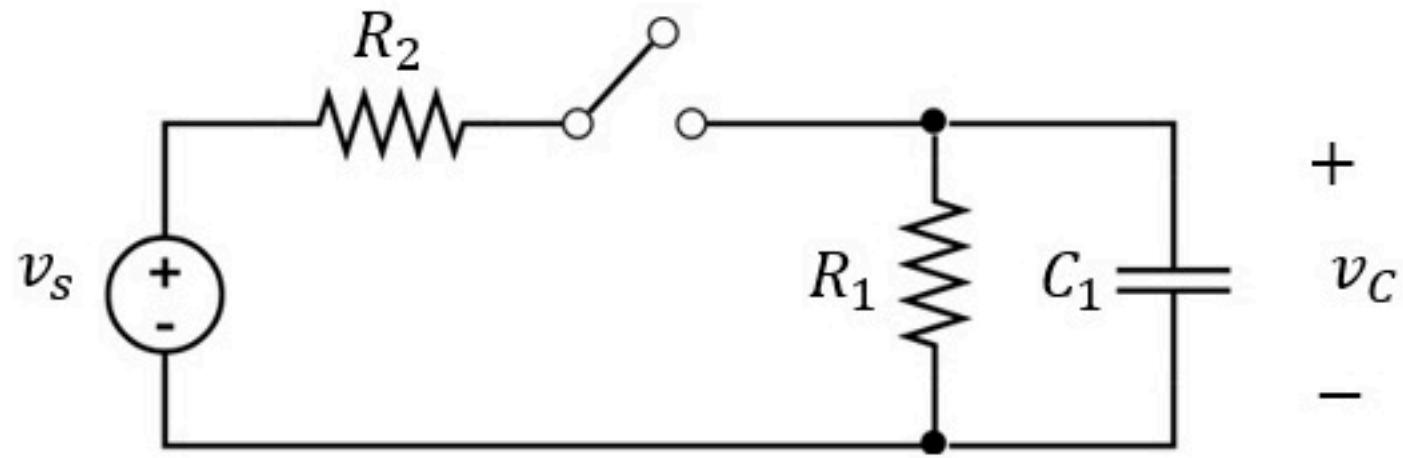The switch is closed for $t < 0$, and opens at time $t = 0$ s.



Find these voltages:

$$v_1 = v_C(0^+) \quad v_2 = v_C(t_0)$$

Note, for your calculations, use: $e^{-1/1.5} \approx 0.5$

Solve without a calculator

Given Variables:

R1 : 6 kohm

R2 : 12 kohm

C1 : 1 nF

A1 : 12 V

t0 : 8 us

Calculate the following:

v1 (V) :

2



v2 (V) :

0.5




In the circuit below, $v_s(t) = A_1 \cdot \cos(25 \cdot 10^4 \cdot t)$.

R1 : 6 kohm

The switch is closed for $t < 0$, and opens at time $t = 0$ s.

R2 : 12 kohm

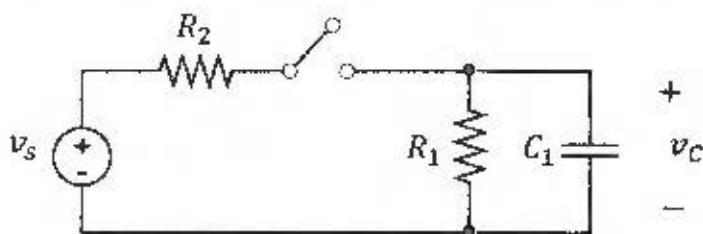

C1 : 1 nF

A1 : 12 V

t0 : 8 us


Find these voltages:

$$v_1 = v_c(0^+) \quad v_2 = v_c(t_0)$$

Note, for your calculations, use: $e^{-1/1.5} \approx 0.5$

Solve without a calculator

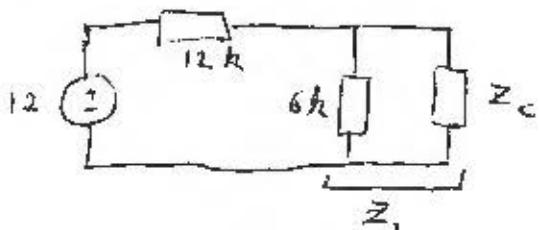① $t < 0$ ASSUME STEADY STATE ② $t = 0^-$



$$Z_c = \frac{1}{j 25 \cdot 10^4 \cdot 10^{-9}} = -(4k) \cdot j$$

$$Z_1 = \frac{1}{\frac{1}{6k} + \frac{j}{4k}} = \frac{24k}{4+6j} = \frac{12k}{2+3j}$$

$$V_c = V_s \frac{Z_1}{Z_1 + R_2} = 12 \cdot \frac{12}{12 + 12(2+3j)} = \frac{12}{3+3j} = \frac{4}{1+j} = \frac{4}{\sqrt{2}} e^{-j45^\circ}$$

$$v_c(t) = \frac{4}{\sqrt{2}} \cos(25 \cdot 10^4 t - \frac{\pi}{4}) \Rightarrow v_c(0^-) = \frac{4}{\sqrt{2}} \cos(-\frac{\pi}{4}) = \frac{4}{\sqrt{2}} \cdot \frac{\sqrt{2}}{2} = 2V$$

$$\textcircled{2} \quad \underline{t = 0^+} \quad v_c(0^+) = v_c(0^-) = 2V \Rightarrow \boxed{v_1 = 2V}$$

③ $t > 0$: TRANSIENT RESPONSE OF RC CIRCUIT

$$v_c(0^+) = 2V \quad R_{TH} = R_1 \Rightarrow Z = R_1 \cdot C$$

$$v_c(\infty) = 0V$$

$$= (6k) \cdot (1n) = 6 \text{ m}\Omega$$

$$v_c(t) = 2 e^{-\frac{t}{6m\Omega}} \quad \text{FOR } t > 0$$

$$v_c(t_0) = v_c(8 \mu s) = 2 e^{-\frac{8}{6}} = 2 \left(e^{-\frac{4}{3}} \right)^2 = \frac{2}{4} = \frac{1}{2}V$$

$$\boxed{v_2 = 0.5V}$$

Phasors 016


2 of 5 attempts made

The AC circuit below is in steady-state, and you are not told the ω of the source. The phasor diagram shows the phasors of i_s and i_a .

The rectangular boxes represent two circuit elements. One of them is an inductor L_1 (but you don't know if it corresponds to i_a or i_b). The other can be a resistor R_2 , a capacitor C_2 or an inductor L_2 .

You are also told that the maximum value of $i_a(t)$ is A_1 and the maximum value of $i_s(t)$ is A_2 .

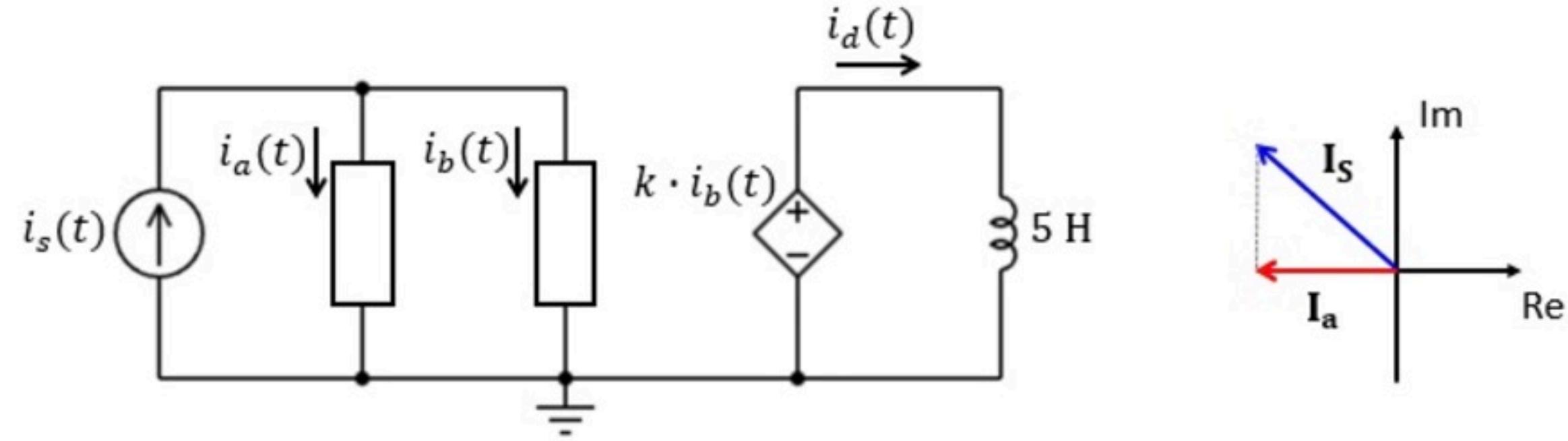- What is the maximum value of the $i_b(t)$ waveform, i_{bmax} ?
- With $i_d(t)$ expressed as $A \cdot \cos(\omega t + B_1)$, what is B_1 ? Constraints: $A > 0$ and $-180^\circ < B_1 \leq 180^\circ$.
- What is the value of ω ?



Given Variables:

$A_1 : 4 \text{ A}$

$A_2 : 5 \text{ A}$

$L_1 : 2 \text{ mH}$

$R_2 : 3 \text{ ohm}$

$C_2 : 10 \text{ mF}$

$L_2 : 3 \text{ mH}$

$k : -5 \text{ V/A}$

Calculate the following:

$i_{bmax} (\text{A}) :$

3



$B_1 (\text{degrees}) :$

180



$\omega (\text{rad/s}) :$

2000



The AC circuit below is in steady-state, and you are not told the ω of the source. The phasor diagram shows the phasors of i_s and i_a .



The rectangular boxes represent two circuit elements. One of them is an inductor L_1 (but you don't know if it corresponds to i_a or i_b). The other can be a resistor R_2 , a capacitor C_2 or an inductor L_2 .

You are also told that the maximum value of $i_a(t)$ is A_1 and the maximum value of $i_s(t)$ is A_2 .

a. What is the maximum value of the $i_b(t)$ waveform, $i_{b,\max}$?

b. With $i_d(t)$ expressed as $A \cdot \cos(\omega t + B_1)$, what is B_1 ? Constraints: $A > 0$ and $-180^\circ < B_1 \leq 180^\circ$.

c. What is the value of ω ?

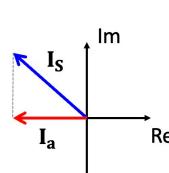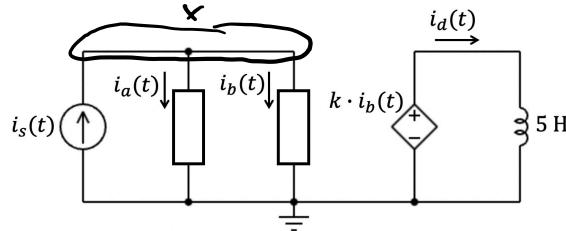

$$A_1 = 4 \text{ A}$$

$$A_2 = 5 \text{ A}$$

$$L_1 = 2 \text{ mH}$$

$$R_2 = 3 \Omega$$


$$C_2 = 10 \text{ mF}$$

$$L_2 = 3 \text{ mH}$$

$$k = -5 \frac{\text{V}}{\text{A}}$$

a. The max value of a sinusoidal waveform is its amplitude $\Rightarrow i_{b,\max} = |I_b|$
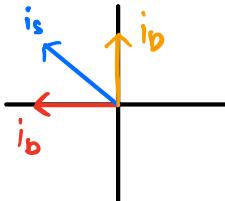
$$\text{KCL at } X : i_s = i_a + i_b \Rightarrow$$



$$\Rightarrow |I_s|^2 = |I_a|^2 + |I_b|^2$$

$$|I_b| = \sqrt{|I_s|^2 - |I_a|^2} = \sqrt{5^2 - 4^2} = \sqrt{25 - 16} = \sqrt{9} = 3 \Rightarrow i_{b,\max} = 3 \text{ A}$$

b. We can see that $I_d = \frac{k \cdot I_b}{j\omega S}$

from part a, $|I_b| = 3 \Rightarrow I_b = 3e^{j\frac{\pi}{2}}$

$$I_d = \frac{-S \cdot 3e^{j\frac{\pi}{2}}}{j\omega S} = \frac{-3e^{j\pi/2}}{j\omega} = -\frac{3}{\omega} = \frac{3}{\omega} e^{j\pi} \Rightarrow i_d(t) = \frac{3}{\omega} \cos(\omega t + \pi) \Rightarrow B_1 = 180^\circ$$

c. Assume Z_a is a resistor and Z_b is the known inductor (I_a goes through Z_a , I_b goes through Z_b)

Define V_a as voltage across Z_a , and V_b across $Z_b \Rightarrow V_a = V_b$ since they are in parallel

Plot the phasors roughly and see if assumption holds


We can see that the resistor current is in phase with the voltage and inductor voltage is ahead of the current

\Rightarrow our assumption is correct ✓

$$Z_a = R_2, Z_b = j\omega L_1 \quad \left. \right\} \quad V_a = V_b \Rightarrow 3 \cdot 4 e^{j\pi} = j\omega \cdot (2 \times 10^{-3}) \cdot 3 e^{j\pi/2}$$

$$V_a = R_2 I_a, V_b = j\omega L_1 I_b \quad \left. \right\} \quad \omega = \frac{3 \cdot 4}{(2 \times 10^{-3}) \cdot 3}$$

$$\omega = 2000 \text{ rad/s}$$

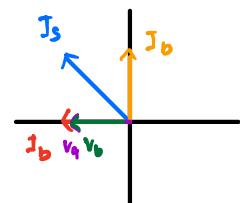


Phasors 017

Problem has been graded.

The circuit below represents an AC circuit in steady-state in the phasor domain (for the complex numbers, you may assume units are V, A, Ω, etc. as appropriate). Both sources in the circuit have the same ω , but you are not told the value of ω . Each box represents the impedance of a single circuit element (a resistor, capacitor or inductor).

- What are the maximum values of waveforms $v_S(t)$ and $i_S(t)$? Enter your answers as Y_1 and Y_2 , with $Y_1 = \frac{v_{Smax}}{\sqrt{2}}$ and $Y_2 = i_{Smax}$.
- We now double ω of both sources but keep everything else the same (such as the capacitor, inductor and resistor values; the amplitude and phase of the sources, etc.). Find the new value of all complex numbers in the circuit (the new value of a_1 is called a_2 , etc.) as well as the new magnitude of the current source $|I_S| = X_2$.

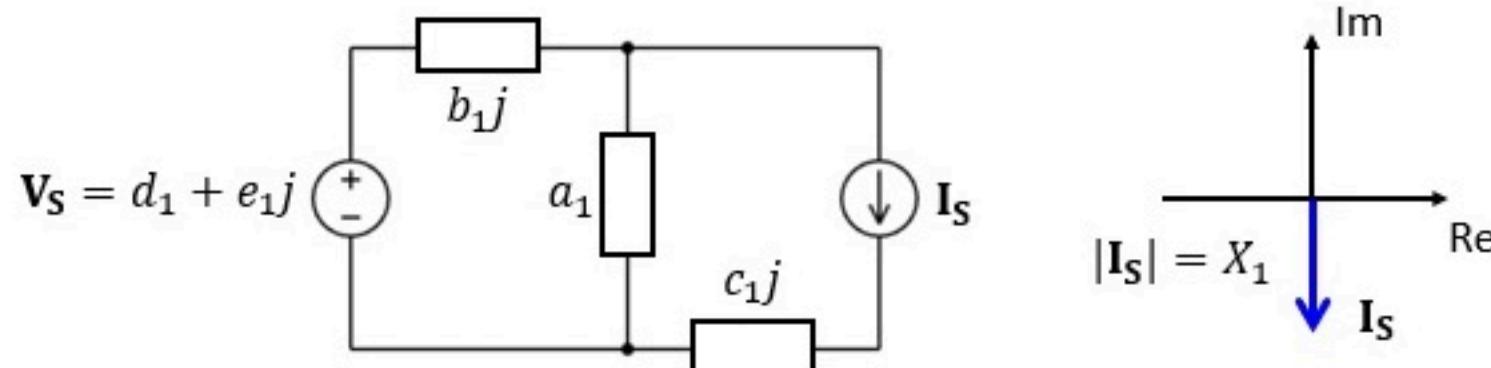

Given Variables:

$a1 : 30$

$b1 : -10$

$c1 : 5$

$d1 : 6$

$e1 : 6$

$X1 : 5 \text{ A}$

Calculate the following:

$Y1 (\text{V}) :$

5.999999999999999



$Y2 (\text{A}) :$

5



$a2 :$

30



$b2 :$

-5



$c2 :$

10



$d2 :$

6



$e2 :$

6




$X2 (\text{A}) :$

5



The circuit below represents an AC circuit in steady-state in the phasor domain (for the complex numbers, you may assume units are V, A, Ω, etc. as appropriate). Both sources in the circuit have the same ω, but you are not told the value of ω. Each box represents the impedance of a single circuit element (a resistor, capacitor or inductor).

- What are the maximum value of $v_S(t)$ and $i_S(t)$, called v_{Smax} and i_{Smax} respectively?
For v_{Smax} , find Y_1 such that $v_{Smax} = Y_1 \sqrt{2}$.
- We now double ω of both sources but keep everything else the same (such as the capacitor, inductor and resistor values; the amplitude and phase of the sources, etc.). Find the new value of all complex numbers in the circuit (the new value of a_1 is called a_2 , etc.) as well as the new magnitude of the current source $|I_S| = X_2$.

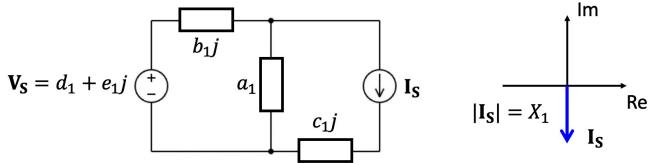

$$\begin{aligned}a_1 &= 50 \\b_1 &= -20 \\c_1 &= 10 \\d_1 &= 1 \\e_1 &= 1 \\X_1 &= SA\end{aligned}$$

- The max value of a sinusoidal waveform is its amplitude

$$v_{S,\max} = |V_S| = \sqrt{d_1^2 + e_1^2} = \sqrt{1^2 + 1^2} = \sqrt{2} \Rightarrow Y_1 = 1$$

$$i_{S,\max} = |I_S| = X_1 \Rightarrow i_{S,\max} = SA$$

- Analyze which elements have a dependence on ω

$$a_1 \text{ is the impedance of a resistor } \Rightarrow Z_R = 50, \text{ this has no dependence on } \omega \text{ so if } \omega \rightarrow 2\omega, 50 \rightarrow 50 \Rightarrow a_2 = 50$$

$b_1 j \Rightarrow -20j$ is the impedance of a capacitor

$$Z_C = \frac{1}{j\omega C} \Rightarrow \text{if } \omega \rightarrow 2\omega, \text{ then } \frac{1}{j2\omega C} = \frac{1}{2(j\omega C)} = \frac{1}{2} \cdot \frac{1}{j\omega C} = \frac{1}{2} Z_C$$

$$\text{if } \omega \rightarrow 2\omega, \text{ then } -20j \rightarrow \frac{1}{2}(-20j) = -10j \Rightarrow b_2 = -10$$

$c_1 j \Rightarrow 10j$ is the impedance of an inductor

$$Z_L = j\omega L \Rightarrow \text{if } \omega \rightarrow 2\omega, \text{ then } j2\omega L = 2(j\omega L) = 2Z_L$$

$$\text{if } \omega \rightarrow 2\omega, \text{ then } 10j \rightarrow 2(10j) = 20j \Rightarrow c_2 = 20$$

$V_S = d_1 + e_1 j = 1 + j$ is the phasor for a source $v_S(t) = \frac{\sqrt{2}}{2} \cos(\omega t + \frac{\pi}{4})$

$$\text{if } \omega \rightarrow 2\omega, \text{ then } v_S(t) = \frac{\sqrt{2}}{2} \cos(2\omega t + \frac{\pi}{4}) \Rightarrow V_S = \frac{\sqrt{2}}{2} e^{j\frac{\pi}{4}} = 1 + j \Rightarrow$$

$$\begin{aligned}d_2 &= 1 \\e_2 &= 1\end{aligned}$$

\Rightarrow the phasor for a voltage waveform does not depend on ω

$$\text{Similarly, } i_S(t) = S \cos(\omega t - \frac{\pi}{2}) \text{ if } \omega \rightarrow 2\omega, i_S(t) = S \cos(2\omega t - \frac{\pi}{2}) \Rightarrow X_2 = SA$$

Phasors 018



0 of 5 attempts made

In the circuit below, the switch moves from position 1 to position 2 at time $t = 0$. For $t < 0$ (switch in position 1), you may assume that the system is in steady state. The voltage source is sinusoidal with $\omega = W_1$.

The diagram shows two phasors, **A** and **B**. (Note that the phasors are not drawn to scale. Also, we show three diagrams to illustrate the situation depending on the value of a you were given. You need to select the diagram that corresponds to your given value.) In your diagram, one phasor represents the capacitor voltage v_C and the other the resistor voltage v_R (but you are not told which one is which).

- Find $i_1 = i_R(0^-)$ (i.e., just before the switch moves to position 2).
- Find $i_2 = i_R(0^+)$ (i.e., just after the switch moves to position 2).

$$|A| = X\sqrt{2}$$

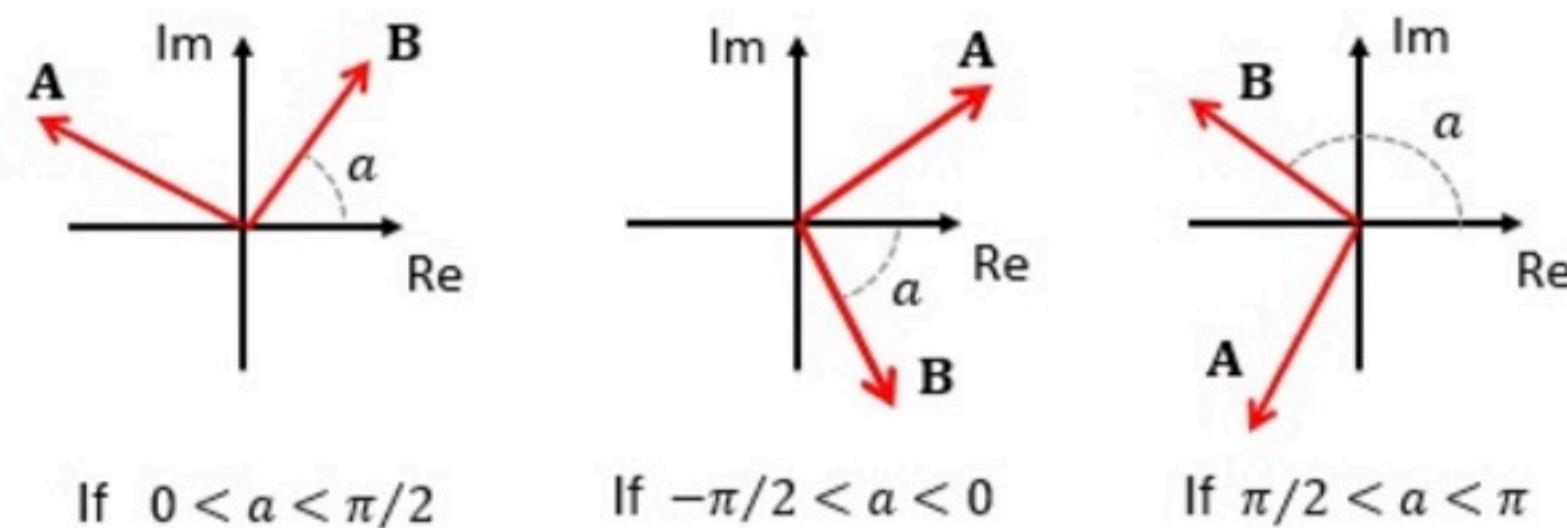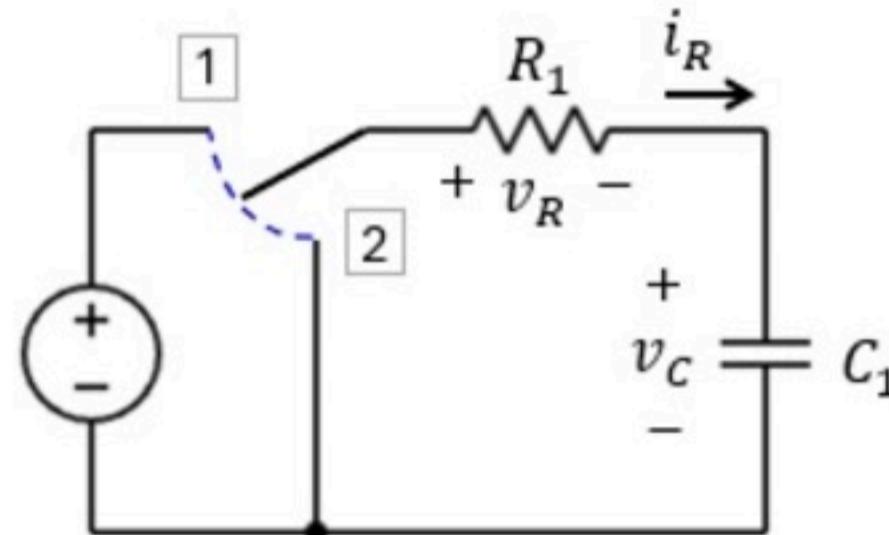

Given Variables:

$W_1 : 1 \text{ rad/s}$

$X : 25$

$a : -45 \text{ degrees}$

$R_1 : 5 \text{ ohm}$

$C_1 : 1 \text{ F}$

Calculate the following:

$i_1 (\text{A}) :$

5



$i_2 (\text{A}) :$

-1





In the circuit below, the switch moves from position 1 to position 2 at time $t = 0$. For $t < 0$ (switch in position 1), you may assume that the system is in steady state. The voltage source is sinusoidal with $\omega = W_1$.

The diagram shows two phasors, **A** and **B**. (Note that the phasors are not drawn to scale. Also, we show three diagrams to illustrate the situation depending on the value of a you were given. You need to select the diagram that corresponds to your given value.) In your diagram, one phasor represents the capacitor voltage v_C and the other the resistor voltage v_R (but you are not told which one is which).

- Find $i_1 = i_R(0^-)$ (i.e., just before the switch moves to position 2).
- Find $i_2 = i_R(0^+)$ (i.e., just after the switch moves to position 2).

$$|A| = X\sqrt{2}$$

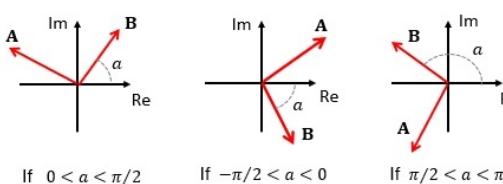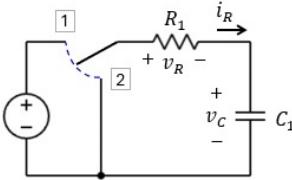

$$\omega_1 = 1 \text{ rad/s}$$

$$X = 10$$


$$q = 45^\circ$$

$$P_1 = 2 \text{ W}$$

$$C_1 = 1 \text{ F}$$

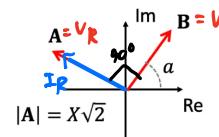a. Assume $A = V_R$ and $B = V_C$

We plot I_R such that it is in phase with V_R



$I_R = I_C$ since the resistor is series with the capacitor

\Rightarrow the capacitor current is ahead of the capacitor voltage \Rightarrow our assumption is correct ✓

At $t = 0^-$

$$V_R = X\sqrt{2} e^{j(a + 90^\circ)} = 10\sqrt{2} e^{j135^\circ}$$

$$i_R = \frac{V_R}{R_1} = \frac{10\sqrt{2} e^{j135^\circ}}{2} = 5\sqrt{2} e^{j135^\circ}$$

$$i_R(t) = 5\sqrt{2} \cos(t + 135^\circ)$$

$$i_R(0^-) = 5\sqrt{2} \cos(0 + 135^\circ) = 5\sqrt{2} \cdot \left(-\frac{\sqrt{2}}{2}\right) \Rightarrow i_1 = -5\text{A}$$

b. At $t = 0^+$, the capacitor voltage cannot change instantaneously


$$Z_C = \frac{1}{j\omega_1 C_1} = \frac{1}{j(1)(1)} = -j$$

$$V_C = i_R \cdot Z_C = 5\sqrt{2} e^{j135^\circ} \cdot -j = 5\sqrt{2} e^{j45^\circ}$$

$$V_C(t) = 5\sqrt{2} \cos(t + 45^\circ)$$

$$V_C(0^+) = 5\sqrt{2} \cos(0 + 45^\circ) = 5\sqrt{2} \cdot \left(\frac{\sqrt{2}}{2}\right) = 5\text{V} \Rightarrow V_C(0^+) = 5\text{V}$$

at $t = 0^+$

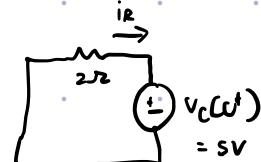

$$i_R(0^+) = \frac{-5}{2} \text{ A}$$



$$i_2 = -2.5 \text{ A}$$

Phasors 019

0 of 5 attempts made

The AC circuit below has $\omega = W_1$ and is in steady state. The phasor diagram shows the phasors of v_s and i_s . You are given the angle a , and vector lengths $|I_s| = A_1$ and $|V_s| = A_2\sqrt{b}$. The diagram is not necessarily drawn to scale (but V_s is along the imaginary axis). The element in the center (rectangular box) is either an inductor or a capacitor but you are not told which.

- At what time does v_R reach its maximum value? Enter $k = t_0 \cdot \frac{12}{\pi}$, where t_0 is the first time that the maximum is reached, for $t_0 \geq 0$. (Hint: convert a to radians first)
- We select the mystery element such that $|I_a|$ is minimized (note that this is the current through the voltage source). What is the mystery element type (enter 1 for capacitor, 2 for inductor)? What is its value X (i.e., either the capacitance or the inductance value, in F or H respectively)?

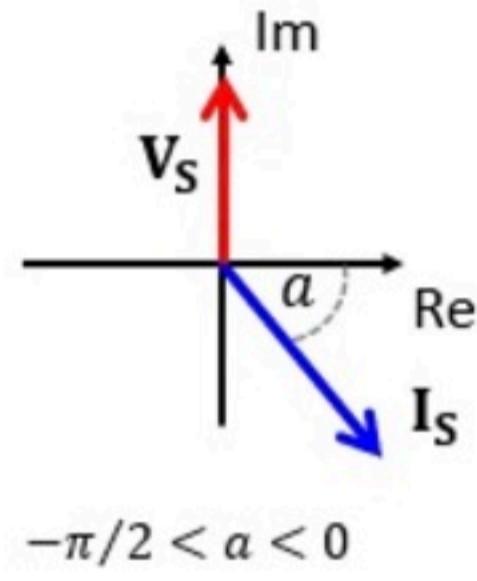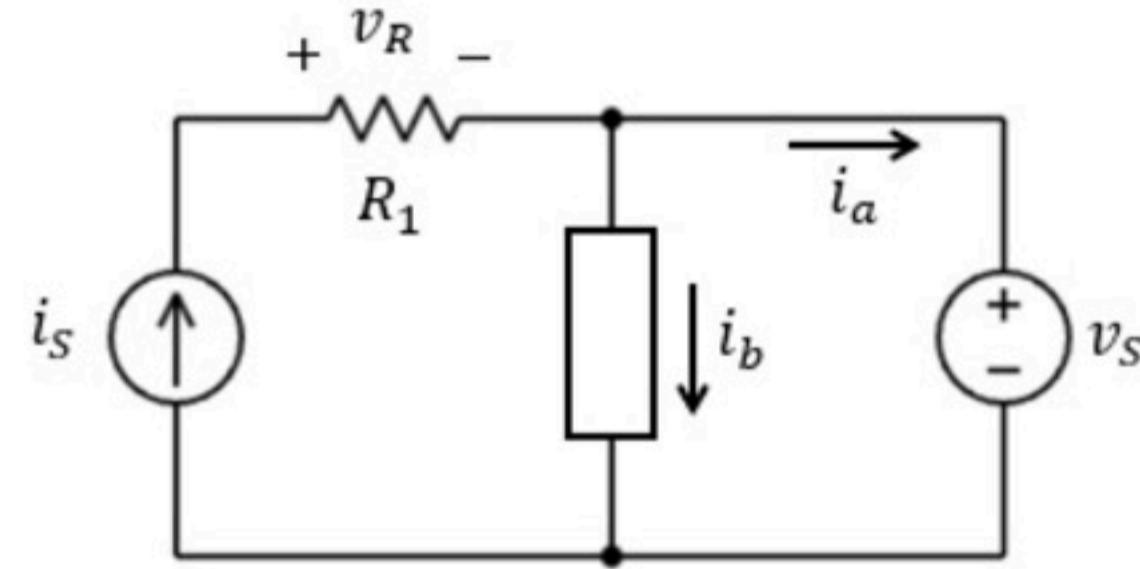

Given Variables:

W1 : 4 rad/s

a : -30 degrees

A1 : 1 A

A2 : 10 V

b : 3

R1 : 1 ohm

Calculate the following:

k (s) :

0.5



Type :

2





X :

5



The AC circuit below has $\omega = W_1$ and is in steady state. The phasor diagram shows the phasors of v_s and i_s . You are given the angle a , and vector lengths $|I_s| = A_1$ and $|V_s| = A_2 \sqrt{b}$. The diagram is not necessarily drawn to scale (but V_s is along the imaginary axis). The element in the center (rectangular box) is either an inductor or a capacitor but you are not told which.

- At what time does v_R reach its maximum value? Enter $k = t_0 \cdot \frac{12}{\pi}$, where t_0 is the first time that the maximum is reached, for $t_0 \geq 0$. (Hint: convert a to radians first)
- We select the mystery element such that $|I_a|$ is minimized (note that this is the current through the voltage source). What is the mystery element type (enter 1 for capacitor, 2 for inductor)? What is its value X (i.e., either the capacitance or the inductance value, in F or H respectively)?

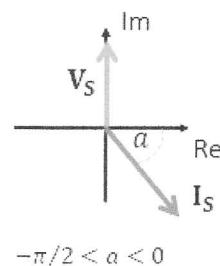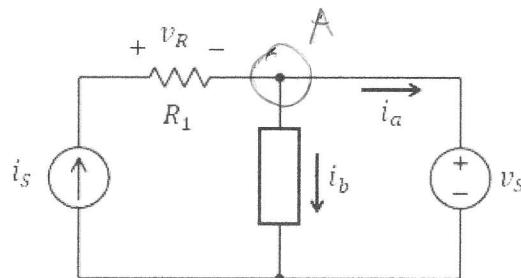

$$W_1 = 2 \text{ rad/s}$$

$$a = -30^\circ$$

$$A_1 = 2 \text{ A}$$

$$A_2 = 10 \text{ V}$$

$$b = 3$$

$$R_1 = 1 \Omega$$

$$\textcircled{a} \quad V_R = R_1 I_s = R_1 \cdot A_1 e^{j\alpha} = 2 e^{-j30^\circ}$$



$$V_{R\max} = |V_R| \quad V_R(t) = 2 \cos(2t - 30^\circ) \quad \text{MAX WHEN } \cos(\theta) = 1$$

$$\theta = 0 \Rightarrow 2t_0 - \frac{\pi}{6} = 0 \Rightarrow t_0 = \frac{\pi}{12} \Rightarrow k = t_0 \cdot \frac{12}{\pi} = 1 \quad \boxed{k=1}$$


$$\textcircled{b} \quad \text{KCL at A: } I_s = I_b + I_a$$

If the mystery element is a capacitor or inductor: I_b is perpendicular to V_s

Let's look at different options

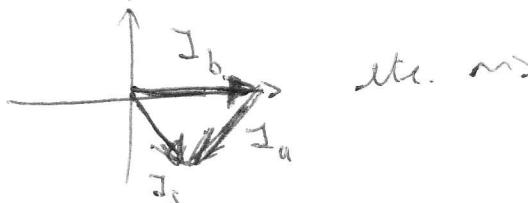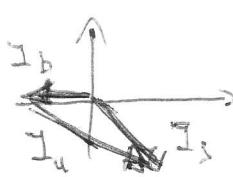

etc. and

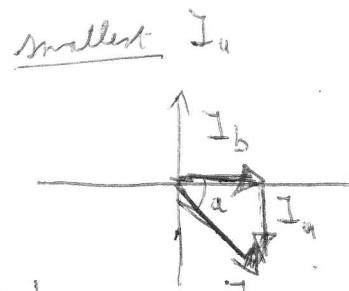

$$\cos(-\alpha) = \frac{|I_b|}{|I_s|} \Rightarrow \cos\left(\frac{\pi}{6}\right) = \frac{\sqrt{3}}{2} = \frac{|I_b|}{2}$$

$$|I_b| = \sqrt{3} \quad \text{on the real axis} \Rightarrow I_b = \sqrt{3}$$

$$\text{also: } V_s = Z \cdot I_b \Rightarrow Z = \frac{V_s}{I_b} = \frac{10\sqrt{3}}{\sqrt{3}} j = 10j$$

$$\text{This must be an inductor: } Z = j\omega L = 10j$$

$$\Rightarrow \omega L = 10 \Rightarrow L = \frac{10}{2} = 5 \text{ H}$$

$$\boxed{x=5}$$


PP Phasors 021

Unlimited Attempts.

Find the Thevenin equivalent model between a and b, in phasor notation:

$$\mathbf{V}_{\text{Th}} = a + jb$$

$$\mathbf{Z}_{\text{Th}} = c + jd$$

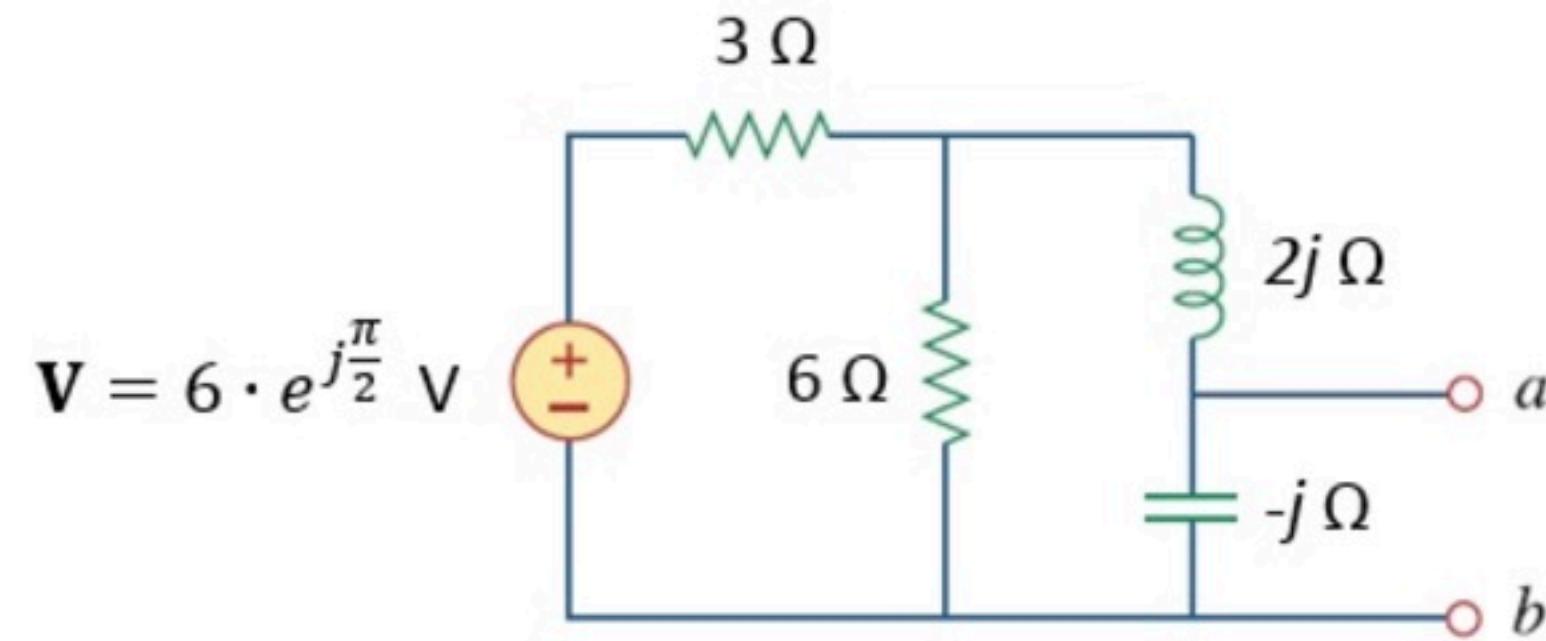

Given Variables:

...

Calculate the following:

a (V) :

1.6



b (V) :

-0.8



c (ohm) :

0.4




d (ohm) :

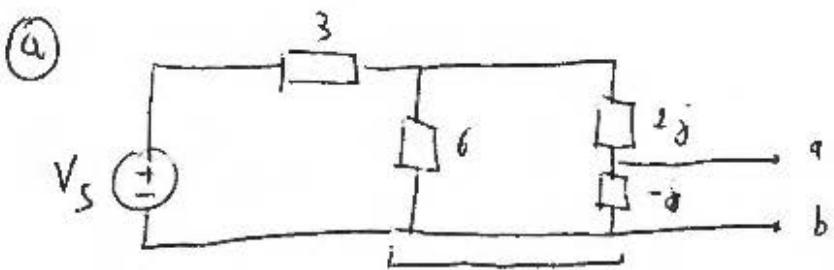-1.2



Hint: You can use voltage divider and series/parallel connections of impedances




$$\rightarrow Z_1 = 6 \parallel (2j - j) = 6 \parallel j = \frac{1}{\frac{1}{6} + \frac{1}{j}} = \frac{6j}{6+j}$$

$$V_{ab} = V_s \cdot \frac{Z_1}{Z_1 + 3} \cdot \frac{-j}{2j - j} = V_s \cdot \frac{6j}{6j + 3(6+j)} \cdot \frac{-j}{j} = -V_s \frac{6j}{18 + 9j}$$

$$= -\frac{6e^{j\frac{\pi}{2}} \cdot 6j}{9(2+j)} \frac{(2-j)}{(2-j)} = \frac{-6j \cdot 6j}{9} \frac{(2-j)}{(4+1)} = \frac{36}{9} \cdot \frac{2-j}{5} = \frac{4}{5}(2-j)$$
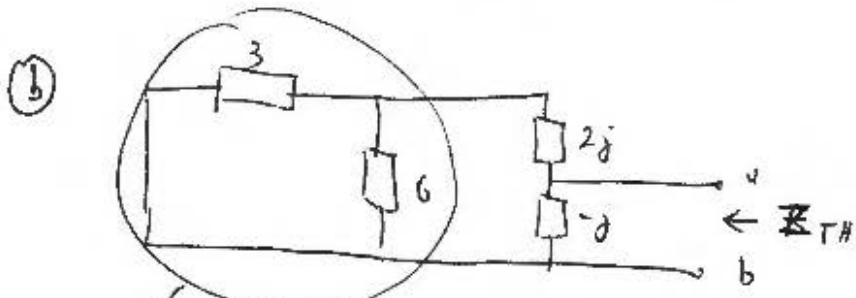
$$V_{TH} = V_{ab} = \frac{8}{5} - \frac{4}{5}j \quad \boxed{a = 1.6V} \quad \boxed{b = -0.8V}$$



$$3 \parallel 6 = \frac{1}{\frac{1}{3} + \frac{1}{6}} = \frac{6}{3} = 2 \Omega$$

$$Z_{TH} = (2+2j) \parallel (-j) = \frac{1}{\frac{1}{2+2j} + \frac{1}{-j}} = \frac{-j(2+2j)}{-j+2+2j} = \frac{2-2j}{2+j}$$

$$= \frac{(2-2j)(2-j)}{(2+j)(2-j)} = \frac{(4-2j-4j-2)}{5} = \frac{2}{5} - \frac{6}{5}j$$

$$Z_{TH} = \frac{2}{5} - \frac{6}{5}j \quad \boxed{c = 0.4 \Omega} \quad \boxed{d = -1.2 \Omega}$$

PP Phasors 001

Unlimited Attempts.

$$v_1(t) = -4 \cdot \cos\left(10t + \frac{\pi}{4}\right) \text{ V}$$

$$v_2(t) = 3 \cdot \sin\left(10t + \frac{\pi}{3}\right) \text{ V}$$

Express as phasors

$$\mathbf{V}_1 = A_1 \cdot e^{jB_1} \quad \text{with } 0 \leq A_1 \text{ and } -180^\circ \leq B_1 \leq 180^\circ$$

$$\mathbf{V}_2 = A_2 \cdot e^{jB_2} \quad \text{with } 0 \leq A_2 \text{ and } -180^\circ \leq B_2 \leq 180^\circ$$

Given Variables:

...

Calculate the following:

A1 (V) :

4



B1 (degrees) :

-135



A2 (V) :

3



B2 (degrees) :

-30



Hint: Convert $\sin()$ to $\cos()$ first

PP Phasors 002

Unlimited Attempts.

$$\mathbf{V}_1 = 5 \cdot e^{j\frac{\pi}{6}}$$

$$\mathbf{V}_2 = 5 \cdot e^{j\frac{5\pi}{6}}$$

$$\mathbf{V}_3 = 6 \cdot e^{-j\frac{\pi}{2}}$$

Find

$$\mathbf{X} = a + jb = \mathbf{V}_1 + \mathbf{V}_2 + \mathbf{V}_3$$

Given Variables:

...

Calculate the following:

a(.) :

0



b(.) :

-1



Hint: Draw the vectors.

PP Phasors 003

Unlimited Attempts.

$$\mathbf{V}_1 = 7 \cdot e^{j\frac{\pi}{4}}$$

$$\mathbf{V}_2 = 7 \cdot e^{j\frac{11\pi}{12}}$$

$$\mathbf{V}_3 = 7 \cdot e^{j\frac{7\pi}{12}}$$

Find

$$\mathbf{X} = a + jb = \mathbf{V}_1 + \mathbf{V}_2 - \mathbf{V}_3$$

Given Variables:

. . .

Calculate the following:

a (.) :

0



b (.) :

0



PP Phasors 004

Unlimited Attempts.

$$v(t) = 2\sqrt{2} \cdot \cos\left(10t + \frac{\pi}{6}\right) + 2\sqrt{2} \cdot \sin\left(10t + \frac{7\pi}{6}\right) \quad \vee$$

Express

$$v(t) = A \cdot \cos(10t + B) \text{ with } 0 \leq A \text{ and } -180^\circ \leq B \leq 180^\circ$$

Given Variables:

...

Calculate the following:

A (V) :

4



B (degrees) :

75



Hint: Convert to phasors; do the algebra in the complex domain (mostly in polar coordinates).

PP Phasors 005


Unlimited Attempts.

Express the current as a time waveform

$$i(t) = A_1 \cdot \cos(2\pi f_1 \cdot t + B_1) \text{ with } 0 \leq A_1 \text{ and } -180^\circ \leq B_1 \leq 180^\circ$$

and as a phasor
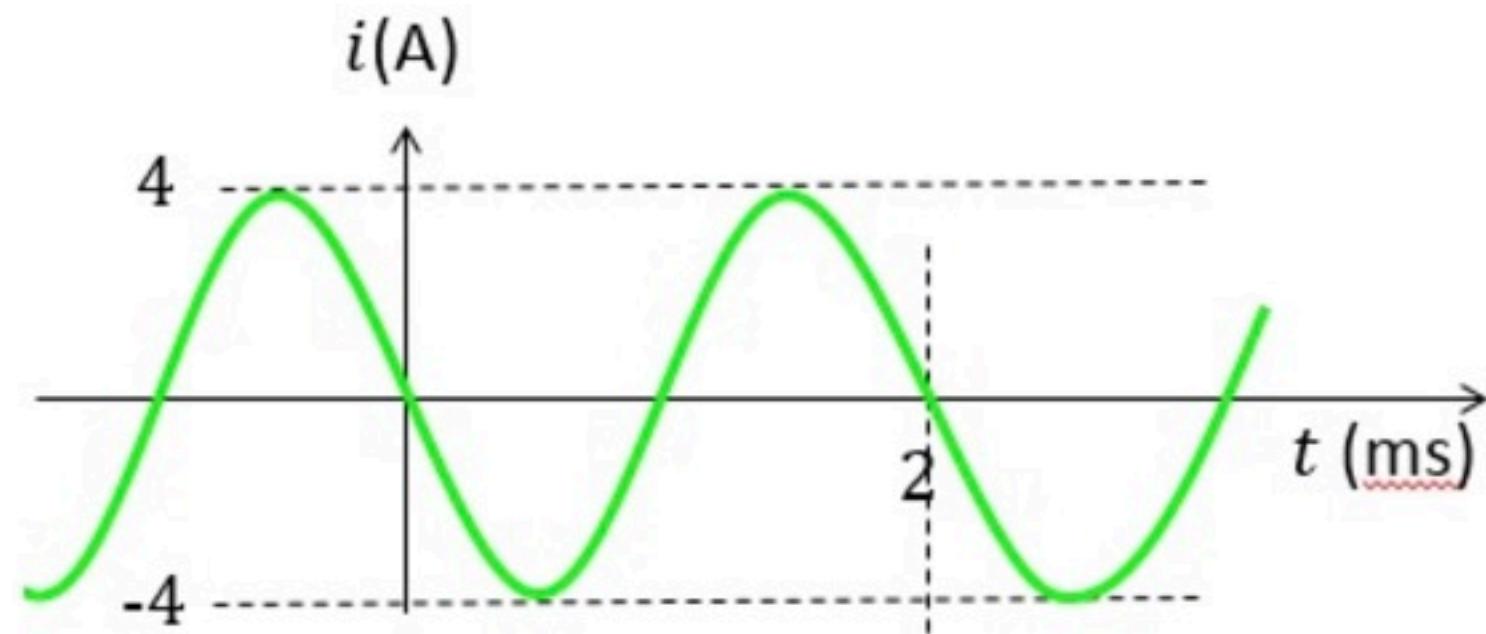
$$\mathbf{I} = A_2 \cdot e^{jB_2} \text{ with } 0 \leq A_2 \text{ and } -180^\circ \leq B_2 \leq 180^\circ$$



Given Variables:

...

Calculate the following:

A1 (A) :

4



f1 (1/s) :

500



B1 (degrees) :

90



A2 (A) :

4



B2 (degrees) :

90



Hint: Convert $\sin()$ to $\cos()$.

PP Phasors 006


Unlimited Attempts.

Express the current as a time waveform

$$i(t) = A_1 \cdot \cos(2\pi f_1 \cdot t + B_1) \text{ with } 0 \leq A_1 \text{ and } -180^\circ \leq B_1 \leq 180^\circ$$

and as a phasor
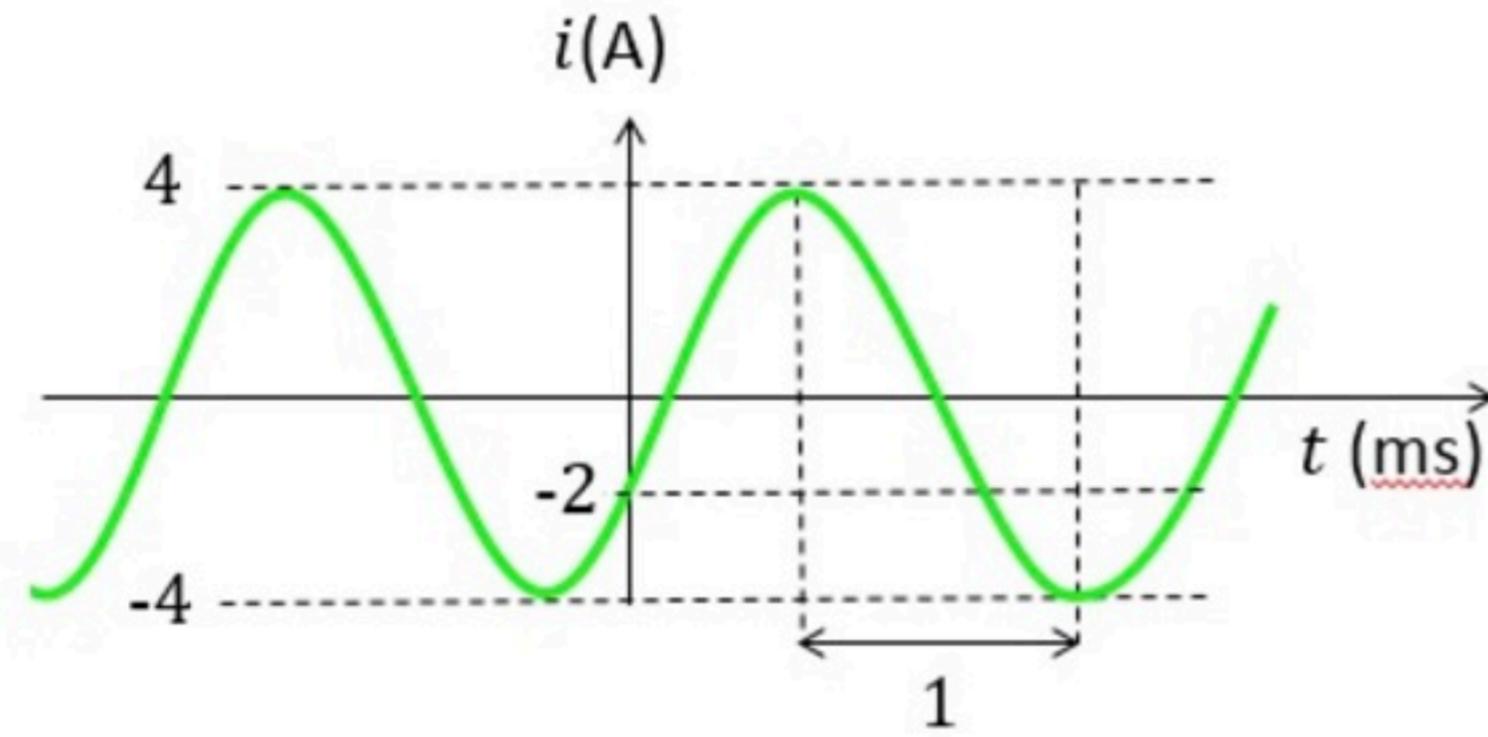
$$\mathbf{I} = A_2 \cdot e^{jB_2} \text{ with } 0 \leq A_2 \text{ and } -180^\circ \leq B_2 \leq 180^\circ$$



Given Variables:

...

Calculate the following:

A1 (A) :

4



f1 (1/s) :

500



B1 (degrees) :

-120



A2 (A) :

4



B2 (degrees) :

-120



Hint: Can we find the phase on the graph?

PP Phasors 007


Unlimited Attempts.

Express the current as a time waveform

$$i(t) = A_1 \cdot \cos(2\pi f_1 \cdot t + B_1) \text{ with } 0 \leq A_1 \text{ and } -180^\circ \leq B_1 \leq 180^\circ$$

and as a phasor
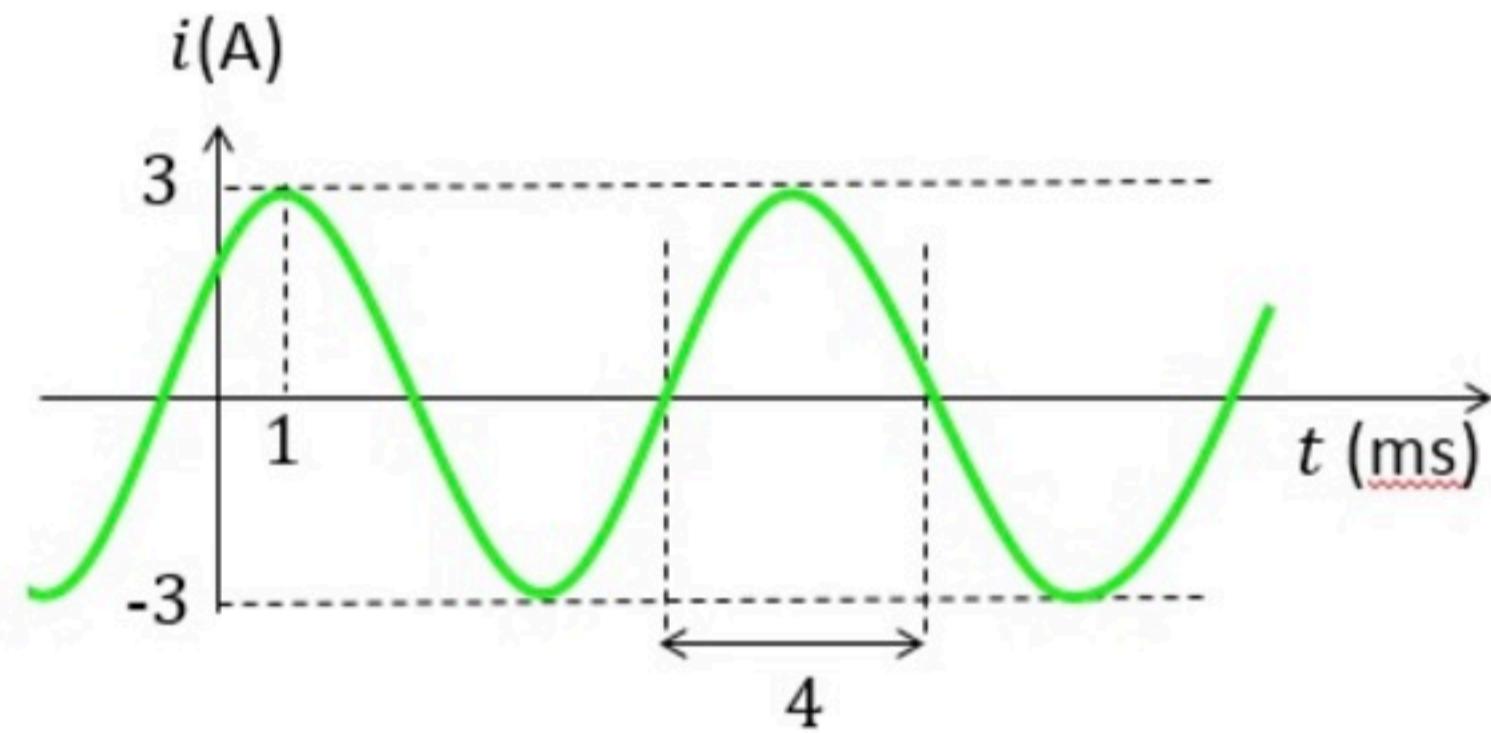
$$\mathbf{I} = A_2 \cdot e^{jB_2} \text{ with } 0 \leq A_2 \text{ and } -180^\circ \leq B_2 \leq 180^\circ$$



Given Variables:

...

Calculate the following:

A1 (A) :

3



f1 (1/s) :

125



B1 (degrees) :

-45



A2 (A) :

3



B2 (degrees) :

-45



Hint: How does phase relates to time delay?

PP Phasors 008


Unlimited Attempts.

Express the current as a time waveform

$$i(t) = A_1 \cdot \cos(2\pi f_1 \cdot t + B_1) \text{ with } 0 \leq A_1 \text{ and } -180^\circ \leq B_1 \leq 180^\circ$$

and as a phasor
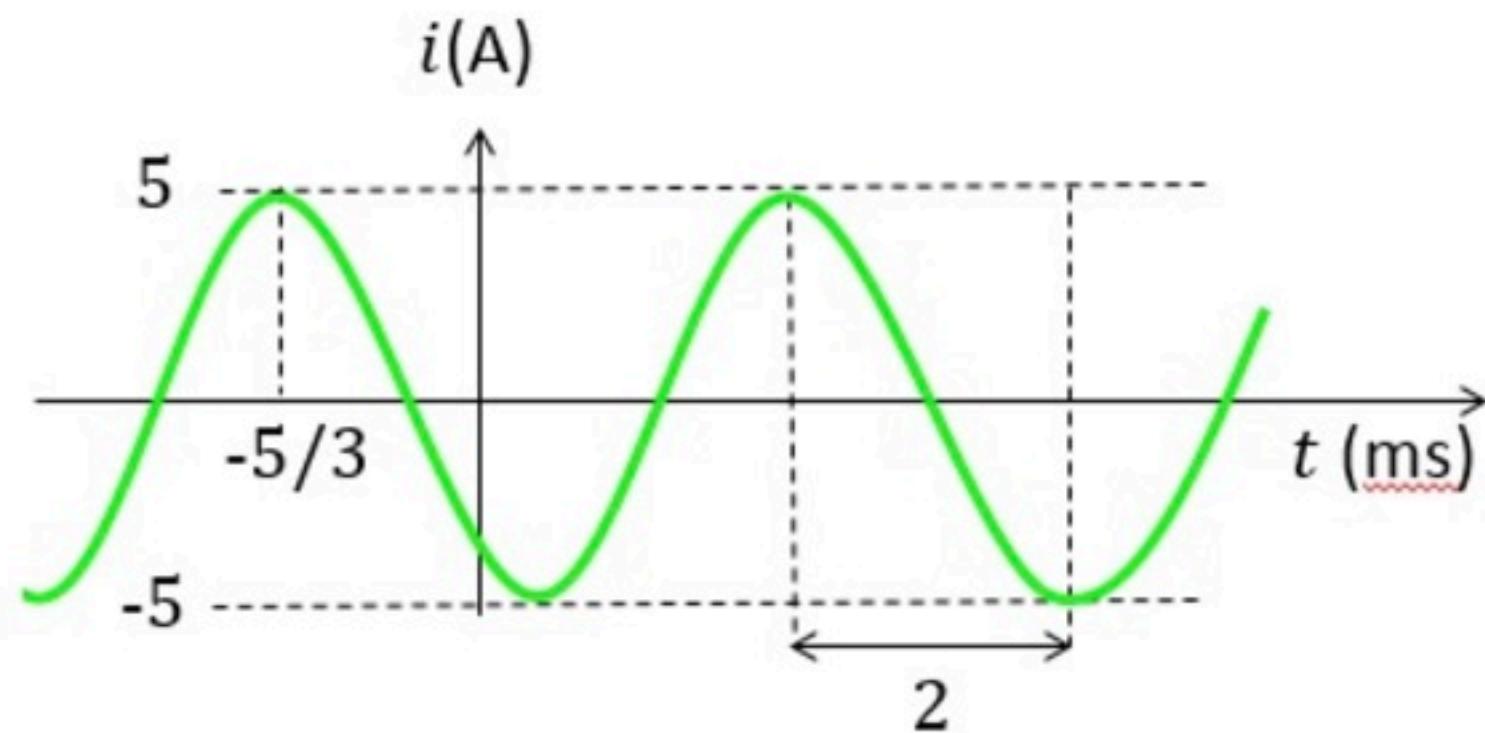
$$\mathbf{I} = A_2 \cdot e^{jB_2} \text{ with } 0 \leq A_2 \text{ and } -180^\circ \leq B_2 \leq 180^\circ$$



Given Variables:

...

Calculate the following:

A1 (A) :

5



f1 (1/s) :

250



B1 (degrees) :

150



A2 (A) :

5



B2 (degrees) :

150



Hint: How does phase relates to time delay?

PP Phasors 009


Unlimited Attempts.

Express the current as a time waveform

$$i(t) = A_1 \cdot \cos(2\pi f_1 \cdot t + B_1) \text{ with } 0 \leq A_1 \text{ and } -180^\circ \leq B_1 \leq 180^\circ$$

and as a phasor
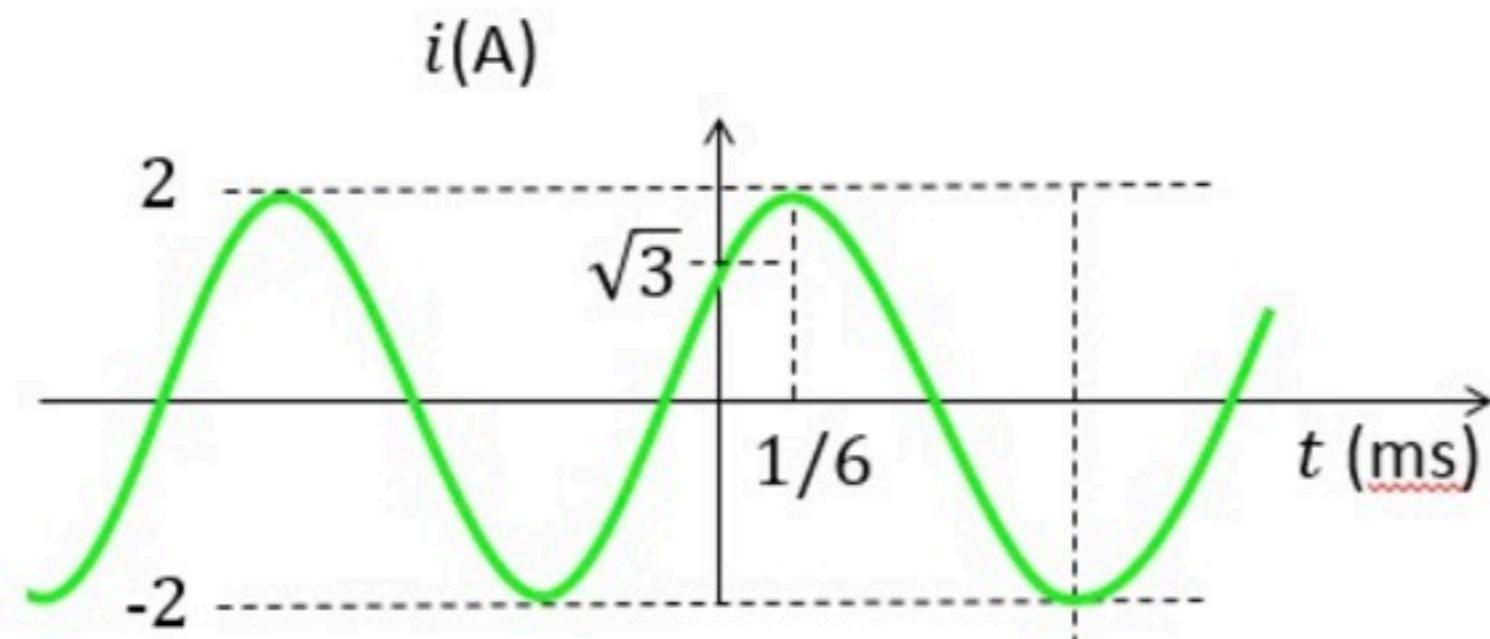
$$\mathbf{I} = A_2 \cdot e^{jB_2} \text{ with } 0 \leq A_2 \text{ and } -180^\circ \leq B_2 \leq 180^\circ$$



Given Variables:

...
...

Calculate the following:

A1 (A) :

2



f1 (1/s) :

500



B1 (degrees) :

-30



A2 (A) :

2



B2 (degrees) :

-30



Hint: How does phase relates to time delay?


PP Phasors 010

Unlimited Attempts.

Find t_1 .

Express the current as a phasor
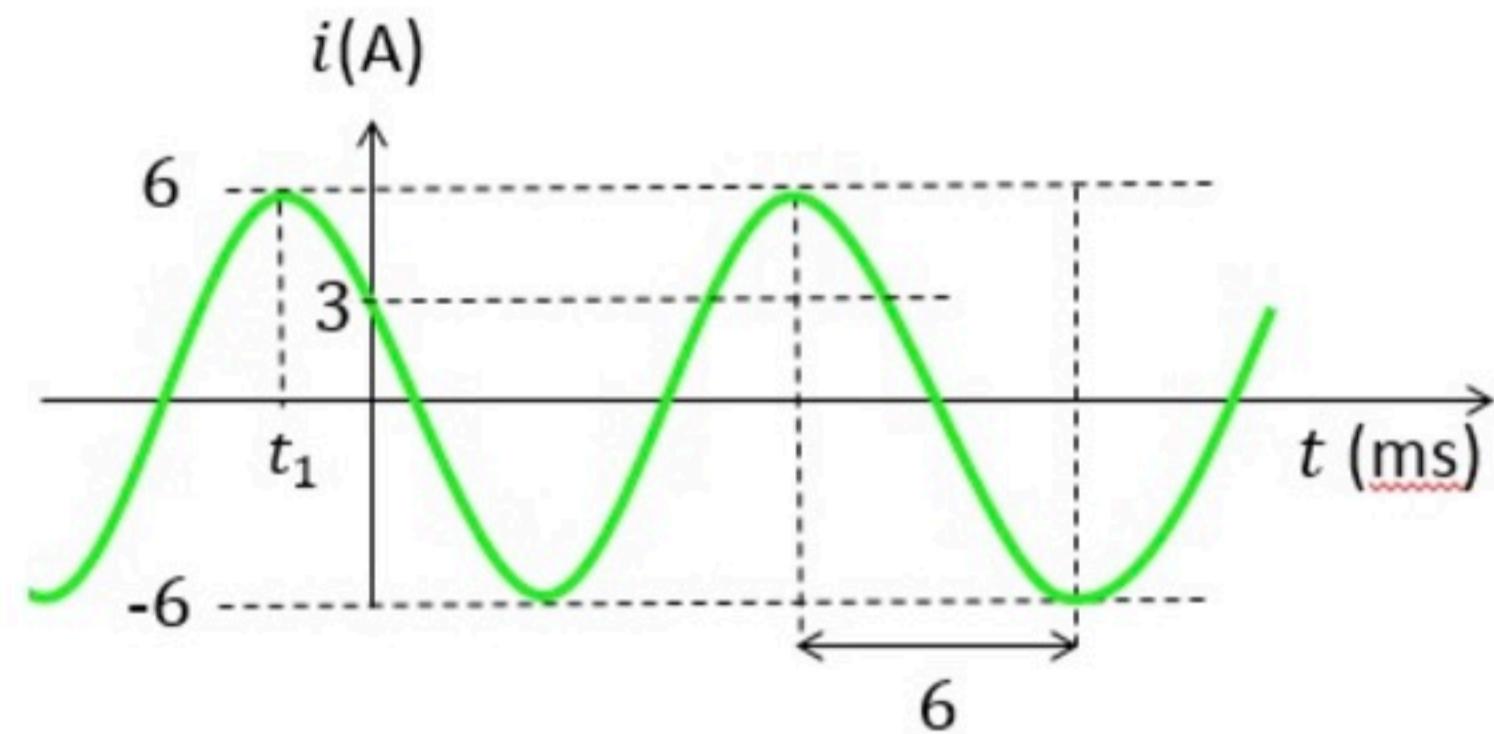
$$\mathbf{I} = A_2 \cdot e^{jB_2} \quad \text{with } 0 \leq A_2 \text{ and } -180^\circ \leq B_2 \leq 180^\circ$$



Given Variables:

...

Calculate the following:

t_1 (ms) :

-2



A_2 (A) :

6



B_2 (degrees) :

60




Hint: Can we find the phase on the graph?

PP Phasors 011

Unlimited Attempts.

Find the phasor $\mathbf{I} = a + jb$.

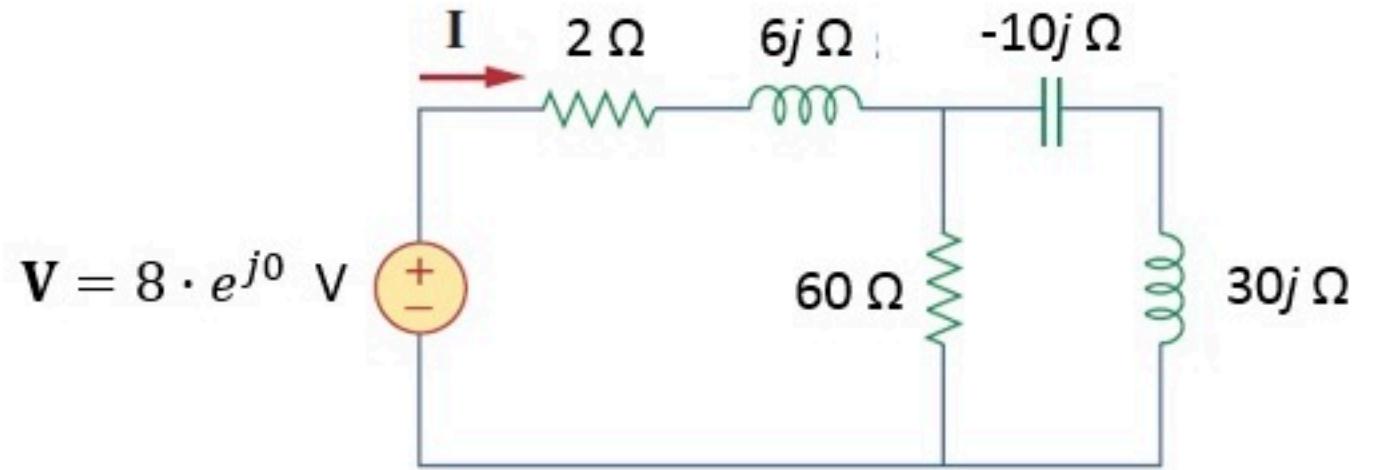

Given Variables:

...

Calculate the following:

a (A) :

0.1



b (A) :

-0.3




PP Phasors 012

Unlimited Attempts.

$$i_x(t) = 3\sqrt{2} \cdot \sin(5000t + 30^\circ) \text{ A}$$

Find $v_s(t) = A \cdot \cos(W \cdot t + B)$.

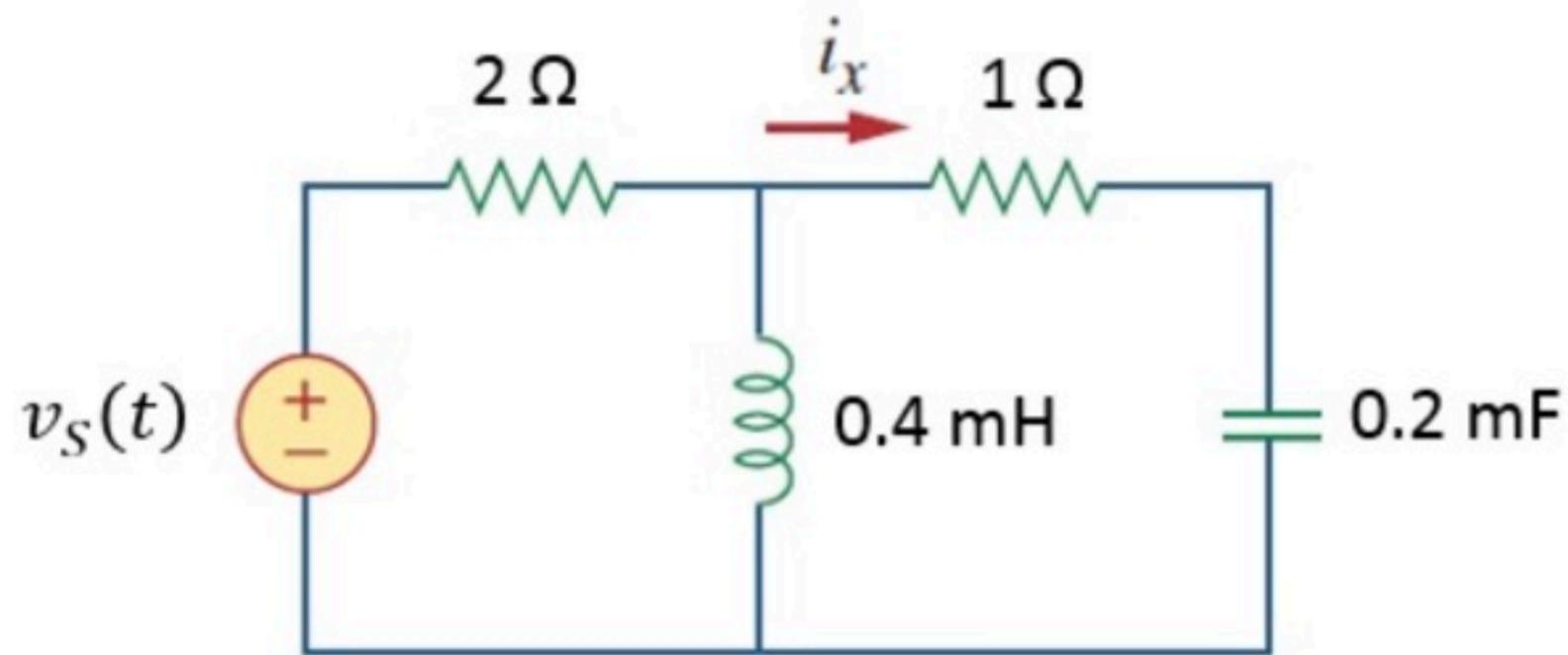(with $0 \leq A$ and $-180^\circ \leq B \leq 180^\circ$)



Given Variables:

...

Calculate the following:

A (V) :

12



W (rad/s) :

5000



B (degrees) :

-105



Hint: Stay algebraic with Vs as long as you can


PP Phasors 013

Unlimited Attempts.

$$v_s(t) = 4\sqrt{2} \cdot \cos(100t + 30^\circ) \text{ V}$$

Find $v_o(t) = A \cdot \cos(W \cdot t + B)$.

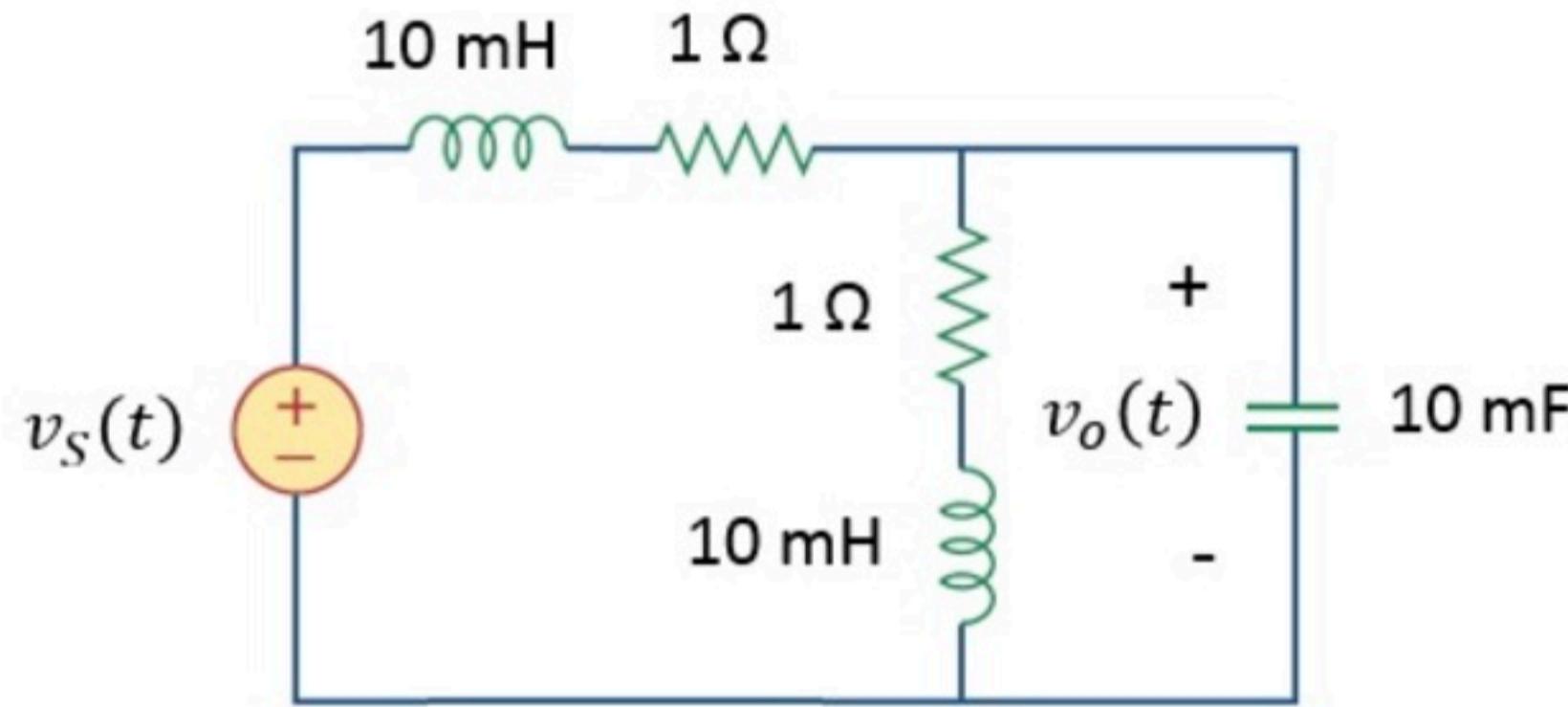(with $0 \leq A$ and $-180^\circ \leq B \leq 180^\circ$)



Given Variables:

...

Calculate the following:

A (V) :

4



W (rad/s) :

100



B (degrees) :

-15



Hint: Use voltage divider.


PP Phasors 014

Unlimited Attempts.

$$v_s(t) = 20 \cdot \sin(1000t + 45^\circ) \text{ V}$$

Find $v_a(t) = A \cdot \cos(W \cdot t + B)$.

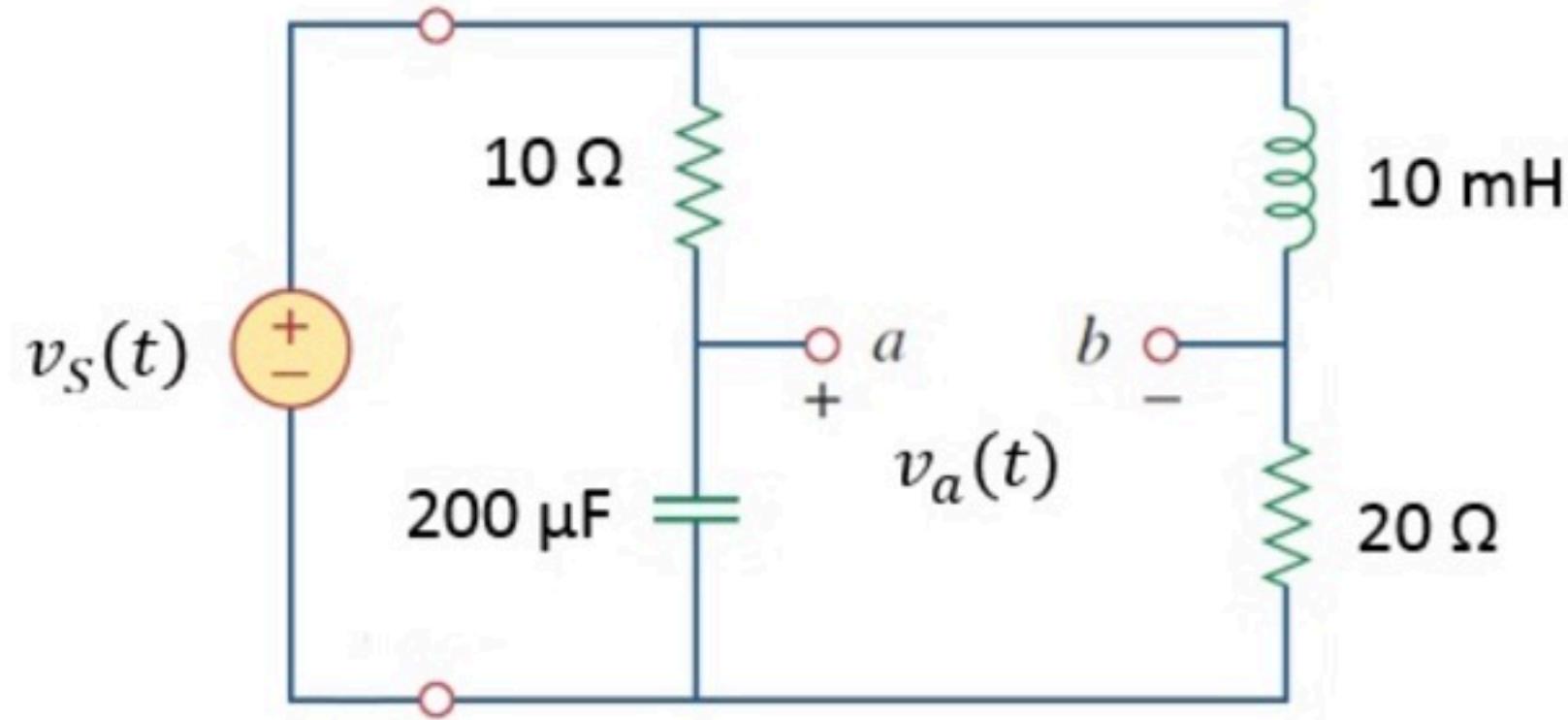(with $0 \leq A$ and $-180^\circ \leq B \leq 180^\circ$)



Given Variables:

...

Calculate the following:

A (V) :

12



W (rad/s) :

1000



B (degrees) :

135




Hint: Use voltage divider.

PP Phasors 015

Unlimited Attempts.

Find the value of ω that results in $v_o = 0$ V.

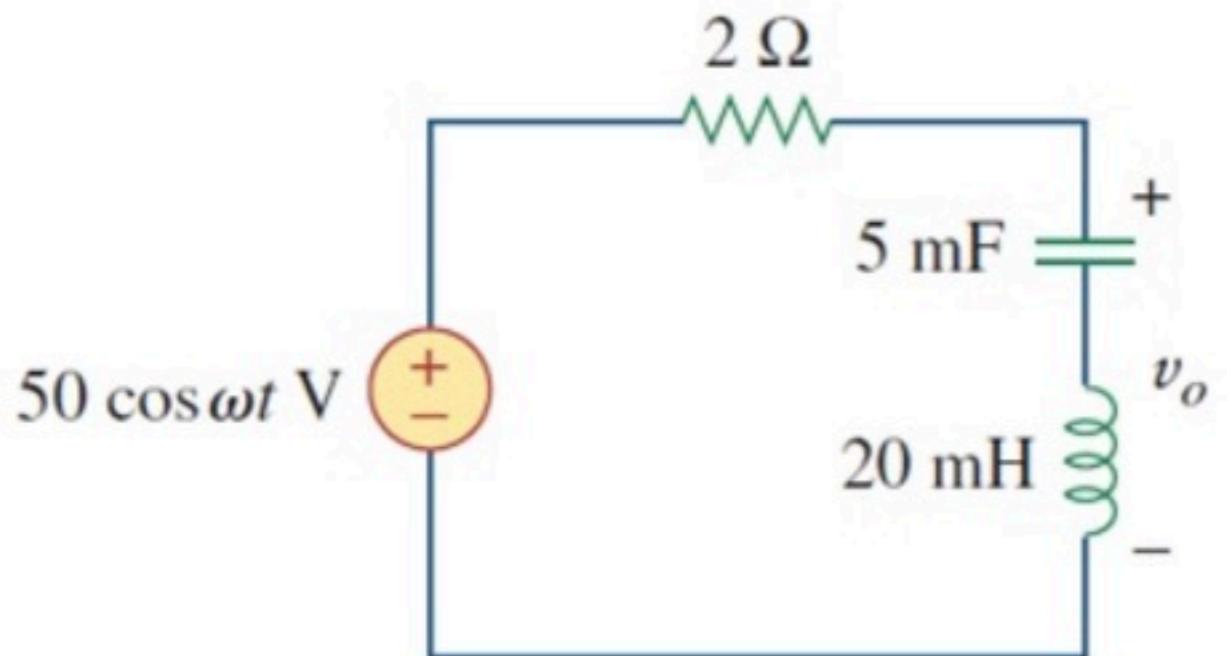(v_o is the voltage across the inductor and capacitor together)



Note: This is an example of 'resonance'. For each ω , the system behaves differently (i.e., v_o is a function of ω). For this one particular value of ω , however, the inductor and capacitor perfectly 'compensate' for each other.

Given Variables:

. . .

Calculate the following:

ω (rad/s) :

100



Hint: What should be the impedance of C and L in series for $v_o = 0$?


PP Phasors 016

Unlimited Attempts.

$$v_S(t) = -\sqrt{2} \cdot \cos(1000t) \text{ V}$$

Find $i_o(t) = A \cdot \cos(W \cdot t + B)$.

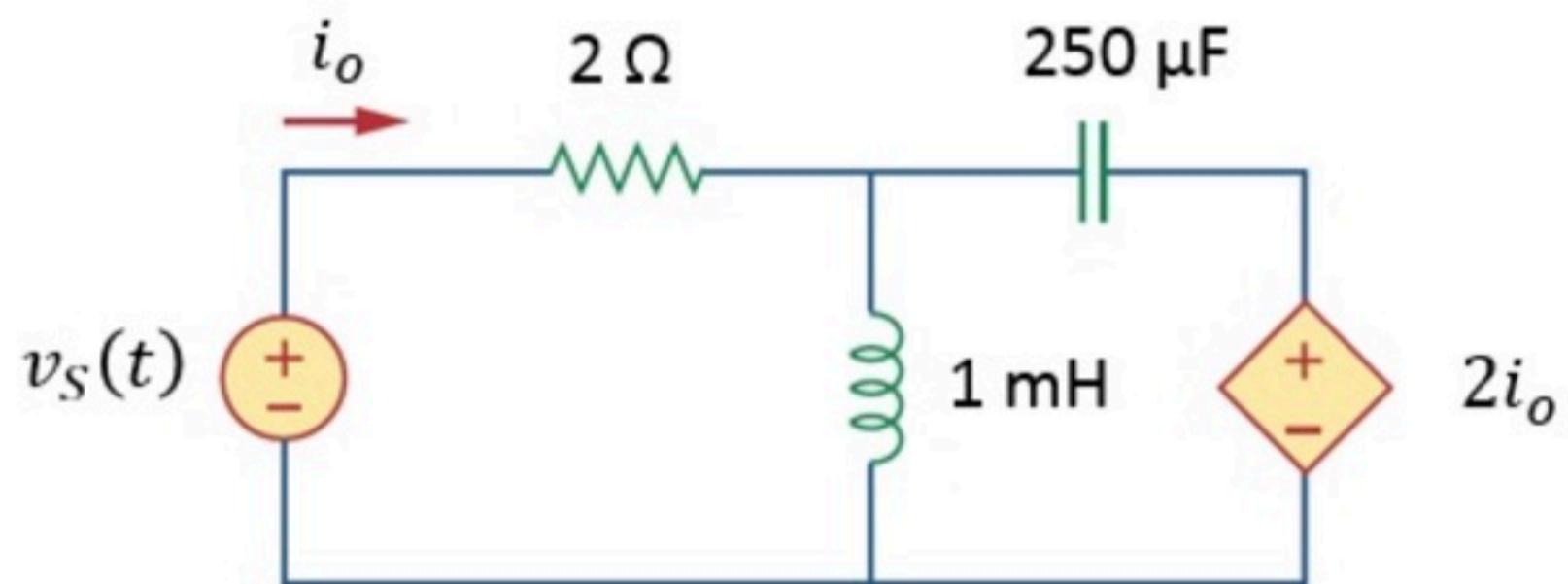(with $0 \leq A$ and $-180^\circ \leq B \leq 180^\circ$)



Given Variables:

...

Calculate the following:

A (A) :

0.75



W (rad/s) :

1000



B (degrees) :

135




Hint: Consider nodal analysis. Leave V algebraic until the end.

PP Phasors 017

Unlimited Attempts.

Find the phasors
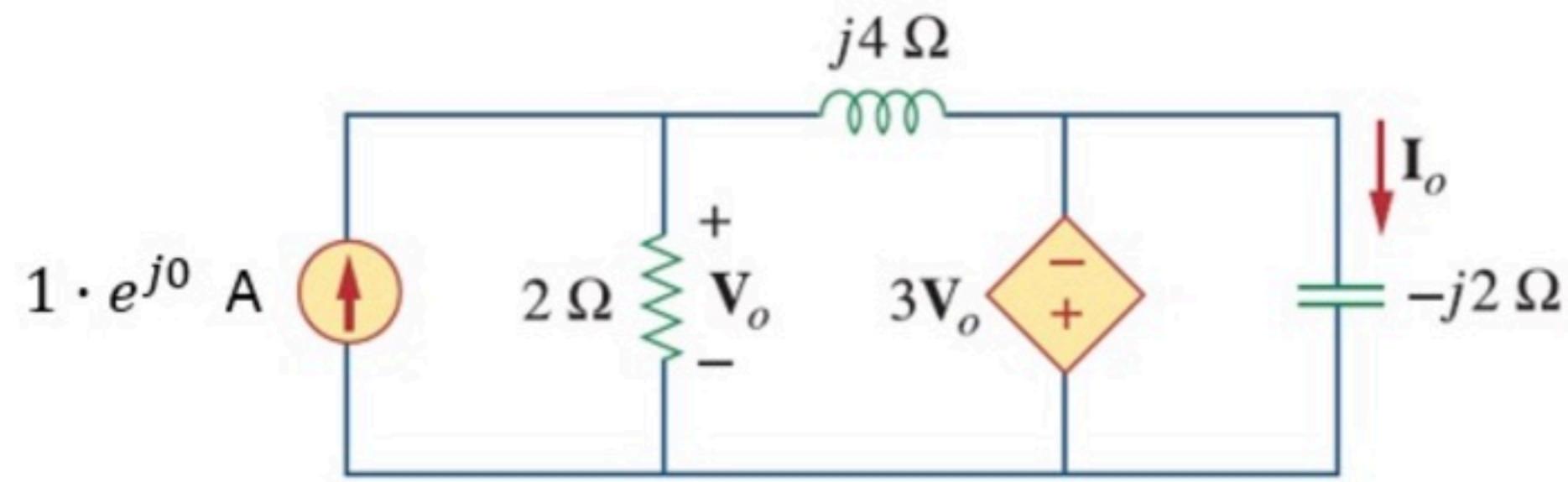
$$\mathbf{V}_o = a + jb \quad \text{and} \quad \mathbf{I}_o = c + jd$$



Given Variables:

. . .

Calculate the following:

a (V) :

0.4



b (V) :

0.8



c (A) :

1.2



d (A) :

-0.6




Hint: Use mesh analysis.

PP Phasors 018

Unlimited Attempts.

Find $i_o(t) = A \cdot \cos(W \cdot t + B) + D$.

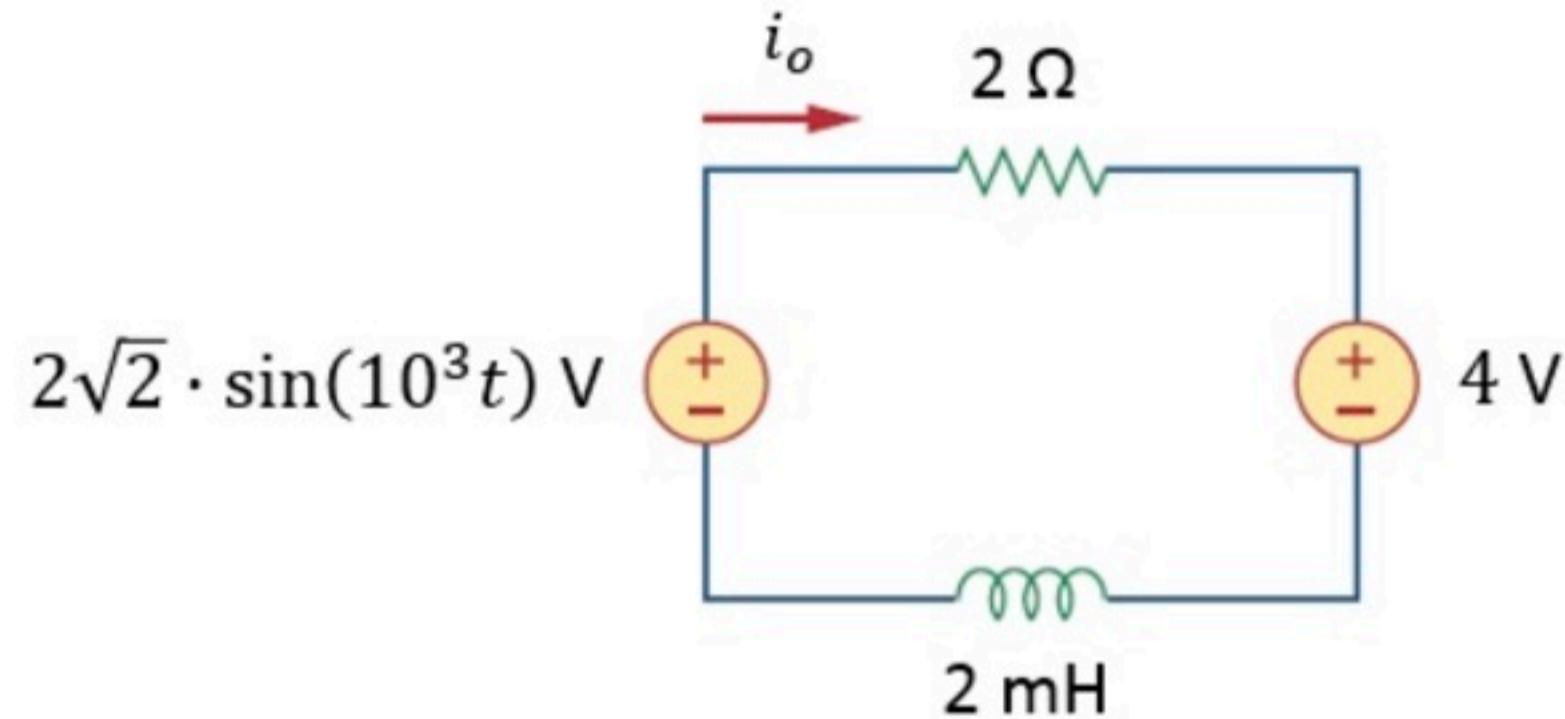(with $0 \leq A$ and $-180^\circ \leq B \leq 180^\circ$)



Given Variables:

...

Calculate the following:

A (A) :

1



W (rad/s) :

1000



B (degrees) :

-135



D (A) :

-2



Hint: Use superposition.

PP Phasors 019


Unlimited Attempts.

$$i_S(t) = 2\sqrt{2} \cdot \cos(1000t) \text{ A}$$

$$v_S(t) = 3\sqrt{2} \cdot \cos(3000t) \text{ V}$$

Find $v_x(t) = A1 \cdot \cos(Wt + B1) + A2 \cdot \cos(3000t + B2)$.

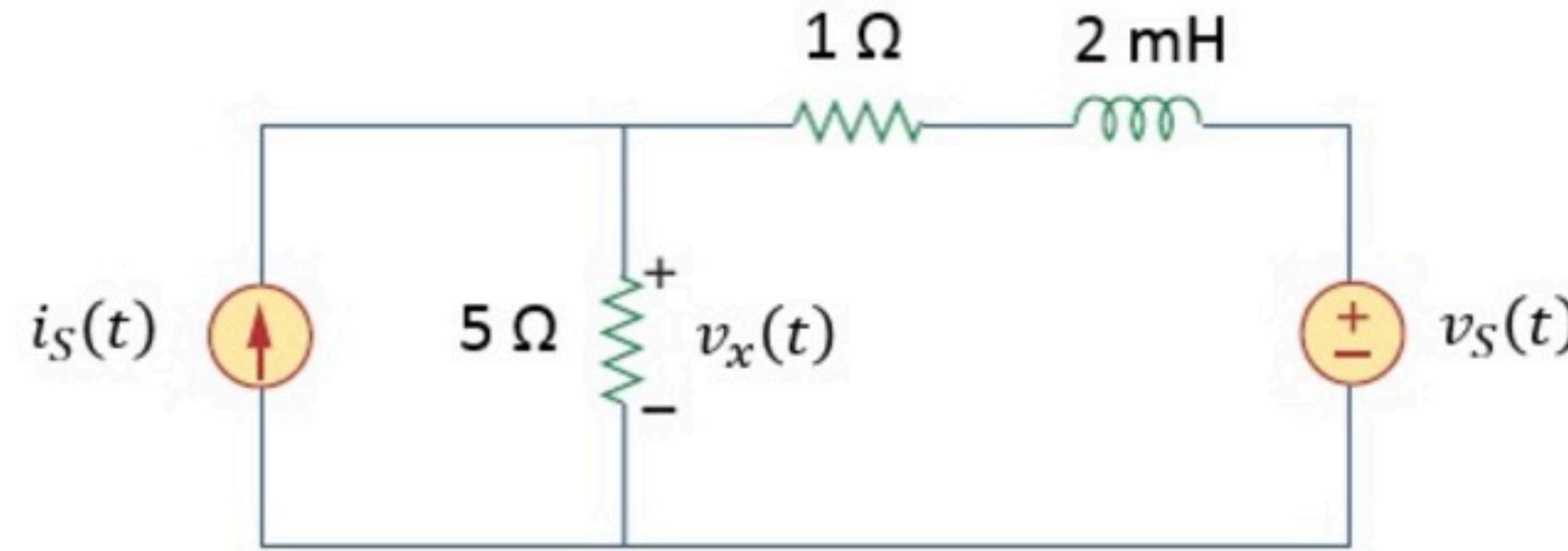(with $0 \leq A1, A2$ and $-180^\circ \leq B1, B2 \leq 180^\circ$)



Given Variables:

...

Calculate the following:

A1 (V) :

5



W (rad/s) :

1000



B1 (degrees) :

45



A2 (V) :

2.5



B2 (degrees) :

-45




Hint: Use superposition.

PP Phasors 020

Unlimited Attempts.

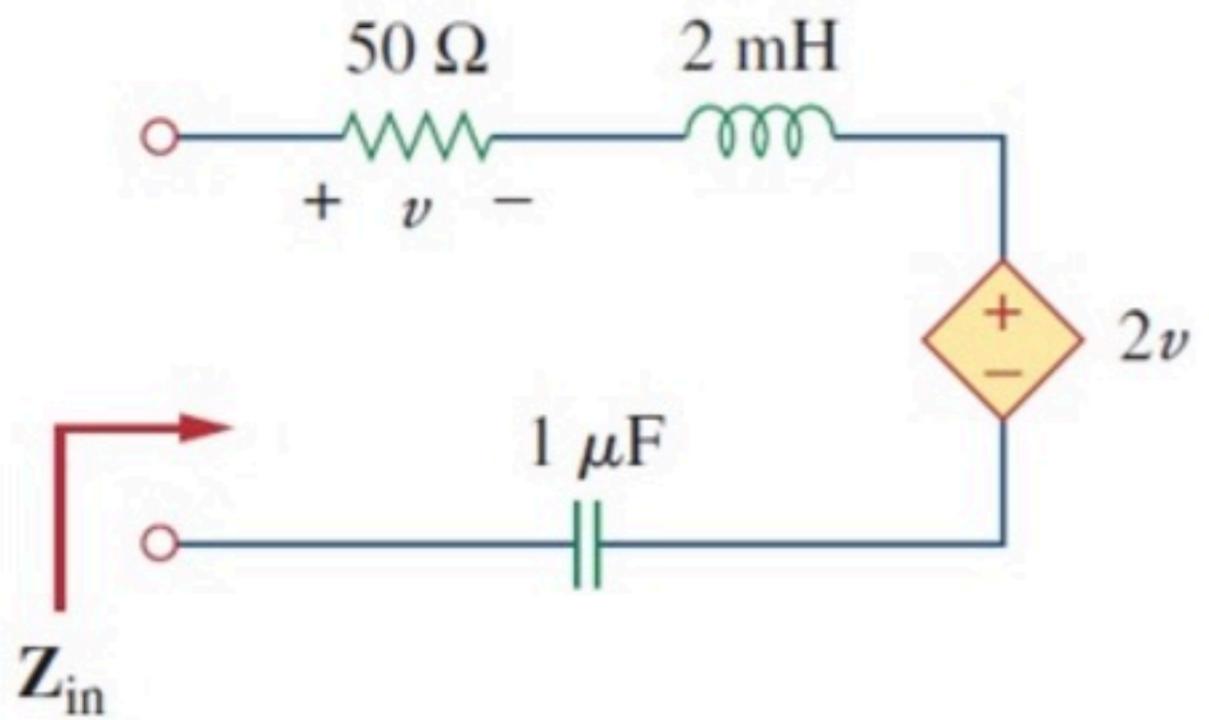Find the impedance $Z_{in} = a + jb$
at $\omega = 10 \text{ krad/s.}$



Given Variables:

. . .

Calculate the following:

a (ohm) :

150



b (ohm) :

-80



Hint: Would you use a test voltage or a test current?

PP Phasors 022


Unlimited Attempts.

$$i_S(t) = -15 \cdot \sin(10^6 t) \text{ A}$$

Find the Norton equivalent model between a and b, in phasor notation:

$$\mathbf{I}_N = a + jb$$

$$\mathbf{Z}_N = c + jd$$

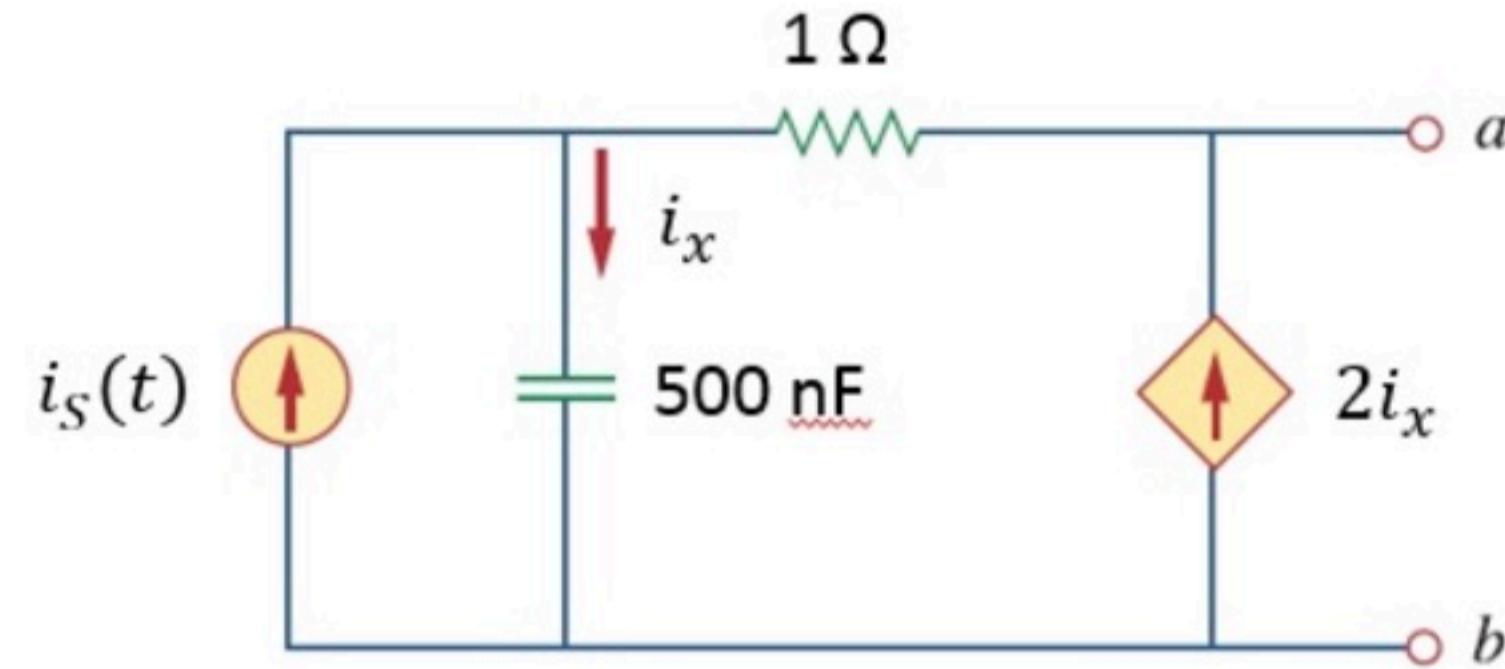

Note: This phasor Norton model is only valid for the particular frequency of the source (in this case, $\omega = 10^6 \text{ rad/s}$).

Given Variables:

...

Calculate the following:

a (A) :

-6



b (A) :

18



c (ohm) :

-1



d (ohm) :

2



Hint: Use a test voltage or current to find Z_N .