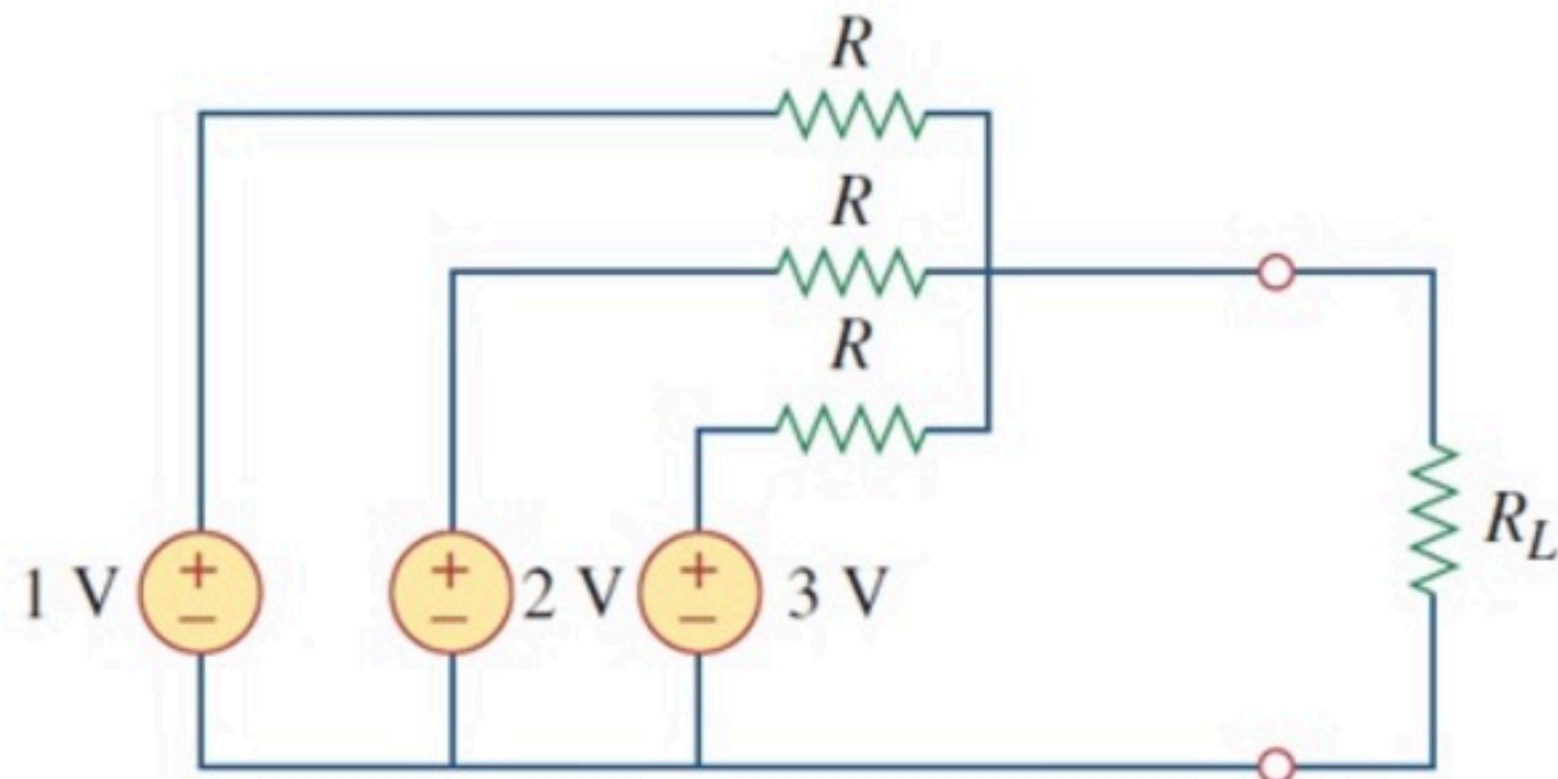


# PP Circuit theorems 016

Unlimited Attempts.

Find  $R$  such that the maximum power delivered to the load is 12 mW.  
[Do not look up the equation for power.]



Given Variables:

...

Calculate the following:

$R$  (ohm) :

250



Hint: Find the Thevenin model first.