


PP First order circuits 005

Unlimited Attempts.

The switch has been closed for a long time.

At time $t = 0$, the switch is opened.

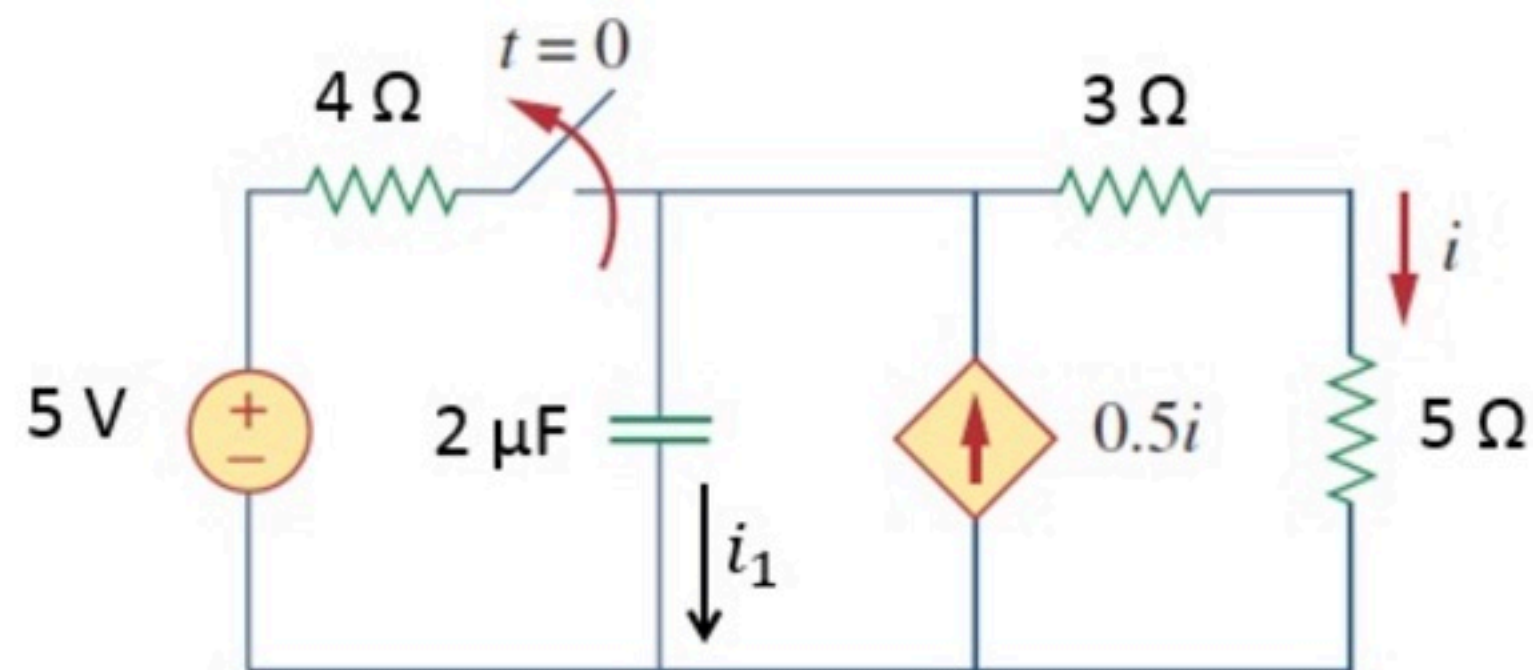Find $i_1(t) = D$ for $t = 0^-$
 $= A \cdot e^{-t/\tau} + B$ for $t > 0$



Given Variables:

...

Calculate the following:

D (A) :

0

✓

A (A) :

-0.25

✓

B (A) :

0

✓

τ (us) :

32

✓

Hint: Use a test source to find Req.