
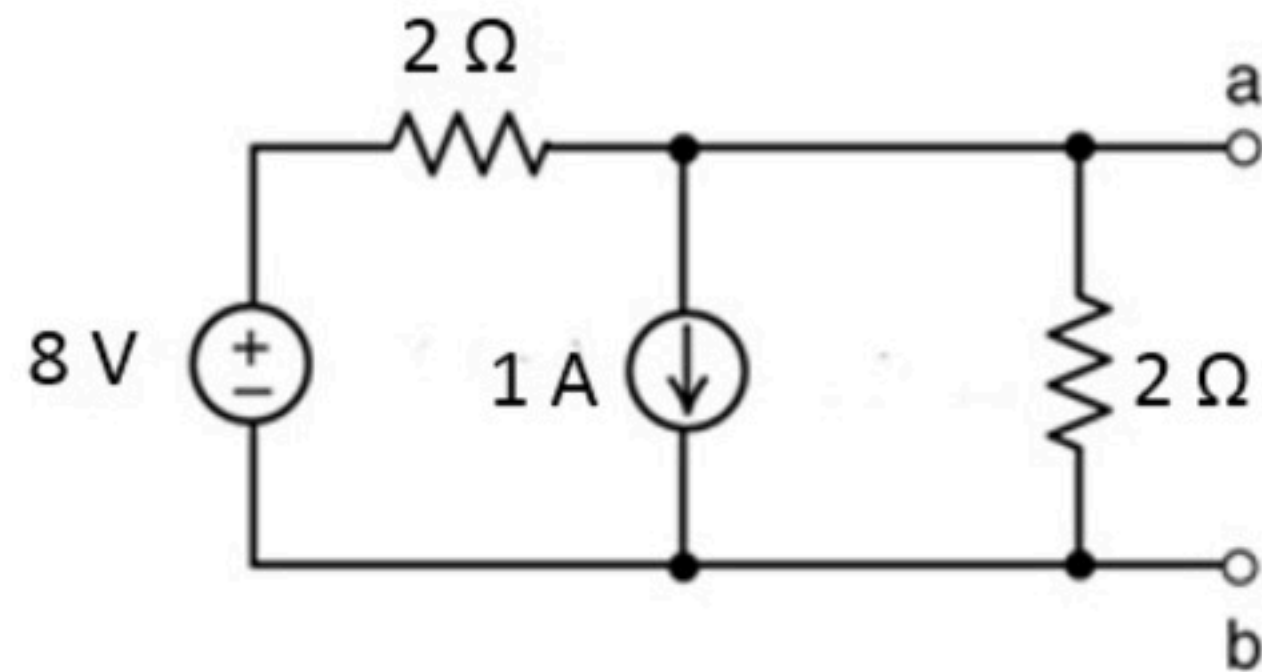


PP Circuit theorems 008

Unlimited Attempts.

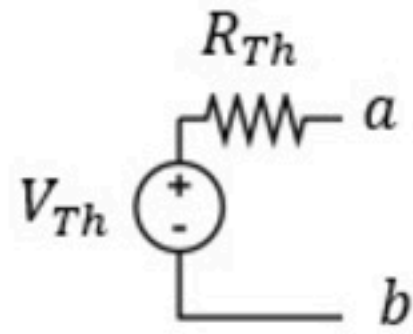Find the Thevenin equivalent model of this circuit, as seen between a and b.



Given Variables:

...

Calculate the following:

V_{th} (V) :

3



R_{th} (ohm) :

1



Hint: Try finding R_{th} directly. Find V_{oc} with superposition.