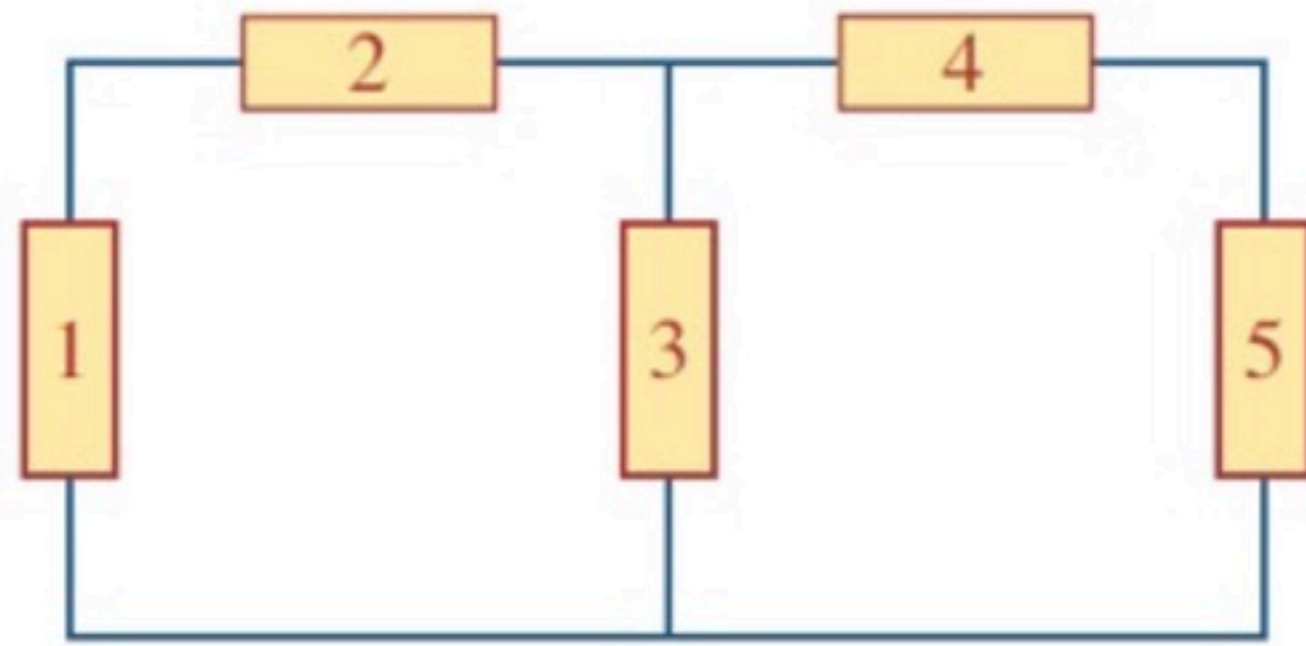


PP - Basic concepts 008

Problem has been graded.

The figure shows a circuit with 5 circuit elements.



Element 1 supplies 3 W
Element 2 supplies -5 W
Element 3 receives 8 W
Element 4 receives -1 W

How much power P does element 5 supply?

Given Variables:

$\therefore \dots$

Calculate the following:

P (W) :

9

