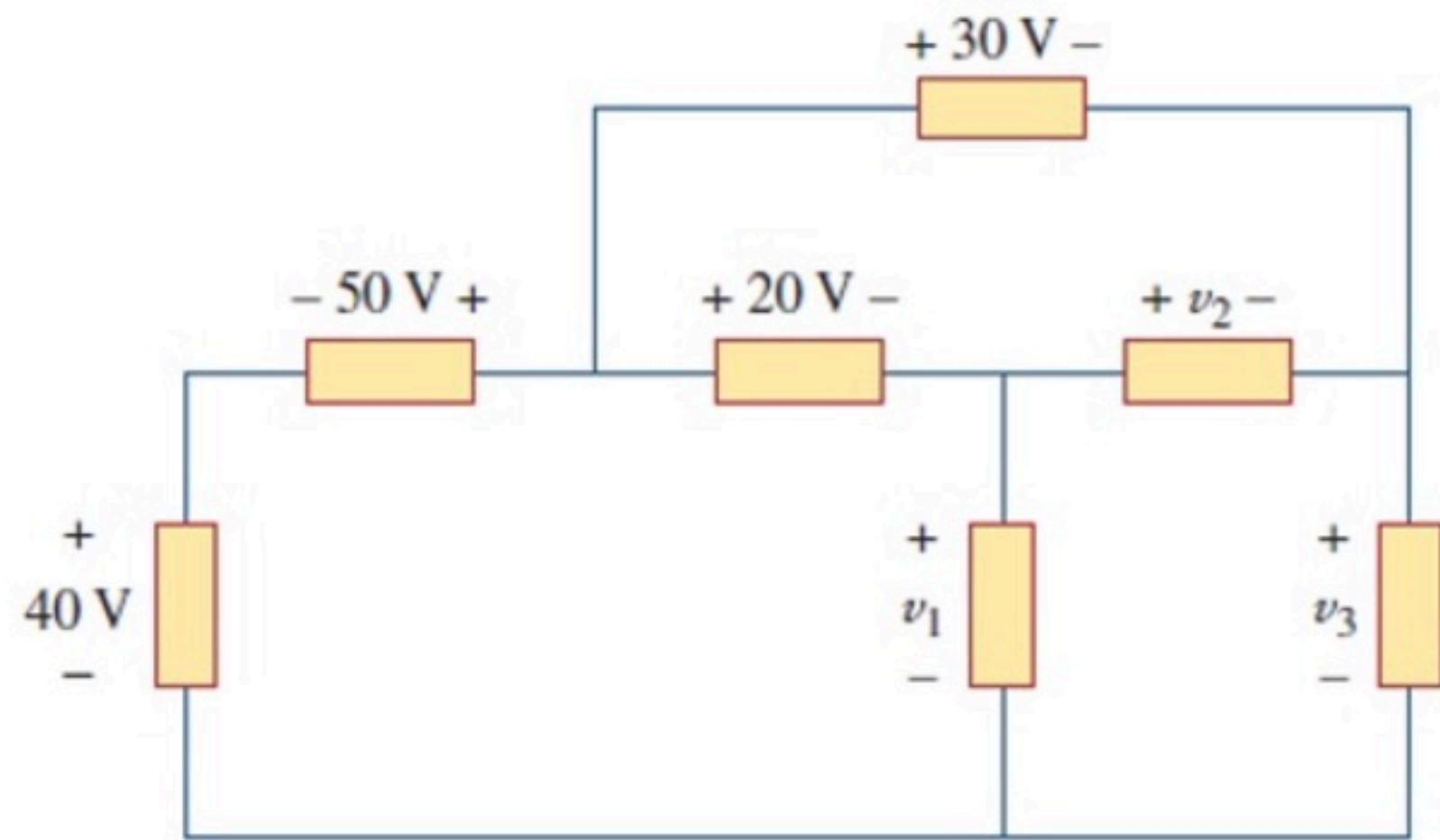


PP - Basic analysis 006

Problem has been graded.

Find the values of the missing voltages.



Given Variables:

. . .

Calculate the following:

v_1 (V) :

70



v_2 (V) :

10



v_3 (V) :

60



Hint: Use KVL