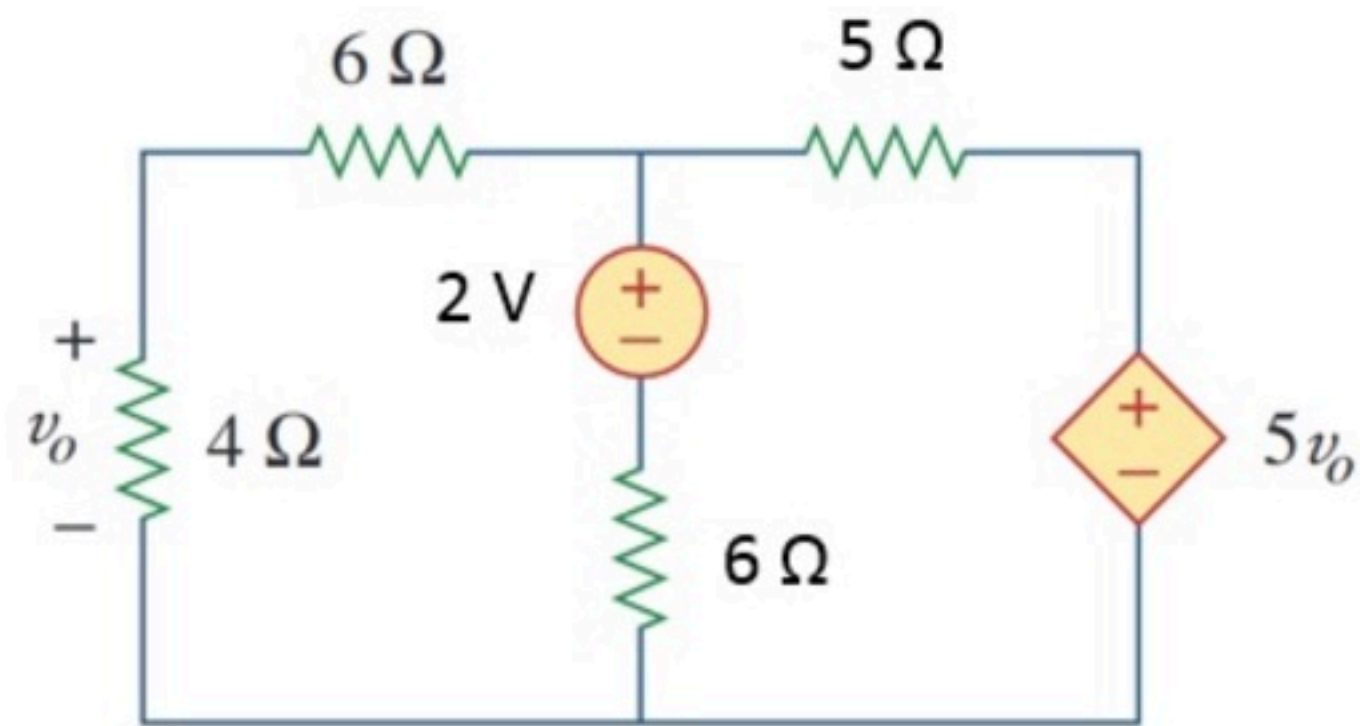


# PP Nodal Mesh 012

Unlimited Attempts.

Find the value of  $v_o$ . Solve using mesh analysis.

For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

...

Calculate the following:

$v_o$  (V) :

2



Hint: Ignore  $v_o$  at the start. Just find the two mesh currents.