

# **ECE 65: Components & Circuits Lab**

## **Lecture 8**

### **Diode waveform shaping circuits**

#### **Peak detector circuits**


Reference notes: sections 2.9

Sedra & Smith (7<sup>th</sup> Ed): sections 4.4-4.6


Saharnaz Baghdadchi

# Course map


## 2. Diodes

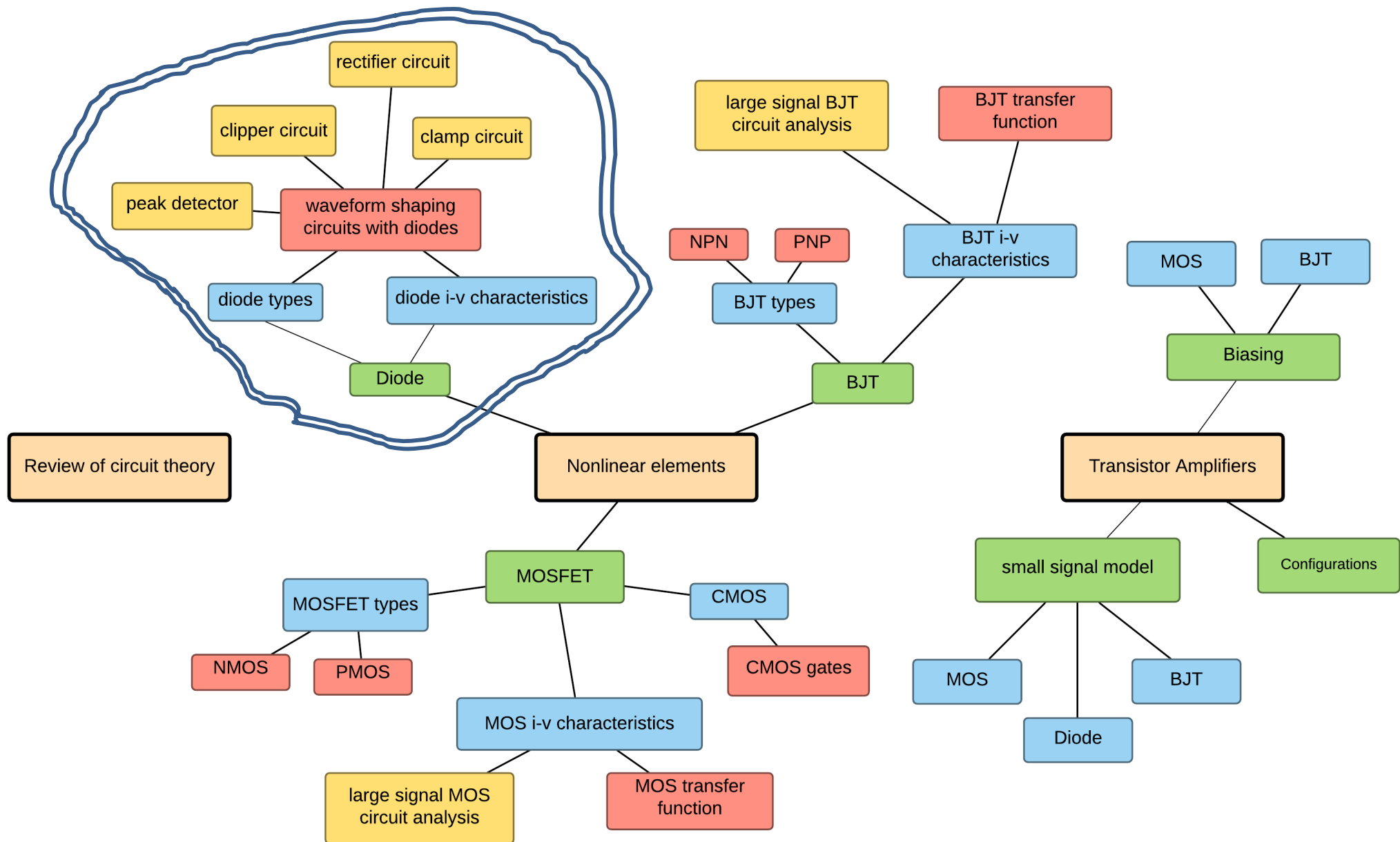


# Ideal Peak Detector Circuit

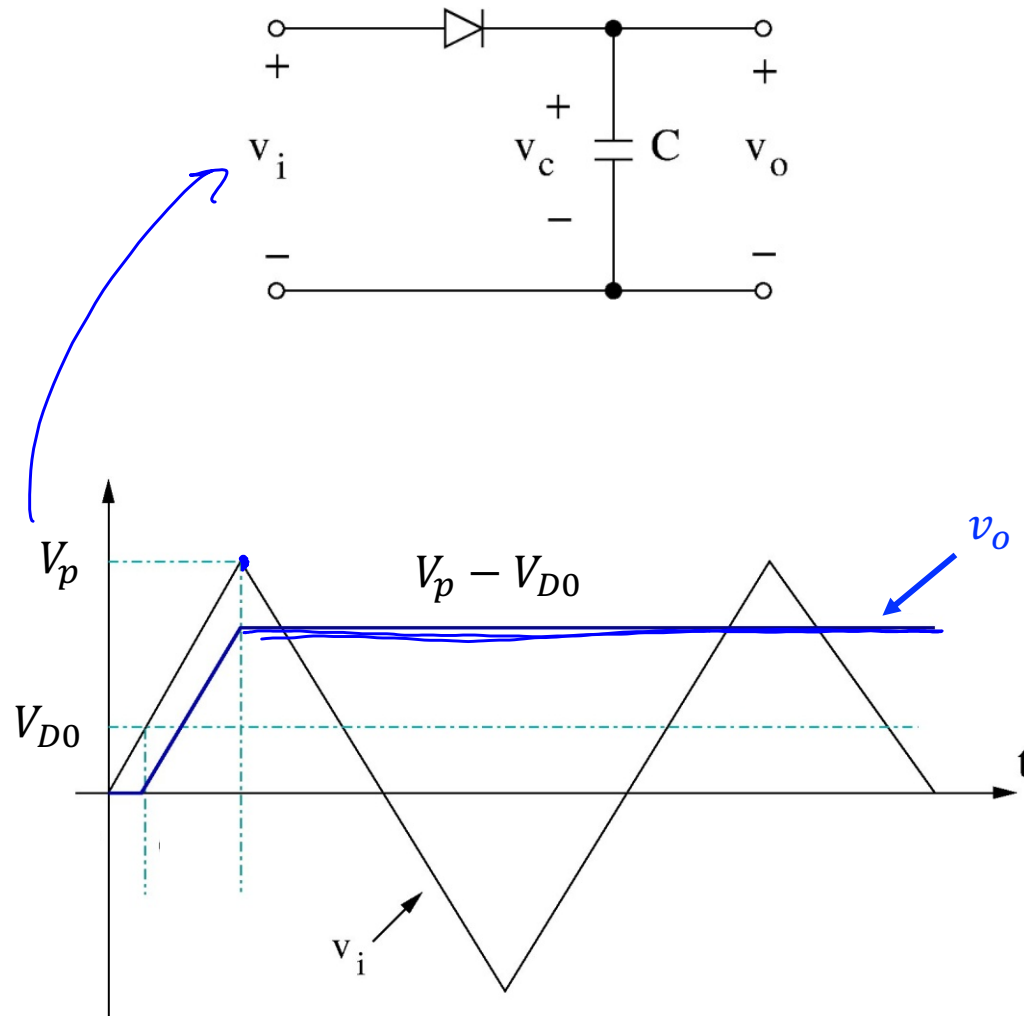

# Ideal Peak Detector Circuit

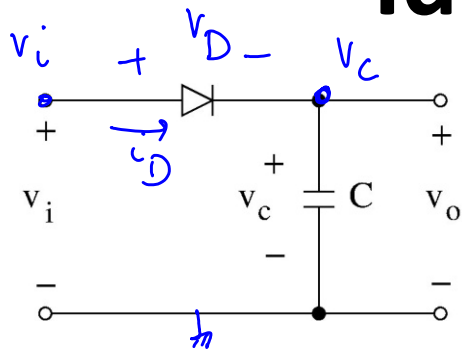


When the Diode is initially OFF:

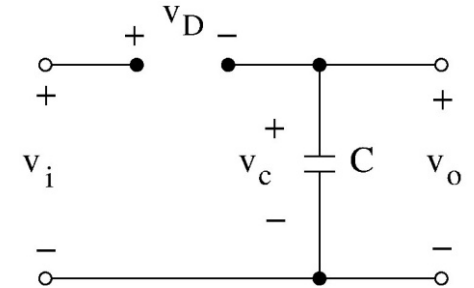


$$V_D = v_i - v_c = v_i$$

$$i_D = 0, V_D < V_{D0}$$


$$\Rightarrow v_i < v_{D0}$$

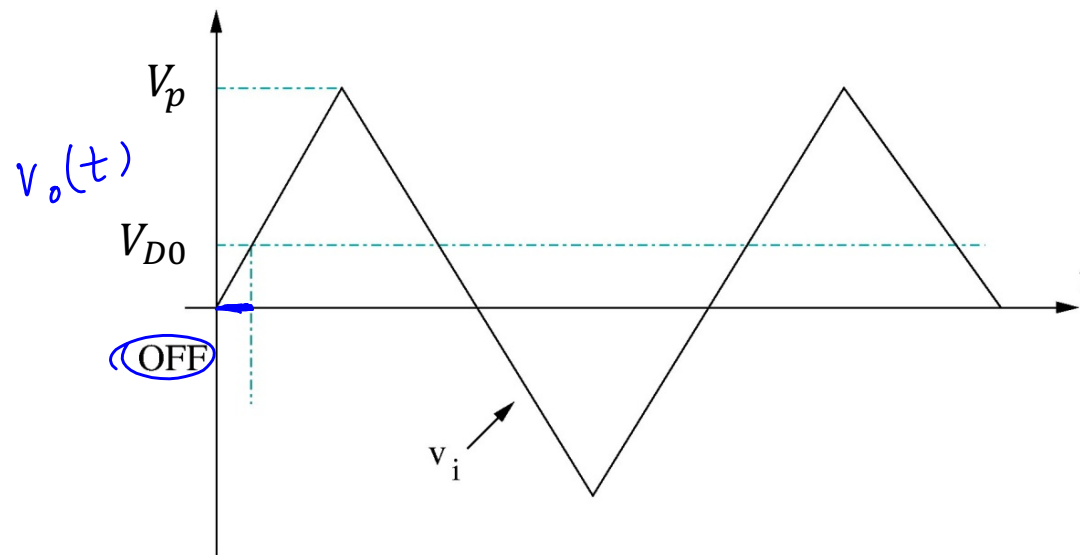

# Ideal Peak Detector Circuit

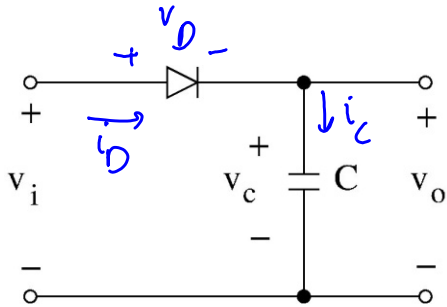

When the Diode is ON:

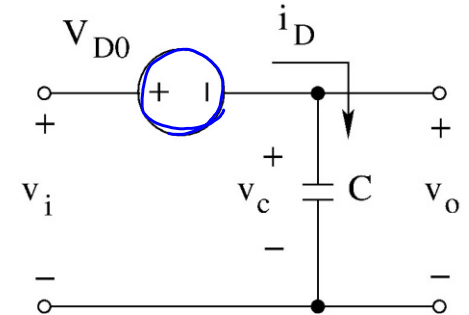


$$V_D = V_{D0}$$

$$i_D \geq 0$$

$$V_o = -V_D + V_i = -V_{D0} + V_i$$


$$i_D = i_C = C \frac{dv_c}{dt} = C \frac{d(v_i - V_{D0})}{dt}$$

$$= C \frac{dv_i}{dt}$$


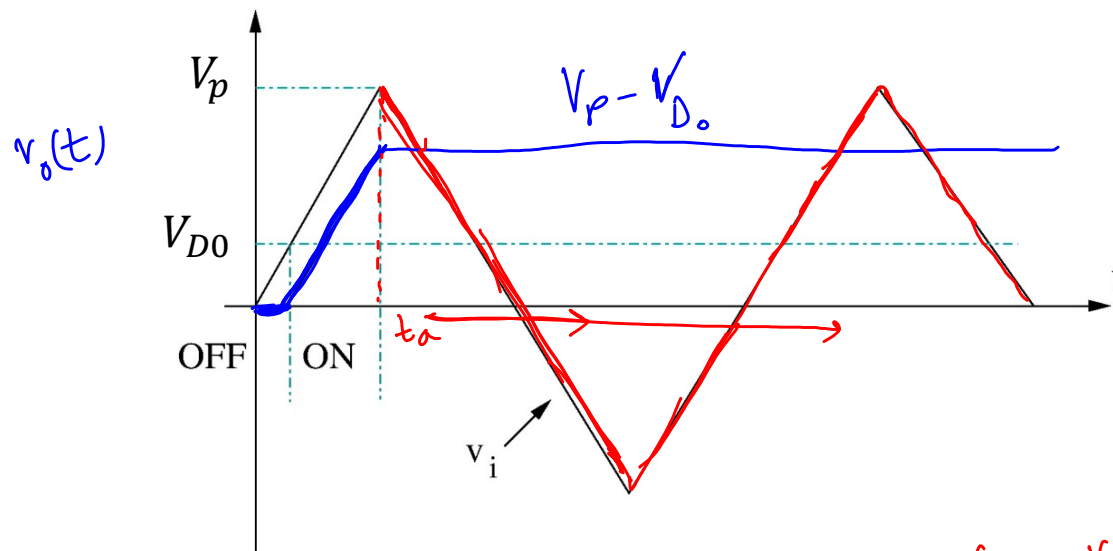


at  $t = t_a$  ,  $V_i = V_p$  ,  $V_c = V_p - V_{D0}$  ,  $V_o = V_i - V_c = V_i - (V_p - V_{D0})$


# Ideal Peak Detector Circuit

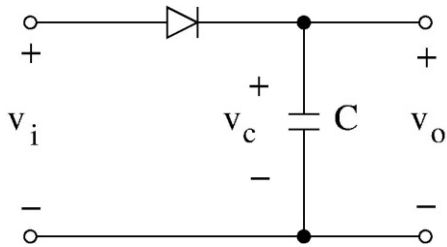

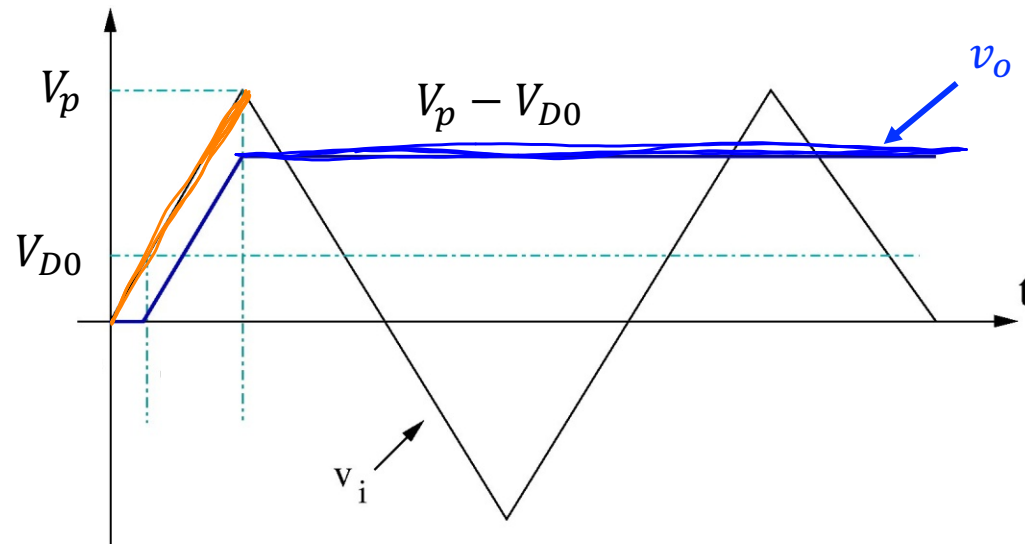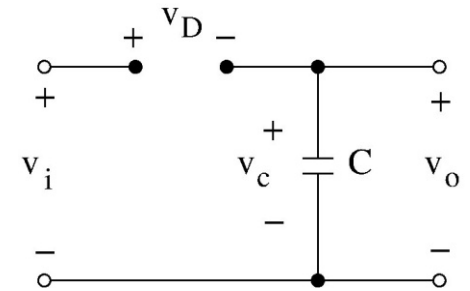After  $v_i$  reached its peak value, the diode does not turn ON anymore.




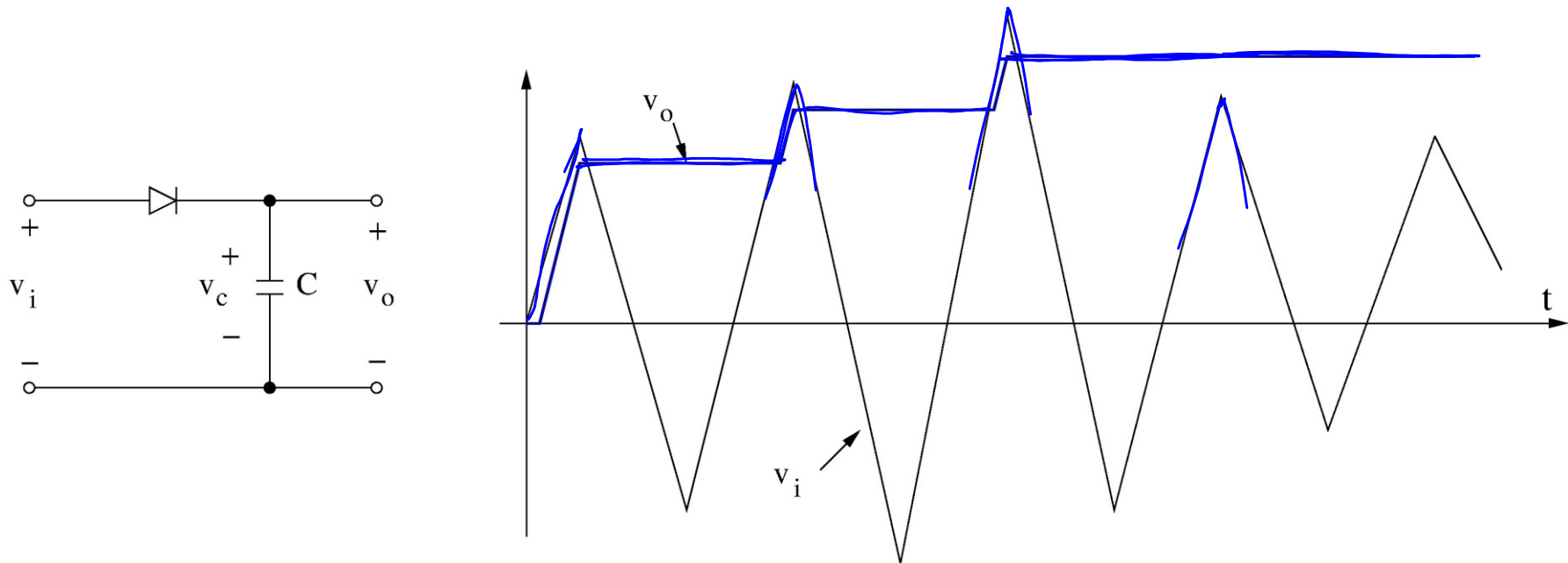
# Response of the Ideal Peak Detector ( $v_i$ amplitude changes)



$v_o$  is the “peak” value of input waveform (  $V_p - V_{D0}$  ):

Note  $v_o$  did not “drop” after the peak was decreased in the 3<sup>rd</sup> cycle.

# Practical Peak Detector Circuit

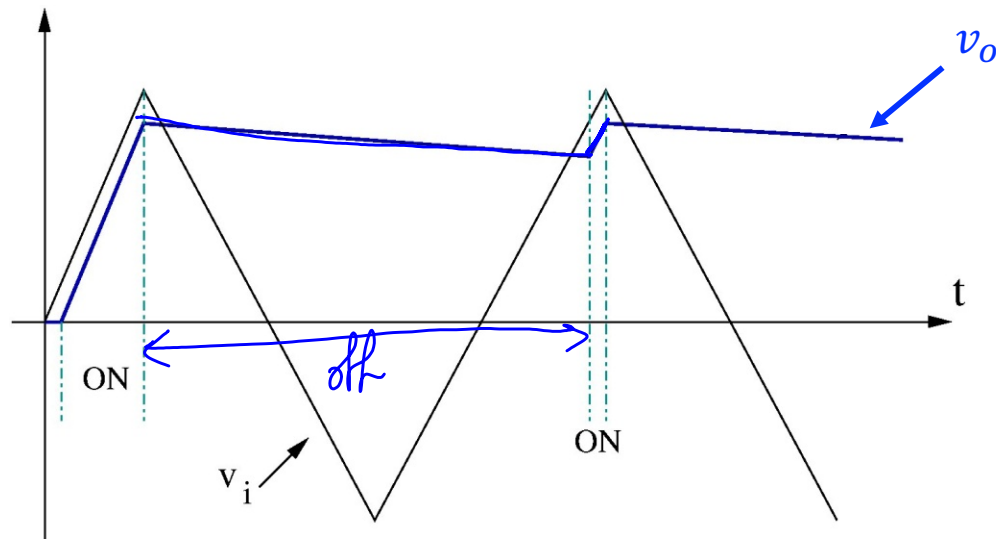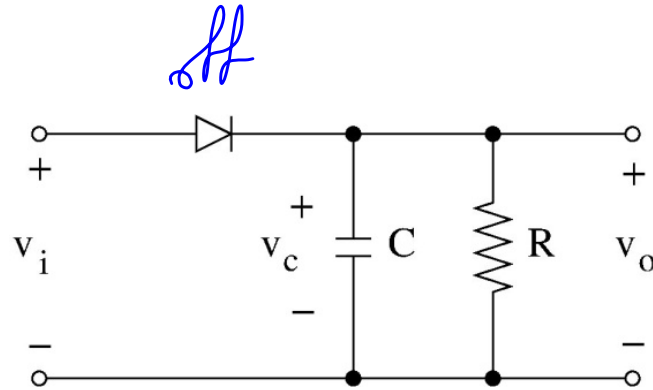



# Practical Peak Detector Circuit




Diode OFF:  $i_D = 0$  and  $v_D < V_{D0}$

Capacitor discharges into the resistor with a time constant of  $\tau = RC$

$$v_o = v_c(t) = v_{c0} e^{-(t-t_0)/\tau}$$

$$v_D = v_i - v_c < V_{D0}$$

$$\rightarrow v_i < v_c(t) + V_{D0}$$

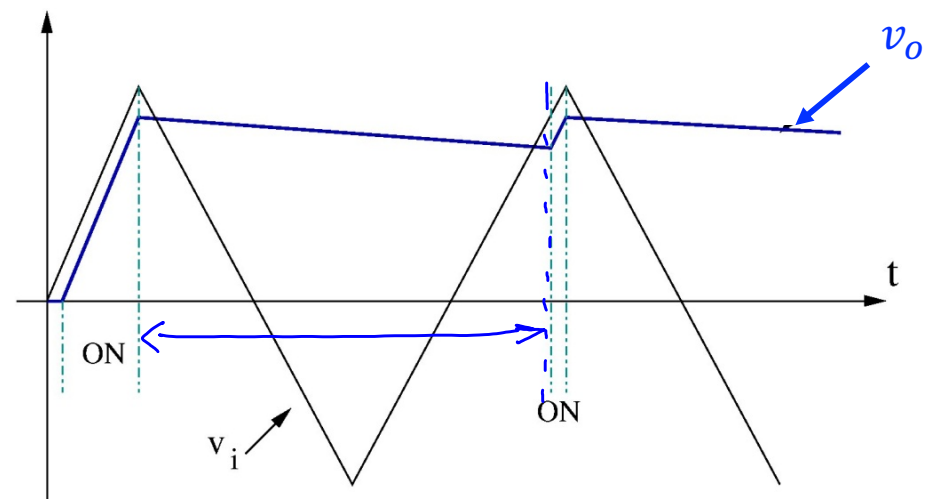
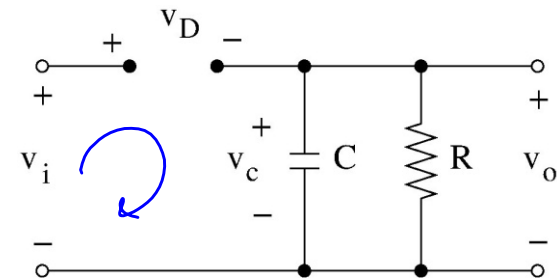
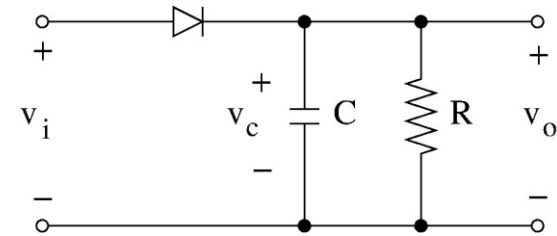


# Practical Peak Detector Circuit

Diode ON:  $v_D = V_{D0}$  and  $i_D \geq 0$

$$v_o = v_C = v_i - V_{D0}$$
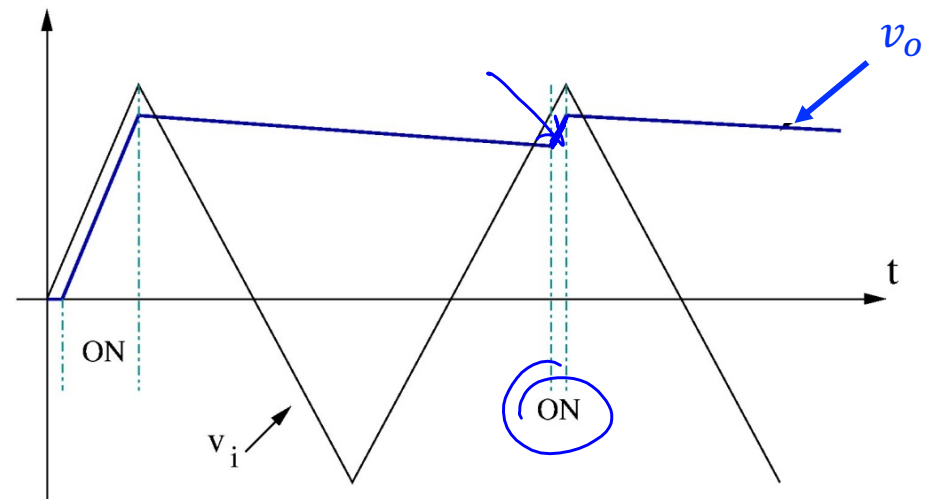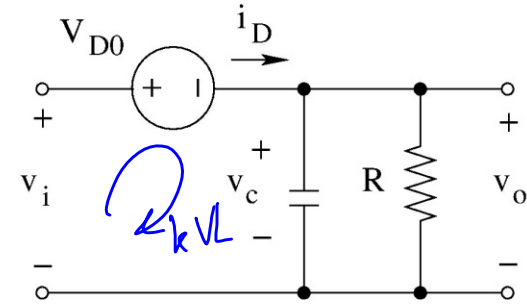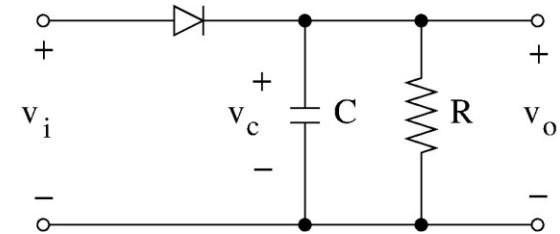
$$i_C = C \frac{dv_C}{dt} = C \frac{d(v_i - V_{D0})}{dt} = C \frac{dv_i}{dt}$$



# Response of the Practical Peak Detector

Shape of output signal depends on the ratio of  $\tau/T$



“ideal” peak detector:  $\tau/T \rightarrow \infty$

“Good” peak detector:  $\tau/T \gg 1$

As  $\tau/T$  decreases, the circuit departs from a peak detector.


For  $\tau/T \ll 1$ , capacitor discharges very fast and circuit resembles a rectifier circuit

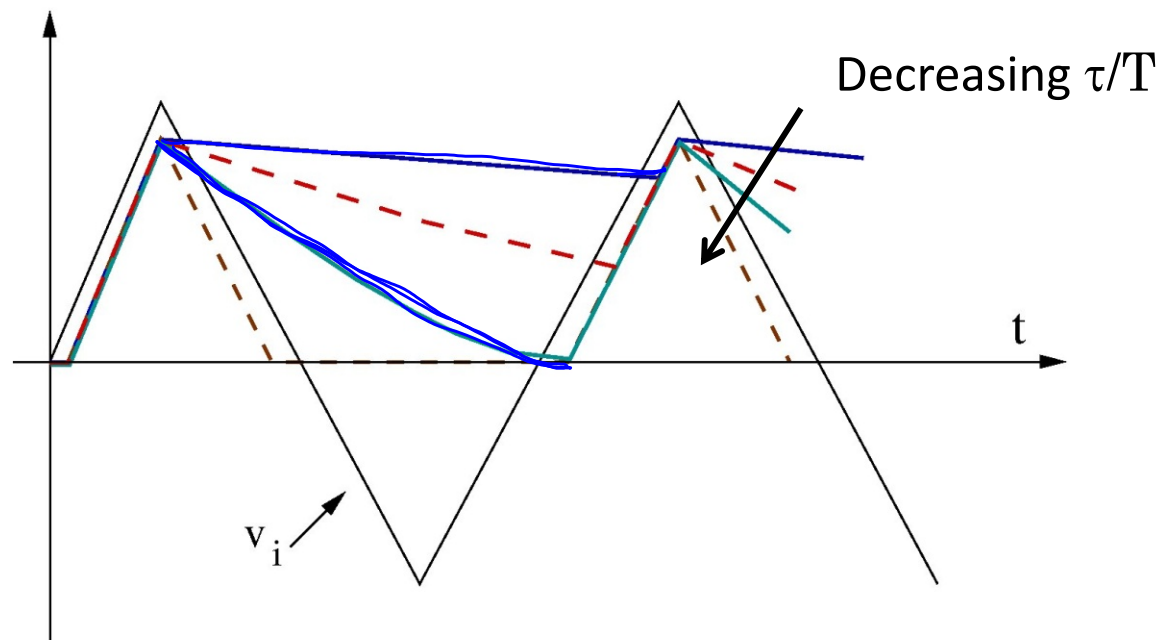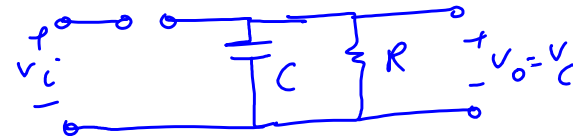$\tau$ : time constant  $= RC$   
 $T$ : period of  $v_i(t)$







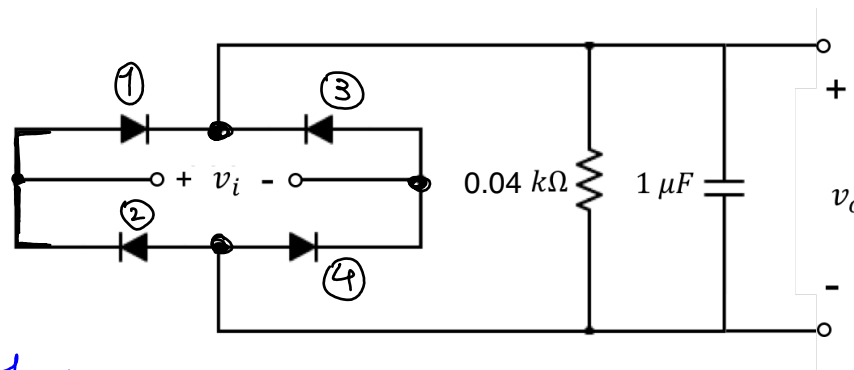
# Lecture 8 reading quiz.

In the following diode circuit, which one of the options could be the input and output voltages for this circuit?  $V_{D0} = 0.7\text{ V}$ .



$$T = 1\text{ms}$$
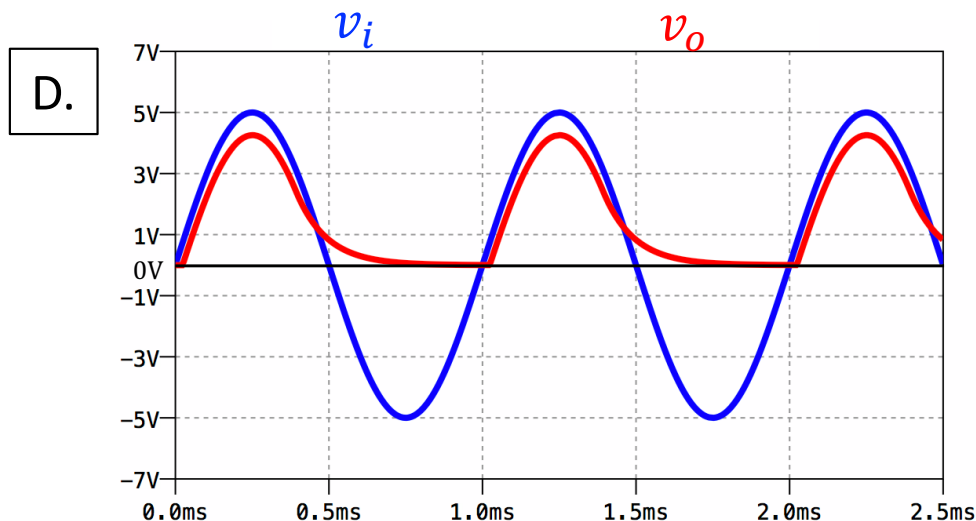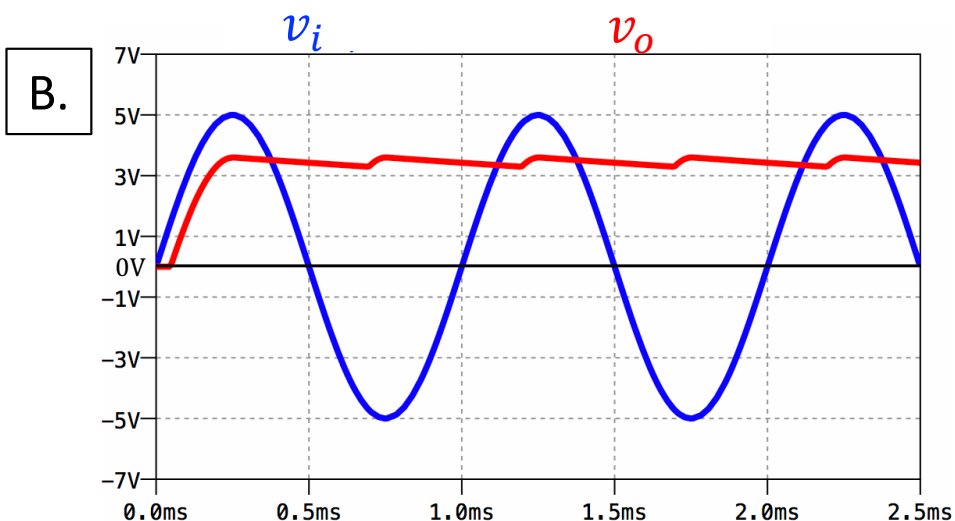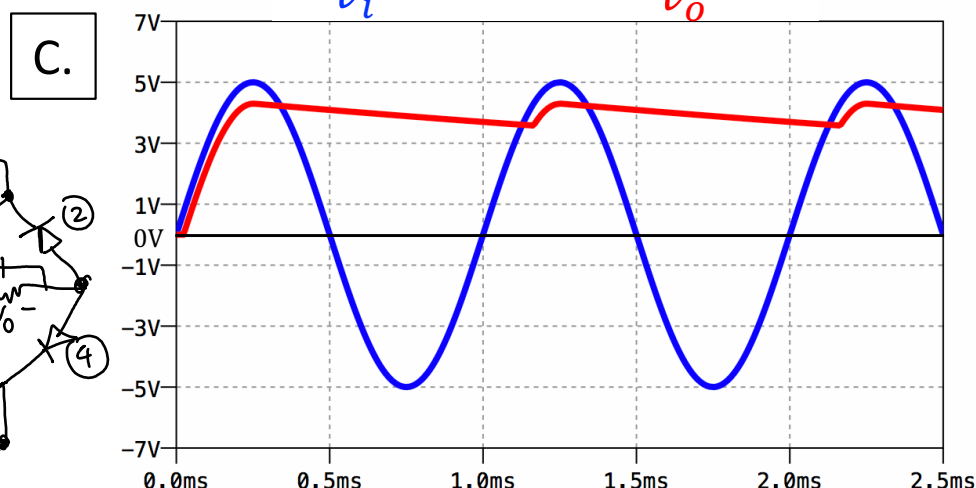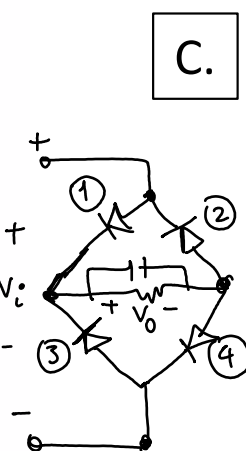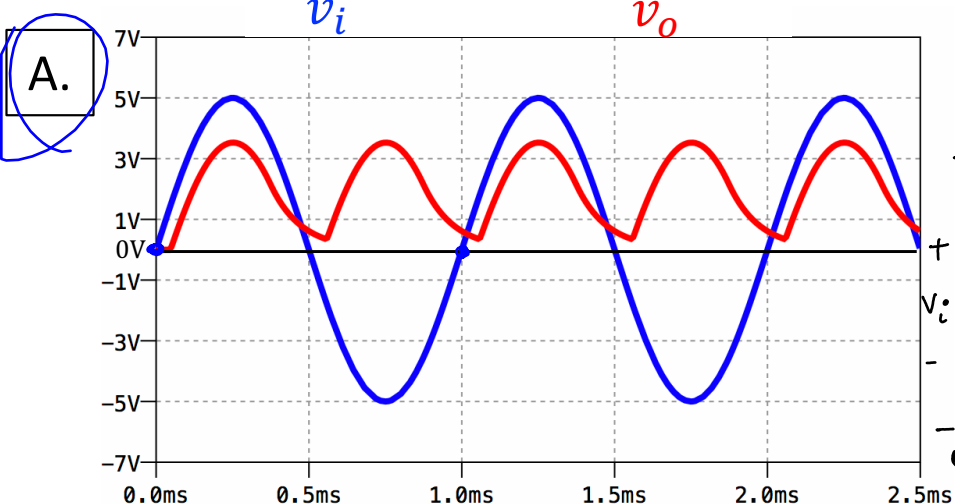
$$\tau = RC = 0.04\text{k}\Omega \times 1\mu\text{F} = 0.04\text{ms} < T/2$$





$$T = \frac{2\pi}{\omega} = \frac{2\pi \text{ (rad)}}{1000 \text{ (rad/s)}} = 2\pi \text{ (ms)} = 2 \times 3.14 \text{ ms}$$
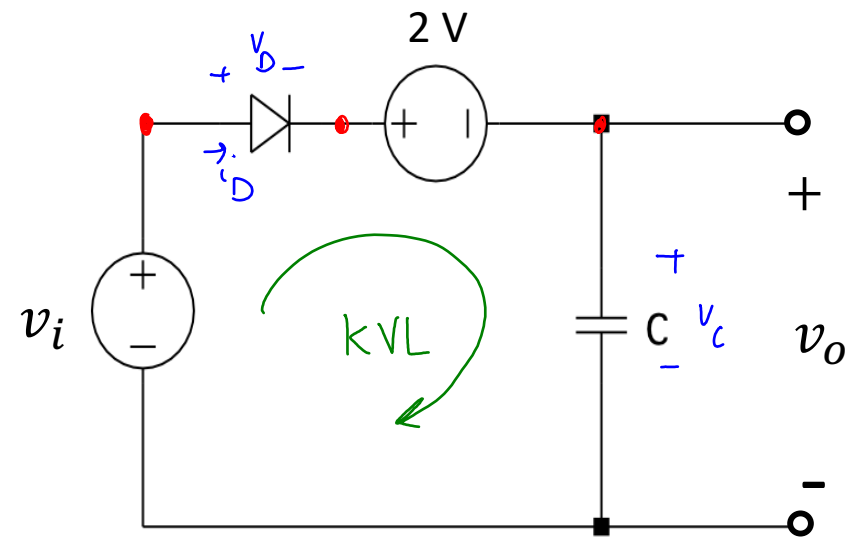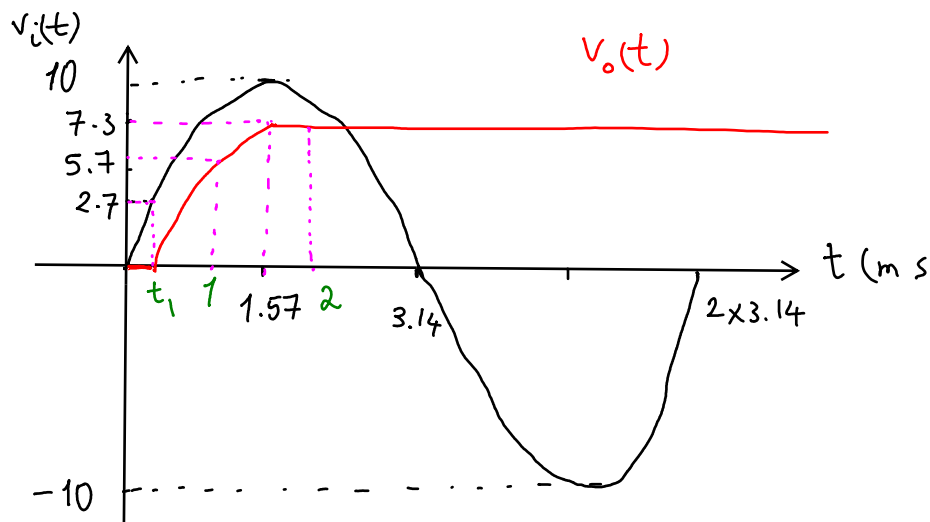
## Discussion question 1.

In the circuit below,  $v_i(t) = 10 \sin(\omega t)$  where  $\omega = 1000 \text{ rad/s}$ ,  $v_c(0) = 0$ .

$V_{D0} = 0.7 \text{ V}$ . What is the value of  $v_o(t)$  at  $t = 1 \text{ ms}$  and  $t = 2 \text{ ms}$ ? Draw one cycle of the input and output waveforms.



For  $0 < t < t_1 \rightarrow$  diode is off  $\rightarrow V_o = V_C = 0$

For  $t_1 \leq t < 1.57 \text{ ms} \rightarrow$  diode is ON and capacitor is charging  $\Rightarrow V_D = V_{D0}$  and

KVL:  $-V_i + V_D + 2\text{V} + V_o = 0$ , here:  $-V_i + 0.7\text{V} + 2\text{V} + V_o = 0 \Rightarrow \boxed{V_o = V_i - 2.7\text{V}}$

$t = 1\text{ms}$  is before the peak of  $V_i$ , ( $t_{\text{peak}} = 1.57\text{ms}$ ).

$$V_i(t = 1\text{ms}) = 10 \sin(1000 \text{ rad/s} \times 1\text{ms}) = 8.4\text{V}$$

$8.4\text{V} > V_i(t = t_1) = 2.7\text{V} \Rightarrow$  diode is ON at  $t = 1\text{ms}$  and the capacitor is charging.

$$V_o(t = 1\text{ms}) = V_i(t = 1\text{ms}) - 2.7\text{V} = 8.4\text{V} - 2.7\text{V} = 5.7\text{V}$$

$t = 2\text{ms}$  is after the peak of  $V_i \Rightarrow$  the diode is off and the voltage across the capacitor is constant even when  $V_i$  changes.

KVL still holds, and  $V_D < V_{D_0}$ .

$$\text{After } t = 1.57\text{ms}, V_o = V_c = 10\text{V} - 2.7\text{V} = 7.3\text{V}$$