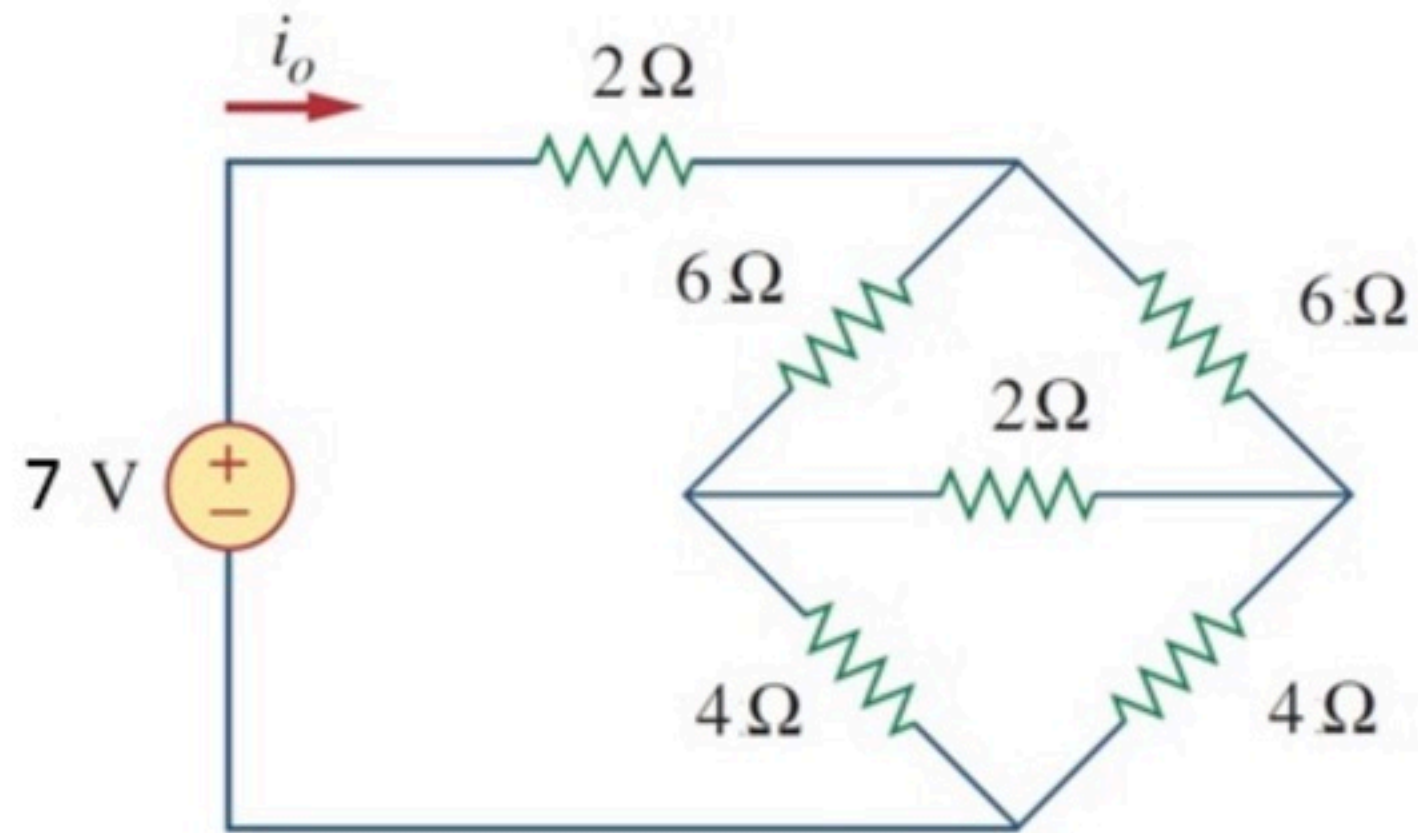


PP Nodal Mesh 014

Unlimited Attempts.

Find the current i_o . Solve using mesh analysis.

For extra practice: Afterwards solve again using nodal analysis.



Given Variables:

...

Calculate the following:

i_o (A) :

1



Hint: Symmetry will result in easier equations