


# PP Capacitors Inductors 002

Unlimited Attempts.

Below is the current through a  $400\ \mu\text{F}$  capacitor. The voltage across the capacitor at time  $t = 0$  is  $5\ \text{V}$ .

What is the voltage  $v_1$  across the capacitor at time  $t = 3\ \text{s}$ ?

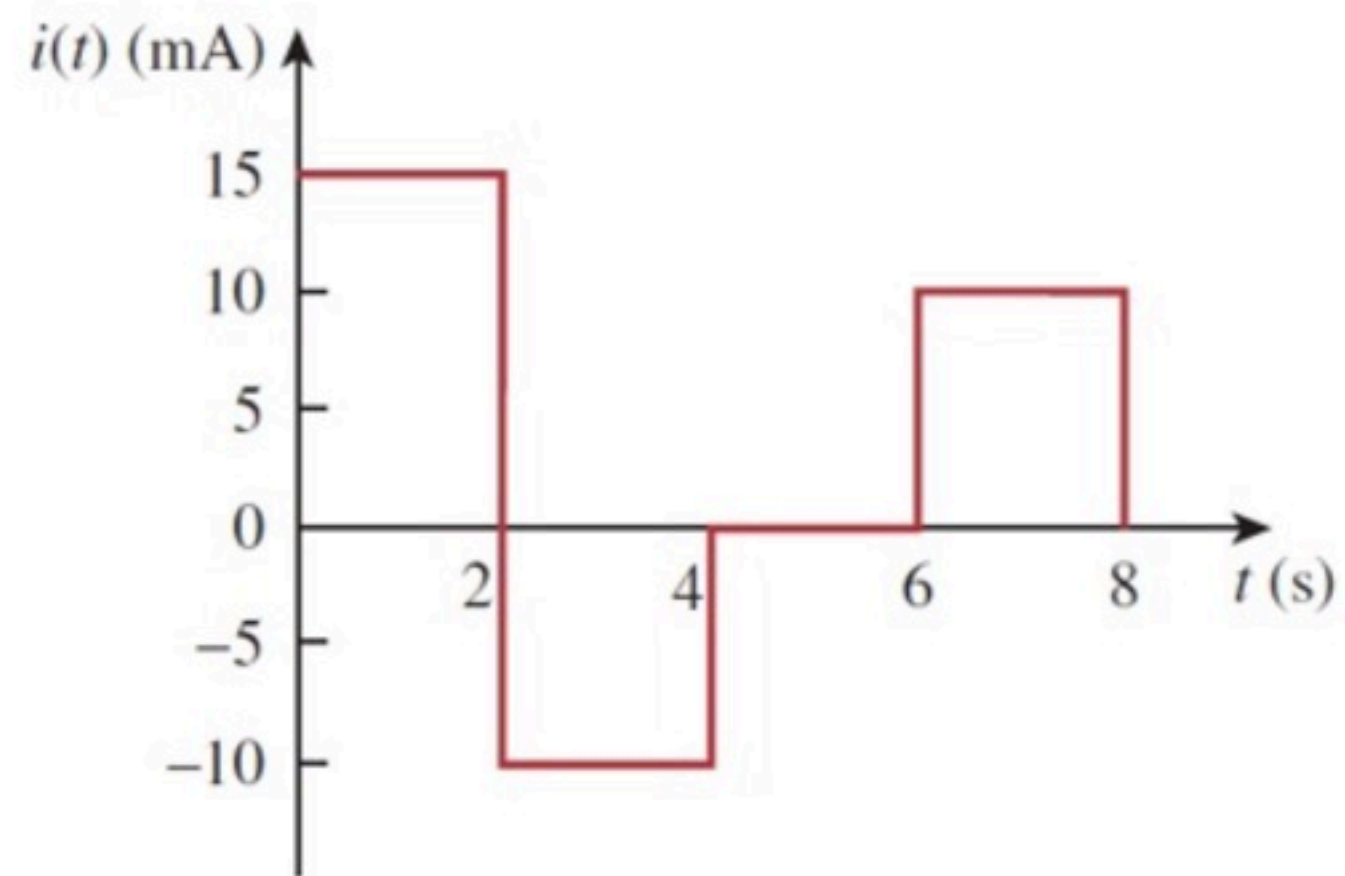What is the voltage  $v_2$  across the capacitor at time  $t = 8\ \text{s}$ ?



Given Variables:

...

Calculate the following:

$v_1$  (V) :

55



$v_2$  (V) :

80



Hint: Check the units.