

# **ECE 65: Components & Circuits Lab**

## **Lecture 20**

### **Transistor Amplifier Biasing**


Reference notes: sections 5.3

Sedra & Smith (7<sup>th</sup> Ed): sections 7.4


Saharnaz Baghdadchi

# Course map
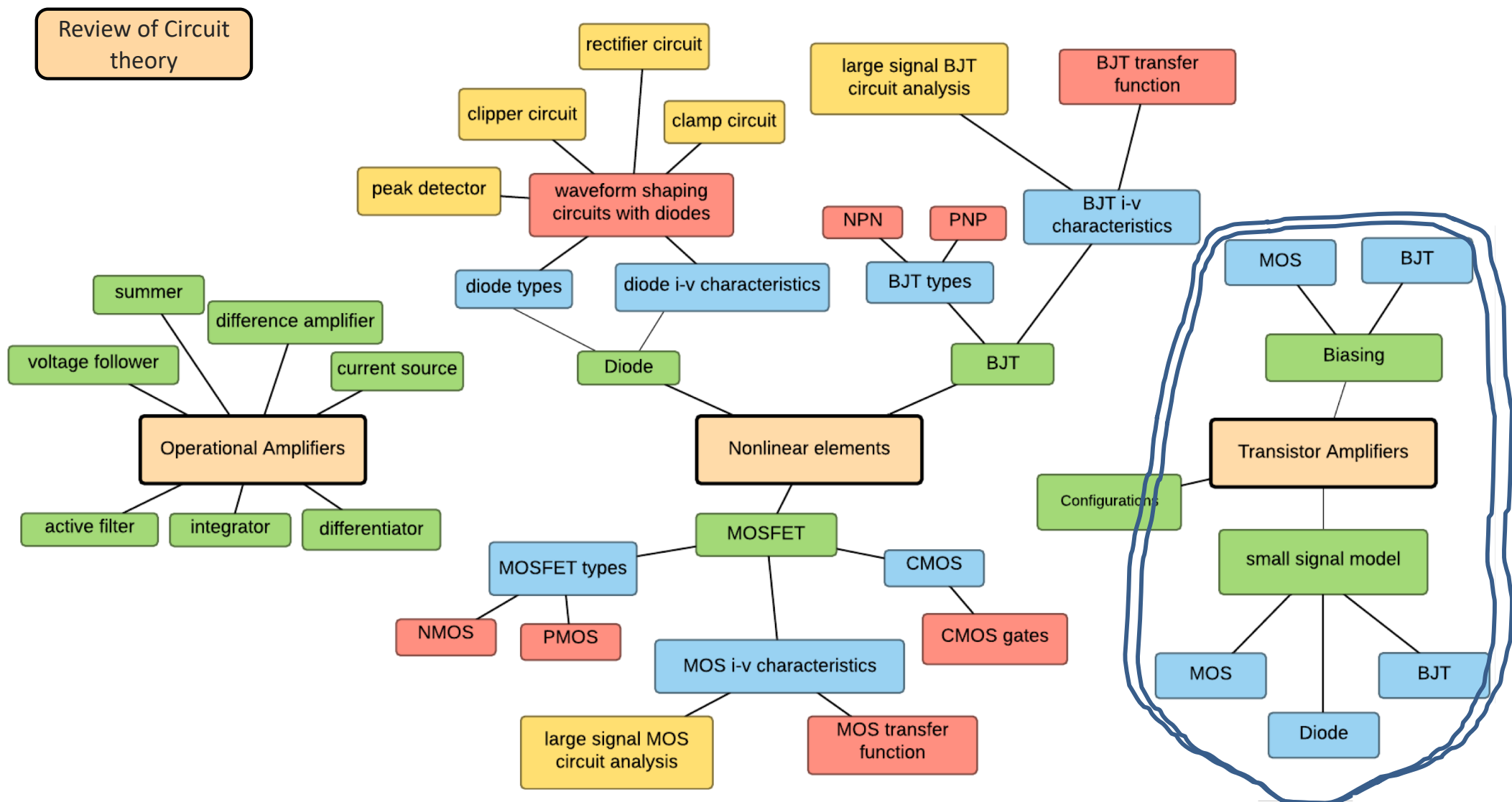
## 6. Transistor Amplifiers – Bias and small signal




# How to establish a Bias point

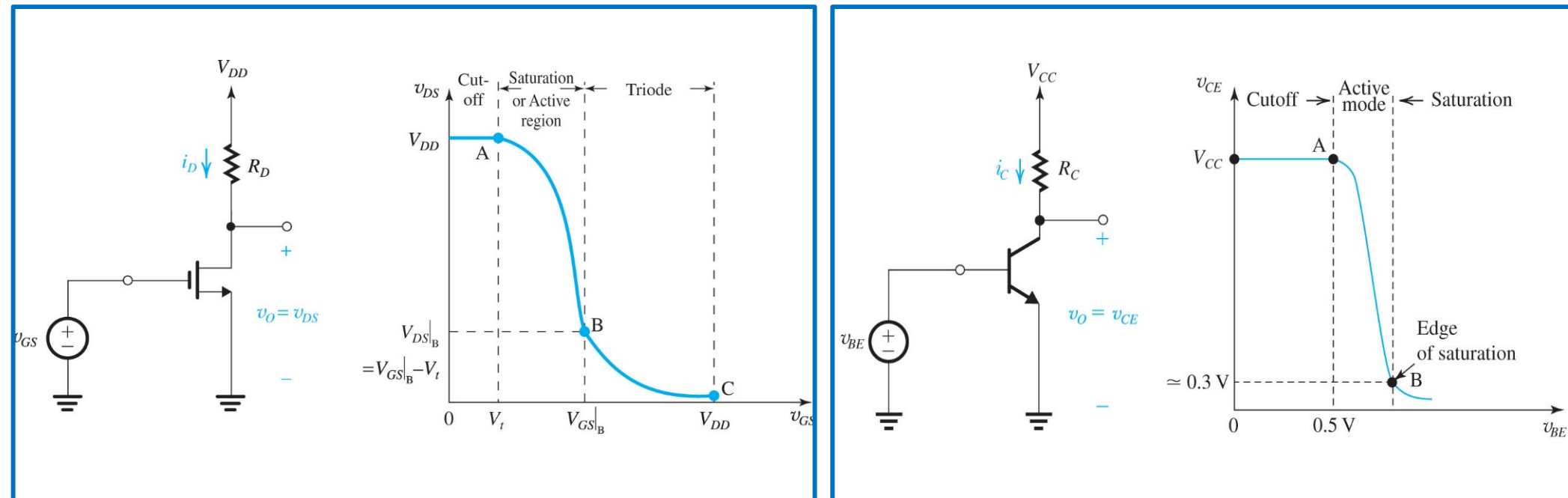

- Stable and robust bias point should be predictable and insensitive to variations in temperature and to the manufacturing variability in the transistor parameter values such as  $V_t$ ,  $\mu_n$ ,  $C_{ox}$ ,  $(W/L)$  and  $\beta$ .
- Bias point details impact the small signal response (e.g., gain of the amplifier).

# BJT Fixed Bias

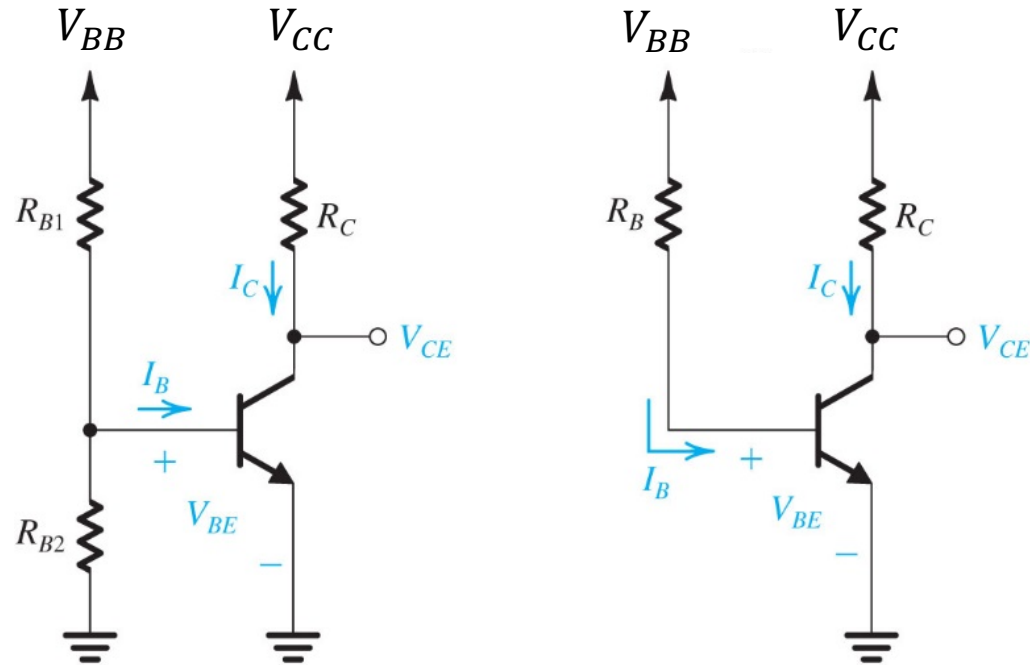


BE KVL:  $V_{BB} = I_B R_B + V_{BE}$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} \quad , \quad I_C = \beta I_B = \beta \frac{V_{BB} - V_{BE}}{R_B}$$

CE KVL:  $V_{CC} = I_C R_C + V_{CE}$
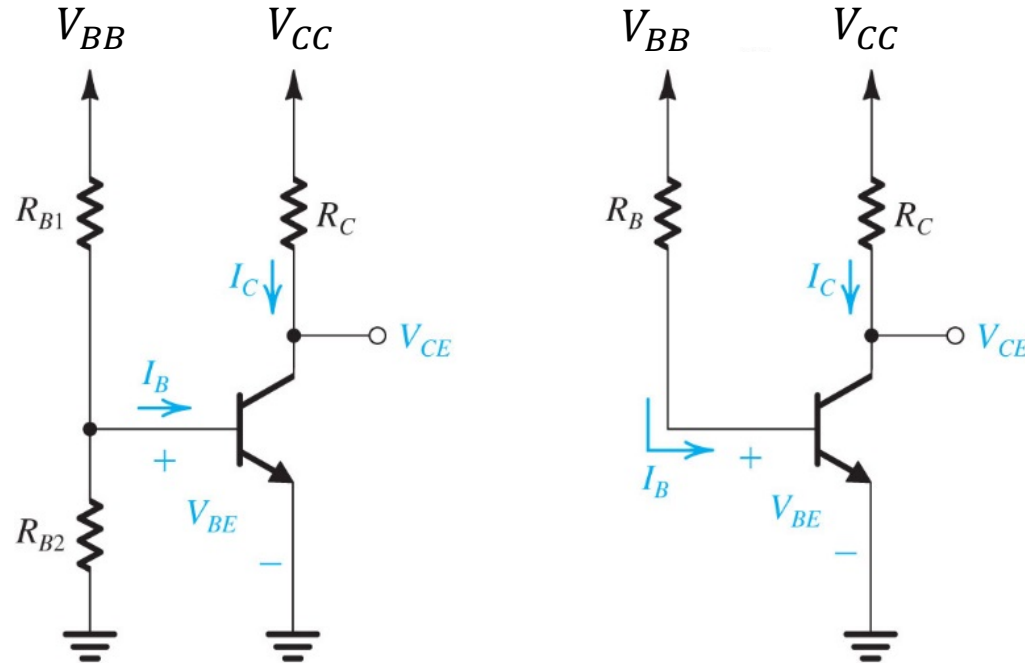
# Why biasing with base voltage (fixed bias) does not work?



Changes in BJT  $\beta$  or  $V_{BE}$  values, changes the bias point drastically.

- BJT can end up in saturation or in cut-off easily.

To operate a BJT in the active region,  $I_C > 0$  ,  $V_{CE} > V_{D0}$

# Biasing with Emitter Degeneration

Requires a resistor in the emitter circuit!

BE KVL:  $V_{BB} = I_B R_B + V_{BE} + I_E R_E$

$$V_{BB} - V_{BE} = I_E \left( \frac{R_B}{\beta + 1} + R_E \right)$$


If  $R_B \ll (\beta + 1)R_E$

$$V_{BB} - V_{BE} \approx I_E R_E$$

$$I_E \approx I_C \approx \frac{V_{BB} - V_{BE}}{R_E}$$




$I_C$  is independent of  $\beta$

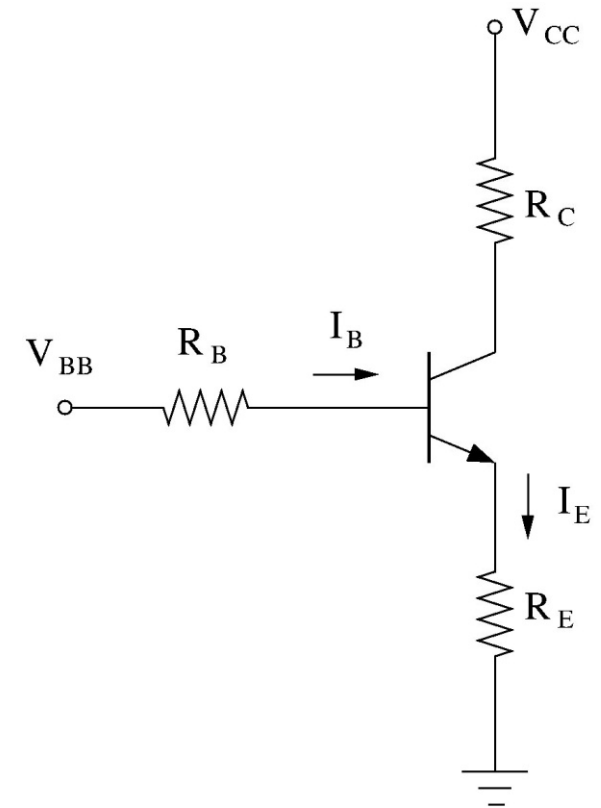
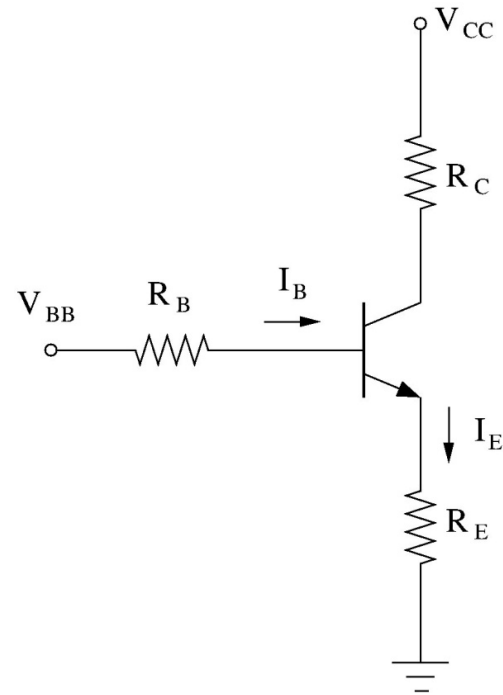
# Emitter resistor provides negative feedback!


$$\left\{ \begin{array}{l} V_{BB} - V_{BE} \approx I_E R_E \\ I_C \propto e^{V_{BE}/V_T} \end{array} \right.$$



## Negative Feedback:


- If  $I_C \approx I_E \uparrow$  (because  $\beta \uparrow$ ),  $\xrightarrow{\text{BE-KVL}} V_{BE} \downarrow \xrightarrow{\text{BE junction}} I_C \approx I_E \downarrow$
- If  $I_C \approx I_E \downarrow$  (because  $\beta \downarrow$ ),  $\xrightarrow{\text{BE-KVL}} V_{BE} \uparrow \xrightarrow{\text{BE junction}} I_C \approx I_E \uparrow$

# Emitter-degeneration bias circuits

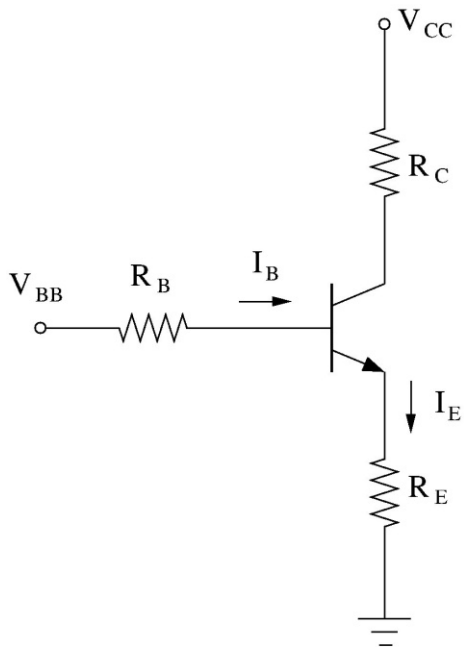


**Basic Arrangement**

$$V_{BB} = I_B R_B + V_{BE} + I_E R_E$$

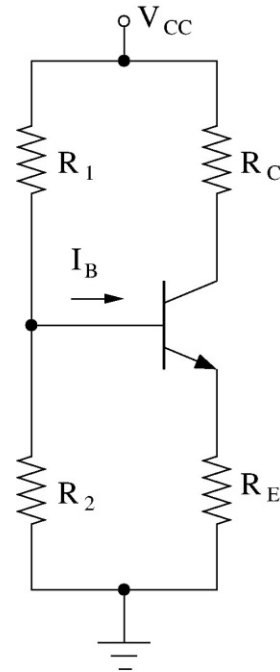

**Bias with one power supply  
(voltage divider)**

$$V_{BB} = I_B R_B + V_{BE} + I_E R_E$$

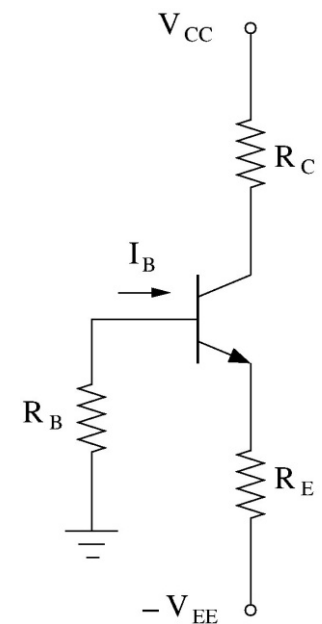

**Bias with two power supplies**


$$V_{EE} = I_B R_B + V_{BE} + I_E R_E$$



# MOS Fixed Bias

$$I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_t)^2$$

$$V_{DS} = V_{DD} - I_D R_D$$

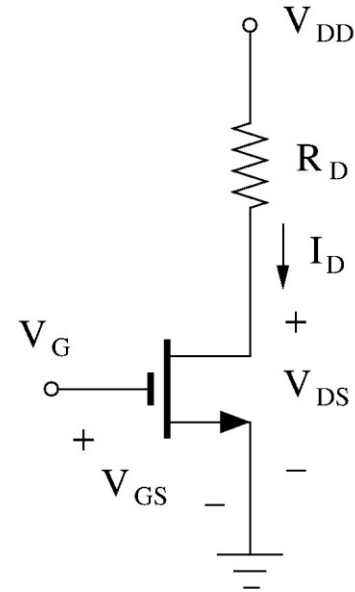


This method is NOT desirable as  $\mu_n C_{ox} (W/L)$  and  $V_t$  vary widely among devices of the same manufacturer's part number.

Bias point (i.e.,  $I_D$  and  $V_{DS}$ ) can change drastically due to temperature and/or manufacturing variability.
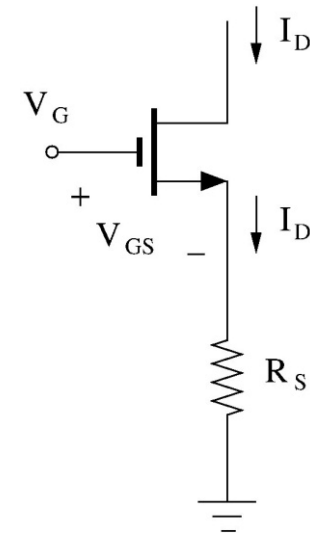
# MOS bias with Source Degeneration

(Resistor  $R_S$  provides negative feedback!)


$$\left\{ \begin{array}{l} V_{GS} = V_G - I_D R_S \\ I_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_t)^2 \end{array} \right.$$



## Negative Feedback:


- If  $I_D \uparrow$  (because  $\mu_n C_{ox} (W/L) \uparrow$  or  $V_t \downarrow$ )  $\xrightarrow{\text{GS KVL}} V_{GS} \downarrow \xrightarrow{I_D \text{ Eq.}} I_D \downarrow$
- If  $I_D \downarrow$  (because  $\mu_n C_{ox} (W/L) \downarrow$  or  $V_t \uparrow$ )  $\xrightarrow{\text{GS KVL}} V_{GS} \uparrow \xrightarrow{I_D \text{ Eq.}} I_D \uparrow$

# Source-degeneration bias circuits

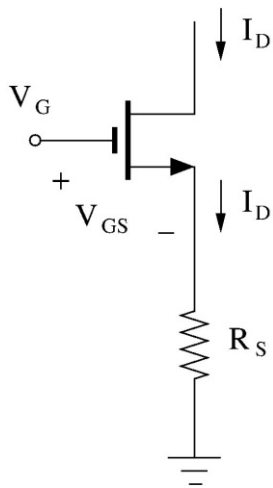


**Basic Arrangement**

$$V_G = V_{GS} + I_D R_S$$

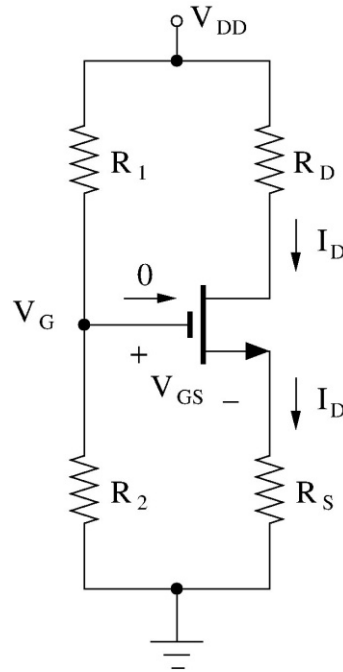

**Bias with one power supply  
(voltage divider)**



$$V_G = V_{GS} + I_D R_S$$

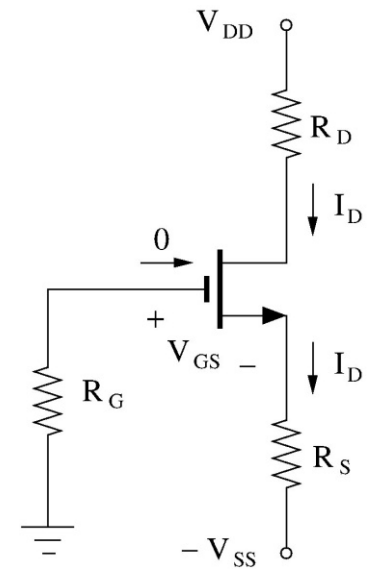


**Bias with two power supplies**

$$V_{SS} = V_{GS} + I_D R_S$$


# Biasing with a current source

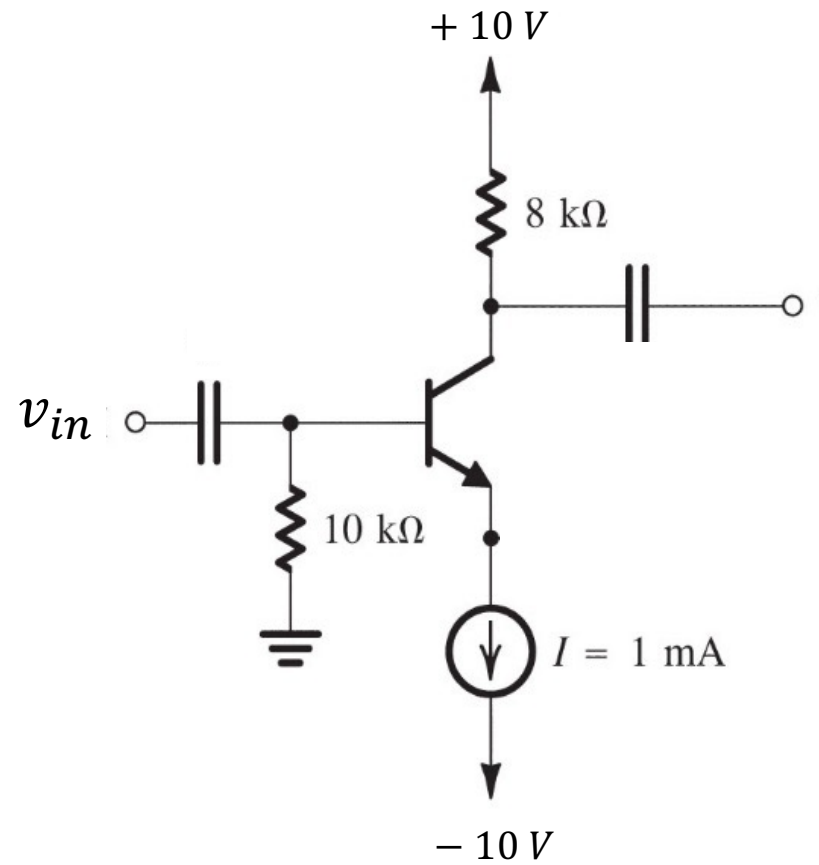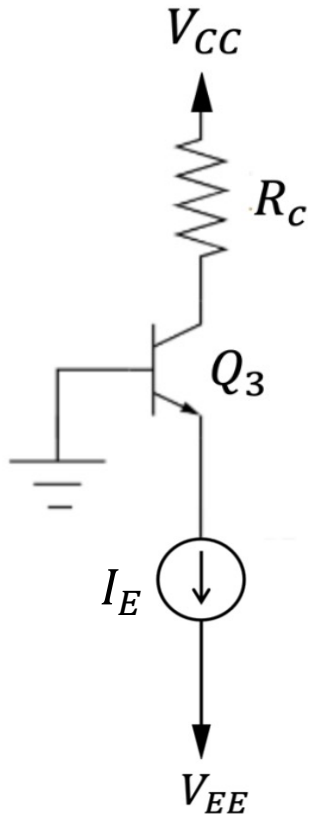

# Biasing with a current source

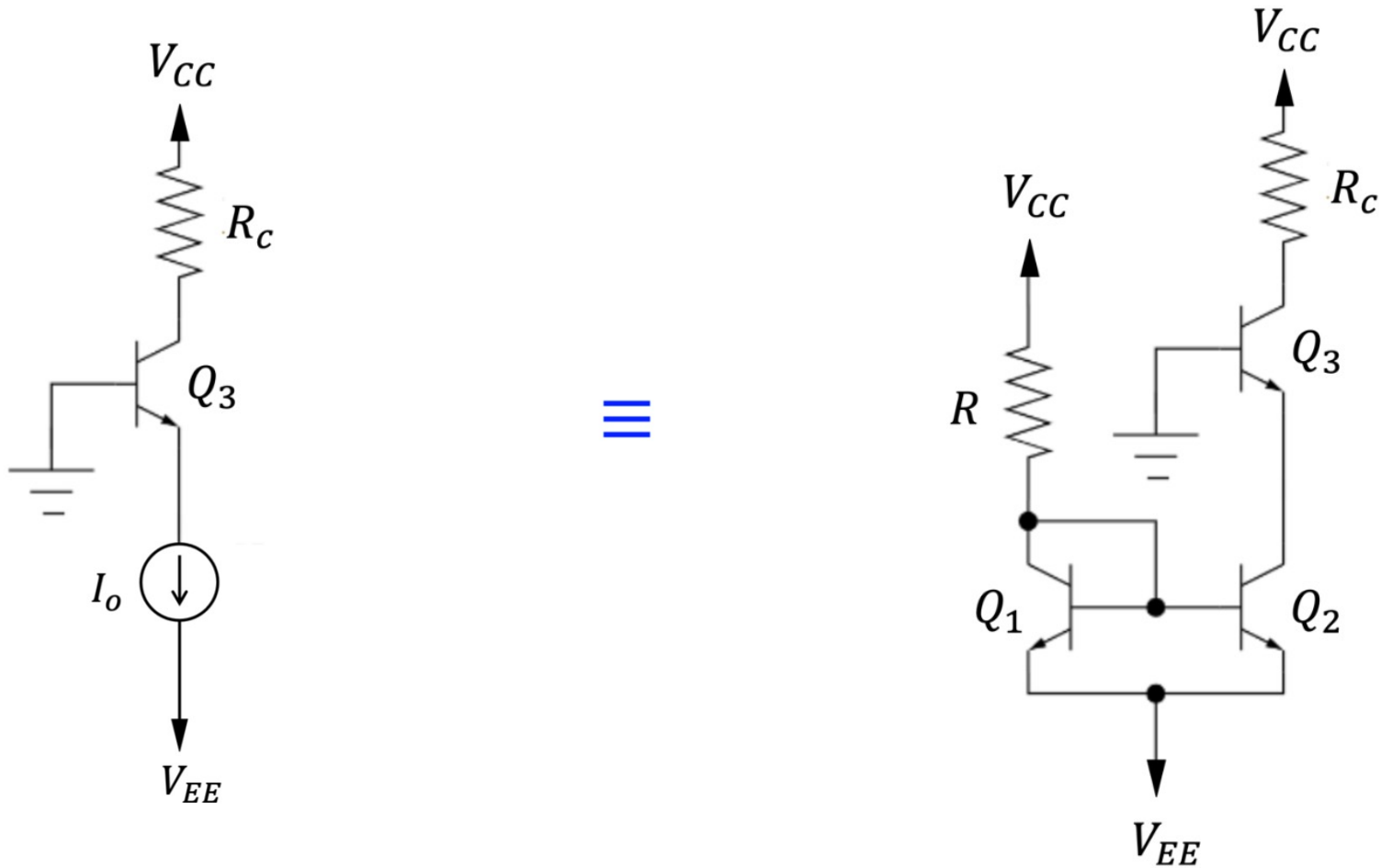

# Biasing with a current source

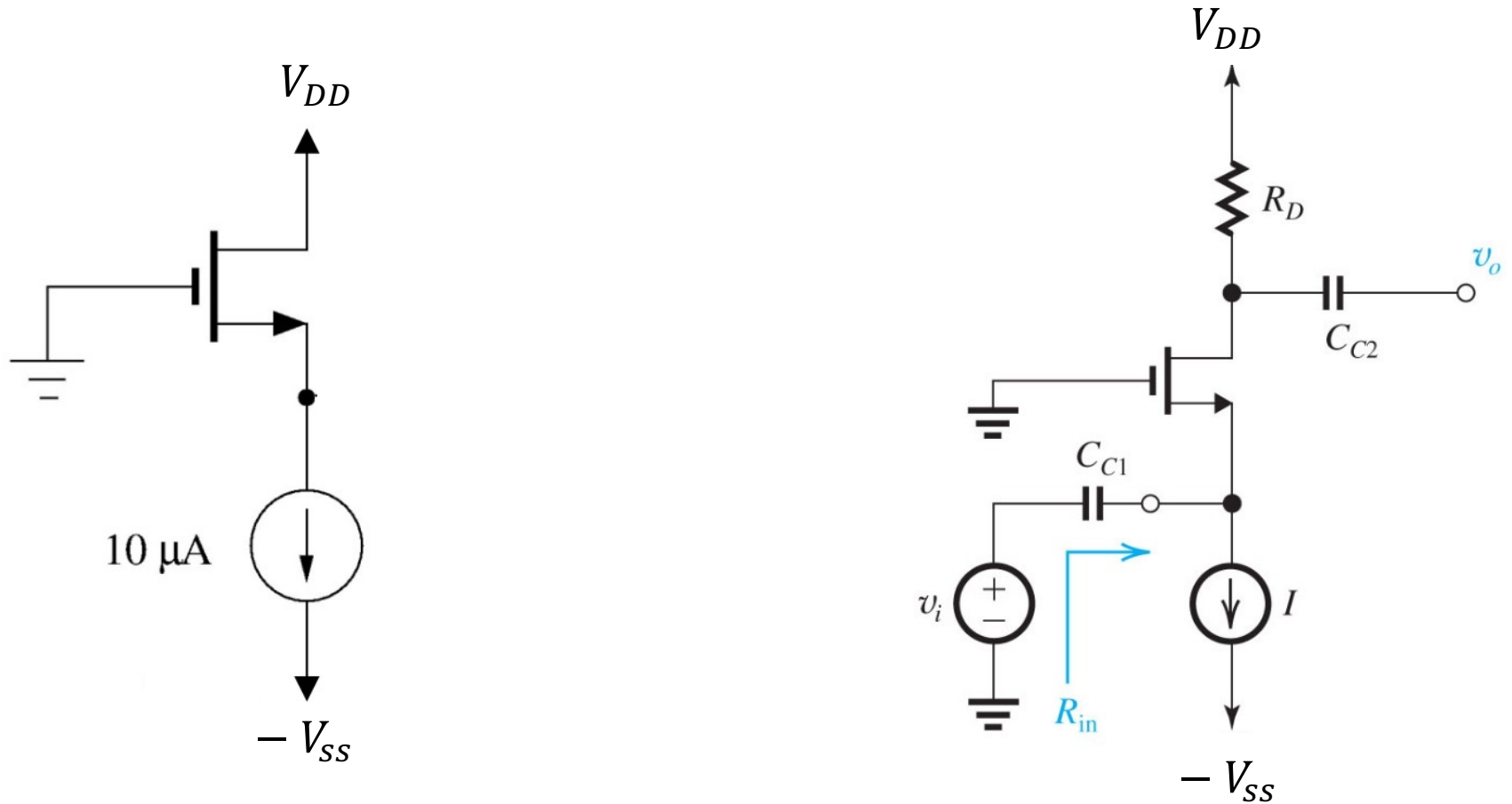

# **Biasing circuit examples**

## Lecture 21 reading quiz.

Find  $R_C$  and  $R_B$  such that BJT would be in active with  $V_{CE} = 5V$  and  $I_C = 25 \text{ mA}$ . ( $V_{CC} = 15 \text{ V}$ , Si BJT with  $\beta = 100$  and  $V_A = \infty$ ).  $V_{D_0} = 0.7 \text{ V}$

$I_C > 0 \rightarrow$  BJT is ON

$V_{CE} > V_{D_0} \rightarrow$  BJT is in active mode


CE KVL:

$$V_{CC} = R_C I_C + V_{CE}$$

$$15 = R_C \times 25 \text{ mA} + 5 \text{ V} \rightarrow R_C = 400 \Omega$$

$$I_C = \beta I_B \rightarrow I_B = \frac{25 \text{ mA}}{100} = 0.25 \text{ mA}$$
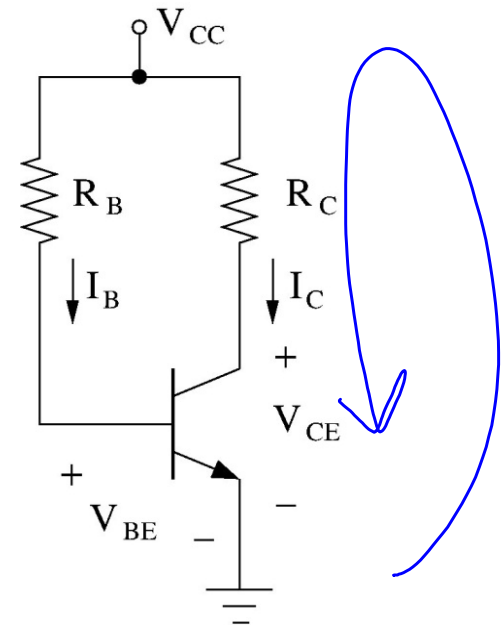
$$\text{BE - KVL} \rightarrow V_{CC} = R_B I_B + V_{BE} \rightarrow R_B = 57.2 \text{ k}\Omega$$





## Discussion question 1.

Consider the circuit designed in the reading quiz ( $R_C = 400 \Omega$ ,  $R_B = 57.2 \text{ k}\Omega$ ,  $V_{CC} = 15 \text{ V}$ ). Find the operating point of BJT if  $\beta = 200$ . ( $V_A = \infty$ ).

BE - KVL :

$$15 = I_B R_B + V_{BE} \rightarrow 15 = I_B \times 57.2 \text{ k} + 0.7$$


$$\rightarrow I_B = 0.25 \text{ mA}$$

$$I_C = \beta I_B = 200 \times 0.25 \text{ mA} = 50 \text{ mA}$$

$$\text{CE KVL: } 15 = R_C I_C + V_{CE} \rightarrow 15 = 0.4 \text{ k}\Omega \times 50 \text{ mA} + V_{CE}$$




$$V_{CE} = -5 \text{ V} < V_{D0} \rightarrow \text{BJT is in saturation!}$$
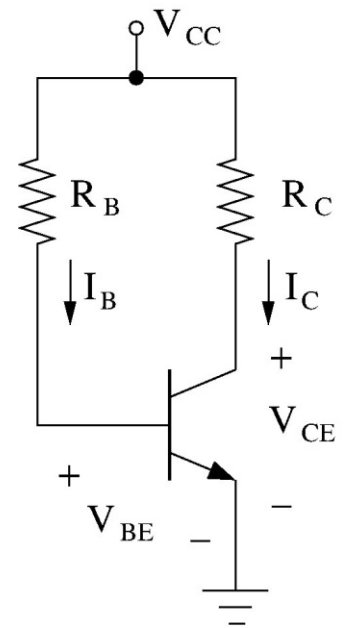
$$V_{CE} = 0.2 \text{ V}, \quad I_C = \frac{15 \text{ V} - 0.2 \text{ V}}{400 \Omega} = 37 \text{ mA}, \quad I_B = 0.25 \text{ mA}$$



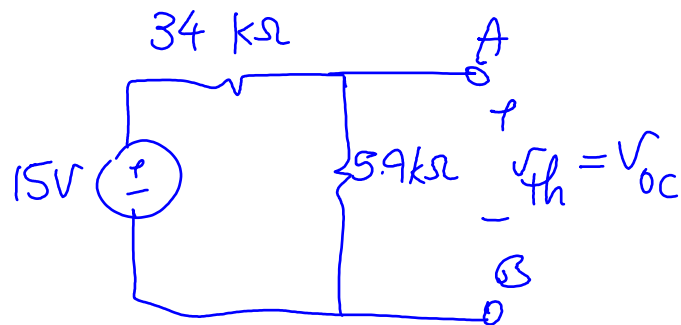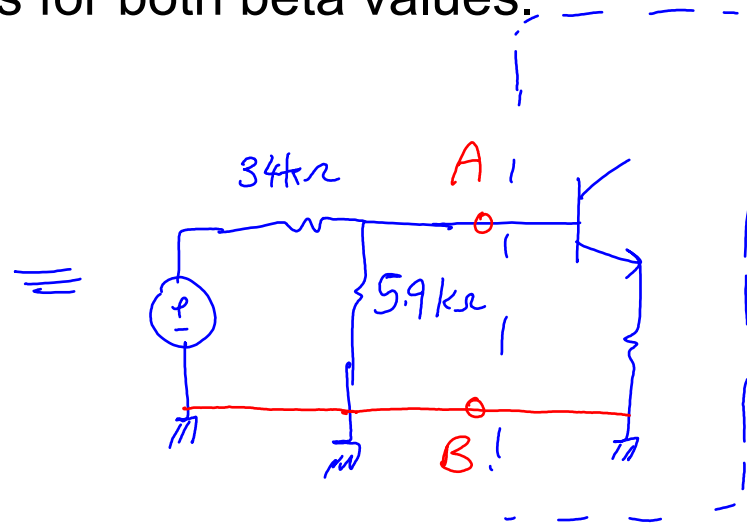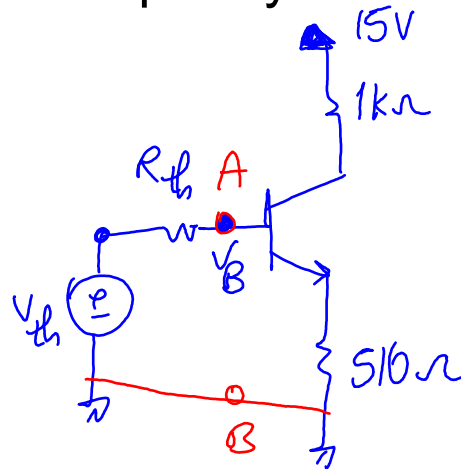
## Discussion question 2.

Find the bias point of the BJT (Si BJT with  $\beta = 200$  and  $V_A = \infty$ ).  
Compare your results for both beta values.



$$R_{th} = 34k\Omega \parallel 5.9k\Omega = 5.03k\Omega$$
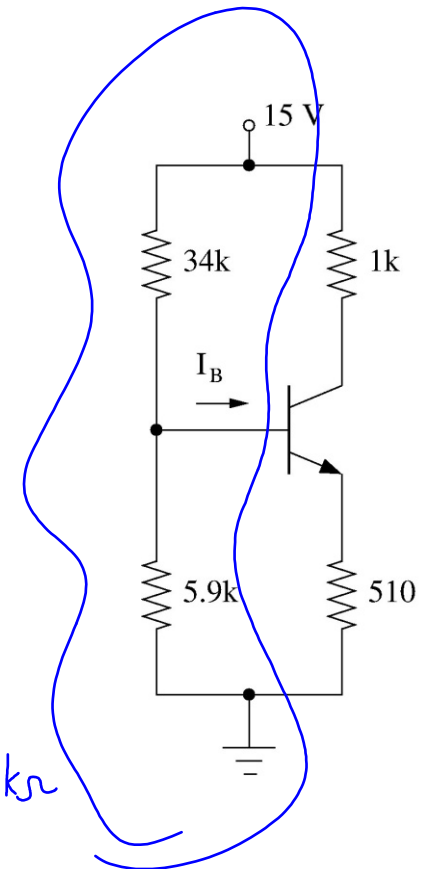
$$V_{th} = \frac{5.9k\Omega}{5.9k\Omega + 34k\Omega} \times 15V = 2.22V$$




## Discussion question 2.

$I_C = \beta I_B$  in active region

Always valid:  $I_E = I_C + I_B \rightarrow I_E = I_B + \beta I_B = (1 + \beta) I_B$

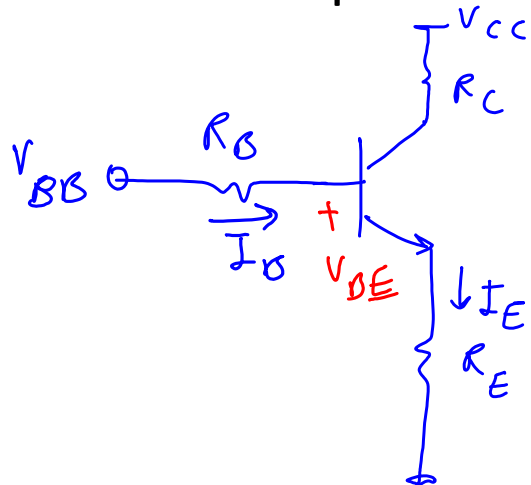Find the bias point of the BJT (Si BJT with  $\beta = 200$  and  $V_A = \infty$ ).  $V_{D_0} = 0.7$




$$R_B = 34k\Omega \parallel 5.9k\Omega = 5.03k\Omega$$

$$V_{BB} = \frac{5.9k}{34k + 5.9k} \times 15 = 2.22V$$

$$\text{BE KVL: } V_{BB} = R_B I_B + V_{BE} + I_E R_E$$

$$2.22 = 5.03k \times \frac{I_E}{1 + \beta} + 0.7 + I_E \times 0.510$$
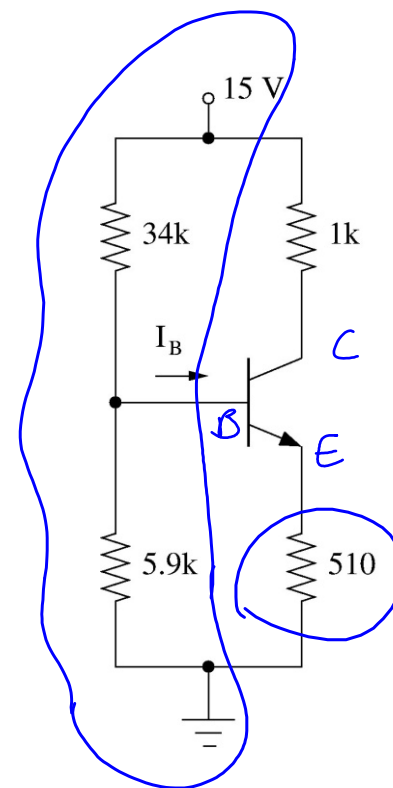
$$I_E = 2.84mA, \quad I_C = \beta I_B = \frac{\beta}{\beta + 1} \times I_E = 2.82mA, \quad I_B = 14.1\mu A$$




## Discussion question 2.

Find the bias point of the BJT (Si BJT with  $\beta = 200$  and  $V_A = \infty$ ).

CE KVL :

$$15 = I_C R_C + V_{CE} + R_E I_E$$

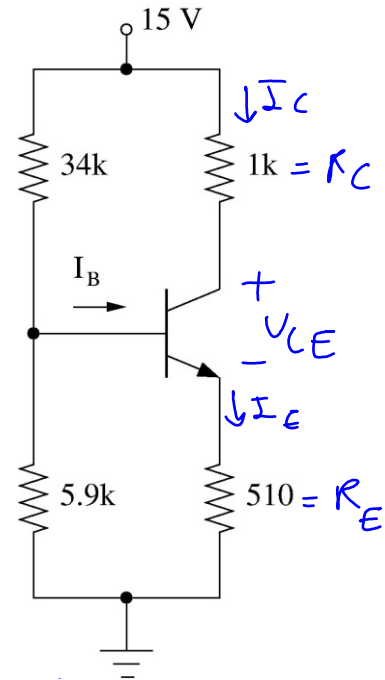$\rightarrow V_{CE} = 10.7\text{ V} > 0.7\text{ V} \rightarrow$  BJT is in active mode



## Discussion question 2.


Find the bias point of the BJT (Si BJT with  $\beta = 200$  and  $V_A = \infty$ ).

If  $\beta$  changes to 100,

$$2.22 = 5.03 \text{ k} \times \frac{I_E}{101} + 0.7 + 0.510 \text{ k} \times I_E$$

$$I_E = 2.71 \text{ mA}$$

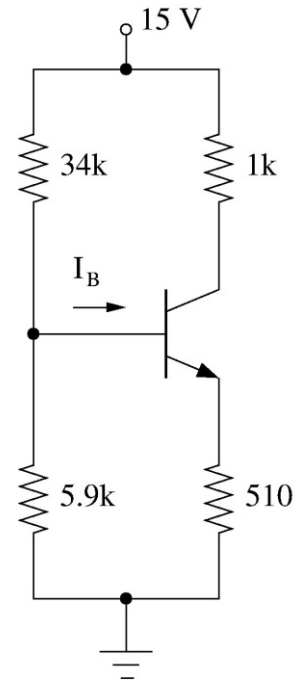
$$V_{CE} = 15 - (1.510 \text{ k}) \times 2.71 \text{ mA} = 10.91 \text{ V} > V_{D0}$$




BJT is still in active mode and  $I_E$  changed by about  $-4\%$ .
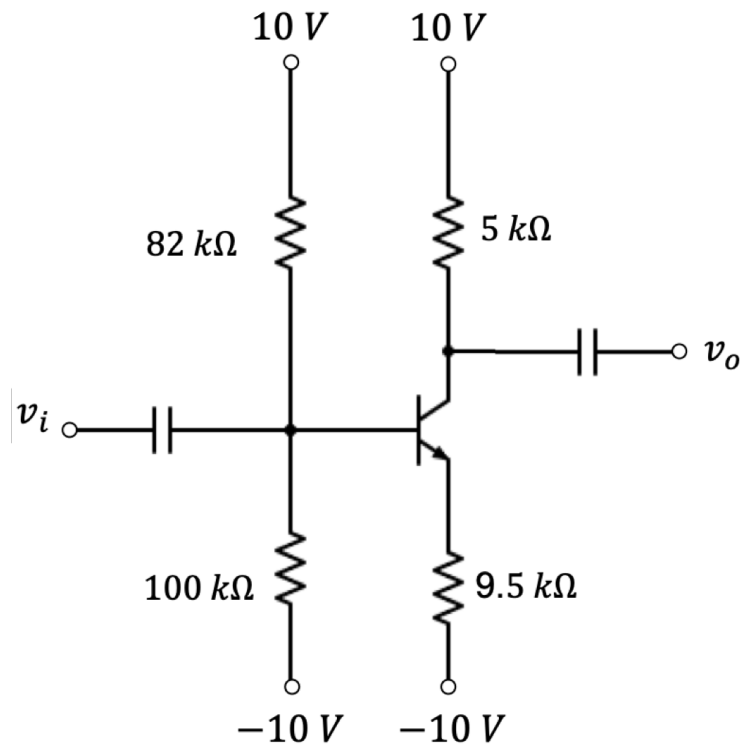
## Example of finding the Bias point/Thevenin equivalent circuit


$$\beta = 100 \quad V_T = 25 \text{ mV} \quad V_A = \infty$$





Bias circuit:

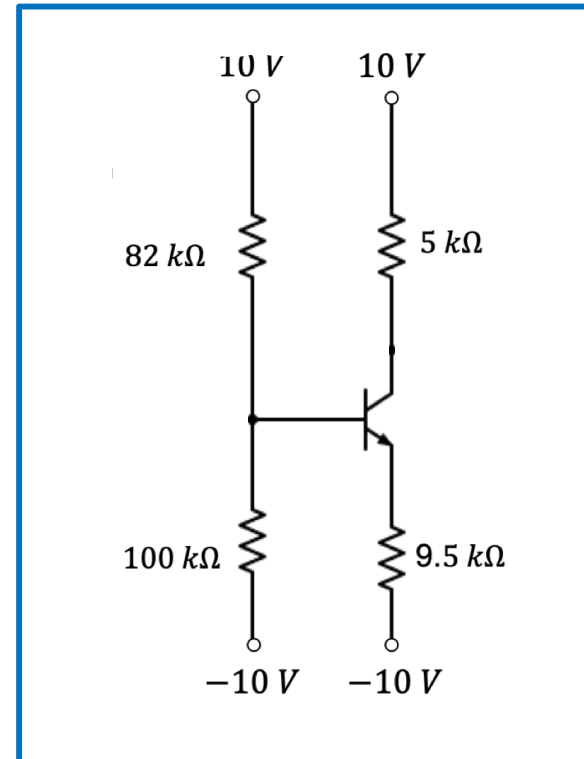

## Example cont.

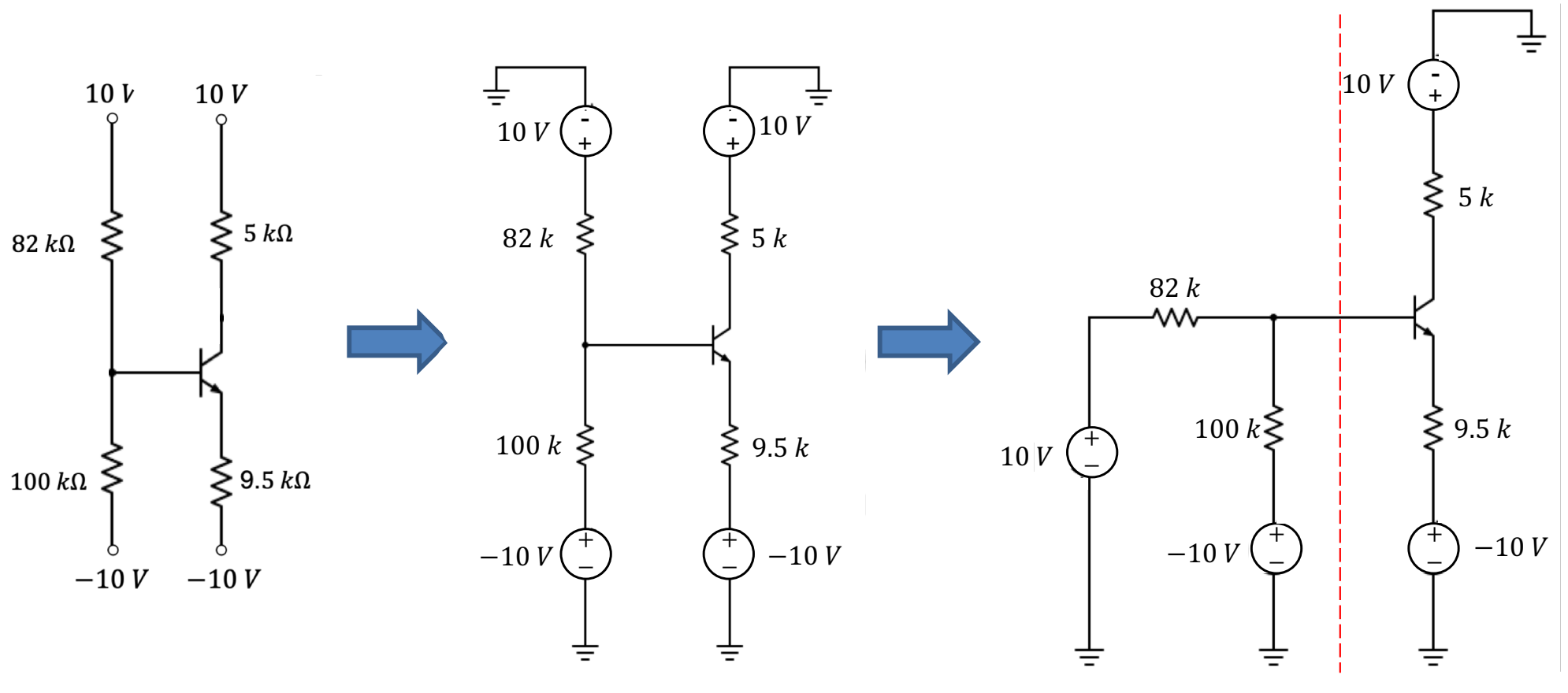


## Example cont.

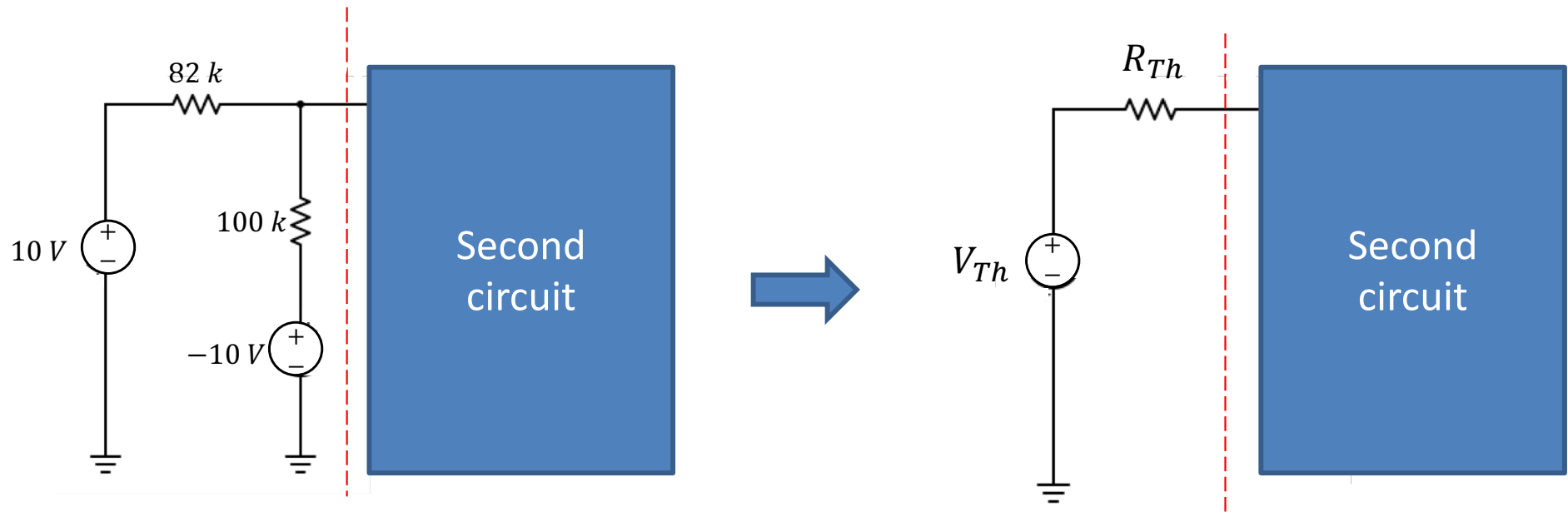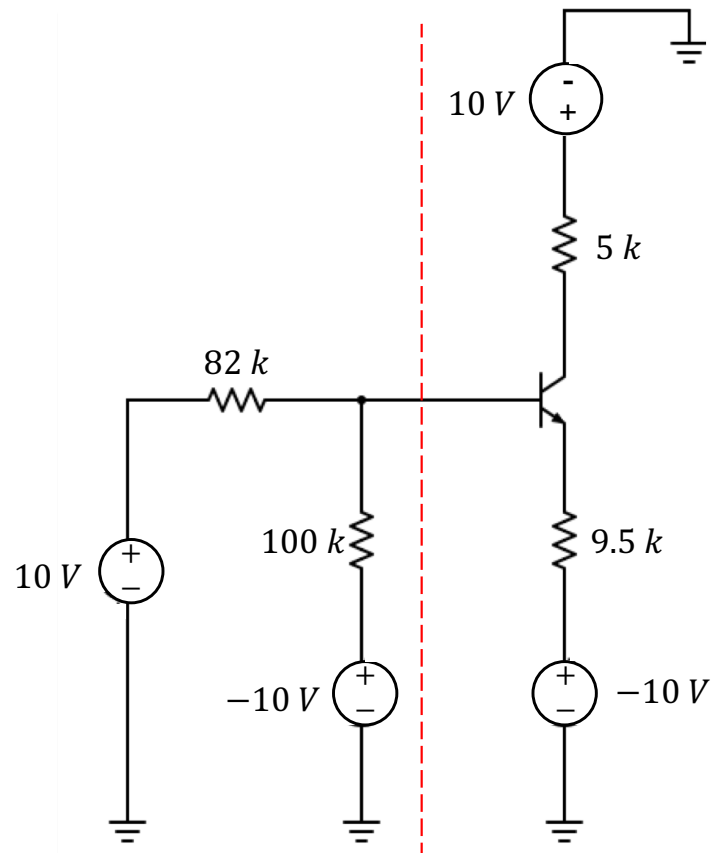




## Example cont.

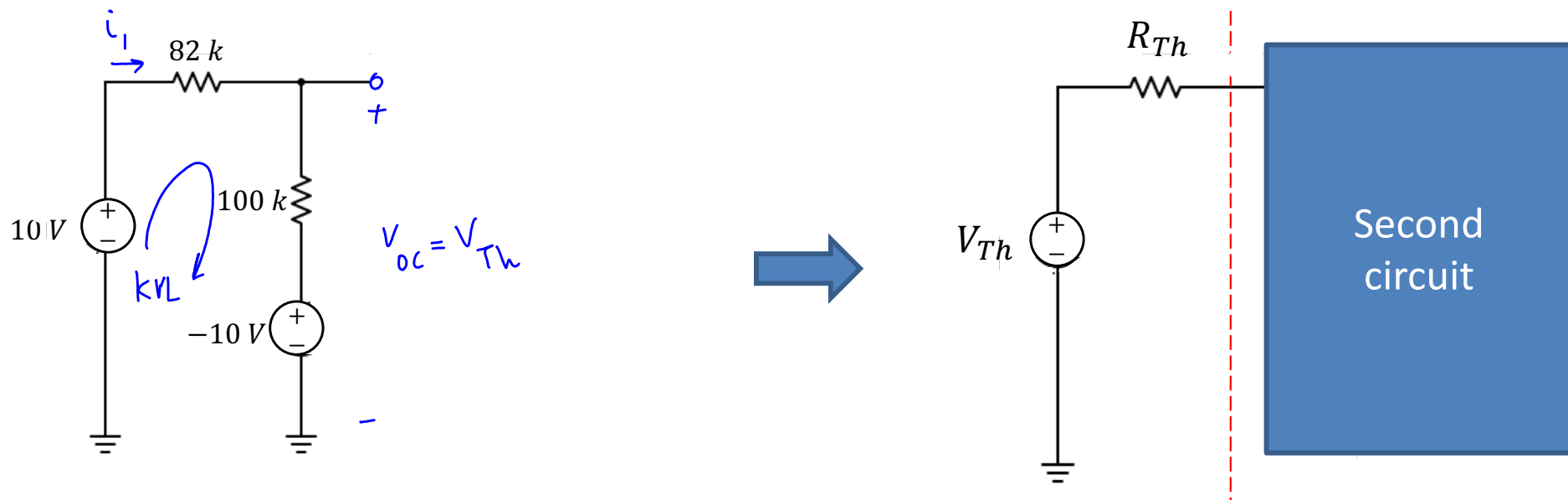

$$\text{KVL: } -10\text{ V} + 82\text{ k} \times i_1 + 100\text{ k} \times i_1 - 10 = 0$$

$$\rightarrow i_1 = \frac{20\text{ V}}{182\text{ k}} \rightarrow V_{Th} = 100\text{ k} \times i_1 - 10\text{ V} \rightarrow V_{Th} = 0.989\text{ V}$$

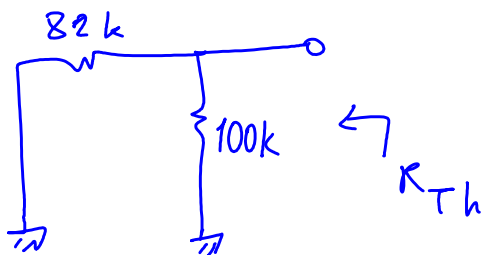$R_{Th}$ : Zero the independent voltage sources.




$$R_{Th} = 100\text{ k} \parallel 82\text{ k} \approx 45.05\text{ k}\Omega$$
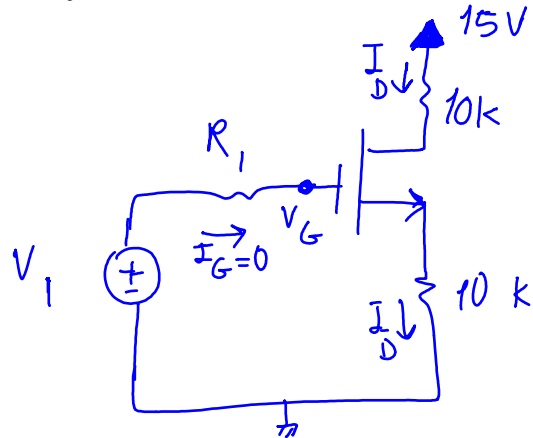
# Clicker question 1.

Which one of the options is correct for the following bias circuit?

$V_t = 1 \text{ V}$  and  $k_n = 1.0 \text{ mA/V}^2$ ,  $\lambda = 0$ .



$$V_1 = \frac{7 \text{ M}\Omega}{7 \text{ M}\Omega + 8 \text{ M}\Omega} \times 15 \text{ V}$$


$$V_1 = 7 \text{ V}$$

$$R_1 = 7 \text{ M}\Omega \parallel 8 \text{ M}\Omega$$

$$\text{Since } I_G = 0 \rightarrow R_1 I_G = 0 \rightarrow V_G = V_1 = 7 \text{ V}$$

$$\begin{cases} V_{GS} = V_G - 10\text{k} \times I_D = 7 \text{ V} - 10\text{k}\Omega \times I_D \\ I_D = \frac{1}{2} k_n (\underbrace{V_{GS}} - V_t)^2 \end{cases}$$

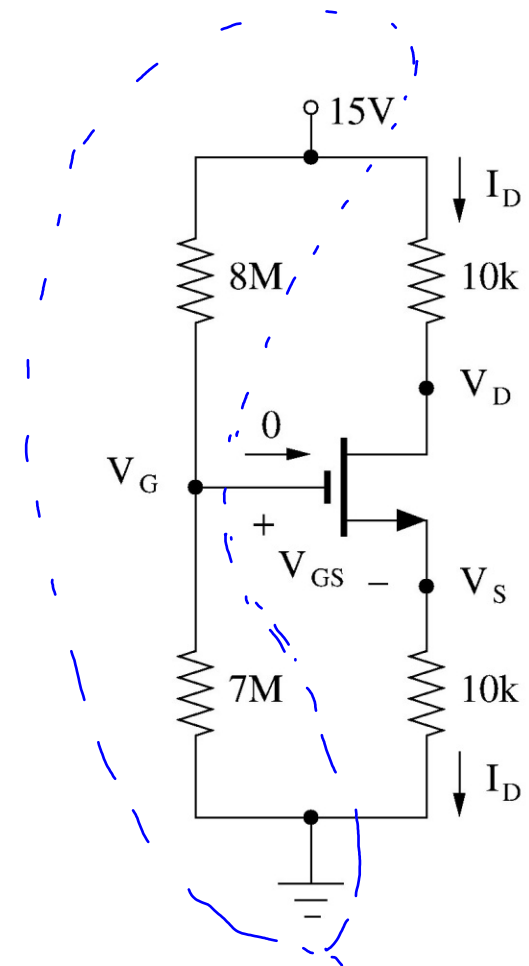
This is an amplifier circuit, so MOS will be in saturation.


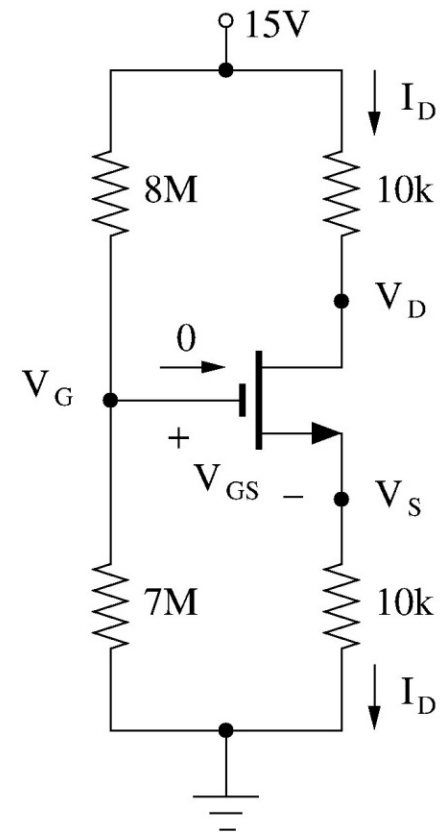
## Clicker question 1.

Which one of the options is correct for the following bias circuit?

$V_t = 1 \text{ V}$  and  $k_n = 1.0 \text{ mA/V}^2$ ,  $\lambda = 0$ .



$$V_{GS} = 7 \text{ V} - 10 \text{ k}\Omega \times I_D$$

$$\underbrace{V_{GS} - V_t}_{V_{ov}} = 7 \text{ V} - 10 \text{ k}\Omega \times I_D - 1$$

$$\left\{ \begin{array}{l} V_{ov} = 6 \text{ V} - 10 \text{ k}\Omega \times I_D \\ I_D = \frac{1}{2} k_n V_{ov}^2 \end{array} \right. \quad \Downarrow$$

$$\Rightarrow V_{ov} = 6 \text{ V} - \frac{10 \text{ k}}{2} \times 1 \left( \frac{\text{mA}}{\text{V}^2} \right) V_{ov}^2$$

$$5 V_{ov}^2 + V_{ov} - 6 = 0$$

$$\rightarrow V_{ov} = \begin{cases} 1 \text{ V} > 0 \\ -6/5 \text{ V} \times \end{cases}$$

$$\rightarrow V_{ov} = 1 \text{ V}$$

## Clicker question 1.

Which one of the options is correct for the following bias circuit?

$V_t = 1\text{ V}$  and  $k_n = 1.0\text{ mA/V}^2$ ,  $\lambda = 0$ .


$$V_{OV} = 1\text{ V} \rightarrow V_{GS} - V_t = 1 \rightarrow V_{GS} = V_t + 1 = 2\text{ V}$$

$$V_{GS} = V_G - V_S = 2\text{ V} \rightarrow 7\text{ V} - V_S = 2\text{ V}$$

$$\rightarrow \boxed{V_S = 5\text{ V}}$$

$$I_D = \frac{1}{2} \times 1\left(\frac{\text{mA}}{\text{V}^2}\right) \times 1^2(\text{V}^2) = 0.5\text{ mA}$$

$$\boxed{I_D = 0.5\text{ mA}}$$

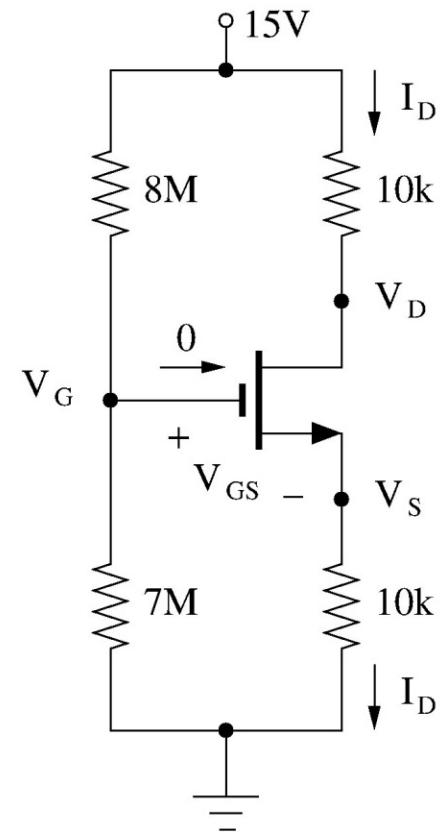

### Discussion question 3.

Design the below circuit so that the transistor operates in saturation with  $V_{SD}$  biased 1-V from the edge of the saturation, with  $I_D = 1 \text{ mA}$  and  $V_D = 3 \text{ V}$ . Use a  $10 \mu\text{A}$  current in the voltage divider.  $|V_t| = 1 \text{ V}$ ,


$$k_p = 0.5 \text{ mA/V}^2$$

In the saturation region :  $v_{SD} \geq v_{ov}$   
 $V_{SD}$  biased 1 volt from the edge of saturation &  
MOS operates in saturation means:

$$V_{SD} = V_{ov} + 1$$

$$I_D = \frac{1}{2} k_n V_{ov}^2 \quad \rightarrow \quad 1 \text{ mA} = \frac{1}{2} \times 0.5 \frac{\text{mA}}{\text{V}^2} \times V_{ov}^2$$

$$\rightarrow V_{ov} = 2 \text{ V} \quad \rightarrow \quad V_{SG} = V_{ov} + |V_t| = 3 \text{ V}$$

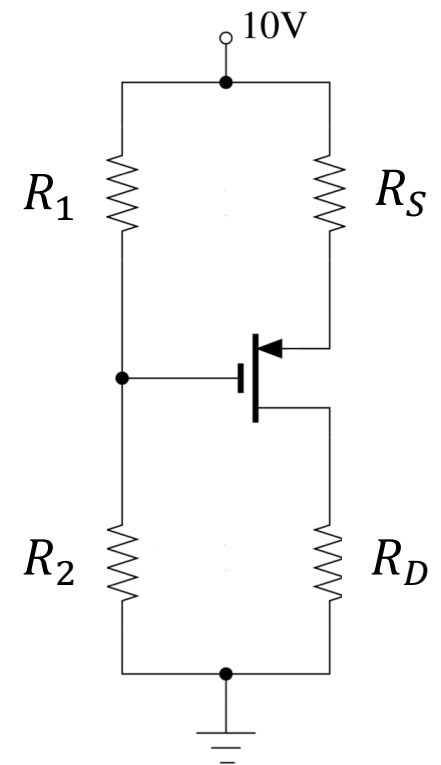

### Discussion question 3.


Design the below circuit so that the transistor operates in saturation with  $V_{SD}$  biased 1-V from the edge of the saturation, with  $I_D = 1\text{ mA}$  and  $V_D = 3\text{ V}$ . Use a  $10\text{ }\mu\text{A}$  current in the voltage divider.  $|V_t| = 1\text{ V}$ ,  $k_p = 0.5\text{ mA/V}^2$

$$V_{SD} = V_{ov} + 1 = 2 + 1 = 3\text{ V}$$

$$V_D = R_D I_D \rightarrow 3\text{ V} = R_D \times 1\text{ mA} \rightarrow \boxed{R_D = 3\text{ k}\Omega}$$

$$V_{SD} = V_S - V_D = V_S - 3\text{ V} = 3\text{ V} \rightarrow V_S = 6\text{ V}$$
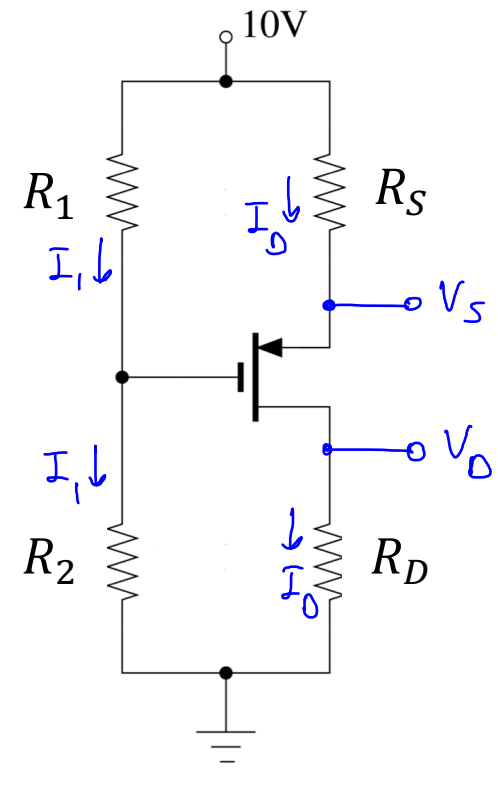
$$V_S = 10\text{ V} - R_S I_D \rightarrow 6\text{ V} = 10\text{ V} - R_S \times 1\text{ mA} \\ \rightarrow \boxed{R_S = 4\text{ k}\Omega}$$



## Discussion question 3.

Design the below circuit so that the transistor operates in saturation with  $V_{SD}$  biased 1-V from the edge of the saturation, with  $I_D = 1\text{ mA}$  and  $V_D = 3\text{ V}$ . Use a  $10\text{ }\mu\text{A}$  current in the voltage divider.  $|V_t| = 1\text{ V}$ ,  $k_p = 0.5\text{ mA/V}^2$

$$V_{SG} = V_S - V_G = 3\text{ V} \rightarrow V_G = V_S - 3\text{ V} = 6 - 3 = 3\text{ V}$$

$$V_G = 10\text{ V} - R_1 I_1 \rightarrow 3\text{ V} = 10\text{ V} - R_1 \times 10\text{ }\mu\text{A}$$

$$R_1 = \frac{7\text{ V}}{10\text{ }\mu\text{A}} = 0.7\text{ M}\Omega$$

$$V_G = R_2 I_2 \rightarrow R_2 = \frac{3\text{ V}}{10\text{ }\mu\text{A}} = 0.3\text{ M}\Omega$$

