

ECE 35, Fall 2022 – Section B
Final

Your sequence number

--

Grade

/ 31

Last name

First + middle
name(s)**PID**

Instructions:

- Do not look at the questions or start writing until it is announced that you can do so.
- You must follow the Final Exam Procedures that were posted on Canvas. If you are unsure of anything, ask. As a reminder:
 - Your phone should be turned off and put inside your bag
 - Calculators are not allowed.
 - This is a closed book exam.
 - Follow the Academic Integrity standards
- These pages contain the exam questions.
 - Do not write any of your work here except for scratch work. It will not be graded.
 - You need to write your final answer in the answer boxes here. Make sure you list units.
 - Keep these question pages stapled together. The last page is the equation sheet; you may detach this if you want.
 - Make sure you write your PID on EACH page.
 - Read each problem completely and thoroughly before beginning.




(1) (7 points)


- (a) The ammeter and voltmeter are ideal.

What is the reading X of the voltmeter?


What is the reading Y of the ammeter?

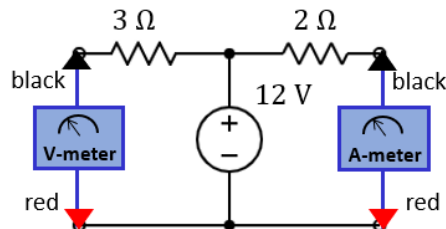 X Y


- (b) What is the voltage v_a ?

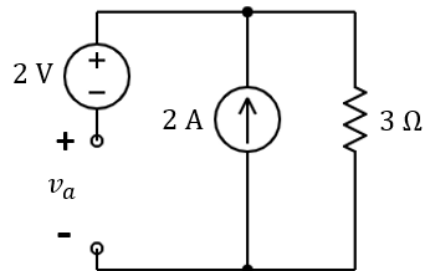 v_a


- (c) What is the power P received by the current source?

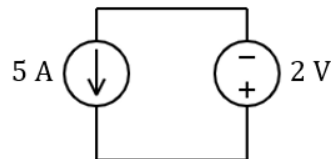 P

- (d) What is the voltage v_b ?
What is the current i_a ?

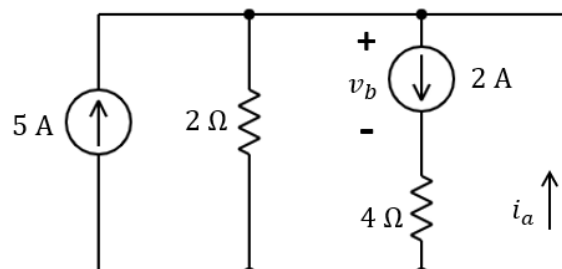
 v_b i_a

- (e) What is the Thevenin resistance R_{th} between A and B?

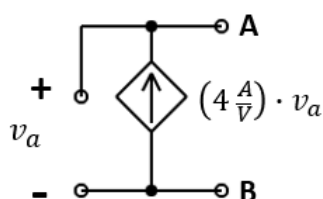 R_{th} 

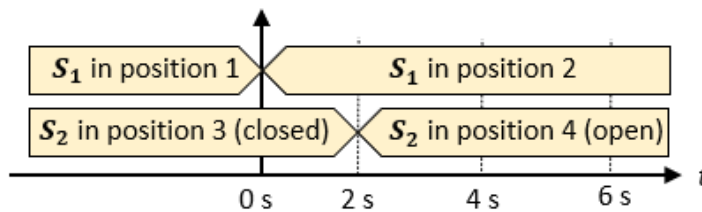(2) (7 points) For this question, you should make reasonable numerical approximations if needed. Consider the circuit below.

- For $t < 0$ s, switch S_1 is in position 1, switch S_2 is in position 3, and the system has reached steady state.
- At time $t = 0$ s, switch S_1 moves from position 1 to position 2 (you may assume that i_{S1} turns off at that point). Switch S_2 stays in position 3 (closed).
- At time $t = 2$ s, switch S_2 moves from position 3 to position 4 (open). Switch S_1 stays in position 2.



(a) Find the capacitor voltage v_c at time $t = 0^-$ s (i.e., immediately before switch S_1 moves).

$v_c(0^-)$

Find the node voltage v_a at time $t = 0^+$ s (i.e., immediately after switch S_1 moves).


$v_a(0^+)$

(b) Find the node voltage v_a at time $t = 2^-$ s (i.e., immediately before switch S_2 moves).

$v_a(2^-)$

(c) Find the node voltage v_a at time $t = 6$ s.

$v_a(6)$

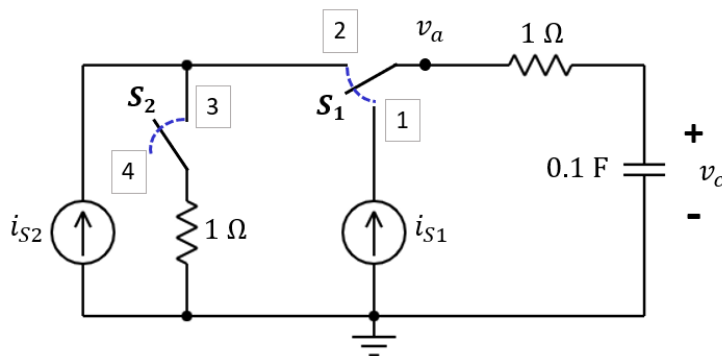

$$i_{S1} = 8 \cos\left(10t - \frac{\pi}{2}\right) \text{ A}$$


$$i_{S2} = 5 \text{ A}$$

(3) (6 points) For all the circuits in this question, you may assume that they are in steady-state.

- (a) Find the phasor of $v_x(t) = 8 \sin\left(20t + \frac{\pi}{4}\right)$ V. You can write your answer in cartesian or polar coordinates.

 V_x

- (b) Find the current i_b at time $t = \frac{\pi}{10}$ s.

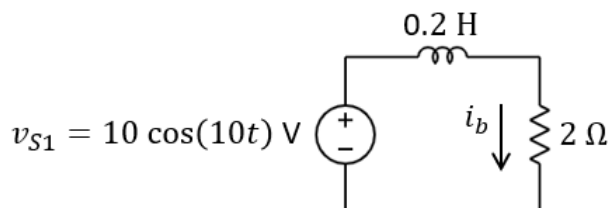
 $i_b\left(\frac{\pi}{10}\text{ s}\right)$ 

- (c) Note the similarity to circuit in part (b).


Find the voltage v_{S2} of the voltage source at time $t = \frac{\pi}{10}$ s.

 $v_{S2}\left(\frac{\pi}{10}\text{ s}\right)$


Find the current i_c at time $t = \frac{\pi}{10}$ s.

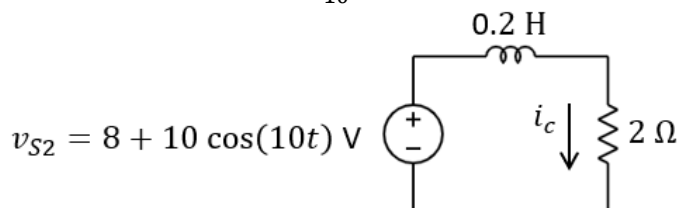 $i_c\left(\frac{\pi}{10}\text{ s}\right)$ 

- (d) Find the current i_d at time $t = \frac{\pi}{10}$ s.

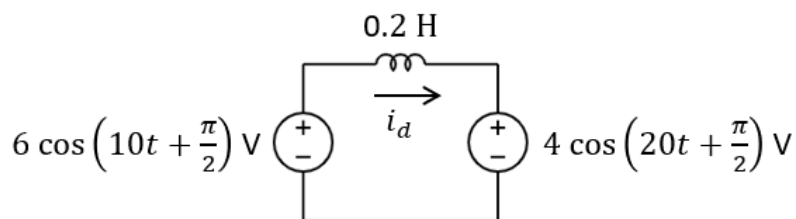
 $i_d\left(\frac{\pi}{10}\text{ s}\right)$ 

- (e) Find the maximum value of the waveform $v_a(t)$.


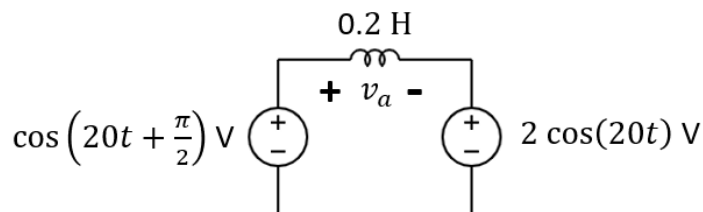
 $v_{a\max}$ 

- (4) (6 points) The circuits below represent AC circuits in steady-state in the phasor domain (for the complex numbers, you may assume units are V, A, Ω , etc. as appropriate). The independent current sources are AC sources with $\omega = 5$ rad/s. Each box represents the impedance of a single circuit element (a resistor, capacitor or inductor).

- (a) Find the phasor V_a . You can write your answer in cartesian or polar coordinates.

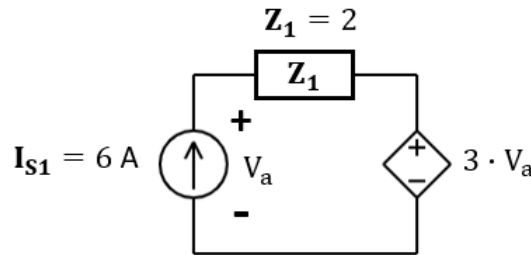 V_a 

- (b) In the circuit below, we set $\alpha = \frac{\pi}{2}$ (the figure is clearly not drawn to scale). Find the average power P_s supplied by the current source I_{s2} .

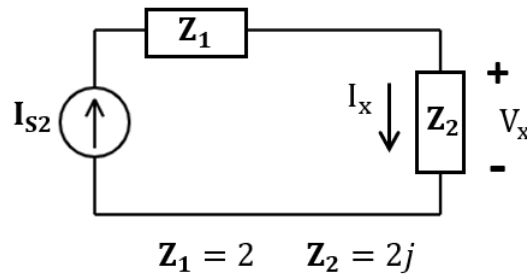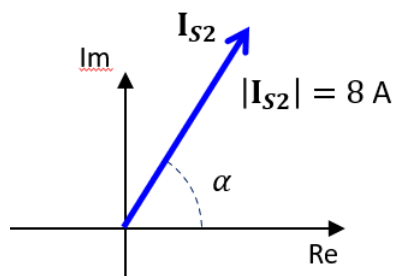 P_s 

- (c) For the same circuit as in part (b), we change α to $\alpha = \frac{\pi}{6}$.

Find the average power P_s supplied by the current source I_{s2} .

 P_s

Find the average power P_1 received by the element with impedance Z_2 .

 P_2

Find the magnitude of the phasor V_x .

 $|V_x|$

Find the RMS value of i_x .


 i_{xRMS}

(5) (5 points)

- (a) Consider the circuit below. You are not given the values of k and V_s (but you are told that all sources are DC sources). We are considering the circuit after the switch closes.


We measure that when the voltage v_c reaches 6 V, the current i_c is 2 A. Similarly, when the voltage v_c becomes 10 V, the current i_c drops to 0 A.

Find the Norton equivalent resistance R_N between A and B when we remove the capacitor from the circuit.

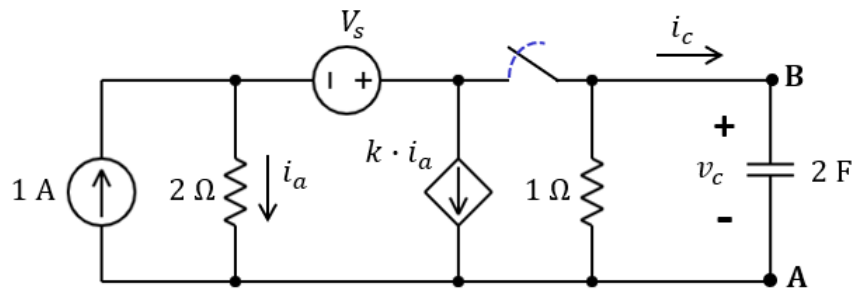 R_N 

- (b) Consider the circuit below. The unknown values of k and V_s are the same as in the circuit above. The switch closes at time $t = 400$ s (you do not know if the system has reached steady state before the switch closes).

Find the time constant τ associated with $i_a(t)$ for $t > 400$ s.

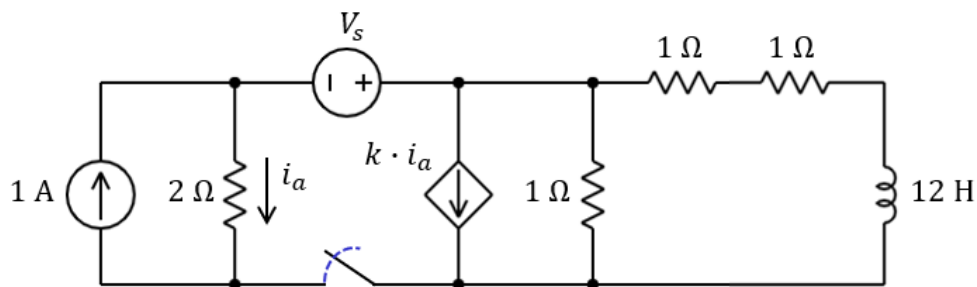 τ 

ECE35 Equation Sheet

Basics: $i \triangleq \frac{dq}{dt}$ $v_{ab} \triangleq \frac{dw}{dq}$ $R = \rho \frac{l}{A}$

Capacitors: $C = \epsilon \cdot \frac{A}{d}$ $Q = C \cdot v$ $w_C = \frac{1}{2} C v^2$

Inductors: $L = \mu \cdot \frac{N^2 A}{l}$ $B \sim i$ $w_L = \frac{1}{2} L i^2$

AC power: $p(t) = \frac{1}{2} V_m I_m \cdot \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cdot \cos(2\omega t + \theta_v + \theta_i)$

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i) \quad X_{rms} = \sqrt{\frac{1}{T} \int_0^T x(t)^2 dt}$$

Trigonometry:

$\sin(-\alpha) = -\sin(\alpha)$	$\cos(-\alpha) = \cos(\alpha)$
$\sin(\pi - \alpha) = \sin(\alpha)$	$\cos(\pi - \alpha) = -\cos(\alpha)$
$\sin\left(\frac{\pi}{2} - \alpha\right) = \cos(\alpha)$	$\cos\left(\frac{\pi}{2} - \alpha\right) = \sin(\alpha)$
$\sin\left(\alpha - \frac{\pi}{2}\right) = -\cos(\alpha)$	$\cos\left(\alpha - \frac{\pi}{2}\right) = \sin(\alpha)$
$\sin(2\alpha) = 2 \sin(\alpha) \cos(\alpha)$	$\cos(2\alpha) = \cos^2(\alpha) - \sin^2(\alpha)$

$$\sin(\alpha \pm \beta) = \sin(\alpha) \cos(\beta) \pm \cos(\alpha) \sin(\beta)$$

$$\cos(\alpha \pm \beta) = \cos(\alpha) \cos(\beta) \mp \sin(\alpha) \sin(\beta)$$

$$\sin(\alpha) \sin(\beta) = 0.5 \cdot (\cos(\alpha - \beta) - \cos(\alpha + \beta))$$

$$\cos(\alpha) \cos(\beta) = 0.5 \cdot (\cos(\alpha - \beta) + \cos(\alpha + \beta))$$

$$\sin(\alpha) \cos(\beta) = 0.5 \cdot (\sin(\alpha - \beta) + \sin(\alpha + \beta))$$

$\alpha:$	0	$\frac{\pi}{6}$	$\frac{\pi}{4}$	$\frac{\pi}{3}$	$\frac{\pi}{2}$
$\sin(\alpha):$	0	$\frac{1}{2}$	$\frac{\sqrt{2}}{2}$	$\frac{\sqrt{3}}{2}$	1
$\tan(\alpha):$	0	$\frac{\sqrt{3}}{3}$	1	$\sqrt{3}$	∞