

Name

PID

UNIVERSITY OF CALIFORNIA, SAN DIEGO

Electrical and Computer Engineering Department

ECE 65 – Fall 2020

Components and Circuits lab

Midterm Exam1 *solutions*


You should submit your handwritten solutions in a PDF format to Gradescope by Wednesday, 10/21, at 11:50 am (Pacific Time).

Problem 1. (15 points)


- a) Design a diode waveform shaping circuit that would have the below transfer function.

You can use PN junction diodes and Zener diodes with $V_{D0} = 0.7\text{ V}$, $V_Z = 1.3\text{ V}$, DC voltage sources, and resistors in your design. You can use any combination in your design.

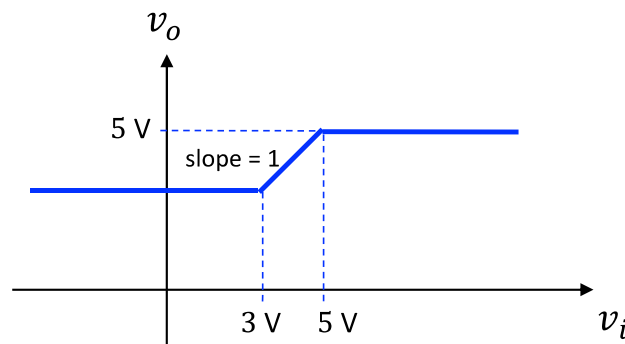- b) Write
- two possible cases**
- of the operation of the diode(s) in your designed circuit, and for each case, include the
- calculation of finding v_o**
- and
- the range of v_i**
- . Show your work.



a)

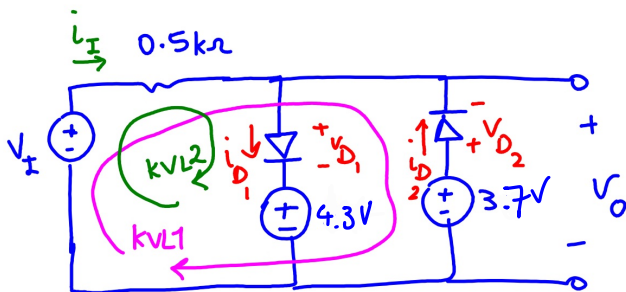

b) case 1: D_1 ON and D_2 OFF : $v_{D1} = 0.7\text{ V}$ & $i_{D1} \geq 0$ & $v_{D2} < 0.7\text{ V}$ & $i_{D2} = 0$

$$\text{KVL 2: } -v_i + 0.5\text{ k}\Omega \times i_I + v_{D1} + 4.3 = 0$$

$$\text{KCL: } i_I = i_{D1} - i_{D2}$$

$$i_{D2} = 0 \rightarrow i_I = i_{D1} \Rightarrow v_i = 0.5\text{ k}\Omega \times i_{D1} + V_{D0} + 4.3\text{ V} = \frac{1}{2} i_{D1} + 5\text{ V}$$

$$i_{D1} = \frac{v_i - 5\text{ V}}{\frac{1}{2}} \quad i_{D1} \geq 0 \rightarrow \frac{v_i - 5\text{ V}}{\frac{1}{2}} \geq 0 \rightarrow v_i \geq 5\text{ V}$$

$$V_o = V_{D_1} + 4.3V = 0.7V + 4.3V = 5V$$

Case 2: D_1 & D_2 off : $V_{D_1} < 0.7V$ & $i_{D_1} = 0$ & $V_{D_2} < 0.7V$ & $i_{D_2} = 0$

$$\text{KVL 2: } -V_i + 0.5k\Omega \times i_I + V_{D_1} + 4.3 = 0$$

$$\text{KVL 1: } -V_i + 0.5k\Omega \times i_I - V_{D_2} + 3.7 = 0$$

$$\text{KCL: } i_I = i_{D_1} - i_{D_2} \rightarrow i_I = 0$$


$$\text{KVL 2: } V_{D_1} = V_i - 4.3, \quad V_{D_1} < 0.7V \rightarrow V_i < 5V \Rightarrow 3V < V_i < 5V$$

$$\text{KVL 1: } V_{D_2} = -V_i + 3.7, \quad V_{D_2} < 0.7V \rightarrow V_i > 3V$$

$$V_o = 0.5k\Omega \times (-i_I) + V_i = 0.5k\Omega \times 0 + V_i \rightarrow V_o = V_i$$

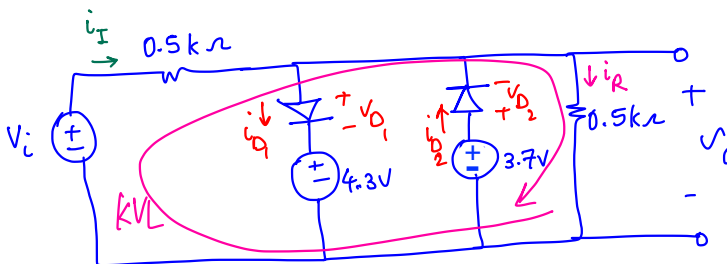Problem 2. (3 points)

Modify the circuit that you designed in problem 1 such that the voltage gain in the nonlimiting range is 0.5 V/V. Sketch the modified circuit.



D_1 & D_2 off

$$i_{D_1} = 0 \text{ \& } i_{D_2} = 0$$

$$i_I = i_R$$

$$\text{KVL: } -V_i + 0.5k\Omega \times i_I + 0.5k\Omega \times i_R = 0$$

$$V_i = 1k\Omega \times i_R$$

$$V_o = 0.5k\Omega \times i_R = \frac{1}{2} V_i$$

The ranges of v_i will be different from the ones included in the original transfer function graph.