
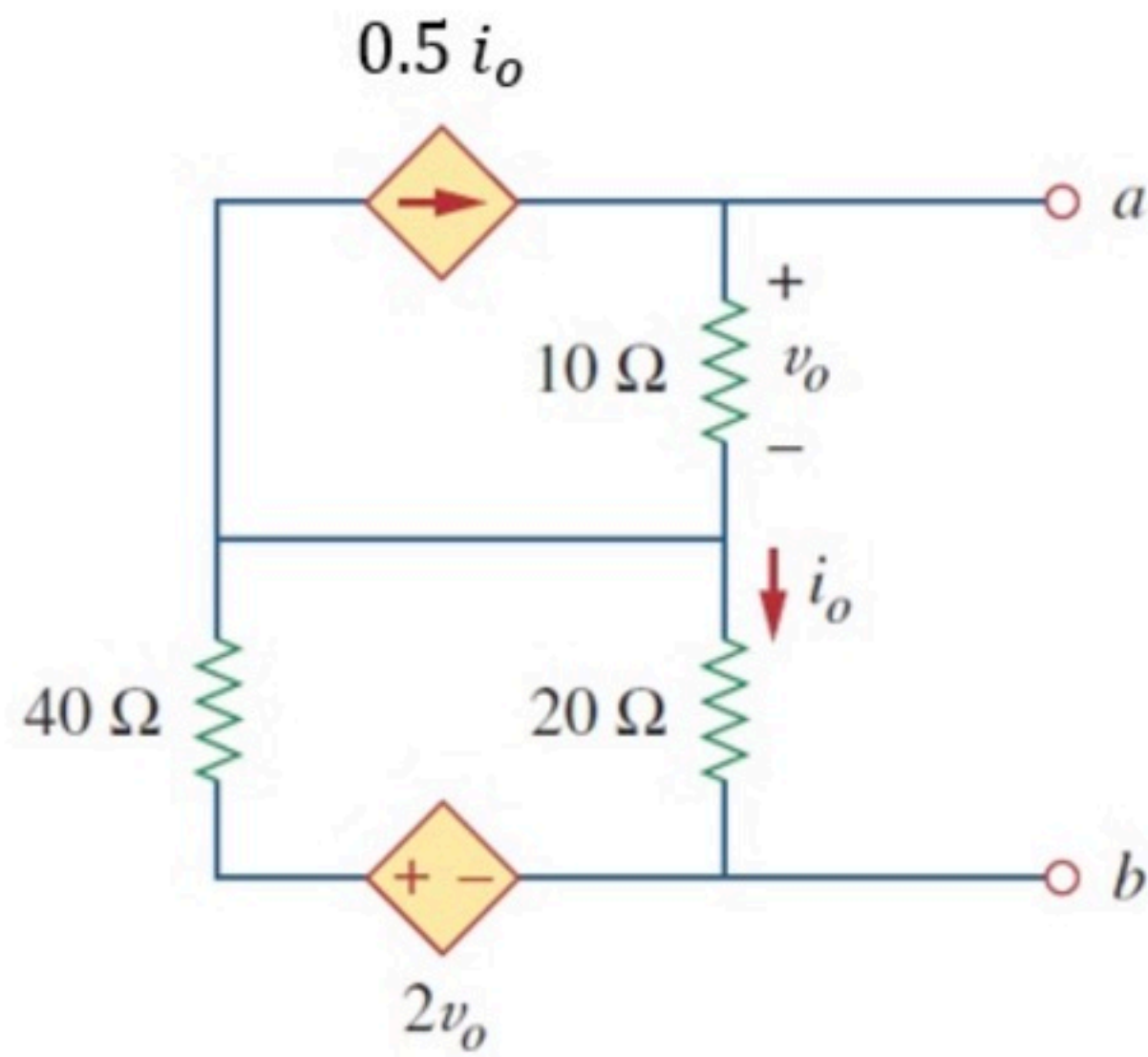


PP Circuit theorems 021

Unlimited Attempts.

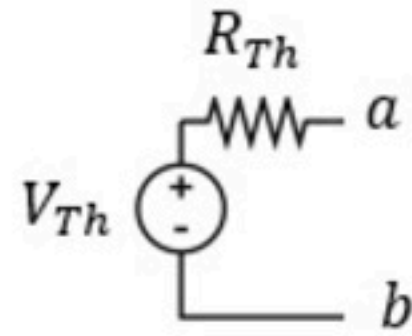Find the Thevenin equivalent model of this circuit, as seen between a and b.



Given Variables:

...

Calculate the following:

V_{th} (V) :

0



R_{th} (ohm) :

40



Hint: Use a test source to find R_{th} .