

ECE 65: Components & Circuits Lab

Review


Saharnaz Baghdadchi

Practice problem 1.

- a) Find and draw the transfer function of the below diode circuit.

Assume $V_{D0} = 0.7\text{ V}$.

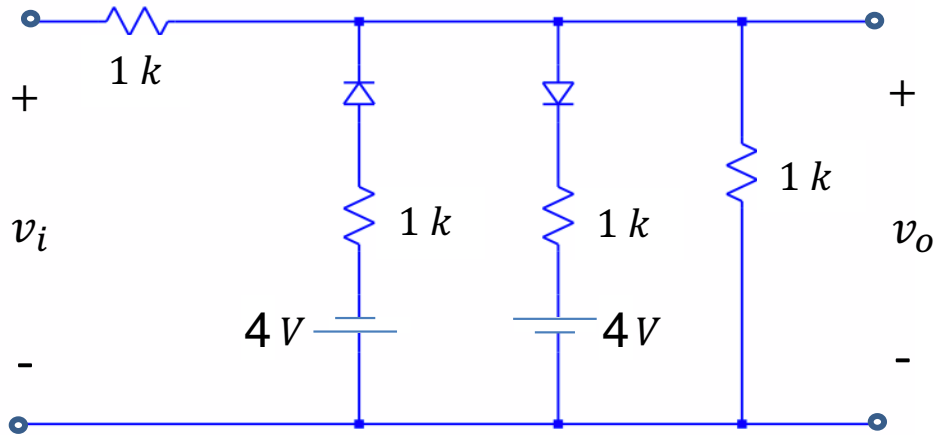- b) Find and draw the output voltage for $v_i = 3 \sin(\omega t)$.





Practice problem 2.

The diode in the below circuit has $V_{D0} = 0.7 \text{ V}$. $v_i(t)$ is a triangular wave shown below.

$$v_o(0) = 0.$$

(a) What is v_o at $t=1\text{ms}$?

(b) What is v_o at $t = 2 \text{ ms}$?

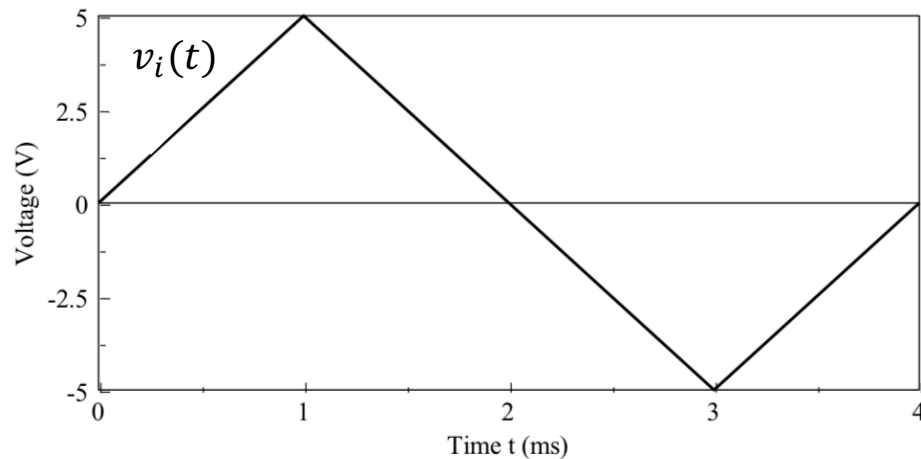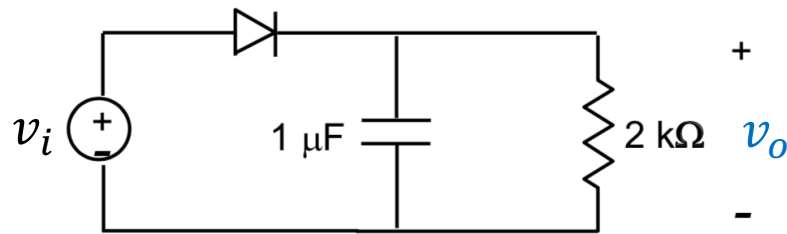

Practice problem 3.

In the following op-amp circuit, the output voltage, V_o , can be varied by turning the wiper of the $100\text{ k}\Omega$ potentiometer.

- Find the range over which V_o can be varied.
- If the potentiometer is a “10-turn” device, find the change in V_o corresponding to each turn of the pot.

