

Phasors 018

0 of 5 attempts made



In the circuit below, the switch moves from position 1 to position 2 at time $t = 0$. For $t < 0$ (switch in position 1), you may assume that the system is in steady state. The voltage source is sinusoidal with $\omega = W_1$.

The diagram shows two phasors, **A** and **B**. (Note that the phasors are not drawn to scale. Also, we show three diagrams to illustrate the situation depending on the value of a you were given. You need to select the diagram that corresponds to your given value.) In your diagram, one phasor represents the capacitor voltage v_C and the other the resistor voltage v_R (but you are not told which one is which).


a. Find $i_1 = i_R(0^-)$ (i.e., just before the switch moves to position 2).

b. Find $i_2 = i_R(0^+)$ (i.e., just after the switch moves to position 2).


$$|A| = X\sqrt{2}$$

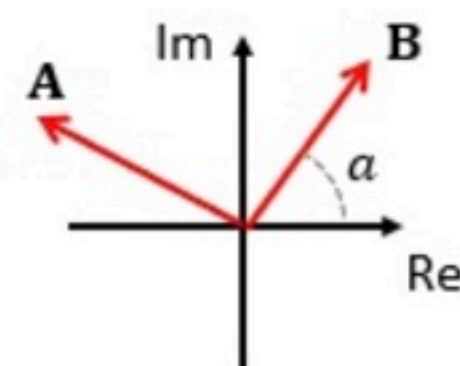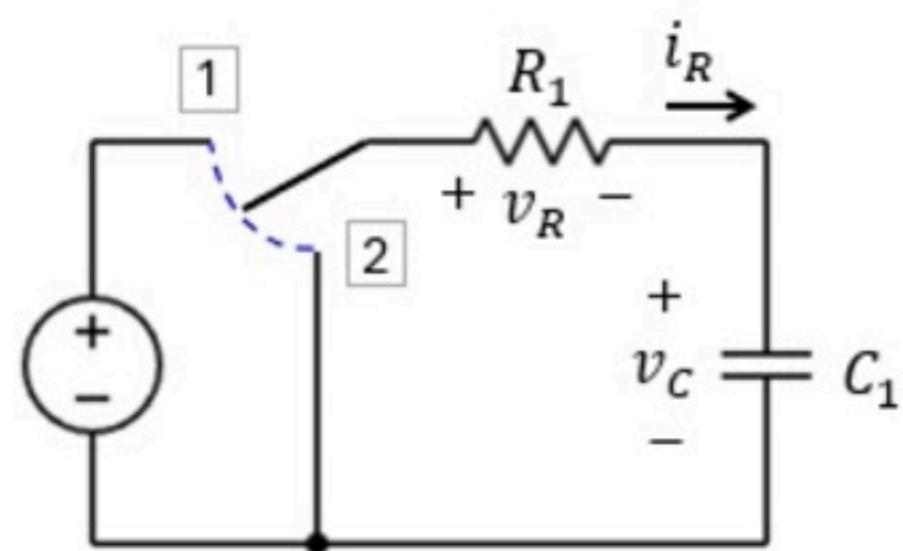

If $0 < a < \pi/2$

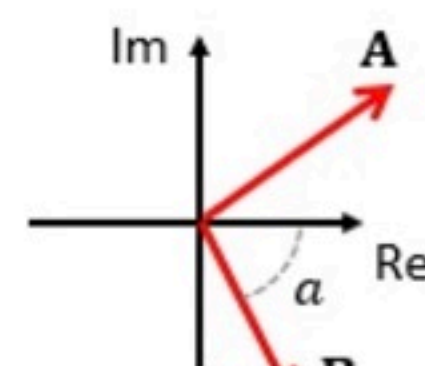

If $-\pi/2 < a < 0$

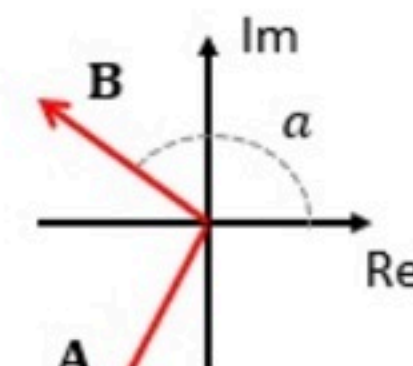

If $\pi/2 < a < \pi$

Given Variables:

W1 : 1 rad/s

X : 25

a : -45 degrees

R1 : 5 ohm

C1 : 1 F

Calculate the following:

i1 (A) :

5



i2 (A) :


-1



In the circuit below, the switch moves from position 1 to position 2 at time $t = 0$. For $t < 0$ (switch in position 1), you may assume that the system is in steady state. The voltage source is sinusoidal with $\omega = \omega_1$.

The diagram shows two phasors, **A** and **B**. (Note that the phasors are not drawn to scale. Also, we show three diagrams to illustrate the situation depending on the value of α you were given. You need to select the diagram that corresponds to your given value.) In your diagram, one phasor represents the capacitor voltage v_C and the other the resistor voltage v_R (but you are not told which one is which).

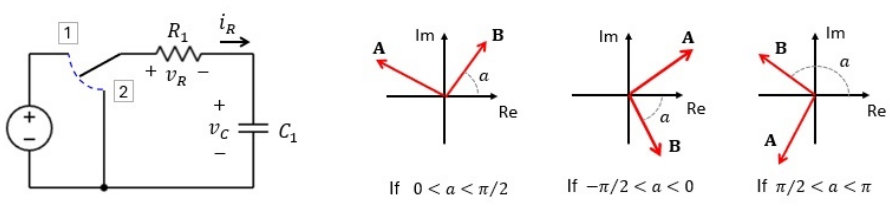
- a. Find $i_1 = i_R(0^-)$ (i.e., just before the switch moves to position 2).
- b. Find $i_2 = i_R(0^+)$ (i.e., just after the switch moves to position 2).



$\omega_1 = 1 \text{ rad/s}$
 $X = 10$
 $\phi = 45^\circ$
 $R_1 = 2 \Omega$
 $C_1 = 1 \text{ F}$

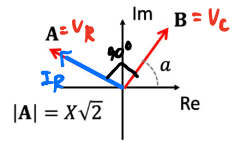a. Assume $A = v_R$ and $B = v_C$

We plot I_R such that it is in phase with v_R



$I_R = I_C$ since the resistor is series with the capacitor

\Rightarrow the capacitor current is ahead of the capacitor voltage \Rightarrow our assumption is correct \checkmark

At $t = 0^-$

$$v_R = X\sqrt{2} e^{j(90 + 90)} = 10\sqrt{2} e^{j135}$$

$$i_R = \frac{v_R}{R_1} = \frac{10\sqrt{2} e^{j135}}{2} = 5\sqrt{2} e^{j135}$$

$$i_R(t) = 5\sqrt{2} \cos(t + 135)$$

$$i_R(0^-) = 5\sqrt{2} \cos(0 + 135) = 5\sqrt{2} \cdot \left(-\frac{\sqrt{2}}{2}\right) \Rightarrow \boxed{i_1 = -5 \text{ A}}$$

b. At $t = 0^+$, the capacitor voltage cannot change instantaneously


$$Z_C = \frac{1}{j\omega C_1} = \frac{1}{j(1)(1)} = -j$$

$$v_C = i_R \cdot Z_C = 5\sqrt{2} e^{j135} \cdot -j = 5\sqrt{2} e^{j45}$$

$$v_C(t) = 5\sqrt{2} \cos(t + 45)$$

$$v_C(0^-) = 5\sqrt{2} \cos(0 + 45) = 5\sqrt{2} \cdot \left(\frac{\sqrt{2}}{2}\right) = 5 \text{ V} \Rightarrow v_C(0^+) = 5 \text{ V}$$

at $t = 0^+$

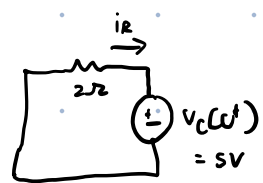

$$i_R(0^+) = \frac{-5}{2} \text{ A}$$

$$\boxed{i_2 = -2.5 \text{ A}}$$