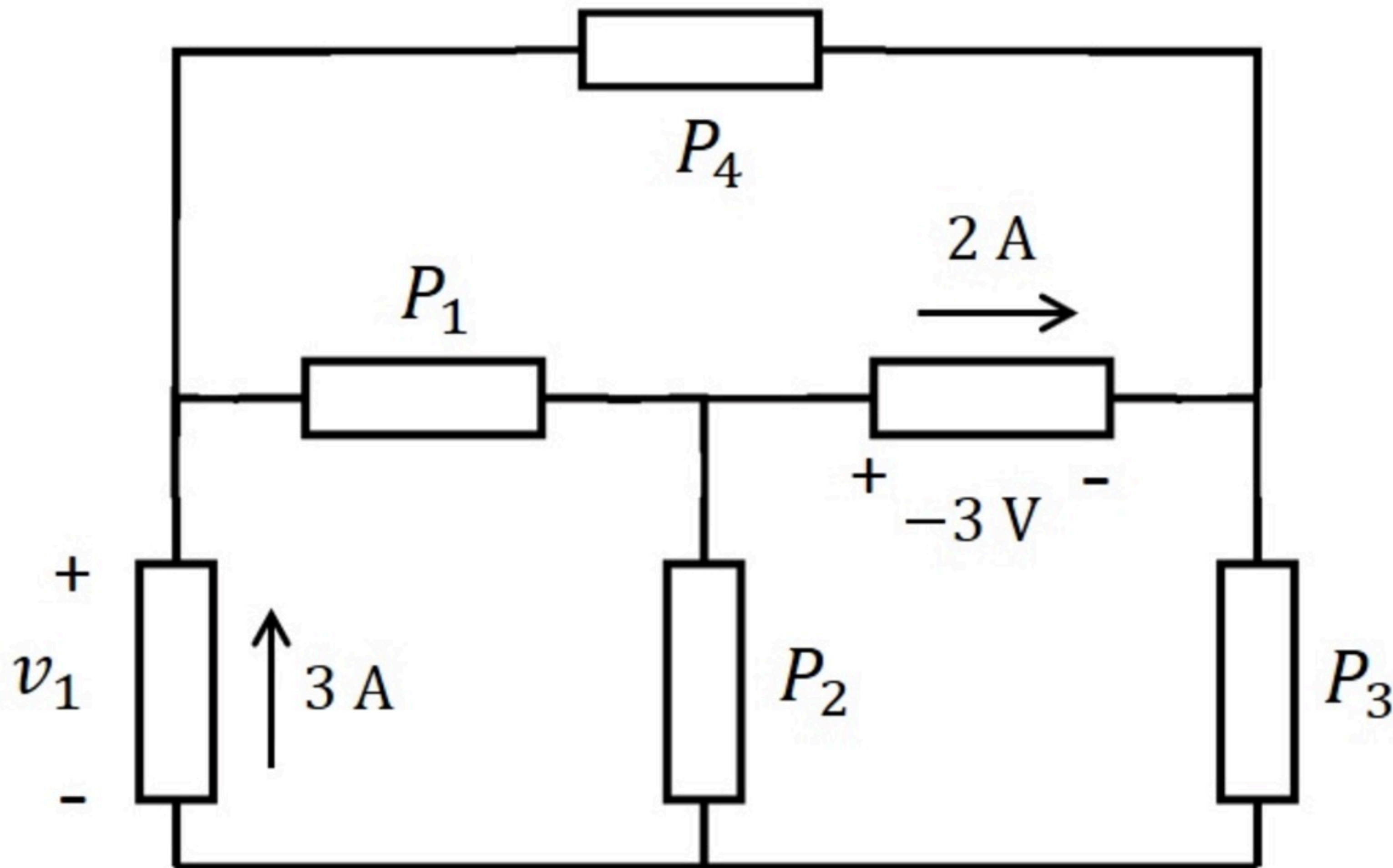


# Basic concepts 004

Problem has been graded.

We are given the power received  $P_1$ ,  $P_2$ ,  $P_3$  and the voltage  $v_1$ . Find the power received  $P_4$ .



Given Variables:

$v_1 : 2 \text{ V}$

$P_1 : 16 \text{ W}$

$P_2 : -4 \text{ W}$


$P_3 : 1 \text{ W}$

Calculate the following:

$P_4 \text{ (W)} :$

Hint: Sum of power received is equal to sum of power supplied.

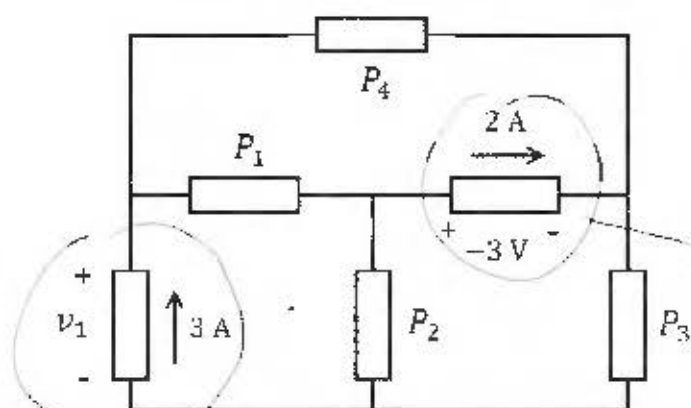We are given the power received  $P_1$ ,  $P_2$ ,  $P_3$  and the voltage  $v_1$ . Find the power received  $P_4$ .




$$v_1 = 1 \text{ V}$$

$$P_1 = 14 \text{ W}$$

$$P_2 = -5 \text{ W}$$

$$P_3 = -4 \text{ W}$$

→ passive sign convention

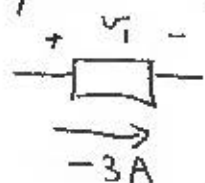

$$P = 1 \cdot (-3) = -3 \text{ W received}$$

→  $P = (-3) \cdot 2 = -6 \text{ W received}$

$$\sum P_{\text{received}} = \sum P_{\text{supplied}} \Rightarrow -3 - 6 + P_1 + P_2 + P_3 + P_4 = 0$$

$$-3 - 6 + 14 - 5 - 4 + P_4 = 0$$

$$\boxed{P_4 = 4 \text{ W}} \text{ received}$$