
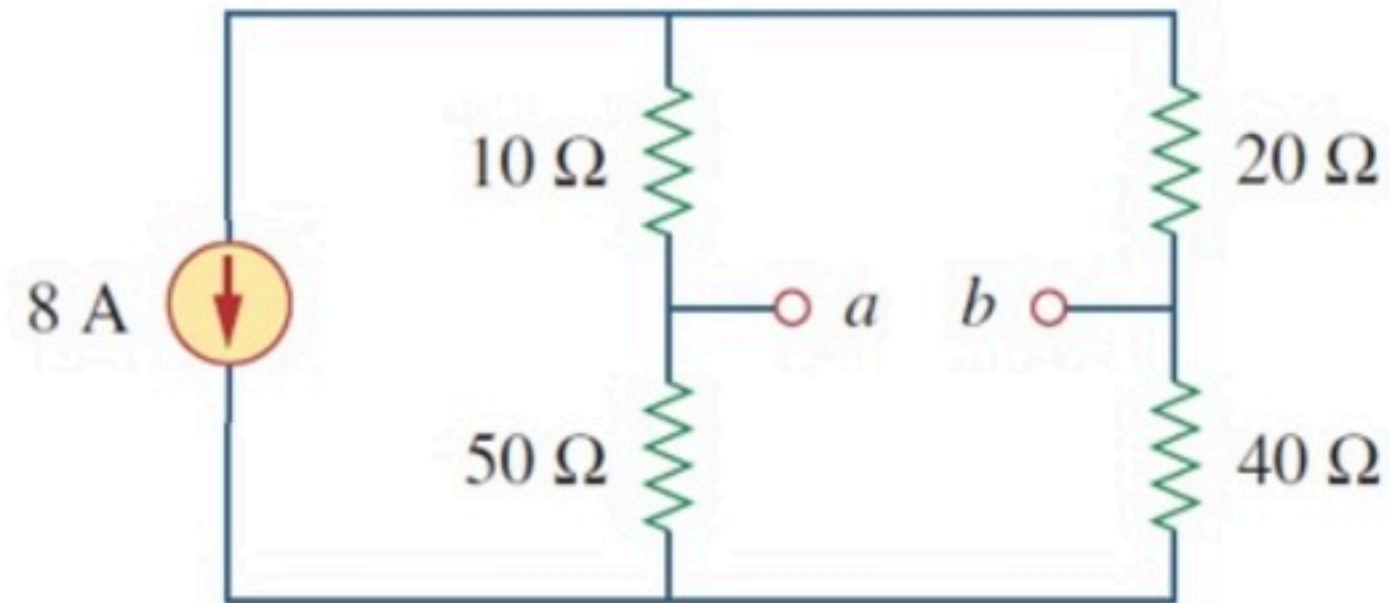


PP Circuit theorems 009

Unlimited Attempts.

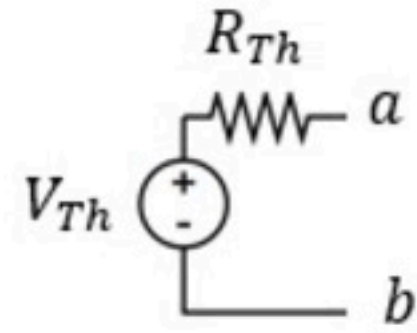Find the Thevenin equivalent model of this circuit, as seen between a and b.



Given Variables:

...

Calculate the following:

V_{th} (V) :

-40



R_{th} (ohm) :

22.5



Hint: Find V_{oc} using current dividers.