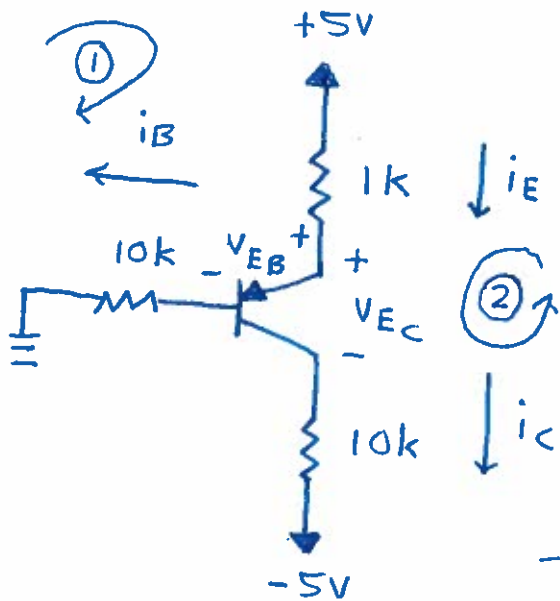


Problem 1,1



Assume cutoff:

$$i_B = 0, i_C = 0 \rightarrow i_E = 0$$

$$\textcircled{1} \quad -5 + 1k \cdot i_E + V_{EB} + 10k \cdot i_B = 0$$

$$\downarrow \quad \downarrow$$

$$0 \quad 0$$

$$V_{EB} = 5 > V_{D0} = 0.7 \quad \times$$

→ Therefore, BJT is not in cutoff

Assume Active:

$\textcircled{1}$

$$i_B \geq 0$$

$$V_{EB} = 0.7V$$

$$\beta i_B = i_C$$

$$V_{EC} \geq 0.7$$

$$-5 + i_E \cdot 1k + V_{EB} + i_B \cdot 10k = 0$$

$$i_B + i_C = i_E \rightarrow i_B + \beta i_B = i_E \rightarrow i_E = (1 + \beta) i_B$$

$$i_E = 101 i_B$$

$$\rightarrow -5 + (101) i_B \cdot 1k + V_{EB} + i_B \cdot 10k = 0 \rightarrow i_B = 0.038 \text{ mA}$$

$$i_C = \beta i_B = 3.8 \text{ mA}$$

$$i_E = 101 i_B = 3.91 \text{ mA}$$

* Now, need to check if actually in

active:

$\textcircled{2}$

$$-5 + i_E \cdot 1k + V_{EC} + i_C \cdot 10k - 5 = 0 \rightarrow V_{EC} = -32 < 0.7 \quad \times$$

→ Therefore, our assumption is incorrect, BJT is not in active.

↪ Not cutoff, not active, must be saturation.

Saturation:

$$V_{E_c} = 0.2V$$

$$i_c < \beta i_B$$

$$V_{E_B} = 0.7V$$

$$i_B \geq 0$$

$$\textcircled{2} \textcircled{\cancel{1}} -5 + 1k \cdot i_E + V_{E_c} + 10k \cdot i_c - 5 = 0$$

$$\underline{-9.8 + 1k \cdot i_E + 10k \cdot i_c = 0}$$

$$\textcircled{1} \textcircled{\cancel{2}} -5 + 1k \cdot i_E + V_{E_B} + 10k \cdot i_B = 0$$

$$\underline{-4.3 + 1k \cdot i_E + 10k \cdot i_B = 0}$$

* Next, we know $i_B + i_c = i_E$

Plugging that into the 2 equations above gives us:

$$-9.8 + 1k(i_B + i_c) + 10k \cdot i_c = 0$$

$$-4.3 + 1k(i_B + i_c) + 10k \cdot i_B = 0$$



$$i_B = 0.3125 \text{ mA}, \quad i_c = 0.8625 \text{ mA}, \quad i_E = 1.175 \text{ mA}$$

$$V_E = 5 - 1k \cdot i_E = 3.825 \text{ V}$$

$$V_C = i_c \cdot 10k - 5 = 3.625 \text{ V}$$



$$V_B = V_E - V_{E_B} = 3.125 \text{ V}$$

Problem 1,2

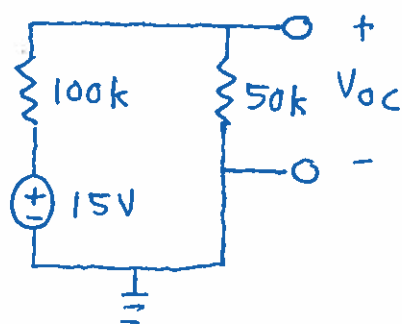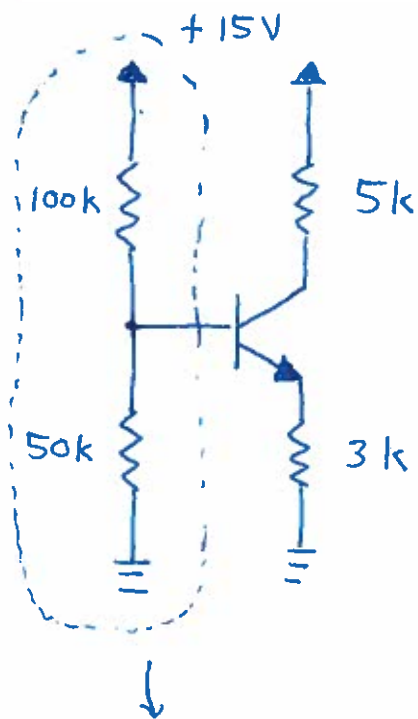

$$V_{th} = 15V \left(\frac{50k}{100k + 50k} \right) = 5V$$

$$R_{th} = 100k \parallel 50k = 33.3k$$

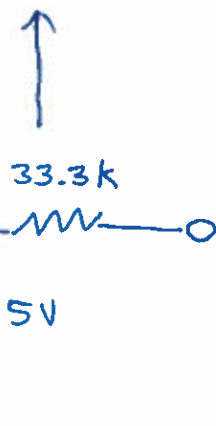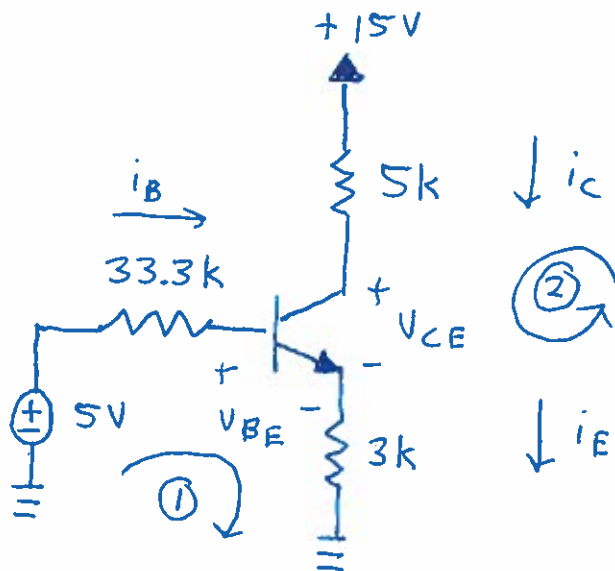

Assume cutoff:

$$i_B = i_C = 0 \rightarrow i_E = 0, V_{BE} < 0.7$$

$$\textcircled{1} \quad -5 + \underset{\downarrow 0}{i_B \cdot 33.3k} + V_{BE} + \underset{\downarrow 0}{i_E \cdot 3k} = 0 \rightarrow V_{BE} = 5 > 0.7 \text{ X}$$

→ Therefore, assumption is incorrect, BJT is not in cutoff.

Assume Active:

$$i_B \geq 0$$

$$V_{BE} = 0.7$$

$$i_C = \beta i_B$$

$$V_{CE} \geq 0.7$$

$$\textcircled{1} \quad -5 + i_B \cdot 33.3k + V_{BE} + i_E \cdot 3k = 0$$

$$(\beta + 1) i_B = i_E$$

$$-5 + i_B \cdot 33.3k + 0.7 + 101 i_B \cdot 3k = 0$$

$$i_B = 0.0128 \text{ mA}$$

$$i_C = \beta i_B = 1.28 \text{ mA}$$

$$i_E = 101 i_B = 1.29 \text{ mA}$$

Next, need to check assumption: (Is $V_{CE} \geq 0.7$?)

$$V_C = 15 - i_C \cdot 5k = 8.6 \text{ V}$$


$$V_E = i_E \cdot 3k = 3.87 \text{ V}$$

$$\rightarrow V_{CE} = V_C - V_E = 4.73 \geq 0.7 \quad \checkmark$$

Therefore, assumption is correct, BJT is operating in active mode.

$$V_B = V_E + V_{BE} = 4.57 \text{ V}$$

Problem 2

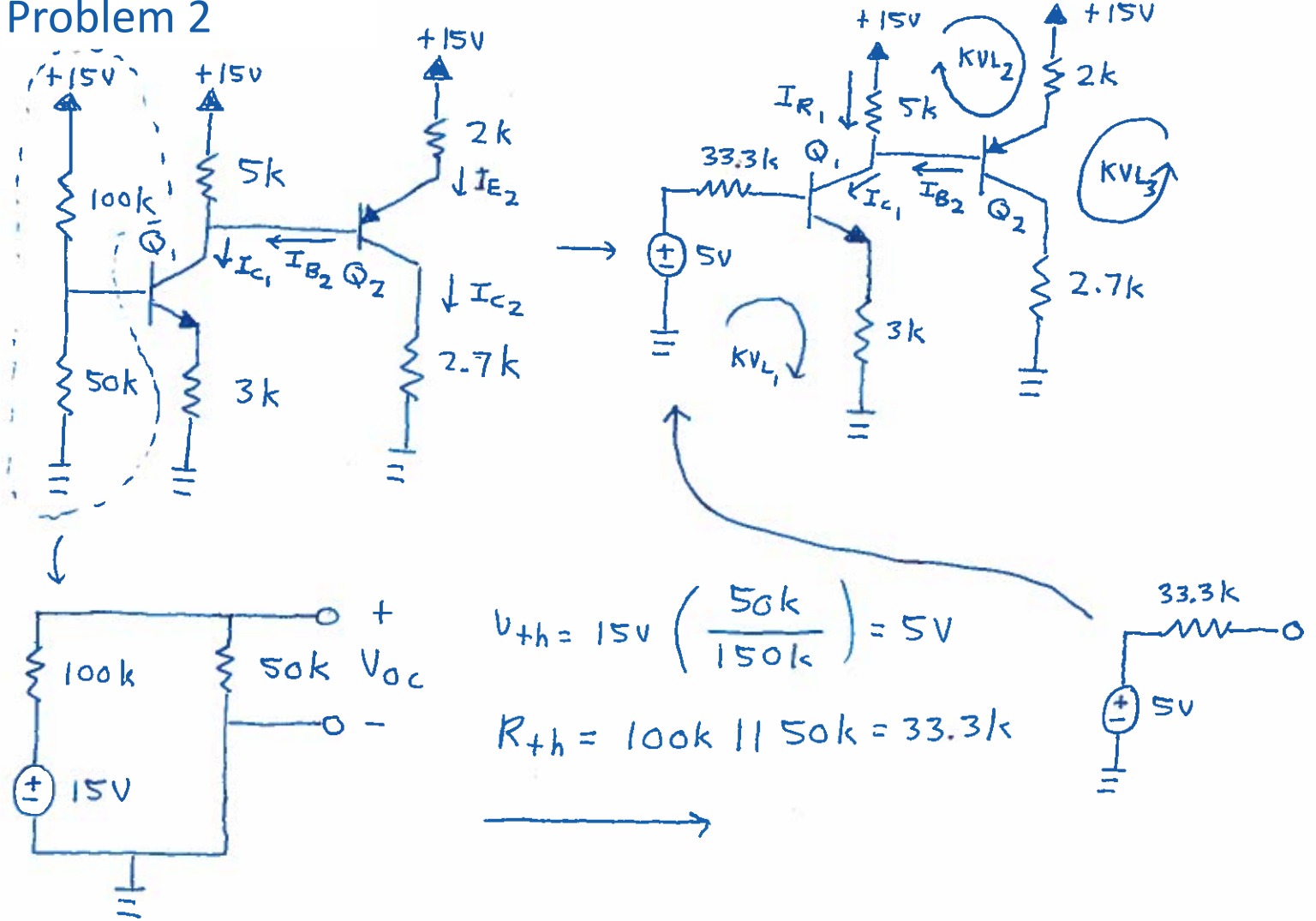

First, need to see if Q_1 is in cutoff:

$$KVL_1: -5 + 33.3k \cdot i_B + V_{BE} + 3k \cdot i_E = 0 \rightarrow V_{BE} = 5 > 0.7 \quad X$$

- Therefore, Q_1 is not in cutoff, must be on.

Assume Q_1 is active:

$$i_{B1} \geq 0$$

$$V_{BE1} = 0.7$$

$$i_{C1} = \beta i_{B1}$$

$$V_{CE1} \geq 0.7$$

$$-5 + 33.3k \cdot i_{B1} + V_{BE1} + 3k \cdot i_{E1} = 0$$

$$(\beta + 1) i_{B1} = i_{E1}$$

$$-5 + 33.3k \cdot i_{B1} + 0.7 + 3k (101) i_{B1} = 0$$

$$i_{B1} = 0.0128 \text{ mA}$$

$$i_{C1} = \beta i_{B1} = 1.28 \text{ mA}$$

$$i_E = 101 i_{B1} = 1.29 \text{ mA}$$

Next, need to check assumption ($V_{CE} \geq 0.7$?)

- However, we don't know V_{C_1} (since I_{B_2} is unknown)

→ So, make assumption of Q_2 (we will come back later)

Assume Q_2 in cutoff: $I_{B_2} = I_{C_2} = 0 \rightarrow I_{E_2} = 0$

$$-15 + 2k \cdot i_{E_2} + V_{EB_2} = V_{C_1}$$

$$I_{B_2} = 0 \rightarrow I_{R_1} = I_{C_1} = 1.28 \text{ mA}$$

$$V_{C_1} = 15 - I_{R_1} \cdot 5k = 8.6 \text{ V}$$

$$V_{EB_2} = 15 - V_{C_1} = 6.4 > 0.7 \text{ X}$$

Assumption incorrect, Q_2 is not in cutoff

Assume Q_2 in active:

$$i_{B_2} \geq 0$$

$$V_{EB_2} \approx 0.7$$

$$i_{C_2} = \beta i_{B_2}$$

$$V_{EC_2} \geq 0.7$$

KVL₂:

$$-15 + 2k \cdot i_{E_2} + V_{EB_2} - I_{R_1} \cdot 5k + 15 = 0$$

$$\uparrow$$
$$i_{E_2} = (\beta + 1) i_{B_2}$$

$$\uparrow$$
$$I_{R_1} = i_{C_1} - i_{B_2}$$
$$\uparrow$$
$$1.28 \text{ mA}$$

$$-15 + 2k (101) i_{B_2} + 0.7 - (1.28 - i_{B_2}) \cdot 5k + 15 = 0$$

$$i_{B_2} = 0.0275 \text{ mA}$$

$$i_{C_2} = 100 i_{B_2} = 2.75 \text{ mA}$$

$$i_{E_2} = 101 \cdot i_{B_2} = 2.78 \text{ mA}$$

Now, we can verify assumption of Q_1 :

$$V_{C_1} = 15 - I_{R_1} \cdot 5k = 8.74V$$

↓

$$I_{R_1} = i_{C_1} - i_{B_2} = (1.28 - 0.0275) \text{ mA}$$

$$V_{CE_1} = V_{C_1} - V_{E_1} = 8.74V - 3.87V = \underline{4.87V} > 0.7 \quad \checkmark$$

$$V_{E_1} = i_{E_1} \cdot 3k = (1.29 \text{ mA}) (3k) = 3.87V$$

Assumption for Q_1 correct, but only if Q_2 is correct

Verify Assumption of Q_2 :

$$\text{KVL}_3: -15 + 2k \cdot i_E + V_{EC_2} + 2.7k \cdot i_C = 0$$

$$V_{EC} = 2.015V > 0.7 \quad \checkmark$$

Assumption correct, Q_2 is in active as well.

- Both Q_1 and Q_2 in active.

$$V_{B_1} = 5 - i_{B_1} (33.3k) = 4.57V$$

$$V_{C_1} = 15 - I_{R_1} \cdot 5k = 8.74V$$


$$V_{E_1} = 3k \cdot i_{E_1} = 3.87V$$

$$V_{B_2} = V_{C_1} = 8.74V$$

$$V_{C_2} = 2.7k \cdot i_{C_2} = 7.43V$$

$$V_{E_2} = 15 - i_{E_2} \cdot 2k = 9.44V$$

Problem 3

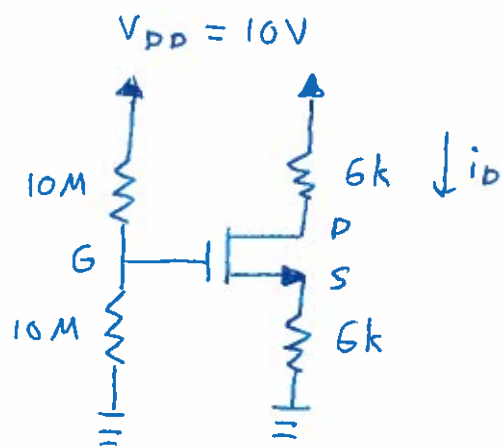

$$V_G = 10V \left(\frac{10M}{10M + 10M} \right) = \boxed{5V}$$

Assume Saturation:

$$i_D = \frac{1}{2} k_n (V_{OV})^2$$

$$= \frac{1}{2} k_n (V_{GS} - V_t)^2$$

$$= \frac{1}{2} k_n (V_G - V_S - V_t)^2$$

$$= \frac{1}{2} k_n (5 - V_S - 1)^2$$

$$= \frac{1}{2} k_n (4 - V_S)^2$$

$$= \frac{1}{2} k_n (4 - i_D \cdot 6k)^2$$

$$V_S = i_D \cdot 6k$$

$$i_D = 18 i_D^2 - 24 i_D + 8 \rightarrow 0 = 18 i_D^2 - 25 i_D + 8$$

$$i_D = \boxed{0.5mA} \text{ or } 0.89mA$$

Not valid: Would result in $V_{OV} < 0$, and transistor not in cutoff


$$V_S = (0.5mA)(6k) = \boxed{3V}$$

$$V_D = V_{DD} - i_D \cdot 6k = 10 - 3 = \boxed{7V}$$

$$V_{OV} \leq V_{DS} ? \rightarrow V_{OV} = 4 - (0.5mA)(6k) = 1V < V_{DS} = 4V \checkmark$$

Yes, in saturation.

Problem 4

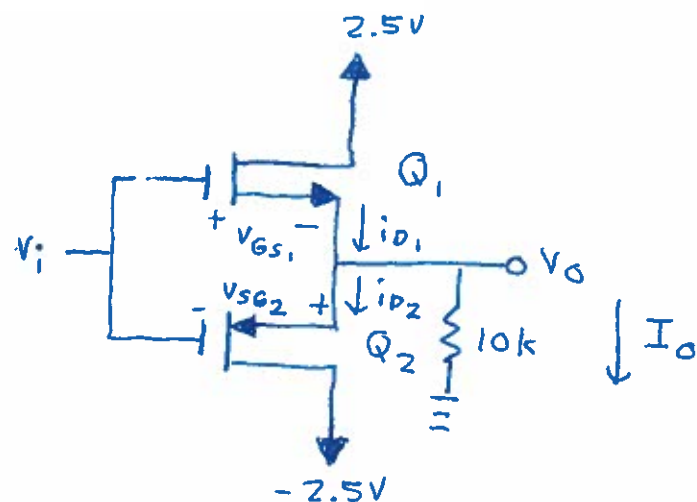

$V_i = 0 \rightarrow$ Assume both in cutoff

$$\boxed{i_{D1} = i_{D2} = 0} \rightarrow V_o = I_o \cdot 10k = 0V$$

$$V_{ov1} < 0? \quad V_{ov2} < 0?$$

$$V_{GS1} = V_i - V_o = 0 \rightarrow V_{ov1} = 0 - 1V < 0 \quad \checkmark$$

$$V_{SG2} = V_o - V_i = 0 \rightarrow V_{ov2} = 0 - 1V < 0 \quad \checkmark$$

Assumption Correct, both are in cutoff ; $\boxed{V_o = 0V}$

$V_i = 2.5V \rightarrow$ Assume Q_1 in sat., Q_2 cutoff

$$i_{D1} = \frac{1}{2} k_n V_{ov1}^2 \quad * I_o = i_{D1} \quad (\text{Since if } Q_2 \text{ is off, all current from } Q_1 \text{ goes to } I_o)$$

$$i_{D2} = 0$$

$$i_{D1} = \frac{1}{2} k_n (V_{GS1} - V_t)^2 = \frac{1}{2} k_n (V_i - V_o - 1)^2 = \frac{1}{2} k_n (1.5 - V_o)^2$$


$$V_o = i_{D1} \cdot 10k \rightarrow i_{D1} = \frac{1}{2} k_n (1.5 - i_{D1} \cdot 10k)^2$$

$$0 = 50i_{D1}^2 - 16i_{D1} + 1.125 \rightarrow \boxed{i_{D1} = 0.104 \text{ mA}} \text{ or } 0.216 \text{ mA}$$

$$V_o = i_{D1} \cdot 10k = \boxed{1.04V}$$

Not valid, because if so,
 $V_{ov1} < 0$, and Q_1 is not in sat.

Problem 5

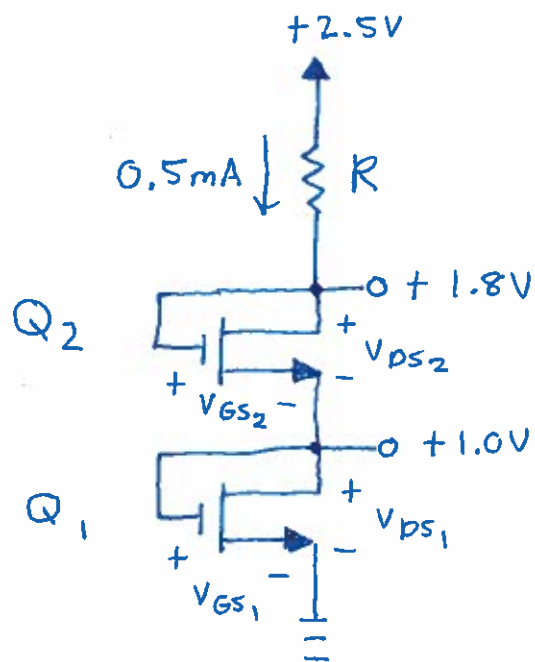

* We know both Q_1 and Q_2 are in saturation, because gate is connected to drain, meaning:

$$V_{GS1} = V_{DS1} \rightarrow V_{OV1} < V_{DS1}$$

$$V_{GS2} = V_{DS2} \rightarrow V_{OV2} < V_{DS2}$$

$$R = \frac{2.5V - 1.8V}{0.5mA} = \boxed{1.4k\Omega}$$

$$i_{D1} = i_{D2} = 0.5mA$$

$$V_{GS2} = 1.8V - 1V = 0.8V \rightarrow V_{OV2} = 0.8V - 0.5V = 0.3V$$

$$V_{GS1} = 1V - 0V = 1V \rightarrow V_{OV1} = 1V - 0.5V = 0.5V$$

$$i_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W_2}{L_2} (V_{OV2})^2 \rightarrow W_2 = \frac{2i_{D2} \cdot L_2}{\mu_n C_{ox} (V_{OV2})^2} = \boxed{11.1\mu m}$$

$$i_{D1} = \frac{1}{2} \mu_n C_{ox} \frac{W_1}{L_1} (V_{OV1})^2 \rightarrow W_1 = \frac{2i_{D1} \cdot L_1}{\mu_n C_{ox} (V_{OV1})^2} = \boxed{4\mu m}$$